



Gate-Level Minimization

Dr. Bassem A. Abdullah
Computer and Systems Department



Outline

1. The Map Method
2. Four-variable Map
3. Five-variable Map
4. Product of Sums Simplification
5. Don't-Care Conditions
6. NAND and NOR Implementation
7. Other Two-level Implementations
8. Exclusive-OR Function

Karnaugh Map (K-Map) Simplification Method

1. A pictorial form of truth table
2. Express any Boolean function as sum of minterms (SoP)
3. Simplify a Boolean function in SoP or PoS standard forms

Two-variable K-map

Presents the four minterms of a two-variable function as follows:

m_0	m_1
m_2	m_3

		y	
		0	1
x	0	m_0 $x'y'$	m_1 $x'y$
	1	m_2 xy'	m_3 xy


Representation of functions in a K-map

$$F = xy$$

		y	
		0	1
x	0	m_0	m_1
1	m_2	m_3	1

Representations of functions in a K-map
 
$$\begin{aligned} F &= x + y \\ &= xy' + xy + x'y \\ &= m_2 + m_3 + m_1 \\ &= \sum(1, 2, 3) \end{aligned}$$



Simplification of functions in a K-map

$$\begin{aligned} F &= \sum(2, 3) \\ &= xy' + xy \\ &= x(y+y') \\ &= x \cdot 1 \\ &= x \end{aligned}$$

	y	
	y'	y
x'	0	1
x	2	3
	1	1

K-map Simplification of a Two-variable Function

- **1** square (minterm) represents a term of **2** literals
- **2** adjacent squares represent a term of **1** literal
- **4** adjacent squares represent the function **1**

Three-variable K-map ($F(x, y, z)$)

Presents the eight minterms of a three-variable function as follows:


Gray code: only one variable changes between 2 adjacent positions

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

		y			
		yz	00	01	11
x	0	m_0 $x'y'z'$	m_1 $x'y'z$	m_3 $x'yz$	m_2 $x'yz'$
	1	m_4 $xy'z'$	m_5 $xy'z$	m_7 xyz	m_6 xyz'
		z			


Representation of functions in a K-map
 
$$\begin{aligned} F &= x'y + xy' \\ &= x'yz' + x'yz + xy'z' + xy'z \\ &= m_2 + m_3 + m_4 + m_5 \\ &= \sum(2, 3, 4, 5) \end{aligned}$$




Simplification of functions in a K-map

$$F(x,y,z) = \Sigma(0,2,4,6) \\ = z'$$

 

Simplification of functions in a K-map

$$F = \sum(3, 4, 6, 7)$$
$$= yz + xz'$$

 


K-map Simplification of a Three-variable Function

- **1** square (minterm) represents a term of **3** literals
- **2** adjacent squares represent a term of **2** literal
- **4** adjacent squares represent a term of **1** literal
- **8** adjacent squares represent the function **1**

 
Example

$$F(x,y,z) = \Sigma(0,2,4,5,6)$$
$$= z' + xy'$$



 Example


$$\begin{aligned} F(A,B,C) &= A'C + A'B + AB'C + BC \\ &= \Sigma (1,2,3,5,7) \\ &= C + A'B \end{aligned}$$



Four-variable K-map (F(w, x, y, z))

Presents the sixteen minterms of a four-variable function as follows:

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

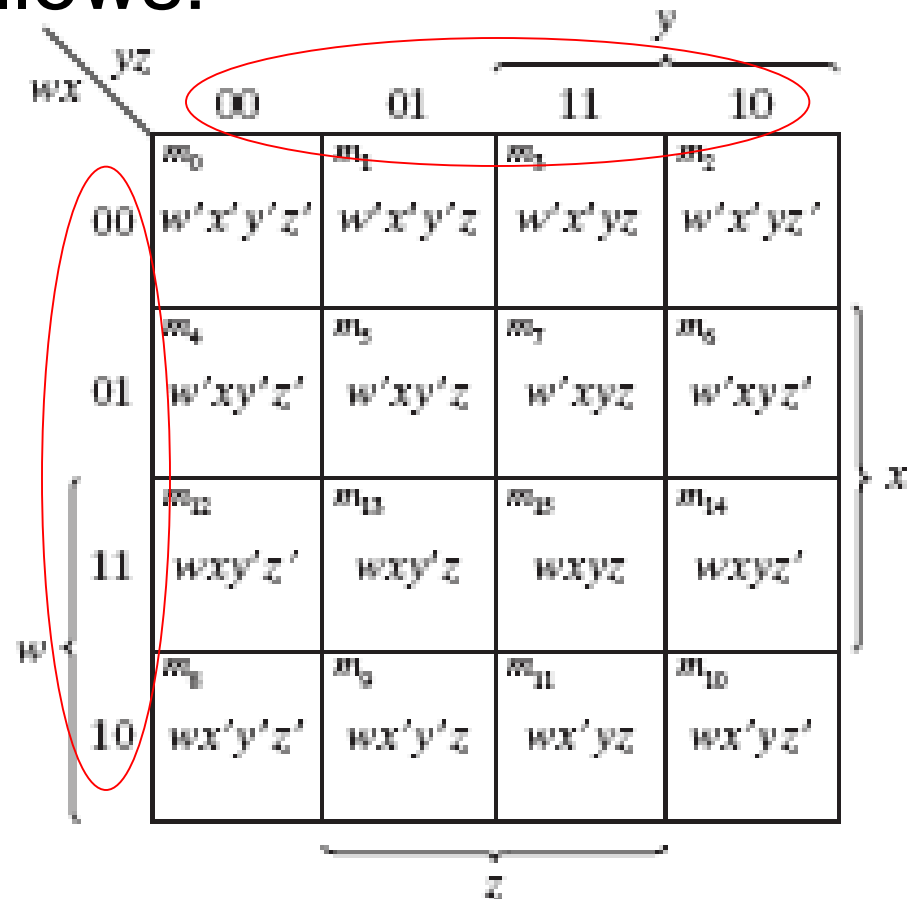


K-map Simplification of a Four-variable Function

- **1** square (minterm) represents a term of **4** literals
- **2** adjacent squares represent a term of **3** literal
- **4** adjacent squares represent a term of **2** literal
- **8** adjacent squares represent a term of **1** literal
- **16** adjacent squares represent the function **1**

 Example

$$F(w, x, y, z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$
$$= y' + w'z' + xz'$$




Example

$F(A, B, C, D)$

$= A'B'C' + B'C'D' + A'BCD' + AB'C'$

 
$= \mathbf{B'D'} + \mathbf{B'C'} + \mathbf{A'CD'}$




Prime Implicants and Essential Prime Implicants

- **Prime Implicant:** A product term containing the maximum possible number of adjacent squares in the k-map.
- **Essential Prime Implicant:** A prime implicant that contains a minterm that is covered by only one prime implicant.

Essential Prime Implicants:
BD and B'D'

 

Prime Implicants:
CD, B'C, AD, and AB'

 

Example


$$F = \sum(0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$$

$$= BD + B'D' + CD + AD$$

$$= BD + B'D' + CD + AB'$$

$$= BD + B'D' + B'C + AD$$

$$= BD + B'D' + B'C + AB'$$

 

Essential Prime Implicants

Five-variable K-map (F(A, B, C, D, E))

Presents the 32 minterms of a five-variable function as follows:

		$A = 0$			
		D			
BC	DE	00	01	11	10
	00	m_0	0	1	3
01	m_4	4	5	7	6
11	m_{12}	12	13	15	14
10	m_8	8	9	11	10


E

		$A = 1$			
		C			
BC	DE	00	01	11	10
	00	m_{16}	16	17	19
01	m_{20}	20	21	23	22
11	m_{28}	28	29	31	30
10	m_{24}	24	25	27	26

E

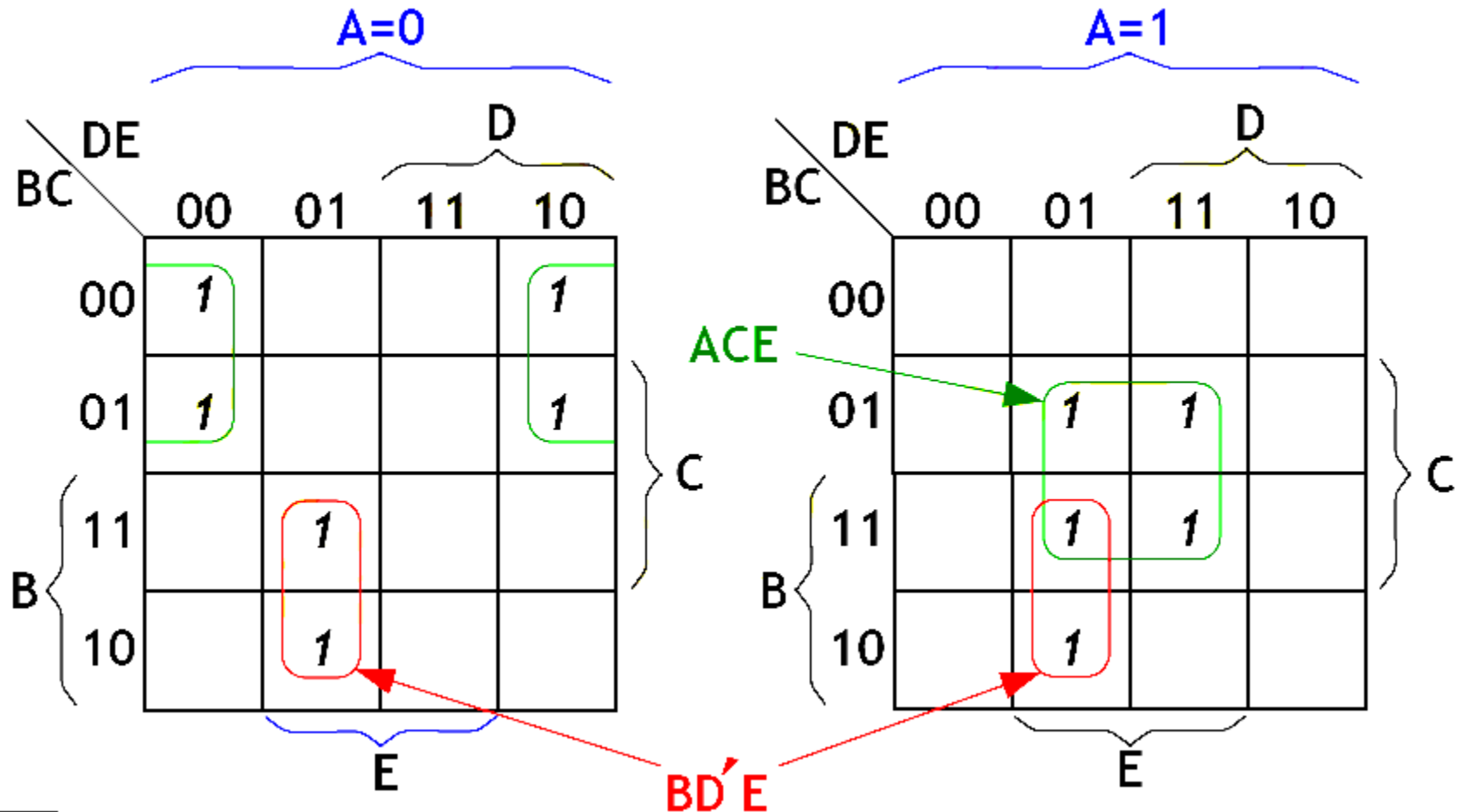
Example

$$F = \sum(0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31) = A'B'E' + BD'E + ACE$$



 Example

$$F = \sum(0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31) = A'B'E' + BD'E + ACE$$



Simplify function in SoP and PoS

$$\begin{aligned} F(A, B, C, D) &= \sum(0, 1, 2, 5, 8, 9, 10) \\ &= B'D' + B'C' + A'C'D \end{aligned}$$


Simplify function in SoP and PoS

$$F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$$


$$= B'D' + B'C' + A'C'D$$

$$F = (F')' = (AB + CD + BD')'$$


$$= (A' + B')(C' + D')(B' + D)$$

 

Gate Implementation

 

(a) $F = B'D' + B'C + A'CD$

 

(b) $F = (A' + B')(C + D')(B' + D)$

Don't-care Terms (x)

- A don't care term is a combination of variables whose logical value is not specified.
- Example:
BCD has 6 don't-care terms

Decimal	BCD
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
10	x
11	x
12	x
13	x
14	x
15	x

Simplification in Presence of Don't-care Terms (x)

- A don't care term can be assigned logic 1 or zero for simplification

Example

$$F(w, x, y, z) = \sum(1, 3, 7, 11, 15)$$

With don't care terms $d = \sum(0, 2, 5)$

		y			
		yz	00	01	11
w	$w'x'$	m_0	m_1	m_3	m_2
	00	X	1	1	X
	m_4	m_5	m_7	m_6	
	01	0	X	1	0
11	m_{12}	m_{13}	m_{15}	m_{14}	
10	m_8	m_9	m_{11}	m_{10}	
		z			

(a) $F = yz + w'x'$




		y			
		yz	00	01	11
w	$w'z$	m_1	m_3	m_7	m_2
	00	X	1	1	X
	m_4	m_5	m_7	m_6	
	01	0	X	1	0
11	m_{12}	m_{13}	m_{15}	m_{14}	
10	m_8	m_9	m_{11}	m_{10}	
		z			

(b) $F = yz + w'z$


NAND and NOR Gates

- NAND and NOR gates are easier to fabricate with electronic components.
- NAND and NOR gates are universal gates; any combinational digital system can be implemented with NAND gates only or NOR gates only.
- NAND and NOR gates are the basic gates in all IC digital family.


NAND Gate

   

Two Symbols for NAND Gates

 

(a) AND-invert

 


(b) Invert-OR



DeMorgan's: $(xyz)' = x' + y' + z'$

Two-Level Implementation with NAND Gates

$$F = AB + CD = [(AB)'(CD)']'$$

 




(a)

  

Example:


Implement $F(x, y, z) = \sum(1, 2, 3, 4, 5, 7)$

$$F = xy' + x'y + z$$

  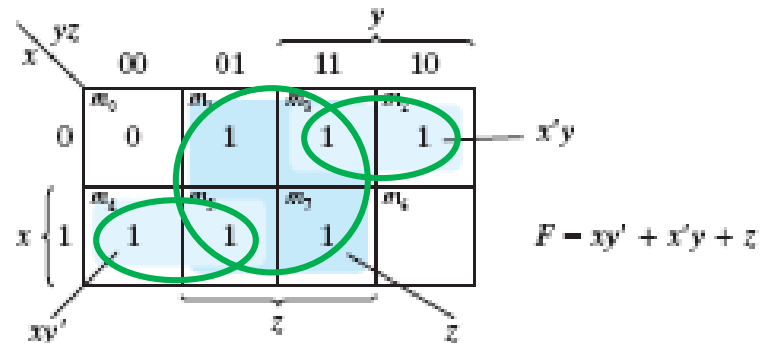


Example

$$F(A, B, C, D) = A(CD + B) + BC'$$

 


(a) AND-OR gates

 


(b) NAND gates

Example

$$F(A, B, C, D) = (AB' + A'B)(C+D')$$



 


(a) AND-OR gates

 


(b) NAND gates


NOR Gate

   

Two Symbols for NOR Gates

 

(a) OR-invert

 


(b) Invert-AND

DeMorgan's: $(x+y+z)' = x' \cdot y' \cdot z'$



Two-Level Implementation with NOR Gates

$$F = (A+B)(C+D)E$$

 

Example

$$F(A, B, C, D) = (AB' + A'B)(C+D')$$

  

Implementation with other two-level forms

Implementation with Other Two-Level Forms

Equivalent Nondegenerate Form		Implements the Function	Simplify F' into	To Get an Output of
(a)	(b)*			
AND-NOR	NAND-AND	AND-OR-INVERT	Sum-of-products form by combining 0's in the map.	F
OR-NAND	NOR-OR	OR-AND-INVERT	Product-of-sums form by combining 1's in the map and then complementing.	F

*Form (b) requires an inverter for a single literal term.

Implementation F with the 4 two-level forms


		yz			
		00	01	y	
x	0	m_0 1	m_1 0	m_2 0	m_3 0
	1	m_4 0	m_5 0	m_6 0	m_7 1

$x'y'z'$ points to the cell (0,00)
 xyz' points to the cell (1,10)


$$F = x'y'z' + xyz'$$

$$F' = x'y + xy' + z$$

$$F = (x'y + xy' + z)'$$

 

AND-NOR

 


NAND-AND

Implementation F with the 4 two-level forms


		yz			
		00	01	y	
x	0	m_0 1	m_1 0	m_2 0	m_3 0
	1	m_4 0	m_5 0	m_6 0	m_7 1

$F = x'y'z' + xyz'$
 $F' = x'y + xy' + z$

$$F = ((x+y+z) (x'+y'+z))'$$

 

OR-NAND

 

NOR-OR

Exclusive-OR (XOR)

Exclusive-OR	$x \oplus y$	$xy' + x'y$
Exclusive-NOR	$(x \oplus y)'$	$xy + x'y'$

Commutative	$x \oplus y = y \oplus x$
Associative	$(x \oplus y) \oplus z = x \oplus (y \oplus z)$

Primitive Exclusive-OR Operations	$x \oplus 0 = x$
	$x \oplus 1 = x'$
	$x \oplus x = 0$
	$x \oplus x' = 1$
	$x \oplus y' = x' \oplus y = (x \oplus y)'$


Odd versus Even function

		B			
		BC	00	01	11
A	0	m_0	m_1 1	m_3	m_2 1
	1	m_4 1	m_5	m_7 1	m_6
		C			


(a) Odd function $F = A \oplus B \oplus C$

		B			
		BC	00	01	11
A	0	m_0 1	m_1	m_3 1	m_2
	1	m_4	m_5 1	m_7	m_6 1
		C			

 (b) Even function $F = (A \oplus B \oplus C)'$




(a) 3-input odd function

 

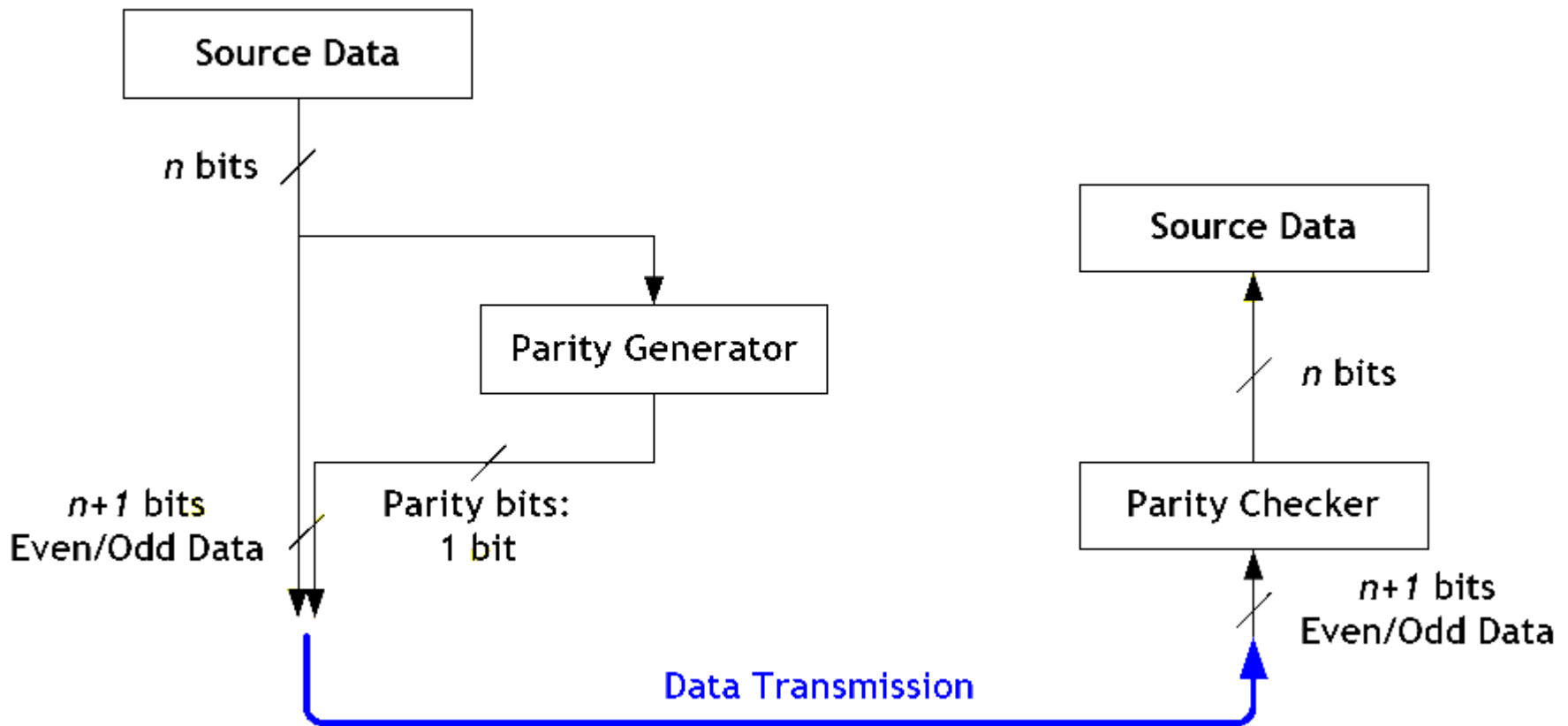(b) 3-input even function

Parity Data transmission System (Parity Generator/Checker)



Even Parity Generator

Even-Parity-Generator Truth Table

Three-Bit Message			Parity Bit
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Even Parity Checker

Even-Parity-Checker Truth Table

Four Bits Received				Parity Error Check	
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>	<i>C</i>	
0	0	0	0	0	
0	0	0	1	1	
0	0	1	0	1	
0	0	1	1	0	
0	1	0	0	1	
0	1	0	1	0	
0	1	1	0	0	
0	1	1	1	1	
1	0	0	0	1	
1	0	0	1	0	
1	0	1	0	0	
1	0	1	1	1	
1	1	0	0	0	
1	1	0	1	1	
1	1	1	0	1	
1	1	1	1	0	

Logic Implementation of Parity Generator and Checker

$$P = x \oplus y \oplus z$$

$$C = x \oplus y \oplus z \oplus P$$

