



Sequential Logic Part 1

Dr. Bassem A. Abdullah
Computer and Systems Department




Outline

1. Sequential Logic
2. Latches
3. Flip-Flops
4. Analysis of clocked sequential circuits
5. State Reduction and assignment
6. Design Procedure

Logic Circuits: Combinational versus Sequential Circuits


■ Combinational Circuits:

 Output only depends on the present combination of inputs




■ Sequential Circuits:

 Output depends on the input and the state of the storage (past inputs)



Block Diagram of Sequential Circuits

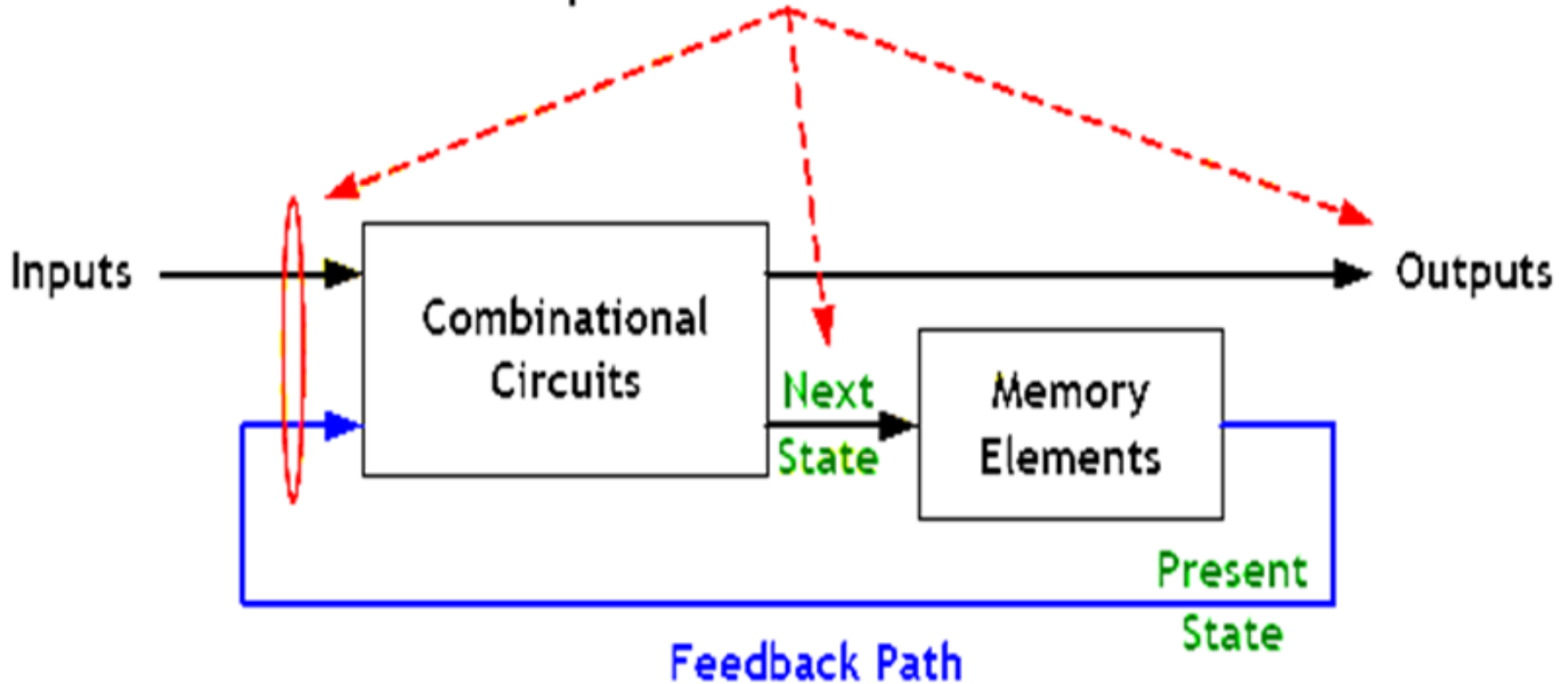
The present state and inputs determine the output and the next state.



Latch / Flip-Flop

- Memory elements: Latches/Flip-Flop
- Latch / Flip-Flop can maintain a binary state indefinitely until directed by an input signal to change the state.

SR Latch with NOR Gates

 


(a) Logic diagram


S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0

(after $S = 1, R = 0$)
 (after $S = 0, R = 1$)
 (forbidden)

(b) Function table

 

SR Latch Characteristic table

 


S	R	Q	Q'	
0	0	No change		
0	1	0	1	Reset
1	0	1	0	Set
1	1	0	0	Indeterminate

SR Latch With Control Input Characteristic table

C	S	R	Q	Q'	
0	x	x	No change		
1	0	0	No change		
1	0	1	0	1	Reset
1	1	0	1	0	Set
1	1	1	0	0	Indeterminate

D Latch

 - Eliminate the undesirable of the indeterminate state in the SR latch



C	D	Q	Q'	
0	X	No change		
1	0	0	1	Reset
0	1	1	0	Set

Latches Versus Flip Flops

- **Trigger:** The response to the change of input control signal to switch state of a latch or flip-flop
- Latch: Level Trigger
- Flip-Flop: Edge Trigger

Positive level trigger



Positive level trigger



Negative level trigger




Classifications of Sequential Circuits

■ Asynchronous Sequential Circuit:

The behavior depends on the input signals at any time instant and the order in which input changes. (**Chapter 9**)

■ Synchronous Sequential Circuit:

 The behavior is defined at discrete instants of time.




(a) Block diagram




(b) Timing diagram of clock pulses

D Flip-Flop

 

(a) Positive-edge

 


(a) Negative-edge


D Flip-Flop

D	Q(t + 1)	
0	0	Reset
1	1	Set


D Latch

 


D Flip-Flop (Positive Edge Triggered)

 

JK Flip-Flop

 

(a) Circuit diagram

 


(b) Graphicsymbol

JK Flip-Flop

J	K	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

T (Toggle) Flip-Flop

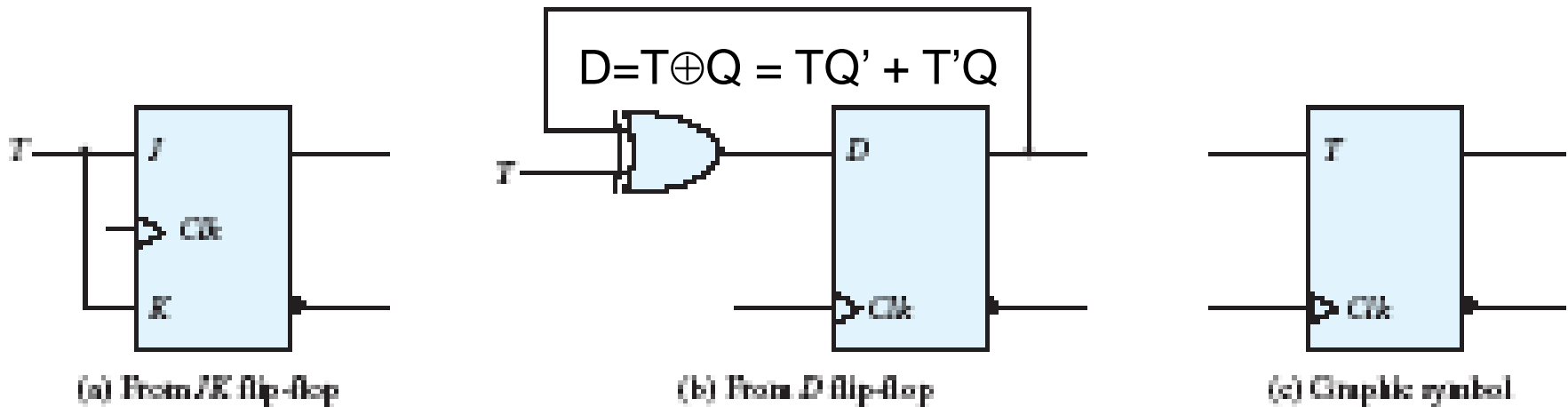

T Flip-Flop

T	Q(t + 1)	
0	Q(t)	No change
1	Q'(t)	Complement

Characteristic Equations

- The logical properties of a flip-flop as described in the characteristic table can be expressed also algebraically with a characteristic equation

$$\mathbf{D\ FF: \quad Q(t+1) = D}$$

$$\mathbf{JK\ FF: \quad Q(t+1) = JQ' + K'Q}$$

$$\mathbf{T\ FF: \quad Q(t+1) = T \oplus Q = TQ' + T'Q}$$

Analysis of Clocked Sequential Circuits


■ State Table (Transition Table)

□ Consists of:

1. Present State
2. Inputs
3. Next State
4. Outputs

■ Example of State Table (Transition Table)

Example \longrightarrow State Table

 

Depend on Circuit

Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0


2^3 items

Analysis of Clocked Sequential Circuits

■ State Equation (Transition Equation):

A **state equation** (also called **transition equation**) specified the next state as a function of the present state and inputs.


■ Example of Sequential Circuit

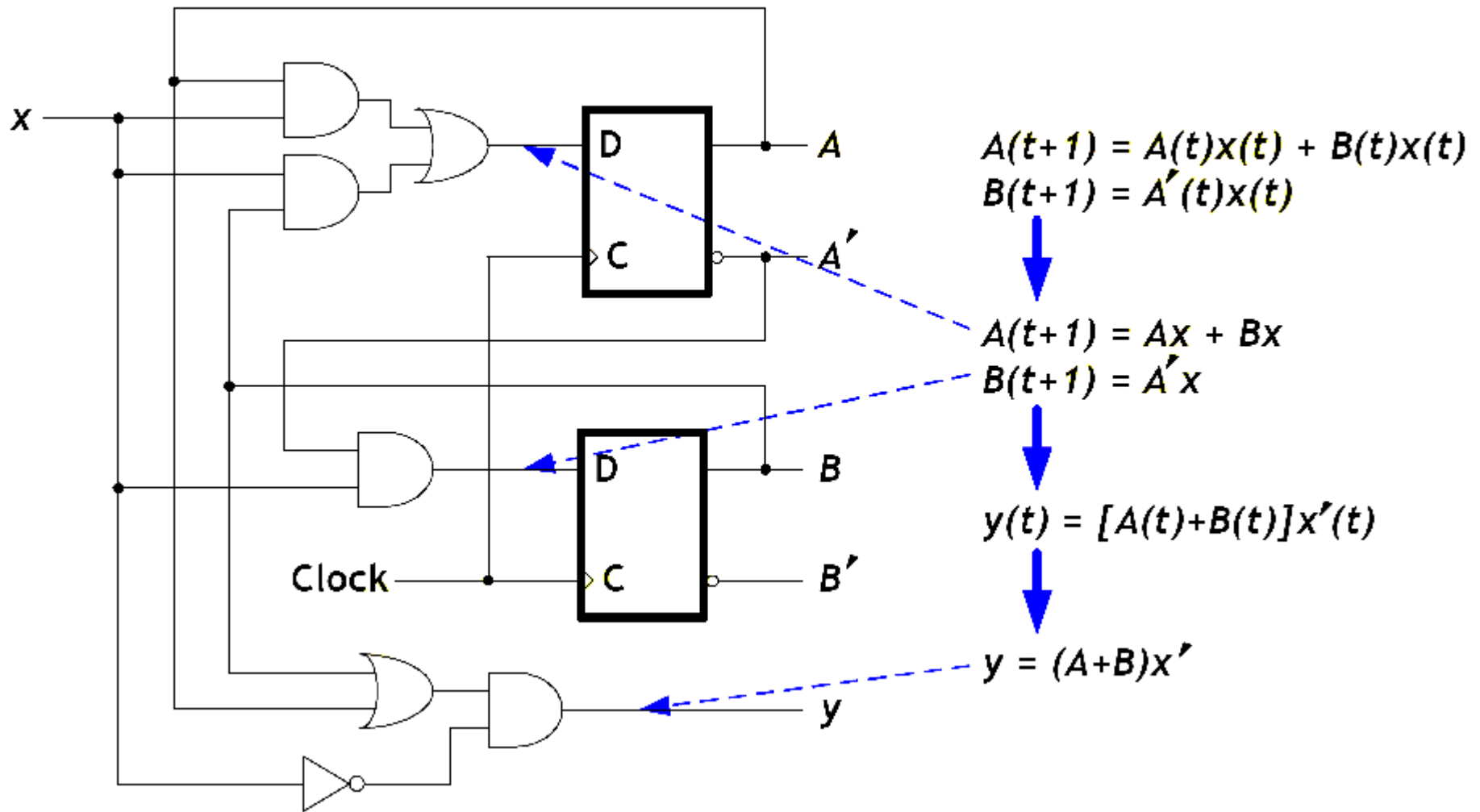

■ Flip-Flop Input Equations

1. The logic diagram of a sequential circuit consists of flip-flops and gates.
2. The part of combination circuit that generates external outputs is described algebraically by a set of Boolean functions called **output equations**.
3. The part of the circuit that generates the inputs to flip-flops is described algebraically by a set of Boolean functions called flip-flop **input equations** (sometimes called **excitation equations**).
4. The designer adopts the convention of using the flip-flop input symbol to denote the input variable and subscript to designate the name of the flip-flop outputs.


■ Example of Flip-Flop Input Equations

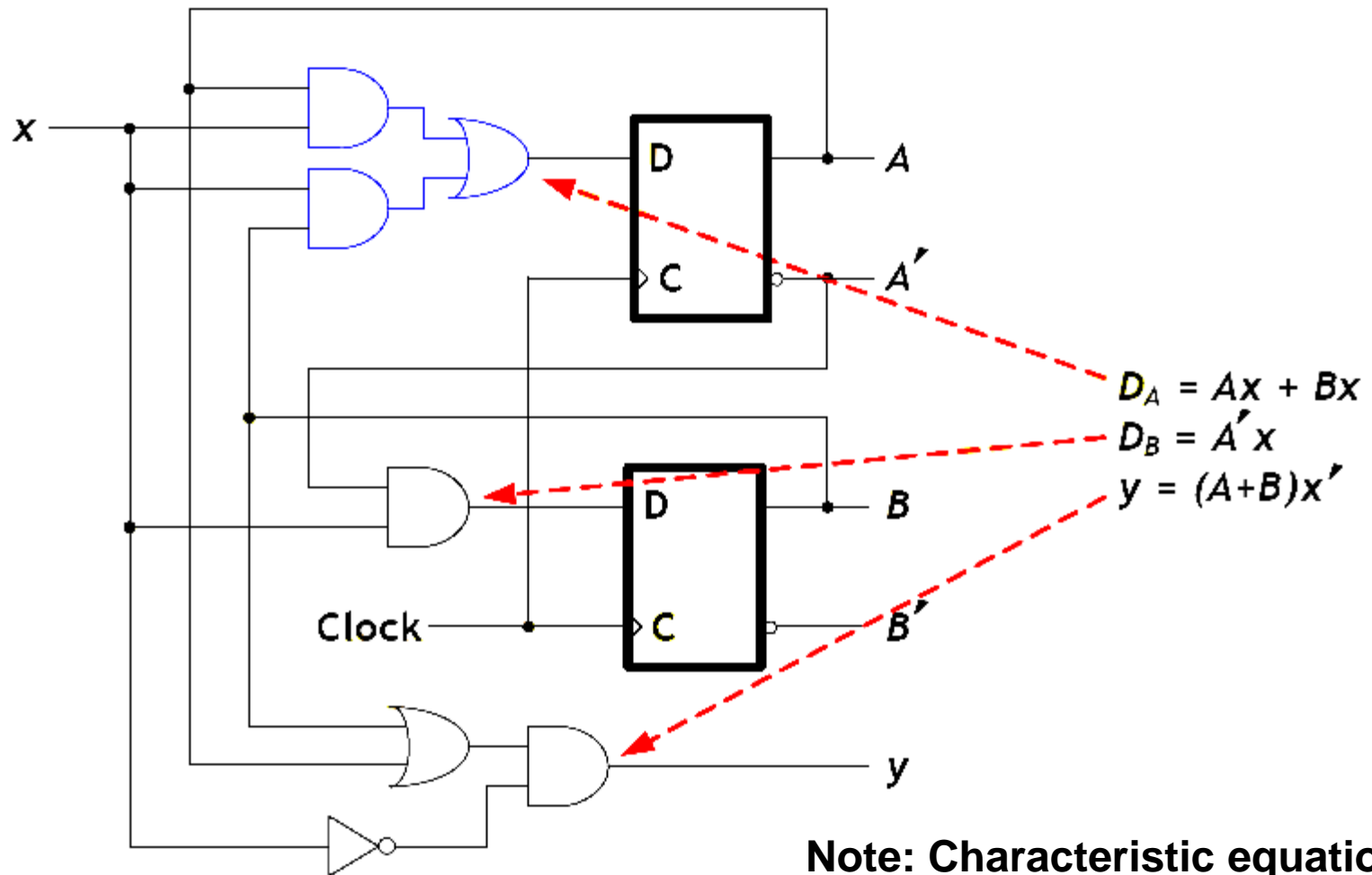


Note: Characteristic equation
 $D_A = A(t+1)$

■ Example of State Table (Transition Table)

 Example \longrightarrow Second Form of the State Table



Present State AB	Next State		Output	
	$x=0$ AB	$x=1$ AB	$x=0$ y	$x=1$ y
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0

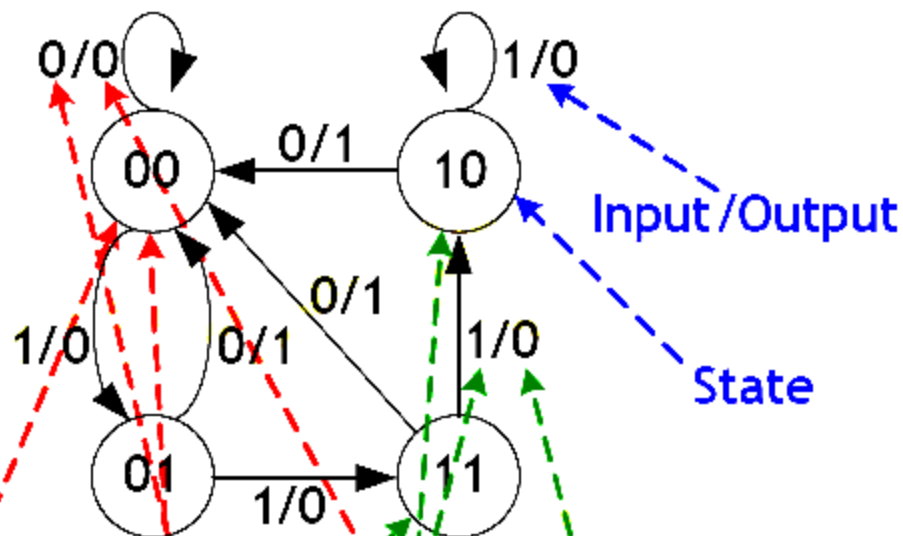


■ State Diagram

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
AB	AB	AB	y	y
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0


■ Analysis with D Flip-Flops

Circuit Diagram

 

$$A(t+1) = A \oplus x \oplus y$$

State Diagram

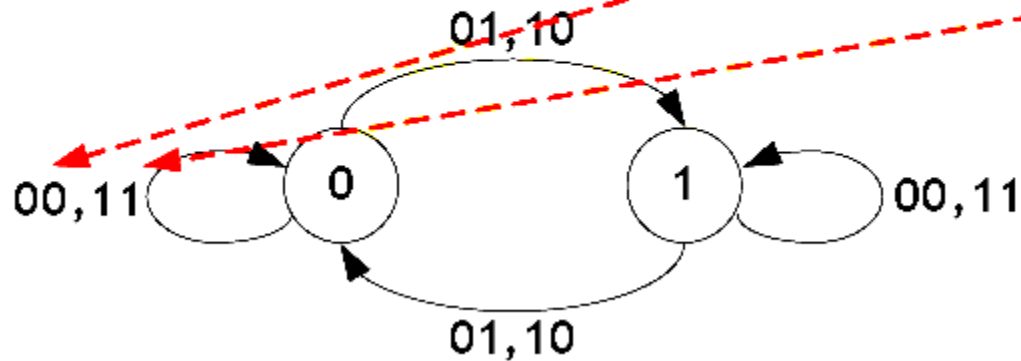


State Table

Present State	Inputs	Next State
A	x y	A
0	00	0
0	01	1
0	10	1
0	11	0
1	00	1
1	01	0
1	10	0
1	11	1

■ Analysis with JK Flip-Flops


Sequential Circuit with JK Flip-Flop

 

Flip=Flop Input Equations

$$\begin{cases} J_A = B \\ K_A = Bx' \end{cases}$$

$$\begin{cases} J_B = x' \\ K_B = A'x + Ax' = A \oplus x \end{cases}$$



■ **The next-state can be derived by following procedure**

1. Determine the flip-flop equations in terms of the present state and input variables
2. List the binary values of each input equation
3. Use the corresponding flip-flop characteristic table to determine the next state values in the state table


■ Analysis with JK Flip-Flops (Continued)

Sequential Circuit with JK Flip-Flop

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

1

2

- 
- The next-state can be obtained by evaluating the state equation from the characteristic equation
1. Determine the flip-flop equations in terms of the present state and input variables
 2. Substitute the input equations into the flip-flop characteristic equation to obtain the state equation
 3. Use the corresponding state equations to determine the next state values in the state table

■ Analysis with JK Flip-Flops (Continued)

JK Flip-Flop Characteristic Equations

$$\begin{cases} A(t+1) = JA' + K'A \\ B(t+1) = JB' + K'B \end{cases}$$


$$\begin{cases} A(t+1) = BA' + (Bx)'A = A'B + AB' + Ax \\ B(t+1) = x'B' + (A \oplus x)B = B'x' + ABx + A'Bx' \end{cases}$$

Flip-Flop Input Equations


$$\begin{cases} J_A = B \\ K_A = Bx' \end{cases}$$

$$\begin{cases} J_B = x' \\ K_B = A'x + Ax' = A \oplus x \end{cases}$$

Sequential Circuit with JK Flip-Flop

 


State Diagram

 

■ Analysis with T Flip-Flops

Sequential Circuit with T FF

 

Characteristic Equation

$$Q(t+1) = T \oplus Q = T'Q + TQ'$$

$$\begin{cases} T_A = Bx \\ T_B = x \\ y = AB \end{cases}$$


$$\begin{cases} A(t+1) = (Bx)'A + (Bx)A' = AB' + Ax' + A'Bx \\ B(t+1) = x \oplus B \end{cases}$$

■ Analysis with T Flip-Flops (Continued)

State Table

Present State AB	Input x	Next State AB	Output y
00	0	00	0
00	1	01	0
01	0	01	0
01	1	10	0
10	0	10	0
10	1	11	0
11	0	11	1
11	1	00	1

State Diagram

 

■ Mealy and Moore Models

Model Classification of Sequential Circuits

Mealy Model (Mealy FSM, Mealy Machine):


The output is a function of both the present state and input.

Moore Model (Moore FSM, Moore Machine):

The output is a function of present state only.

The output are synchronous with the clock.

Mealy FSM

 

■ State Diagram

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
AB	AB	AB	y	y
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0


■ Analysis with T Flip-Flops (Continued)

Moore FSM

State Table

Present State AB	Input x	Next State AB	Output y
00	0	00	0
00	1	01	0
01	0	01	0
01	1	10	0
10	0	10	0
10	1	11	0
11	0	11	1
11	1	00	1


State Diagram

 

■ State Reduction of Sequential Circuits

1. State Reduction: Lower the requirement of flip-flop
2. m flip-flop produce 2^m states
3. The characteristic of a sequential circuit: **input-output sequences** (not the internal circuits)

■ Example of State Reduction

 

Initial state a, I/O sequence:

State	a	a	b	c	d	e	f	f	g	f	g	a
Input	0	1	0	1	0	1	1	0	1	0	0	
Output	0	0	0	0	0	1	1	0	1	0	0	



■ Example of State Reduction (Continued)

State Table

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

■ Example of State Reduction (Continued)

State Table

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1

g replaced by e

■ Example of State Reduction (Continued)

State Table

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

■ Example of State Reduction (Continued)

State Table

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1

← f replaced by d


■ Example of State Reduction (Continued)

State Table

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1

■ Example of State Reduction (Continued)

State Diagram

 

Initial state a, I/O sequence:

State	a	a	b	c	d	e	d	d	e	d	e	a
Input	0	1	0	1	0	1	1	0	1	0	0	
Output	0	0	0	0	0	1	1	0	1	0	0	

■ State Assignment

Possible Binary State Assignments

State	Assignment 1 Binary	Assignment 2 Gray Code	Assignment 3 One-hot
a	000	000	00001
b	001	001	00010
c	010	011	00100
d	011	010	01000
e	111	110	10000

Reduced State Table with Binary Assignment 1

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
000	000	001	0	0
001	010	011	0	0
010	000	011	0	0
011	100	011	0	1
100	000	011	0	1

■ Design Procedure for Synchronous Sequential Circuits


1. Derive a state diagram
2. Reduce the number of states if necessary
3. Assign binary values to the state
4. Obtain the binary-coded state table
5. Choose the type of flip-flops to be used
6. Derive the simplified flip-flop input equations and output equations
7. Draw the logic diagram



■ Design Example: Problem Description

Design a circuit that detects three or more consecutive 1's in a string of bits coming through an input line.

State Diagram

 



■ State Reduction

- No State Reduction is possible for this example



■ Assign Binary Code to the States

$S_0 \Rightarrow 00$ (AB)

$S_1 \Rightarrow 01$ (AB)

$S_2 \Rightarrow 10$ (AB)

$S_3 \Rightarrow 11$ (AB)



■ Synthesis using D flip-flop

- Most easy way since
 $Q(t+1) = D$

■ List State Table with D FFs

State Table

	<u>Present State</u> <i>AB</i>	<u>Input</u> <i>x</i>	<u>Next State</u> <i>AB</i>	<u>Output</u> <i>y</i>
<i>m</i> ₀	00	0	00	0
<i>m</i> ₁	00	1	01	0
<i>m</i> ₂	01	0	00	0
<i>m</i> ₃	01	1	10	0
<i>m</i> ₄	10	0	00	0
<i>m</i> ₅	10	1	11	0
<i>m</i> ₆	11	0	00	1
<i>m</i> ₇	11	1	11	1


■ Find the Next State and Output Equations

$$\left\{ \begin{array}{l} A(t+1) = D_A(A, B, x) = \Sigma(3, 5, 7) \\ B(t+1) = D_B(A, B, x) = \Sigma(1, 5, 7) \\ y = (A, B, x) = \Sigma(6, 7) \end{array} \right.$$




$$\left\{ \begin{array}{l} D_A = AX + BX \\ D_B = AX + B'x \\ y = AB \end{array} \right.$$


Logic Simplification

 

$$D_A = Ax + Bx$$

 


$$D_B = Ax + B'x$$

 

$$y = AB$$

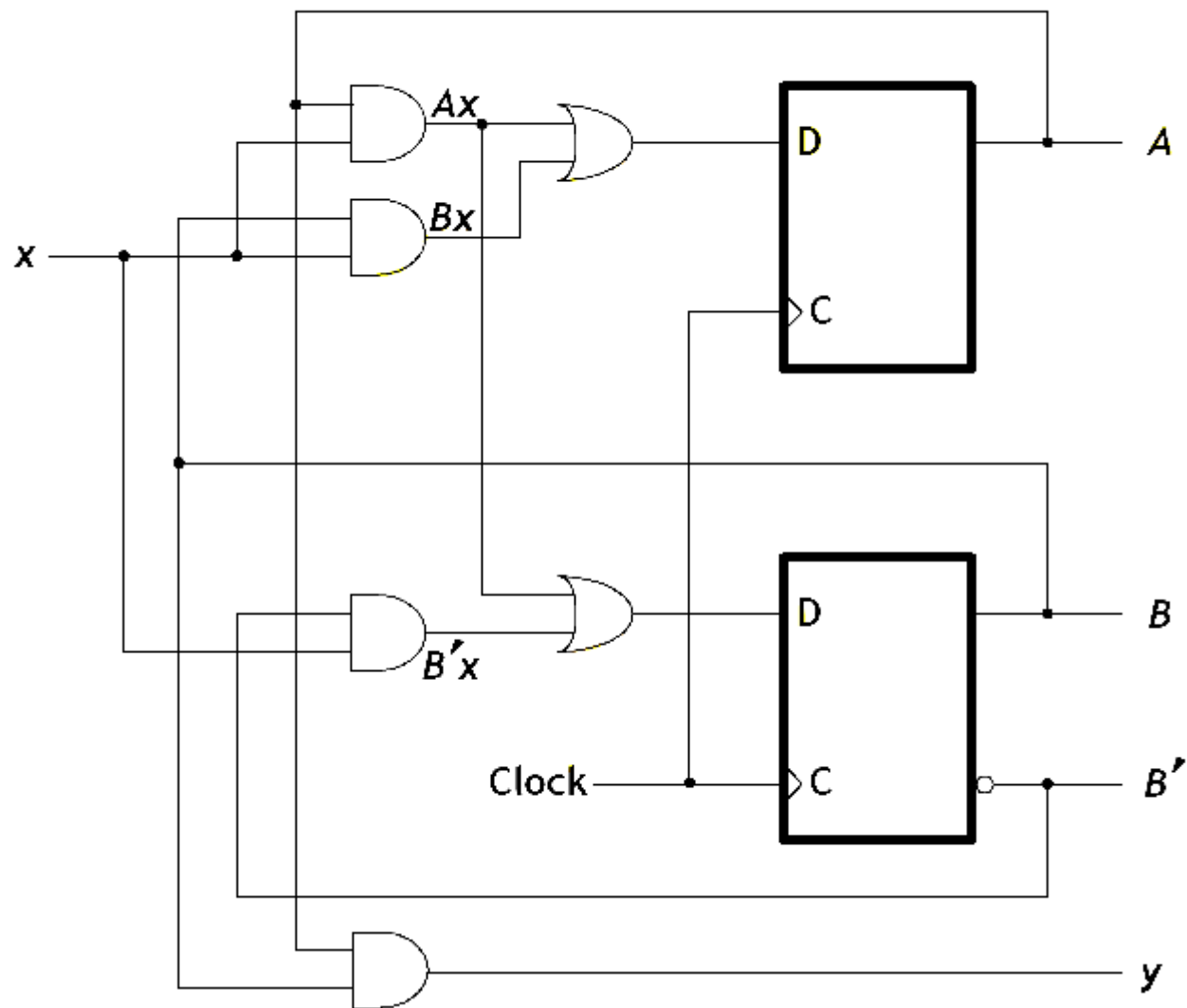■ Draw the Logic Diagram of Sequential Circuits



■ Excitation Tables

A table lists the **required inputs** for a given **change of state**. $Q(t) \Rightarrow Q(t+1)$

JK Flip-Flop

J	K	$Q(t+1)$	
0	x	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

→

$Q(t)$	$Q(t+1)$	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Excitation Table

Characteristic Table

Excitation Table

■ Excitation Tables (Continued)

T Flip-Flop

T	$Q(t+1)$
0	$Q(t)$ No Change
1	$Q'(t)$ Complement



$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

■ Synthesis Using JK Flip-Flops

State Table

Present State		Input	Next State		Flip-Flop Input			
AB	x		AB	J_A	K_A	J_B	K_B	
00	0	00	0	x	0	x		
00	1	01	0	x	1	x		
01	0	10	1	x	x	1		
01	1	01	0	x	x	0		
10	0	10	x	0	0	x		
10	1	11	x	0	1	x		
11	0	11	x	0	x	0		
11	1	00	x	1	x	1		

■ K-Map Logic Simplification

$$J_A = Bx'$$

		B=1			
		00	01	11	10
A=1 {	0			1	
	1	x	x	x	x
		x=1			

$$K_A = Bx$$

		B=1			
		00	01	11	10
A=1 {	0	x	x	x	x
	1		1		
		x=1			


$$J_B = x$$

		B=1			
		00	01	11	10
A=1 {	0	1	x	x	
	1	1	x	x	
		x=1			

$$K_B = (A \oplus x)'$$

		B=1			
		00	01	11	10
A=1 {	0	x	x	1	
	1	x	x	1	
		x=1			

 ■ Draw the Sequential Circuits with JK FFs




■ Synthesis Using T Flip-Flops

Design Example: 3-bit Binary Counter Using T FFs

- 1. N-bit binary counter consists of n flip-flops**
- 2. N-bit binary counter can count 0 to 2^n-1**
- 3. 3-bit counter 0 to 7**
- 4. 3-bit counter internal states 000 to 111**

State Diagram and State Table of 3-bit Binary Counter

State Diagram



 


State Table

Present State	Next State	Flip-Flop Inputs
$A_2 A_1 A_0$	$A_2 A_1 A_0$	$T_{A2} T_{A1} T_{A0}$
0 0 0	0 0 1	0 0 1
0 0 1	0 1 0	0 1 1
0 1 0	0 1 1	0 0 1
0 1 1	1 0 0	1 1 1
1 0 0	1 0 1	0 0 1
1 0 1	1 1 0	0 1 1
1 1 0	1 1 1	0 1 1
1 1 1	0 0 0	1 1 1

Refer to T-FF Excitation Table

   K-Map Logic Simplification for 3-bit Binary Counter



■ Draw the 3-bit Binary Counter Circuits with T FFs

