



Faculty of Engineering

CSE115: Digital Design

**Lecture 11:
Simplifying Product of Sums**

Suggested Reading

- Sections 4.3.6

Simplifying the Product of Sums

1. **Plot 0s** corresponding to **maxterms** of function.
2. **Circle largest** possible rectangular **sets of 0s**.
 - # of 0s in set must be power of 2
 - OK to cross edges
3. Read off product terms, one per circled set.
 - Variable is 0 \rightarrow include variable
 - Variable is 1 \rightarrow include complement of variable
 - Variable is both 1 and 0 \rightarrow variable not included
4. Circled sets and corresponding product terms are called '**prime implicants**'
5. Minimum number of gates and gate inputs

Example 1

The prime implicants:


Cells (0,1,8,9): $X=0, Y=0$

The sum term: $X+Y$

Cells (8,10,12,14): $W=1, Z=0$

The sum term: $W'+Z$

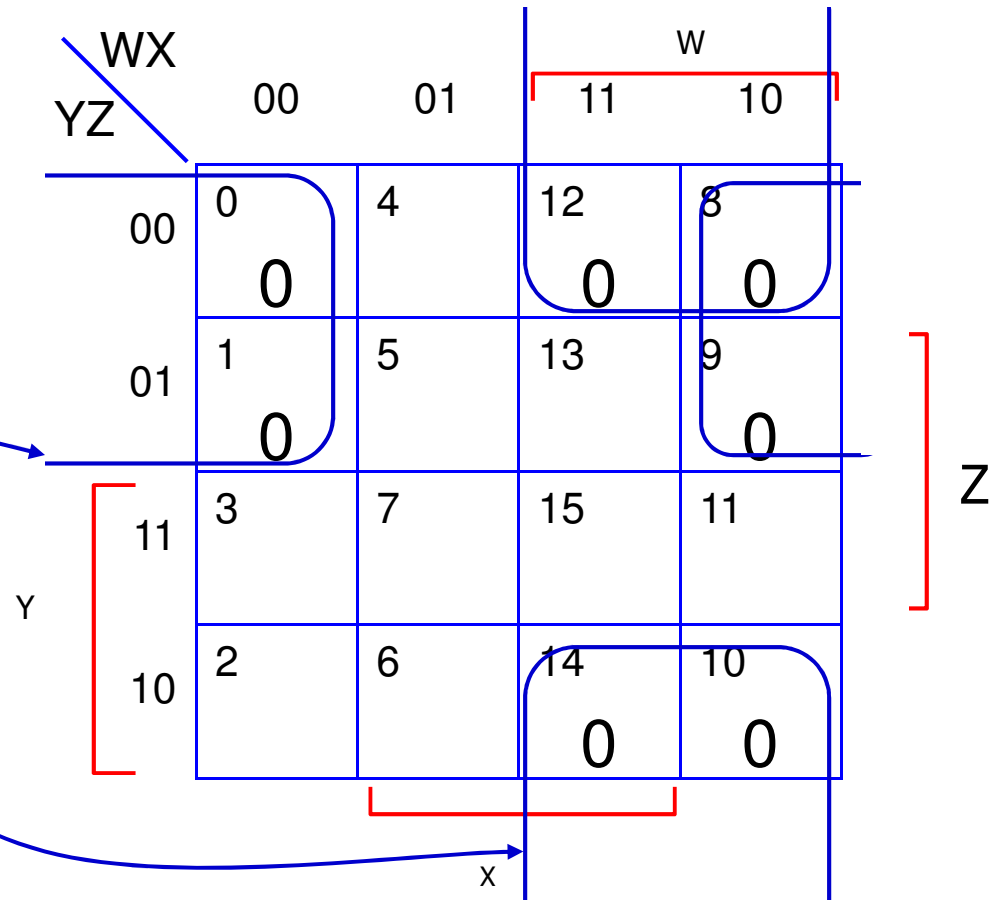
The two prime implicants are essential prime implicants and cover all zeros



The minimal product of sums: $F = (X + Y) \cdot (W' + Z)$

Exercise

Row	W	X	Y	Z	F
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	0

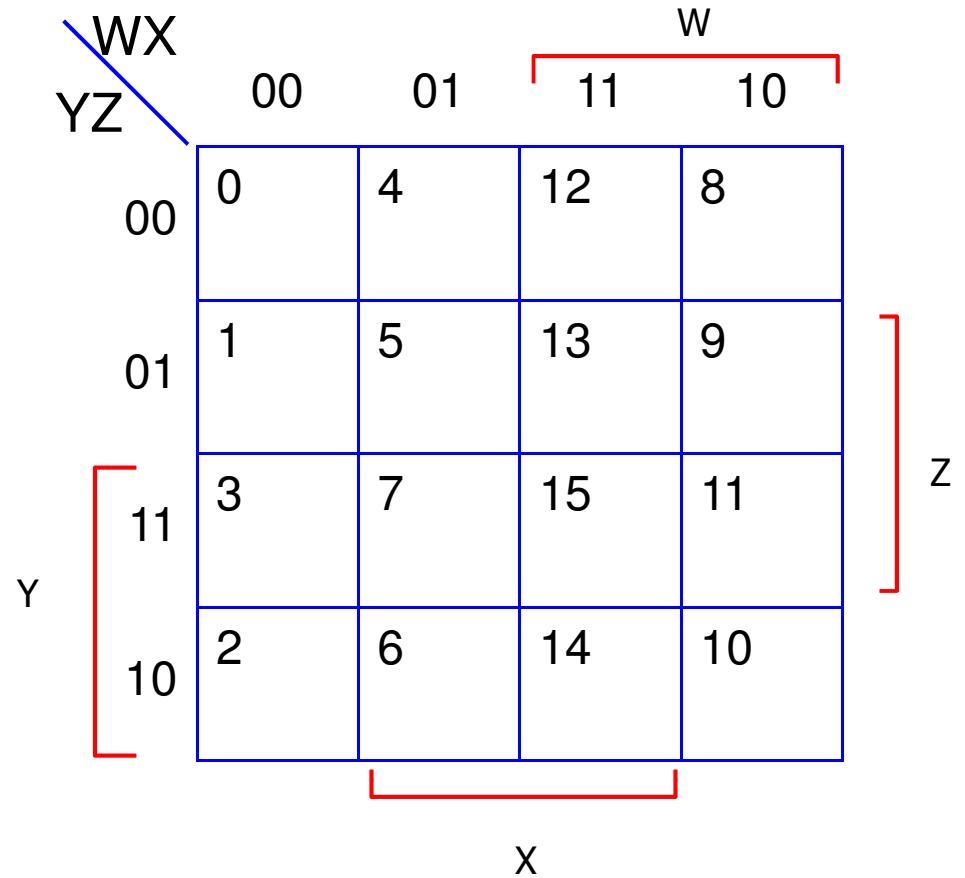

Essential prime implicants:

(3,7,15,11): $Z=1, Y=1$; The sum term: $Z'+Y'$

(10,11): $W=1, X=0, Y=1$; The sum term: $W'+X+Y'$

$$F=(Z'+Y').(W'+X+Y')$$

Simplifying POS - Another method


Complement the function. Use K-map to get the **minimal sum** of the complement function. **Complement the minimal sum** to get the minimal product

1. The function is complemented and represented using K-map:

2. The essential prime implicants are:
 WZ' , $X'Y$

3. The minimal Sum: $M = X'Y' + WZ'$

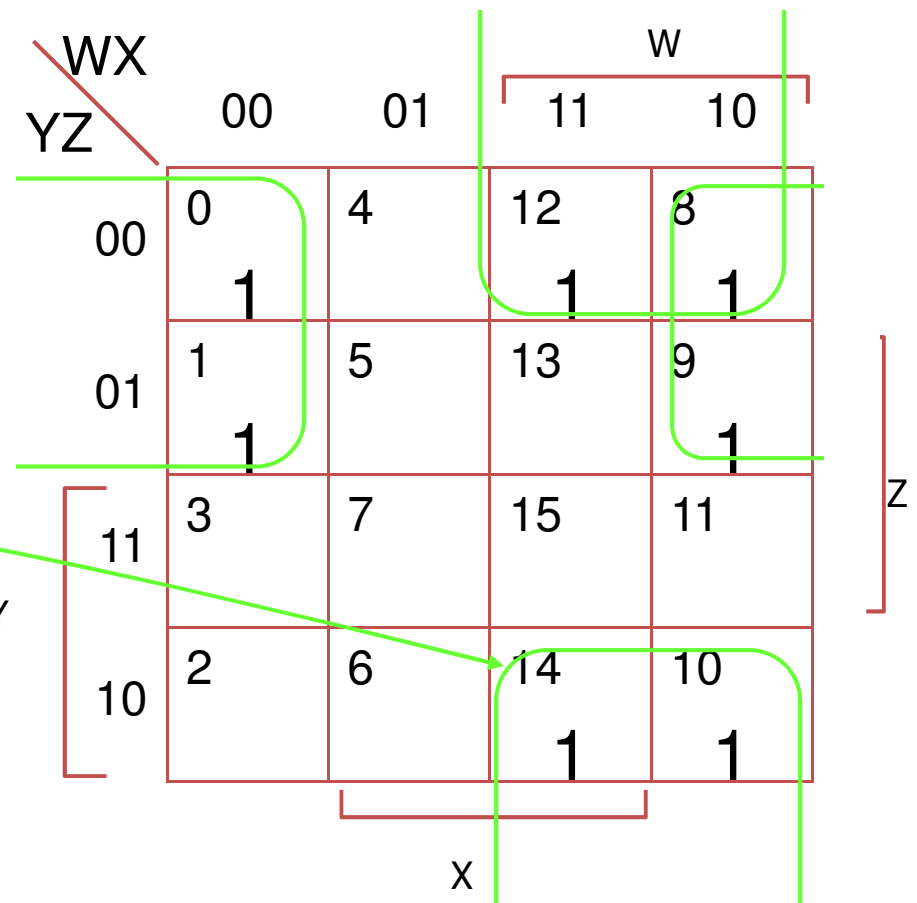4. $F = M' = (X'Y' + WZ')' = (X+Y).(W'+Z)$



Minimal Product of Sums vs. Minimal Sum of Products:

Compare the minimal product and the minimal sum designs to find the best (least # of gates) realization.


In the previous example:

The minimal sum is: $F = W'X + W'Y + XZ + YZ$


The minimal product: $F = (X + Y) \cdot (W' + Z)$

∴ The **minimal product** implementation is cheaper.

Prime-Number Detector (again)

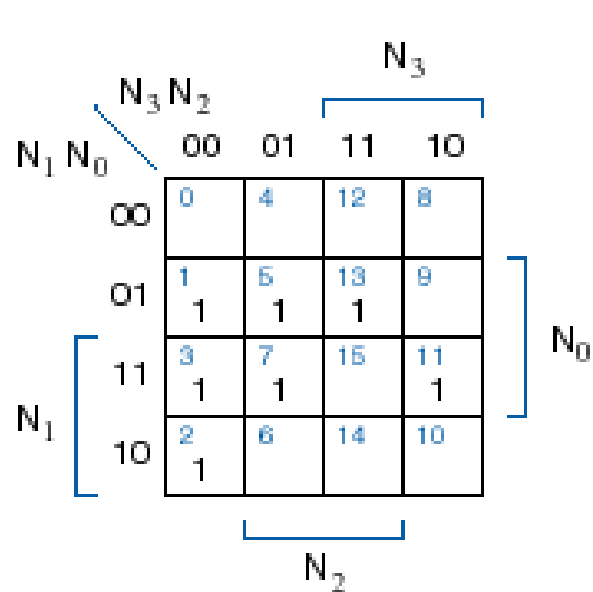

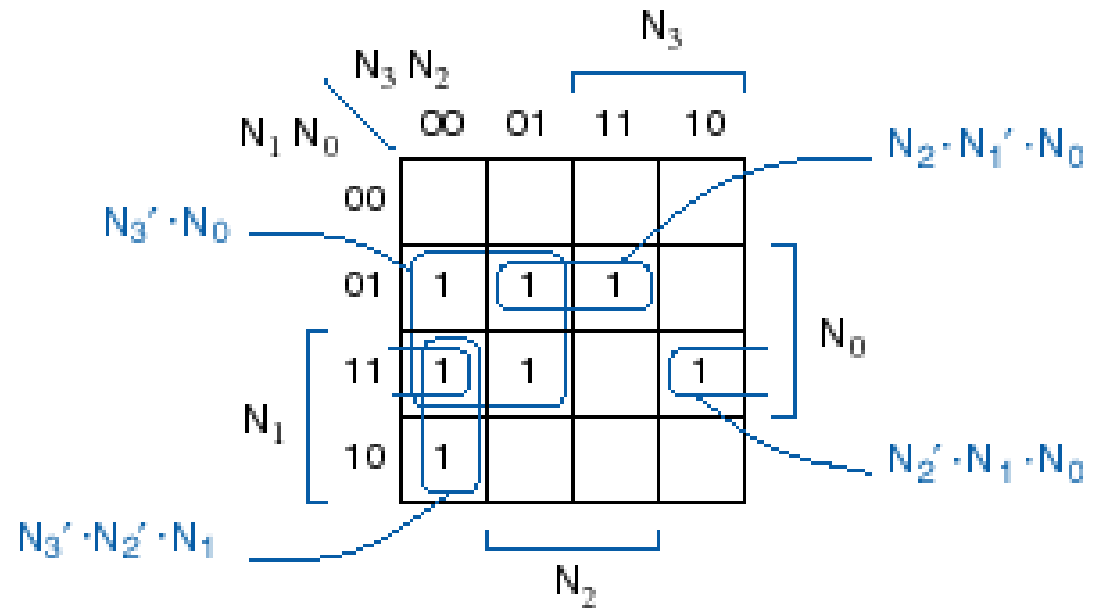
$$F = \sum_{N_3, N_2, N_1, N_0} (1, 2, 3, 5, 7, 11, 13)$$



$$F = N_3' \cdot N_0 + N_3' \cdot N_2' \cdot N_1 + N_2' \cdot N_1 \cdot N_0 + N_2 \cdot N_1' \cdot N_0$$

Prime-Number detector (contd.)

When we solved algebraically, we missed one simplification -- the circuit below has three less gate inputs.

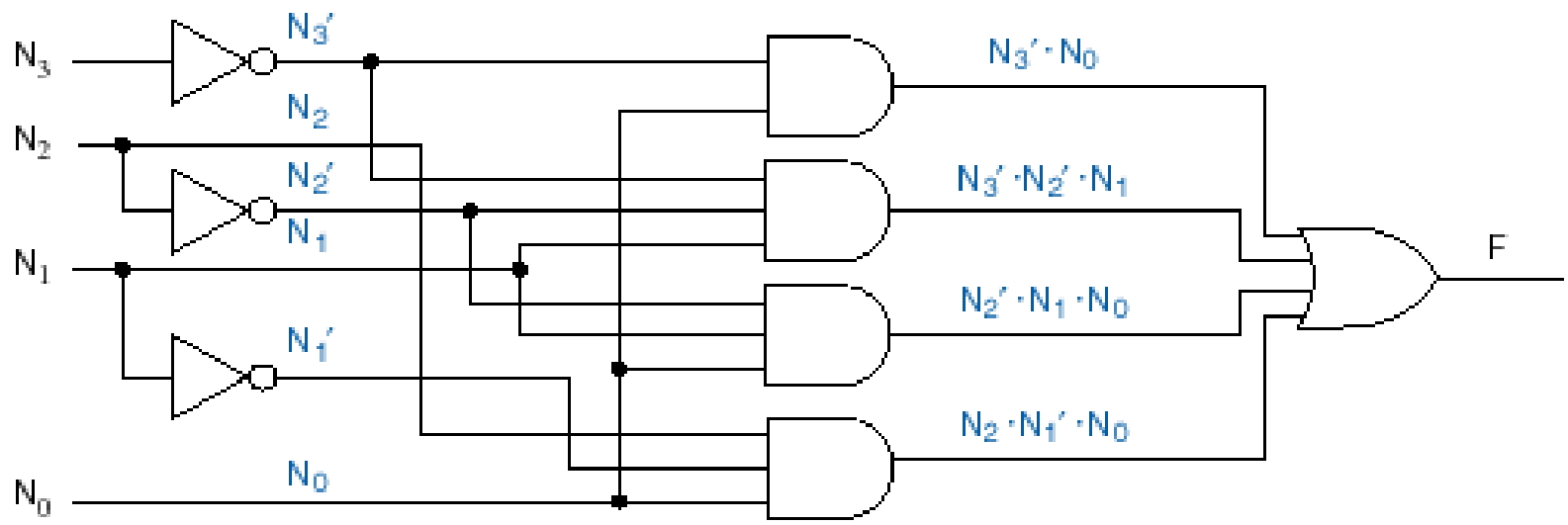

Example 2

		W X		W	
		00	01	11	10
Y Z	00	0	4	12 1	8
	01	1	5 1	13 1	9
	11	3	7 1	15 1	11
	10	2	6	14 1	10

X

Z

$$F = \Sigma_{W,X,Y,Z}(5,7,12,13,14,15)$$

		W X		W	
		00	01	11	10
Y Z	00			1	
	01		1	1	
	11		1	1	
	10			1	

X

Z

$$F = X \cdot Z + W \cdot X$$

Example 3

		WX		W		
		00	01	11	10	
YZ	00	0	4 1	12 1	8	Z
	01	1	5 1	13 1	9 1	
Y	11	3 1	7	15 1	11 1	
	10	2	6 1	14 1	10	
		X				

$$F = \sum_{W,X,Y,Z}(1, 3, 4, 5, 9, 11, 12, 13, 14, 15)$$

		WX		W		
		00	01	11	10	
YZ	00		1	1		Z
	01	1	1	1	1	
Y	11	1		1	1	
	10			1		
		X				

$$F = X \cdot Y' + X' \cdot Z + W \cdot X$$