



Faculty of Engineering

CSE115: Digital Design

**Lecture 12:
Don't Care Conditions**

Suggested Reading

- Sections 4.3.7-4.3.8

Don't Care Conditions

In some applications, the Boolean function for certain combinations of the input variables is not specified. The corresponding minterms (maxterms) are called “don't care minterms(maxterms)”.

In K-map , these are represented by 'x'.

Since the output function for those minterms(maxterms) is not specified, those minterms(maxterms) could be combined with the adjacent 1 cells (0-cells) to get a more simplified sum-of-products (product-of-sums) expression.

Example 1

- Build a logic circuit that determines if a **decimal digit** is ≥ 5
 1. The decimal digits (0,1,2,...,9) are represented by 4 bit BCD code.
 2. The logic circuit should have **4 input** variables and **1 output**.
 3. There are 16 different input combinations but only 10 of them are used.
 4. The logic function should produce 0 if the number is < 5 , and 1 if it is ≥ 5 .

Example 1 (Contd.): Truth Table

Row	W	X	Y	Z	F
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	x
11	1	0	1	1	x
12	1	1	0	0	x
13	1	1	0	1	x
14	1	1	1	0	x
15	1	1	1	1	x

Example 1(Contd.)- K-Map


The Minimal Sum:

Combining the '1' cells only,
the minimal sum is:

$$F = WX'Y' + W'XZ + W'XY$$

Combining the don't care
minterms with the '1' cells,
the minimal sum is:


$$F = W + XZ + XY$$

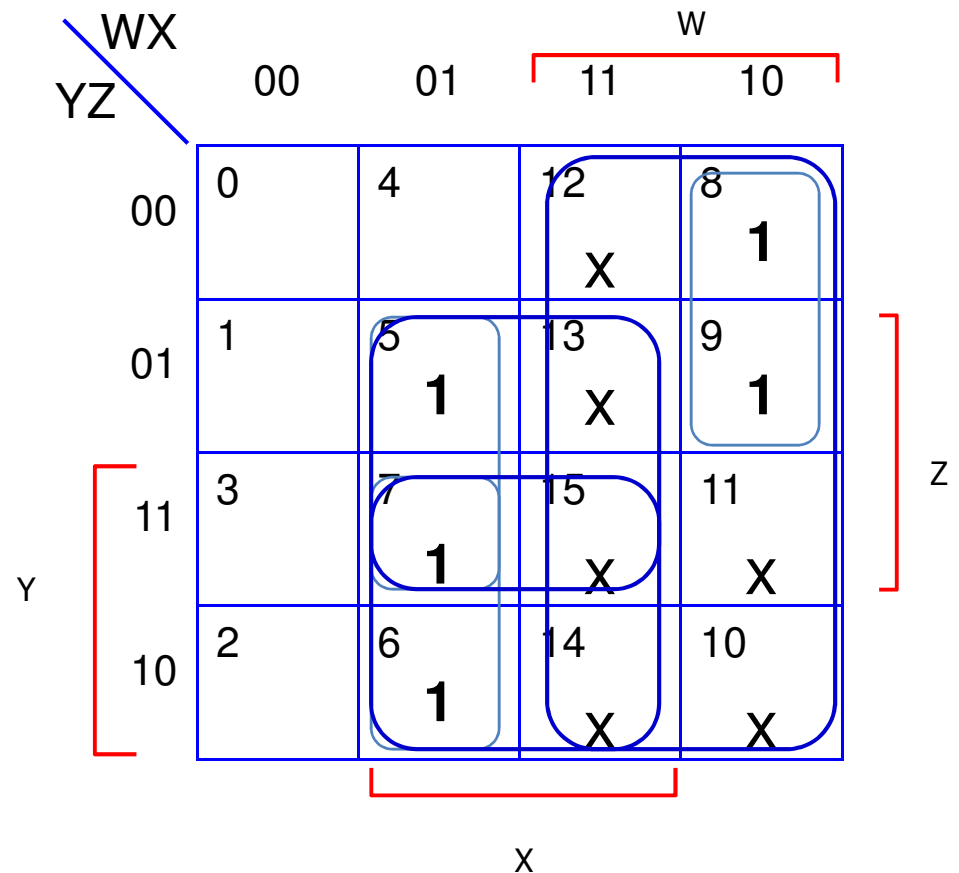

Example 1 (Cont.): Minimal Product


The Minimal Product:

$$F = (W+X).(W+Y+Z)$$


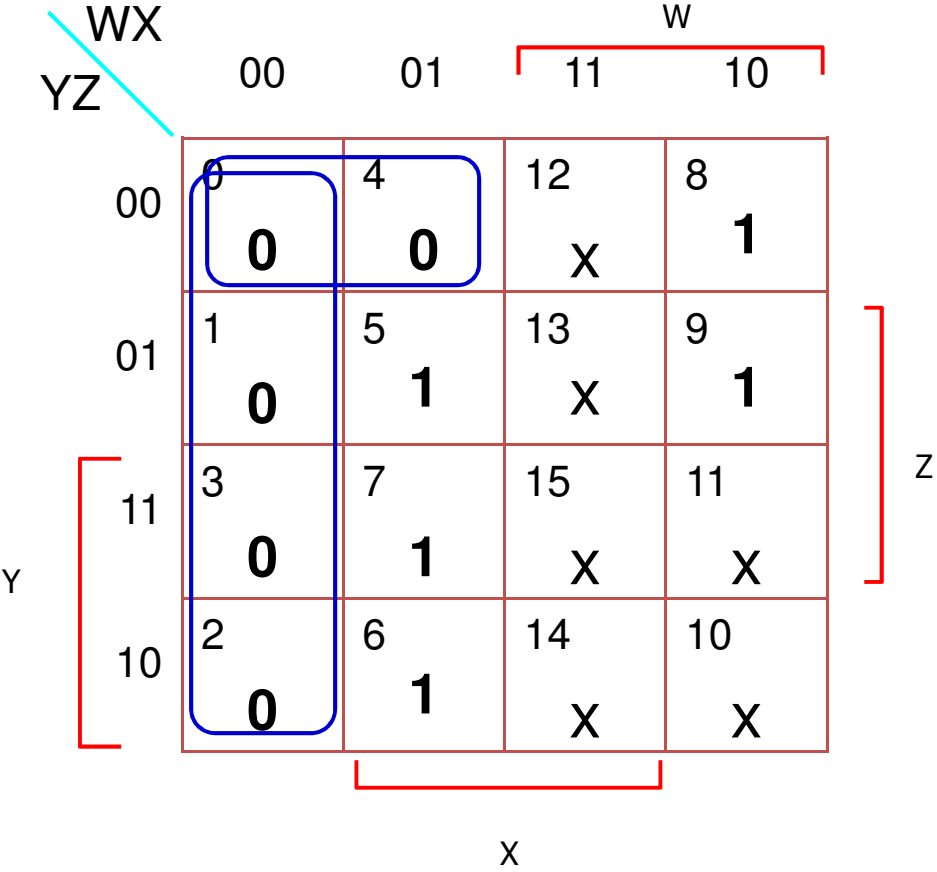


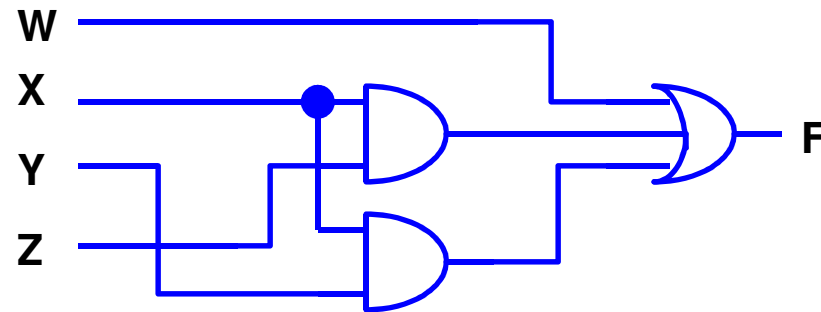Example 1 (Contd.): Implementation

The minimal sum implementation: $F = W + XZ + XY$




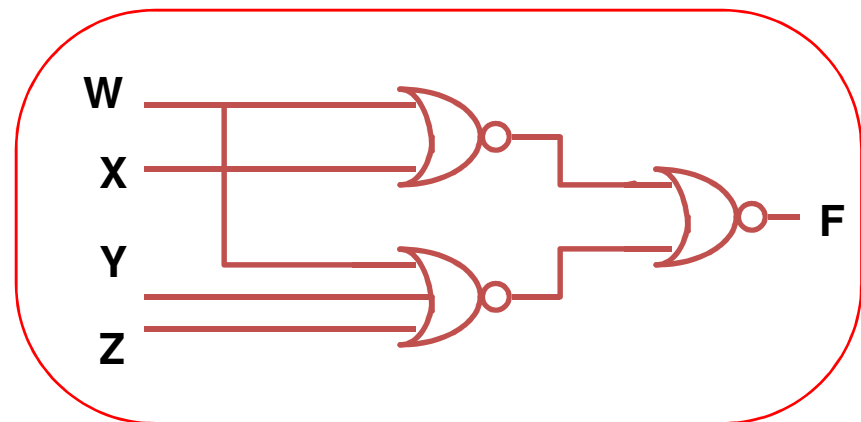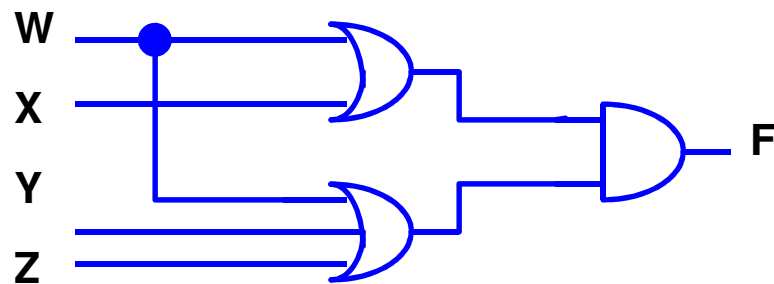The minimal product implementation: $F = (W + X) \cdot (W + Y + Z)$



Multiple-Output Minimization

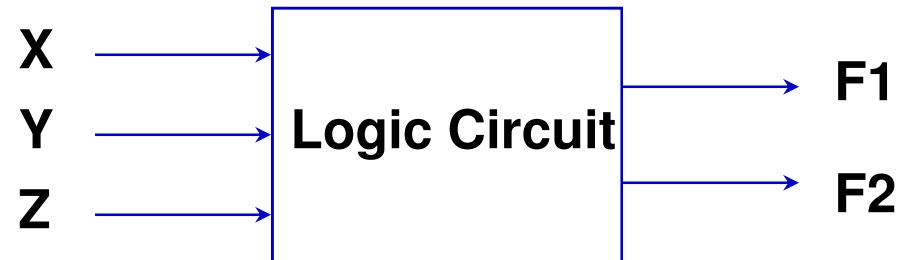Most digital applications require multiple outputs derived from the same input variables.






1. Each output function could be minimized using K-map and realized independently.
2. The output functions could share one or more product terms (prime implicant) which reduces the total number of gates.

Example 2

$$F1 = XZ + YZ'$$

$$F2 = XY' + YZ'$$

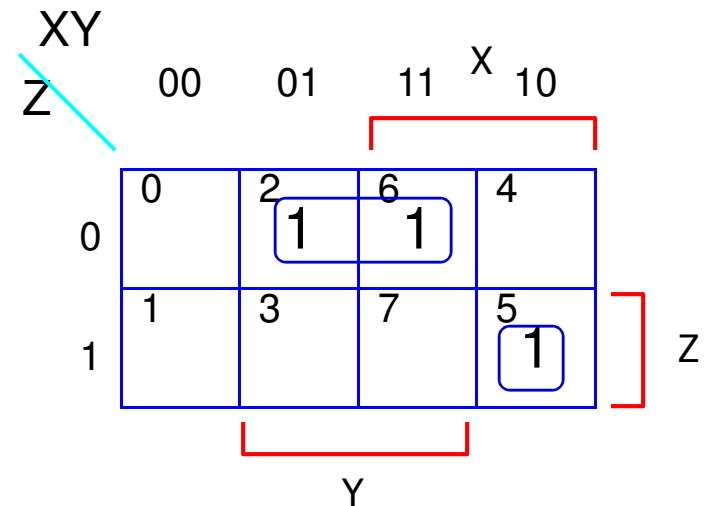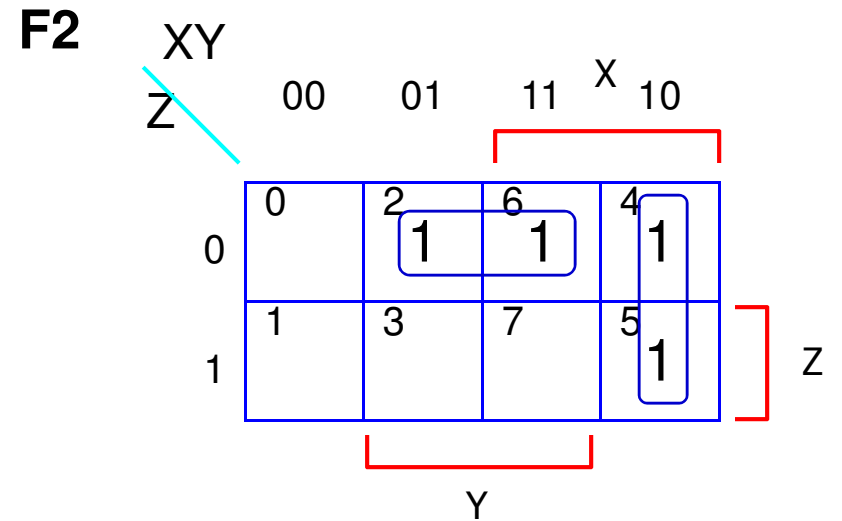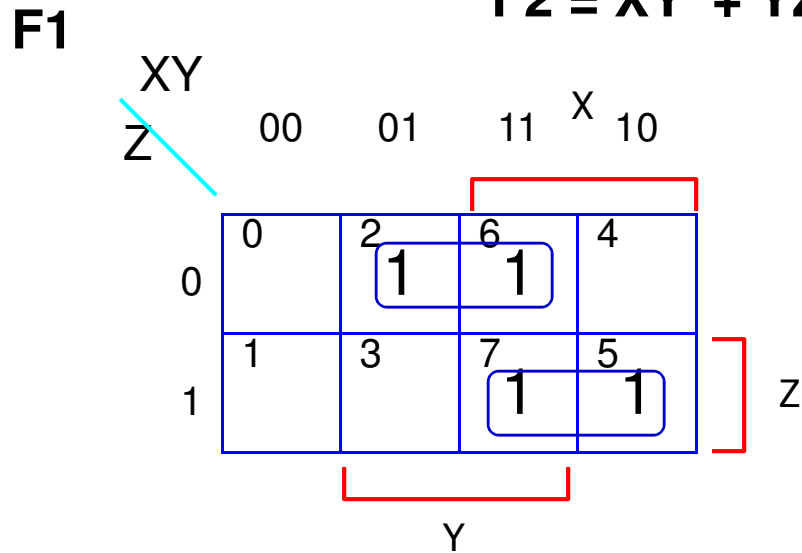

To find the common terms multiply the two functions (F1.F2)

The common terms are: **YZ'** , **$XY'Z$**

Example 2 (Contd.) – Logic Diagram

Independent realization
Minimal realization

$$F1 = XZ + YZ'$$

$$F2 = XY' + YZ'$$

