



Faculty of Engineering

CSE115: Digital Design

Lecture 13:
Combinational Logic Design Practices


Suggested Reading

- Sections 5.1-5.2

Documentation Standards

- Block Diagrams
 - First step in hierarchical design
- Schematic Diagrams
- HDL Programs (ABEL, Verilog, VHDL)
- Timing Diagrams
- Circuit Descriptions


Block Diagram

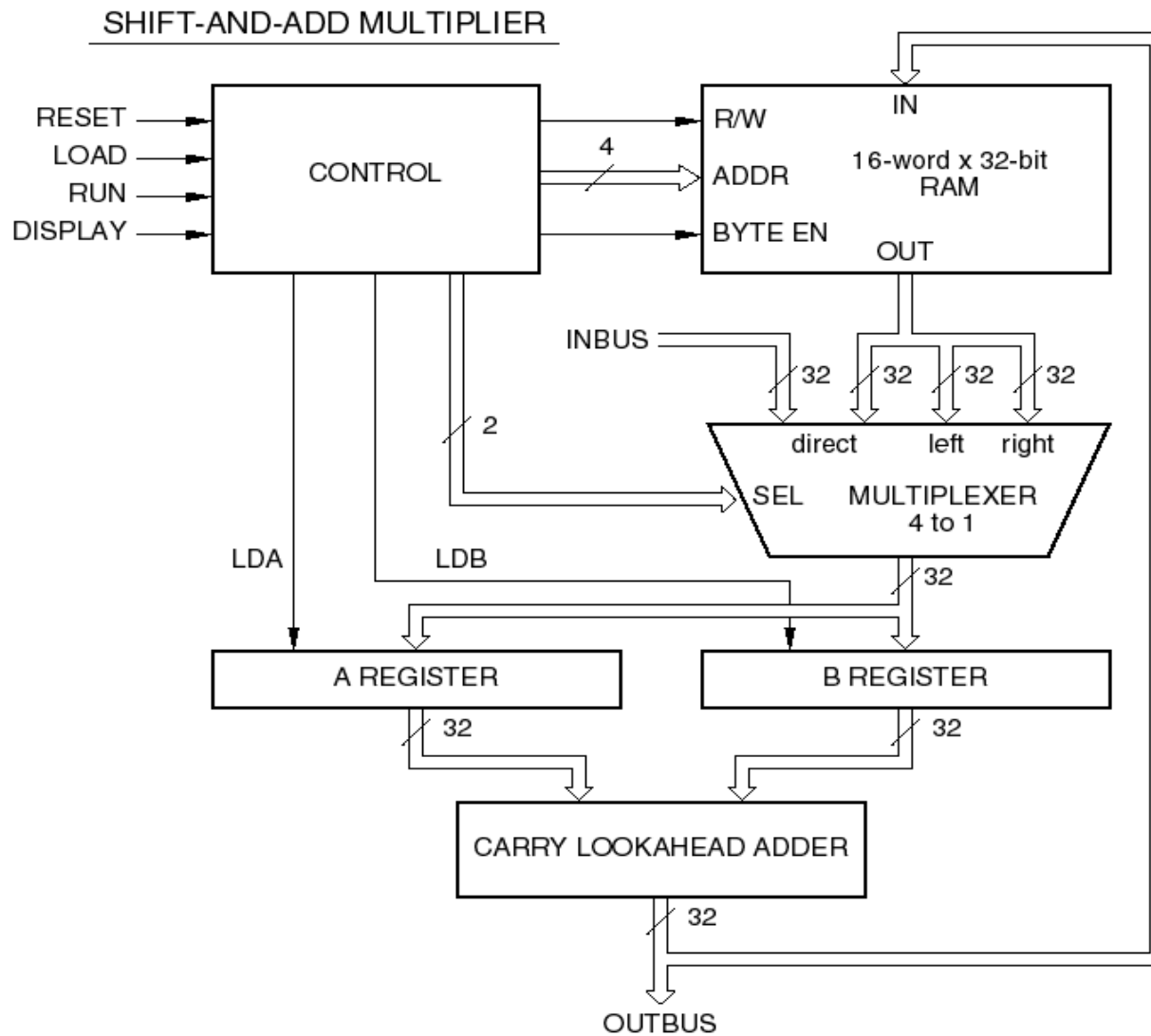

Schematic Diagrams


- Details of component inputs, outputs, and interconnections
- Pin numbers
- Title blocks
- Names for all signals
- Page-to-page connectors

Example Schematic

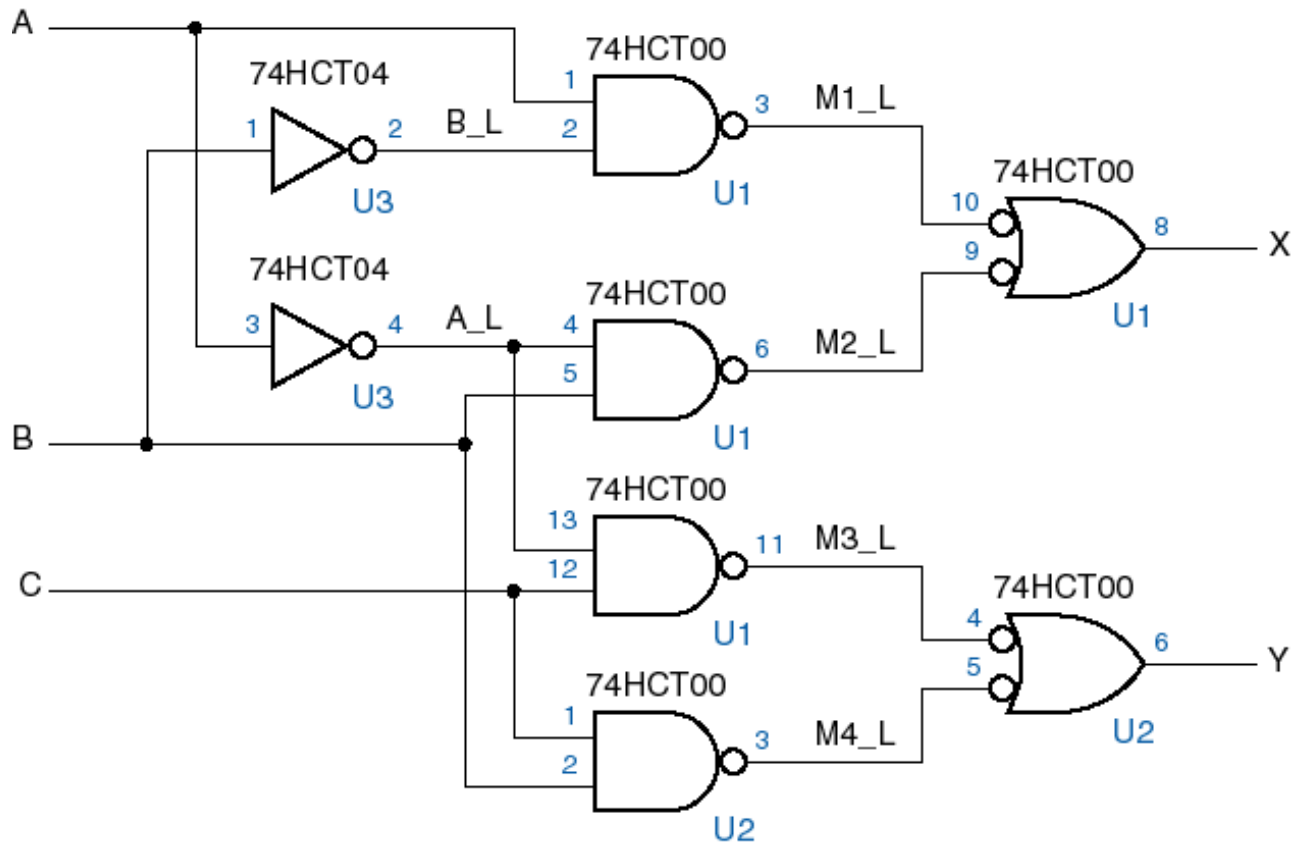


Schematic diagram/Logic Diagram


Logic Diagram

 


Schematic Diagram

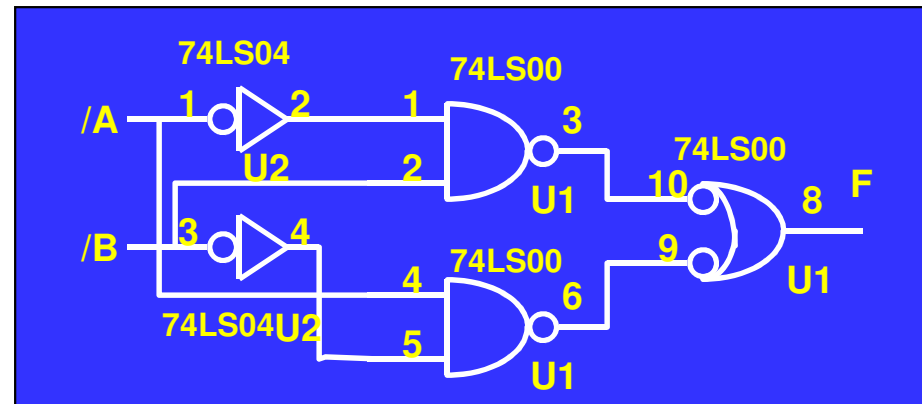

Flat Schematic Structure

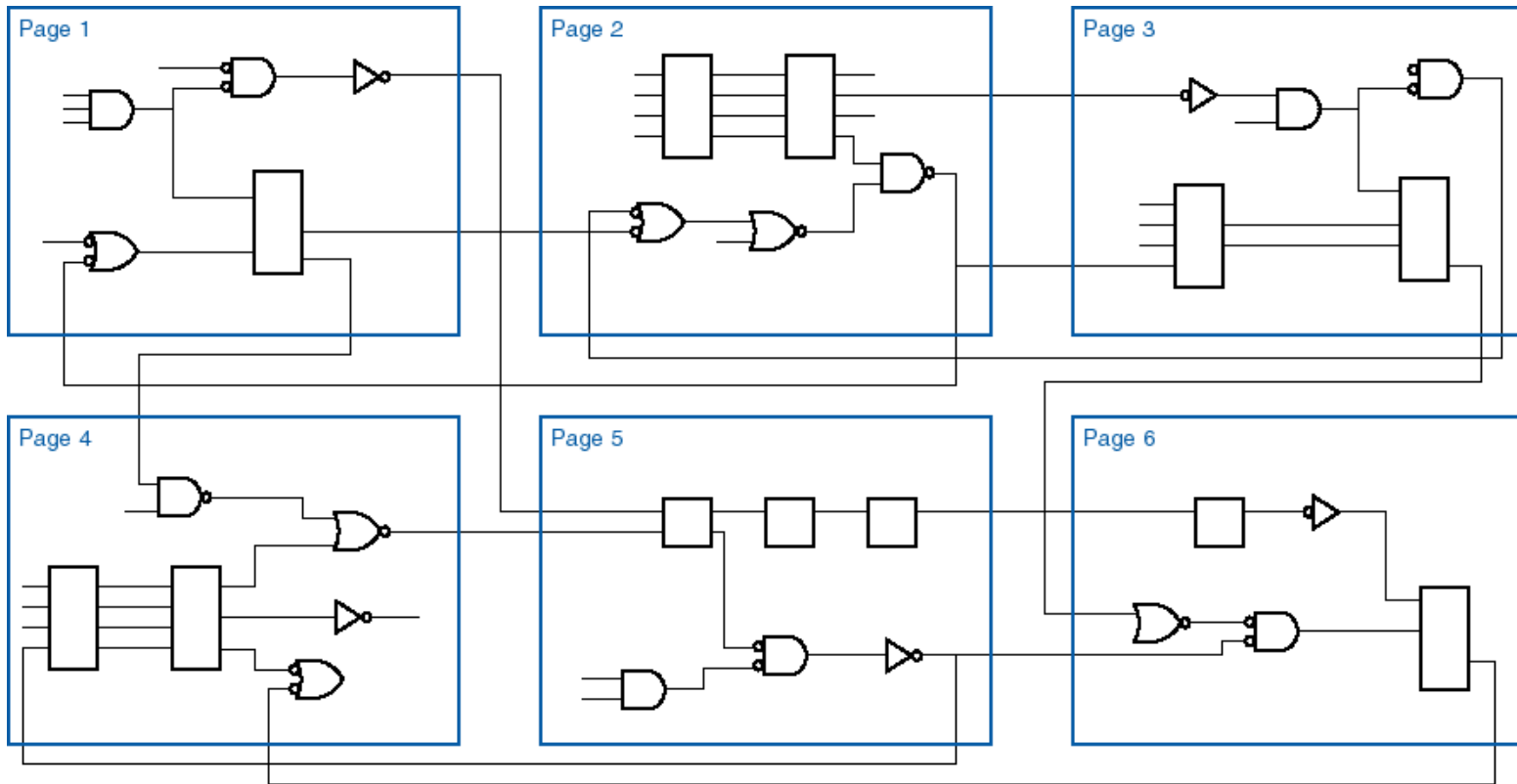

Hierarchical Schematic Structure

 

Other Documentation









Timing diagrams

- Output from simulator
- Specialized timing-diagram drawing tools


Circuit descriptions

- Text (word processing)
- Can be as big as a book (e.g., typical Cisco ASIC descriptions)
- Typically incorporate other elements (block diagrams, timing diagrams, etc.)

Gate Symbols

        

DeMorgan Equivalent Symbols

 

Which symbol to use?

Answer depends on signal **names** and **active levels**.


Signal Names and Active Levels

Signal names are chosen to be descriptive.

Active levels: HIGH or LOW

<i>Active Low</i>	<i>Active High</i>
READY-	READY+
ERROR.L	ERROR.H
ADDR15(L)	ADDR15(H)
RESET*	RESET
ENABLE~	ENABLE
~GO	GO
/RECEIVE	RECEIVE
TRANSMIT_L	TRANSMIT


Example

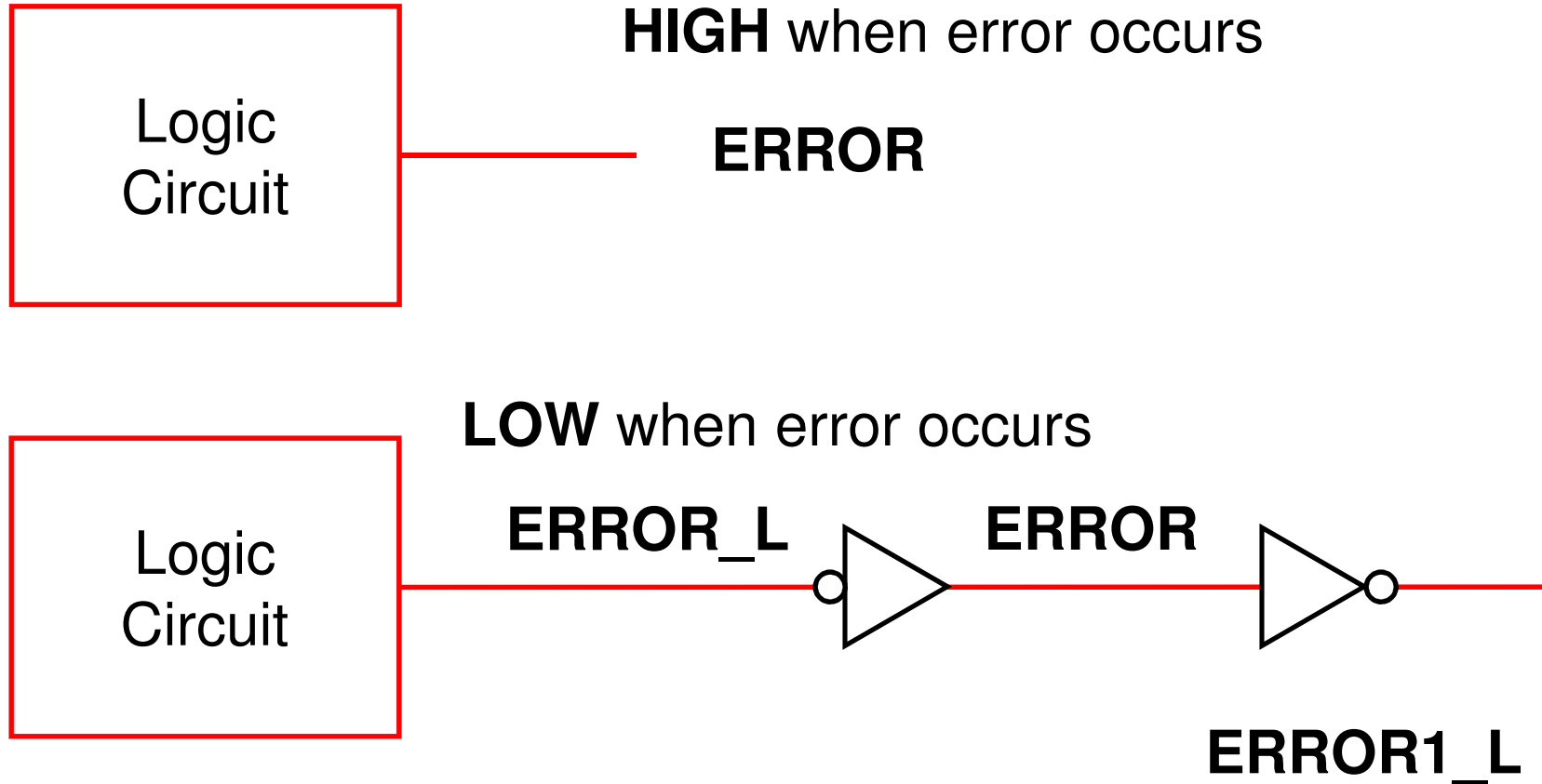

Active Levels for Pins

In logic gates and logic structures the **inversion bubble** indicates the **active** level of the signal


Examples: 2-to-4 Decoder

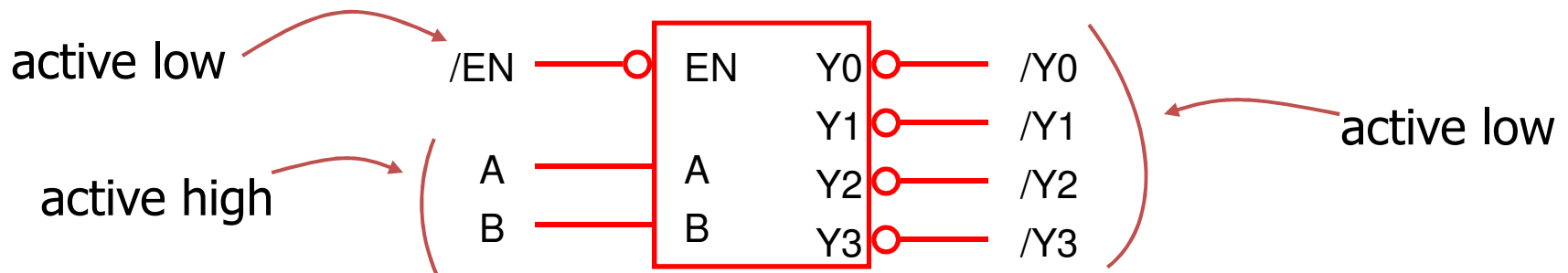


Bubble-to-Bubble Logic Design

Rules:

 The active level of the **output signal** of a logic device should match the active level of the device's **output pin**.





 The active level of the **input signal** of a logic device should match the active level of the device's **input pin**.



Bubble-to-Bubble Logic Design

 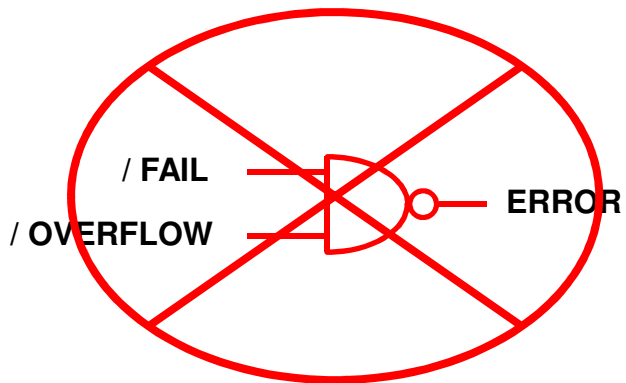Purpose: To make it easy to understand the function of the Logic circuit



Drawing Layouts


Inputs to the left, outputs to the right. Signals flow from left to right.

Crossing lines/Connected lines (T-type connection)




Buses should be named: DATA[0-7], CONTROL

 
A signal extracted from a bus should be named



 Broken signal paths should be flagged to indicate the source or destination and direction.





Timing Diagrams


 


Delay depends on

  - Internal circuit structure
- Logic Family type
- Source Voltage
- Temperature



Timing Diagram for Data Signals (Bus)

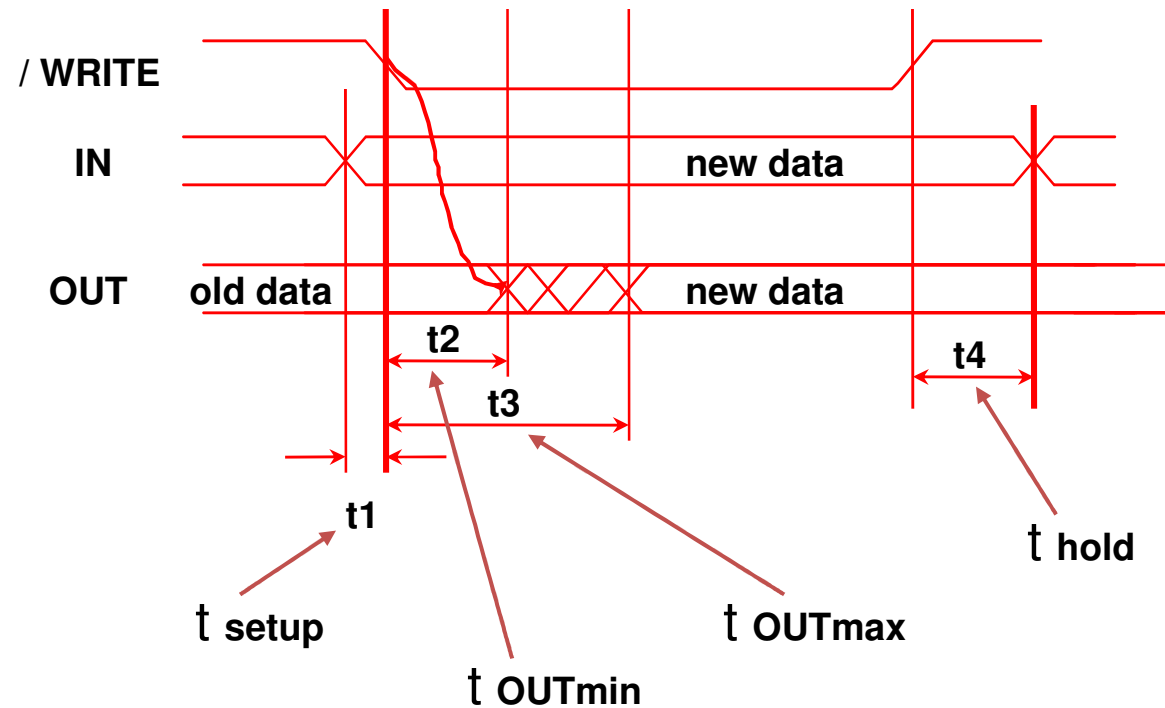 

Propagation Delay

The Propagation Delay is the delay time between input transitions and the output transitions due to the propagation delay of the the logic gates

t_p of a signal depends on the signal path inside the logic circuit

To find t_p for a signal, add the propagation delays of all gates along the path of the signal

For a logic gate t_{pLH} may not equal t_{pHL}

t_p is specified in the manufacturer data sheets of the IC's

Example:	Typical (ns)		Maximum (ns)	
	t_{pLH}	t_{pHL}	t_{pLH}	t_{pHL}
74LS00	9	10	15	15
74ACT00	5.5	4.0	9.5	8.0