



Faculty of Engineering

CSE115: Digital Design

Lecture 14:
Programmable Logic Arrays

Suggested Reading

- Sections 5.3

Programmable Logic Arrays (PLAs)

Any combinational logic function can be realized as a sum of products.

Idea: Build a large AND-OR array with lots of inputs and product terms, and programmable connections.

- n inputs


AND gates have $2n$ inputs -true and complement of each variable

- m outputs, driven by large OR gates


Each AND gate is programmably connected to each output's OR gate

- p AND gates ($p \ll 2^n$)

Example: 4x3 PLA, 6 Product Terms

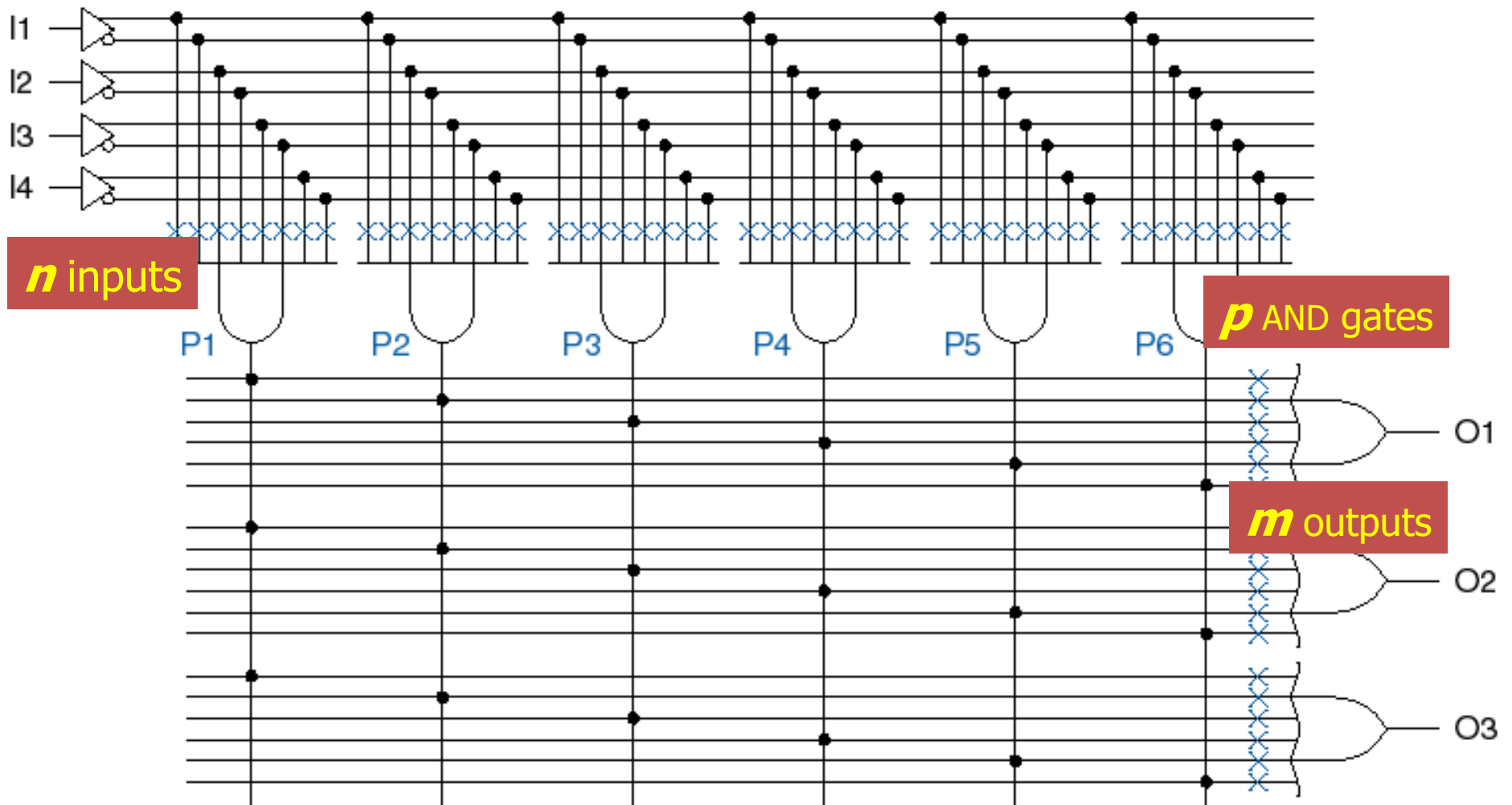


Compact Representation

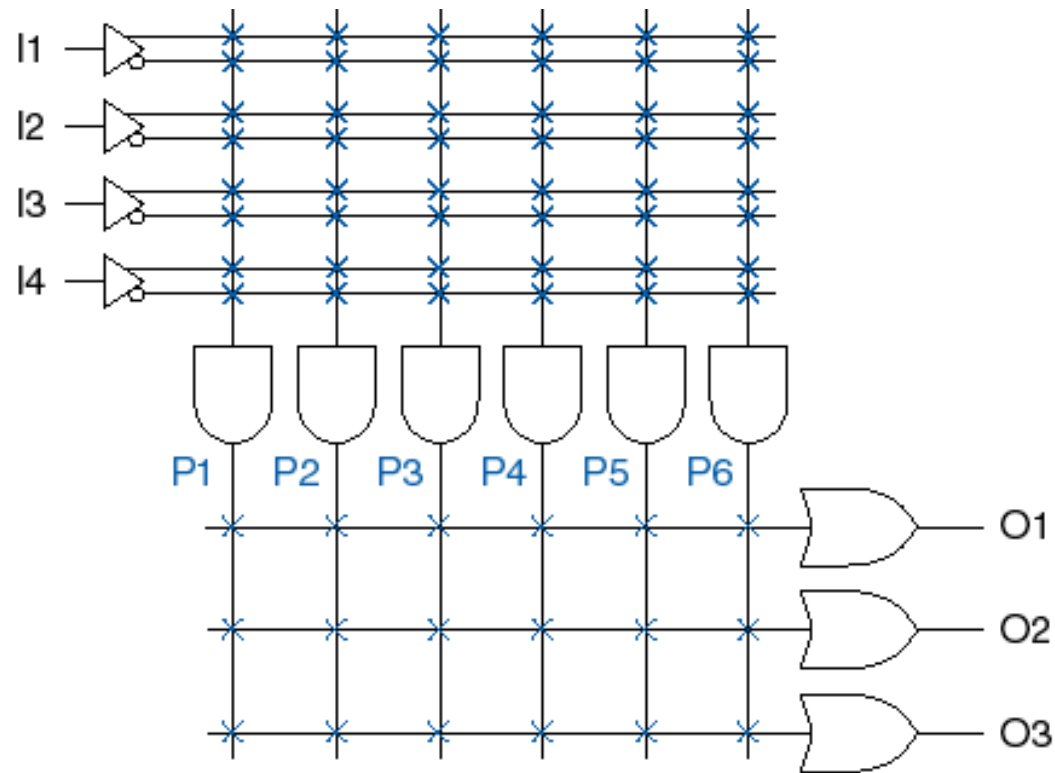


Actually, closer to physical layout ('wired logic')

Some Product Terms

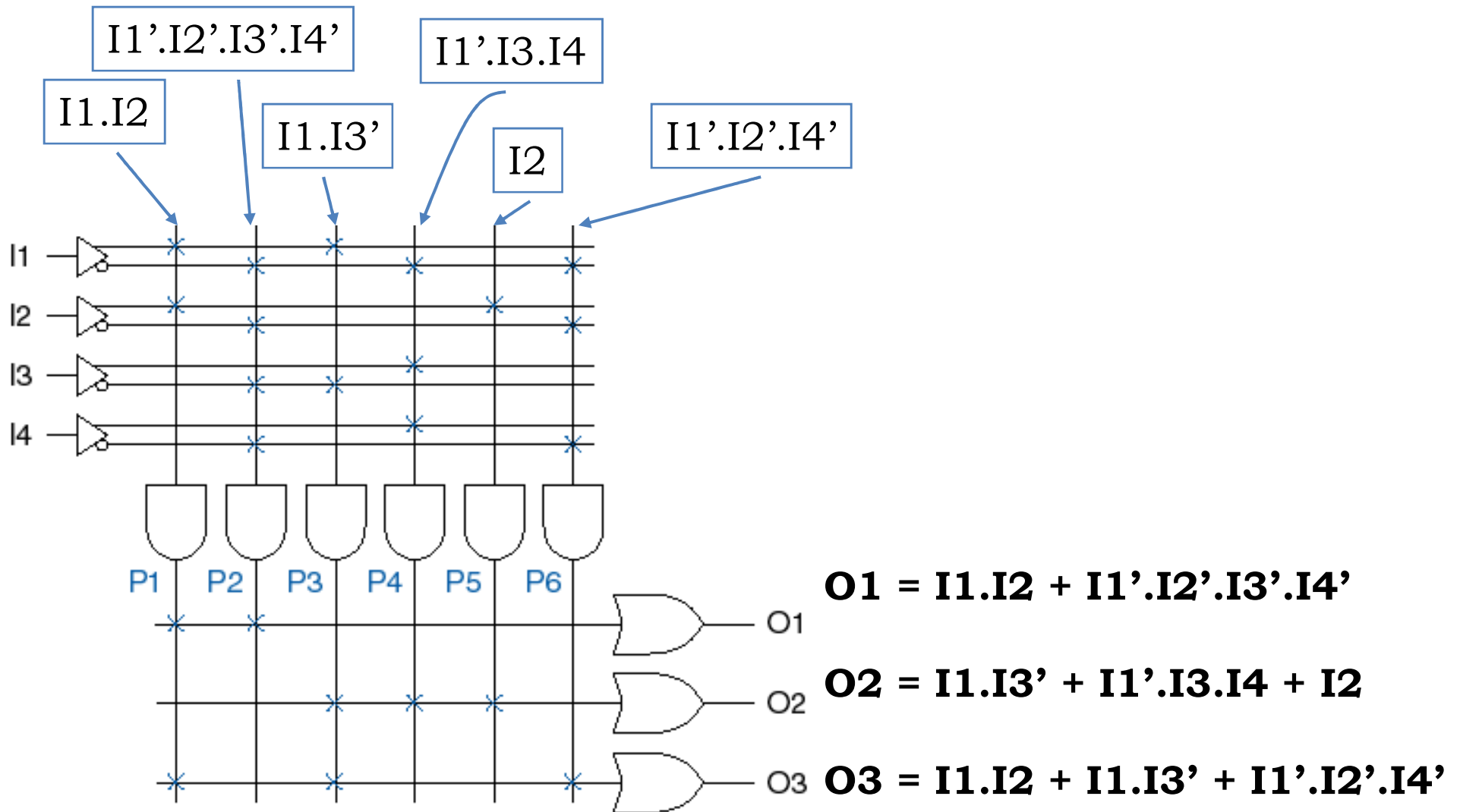

PLA Electrical Design

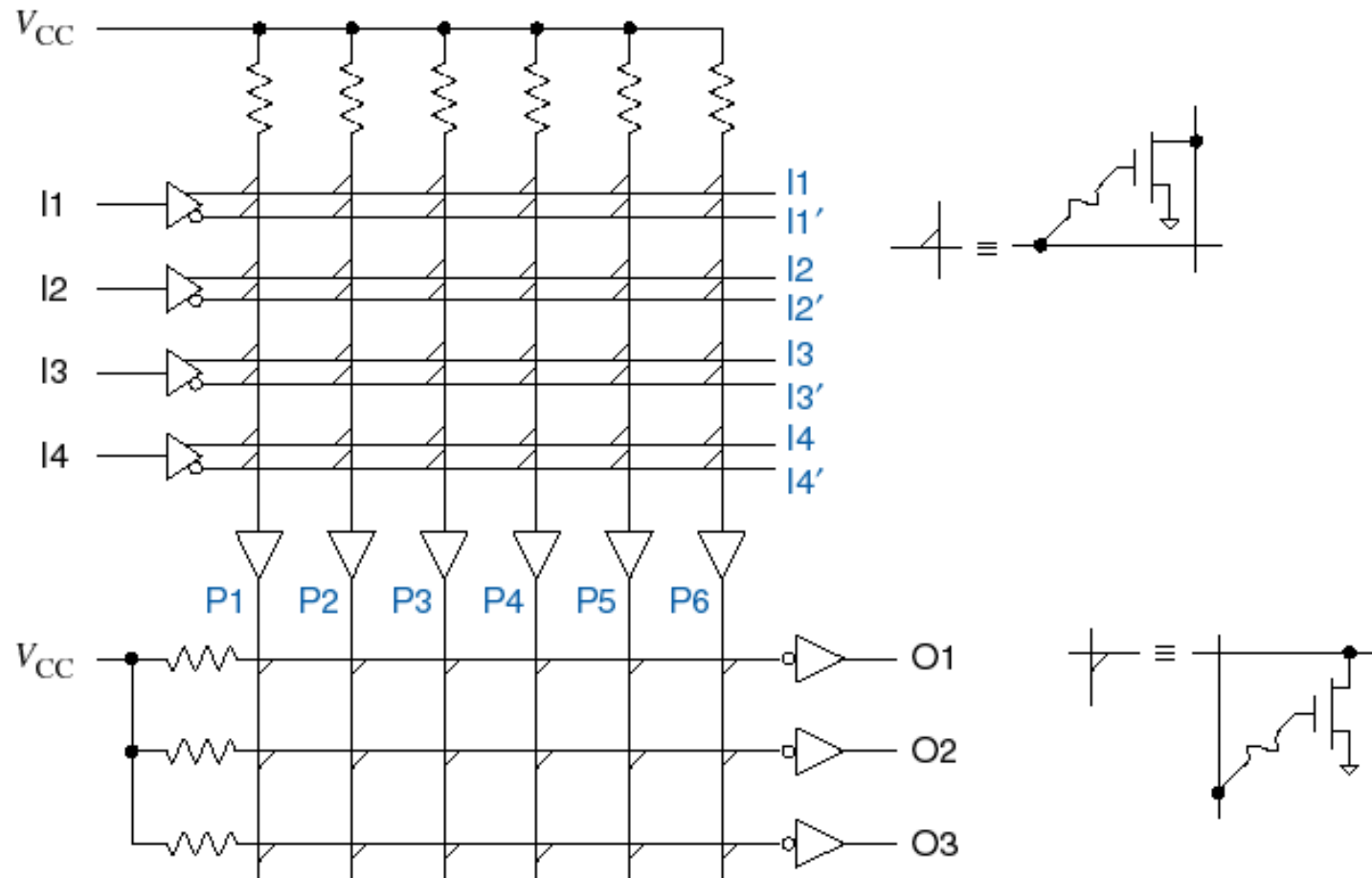


Programmable Array Logic (PALs)

How beneficial is product sharing?


Not enough to justify the extra **AND** array

PALs → fixed **OR** array

Example: PAL16L8

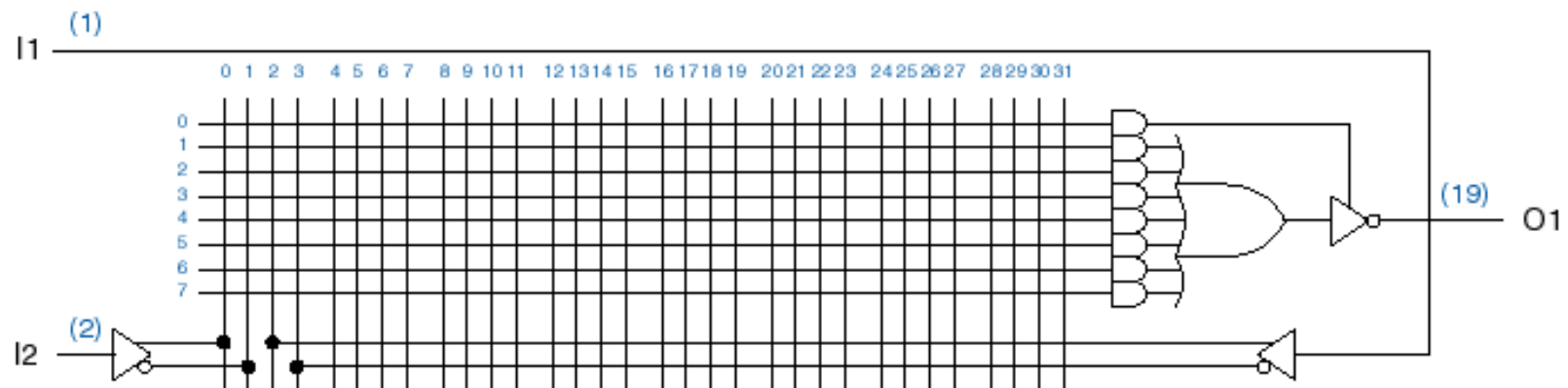

10 primary inputs

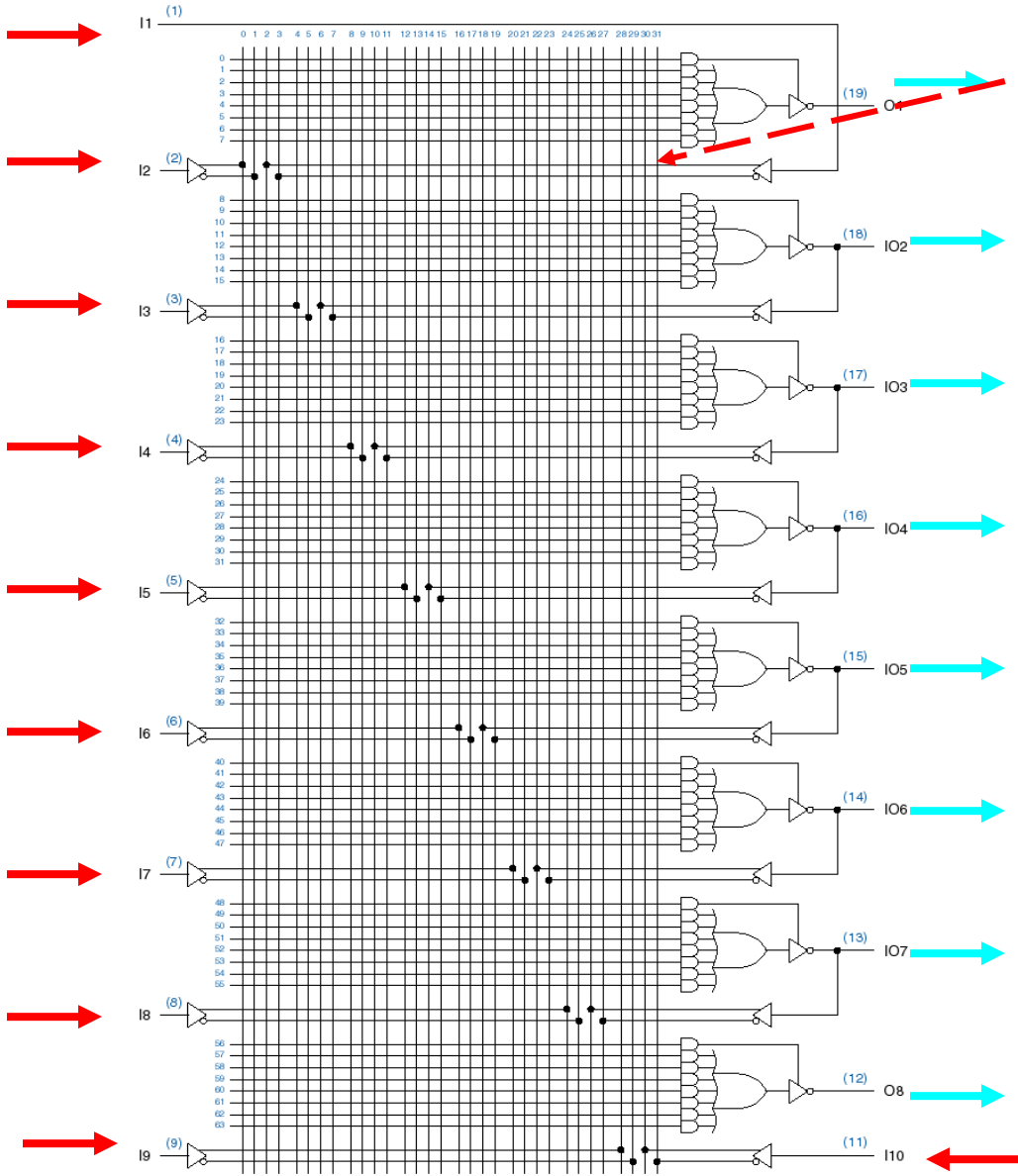

7 ANDs per output and
1 AND for 3-state enable

8 outputs
6 outputs available as inputs