



Faculty of Engineering


## **CSE115: Digital Design**

# **Lecture 17: Three State Logic**

# Suggested Reading

- Sections 5.6

# Three-State Buffers

 

Output = LOW, HIGH, or Hi-Z.

**Hi-Z:** The output is floating (High Impedance) when the enable input is deasserted →

**The input is isolated from the output**

EN	A	OUT
L	L	Hi-Z
L	H	Hi-Z
H	L	L
H	H	H

## Application:

- ❑ Can tie multiple outputs together, if at most one at a time is driven.
- ❑ Controlling the access of a **single line/bus** by multiple devices.

# Different Types



Active High Enable    Active Low Enable


## Buffers




Active High Enable    Active Low Enable

## Inverters

# 8 Data Sources Sharing One Line

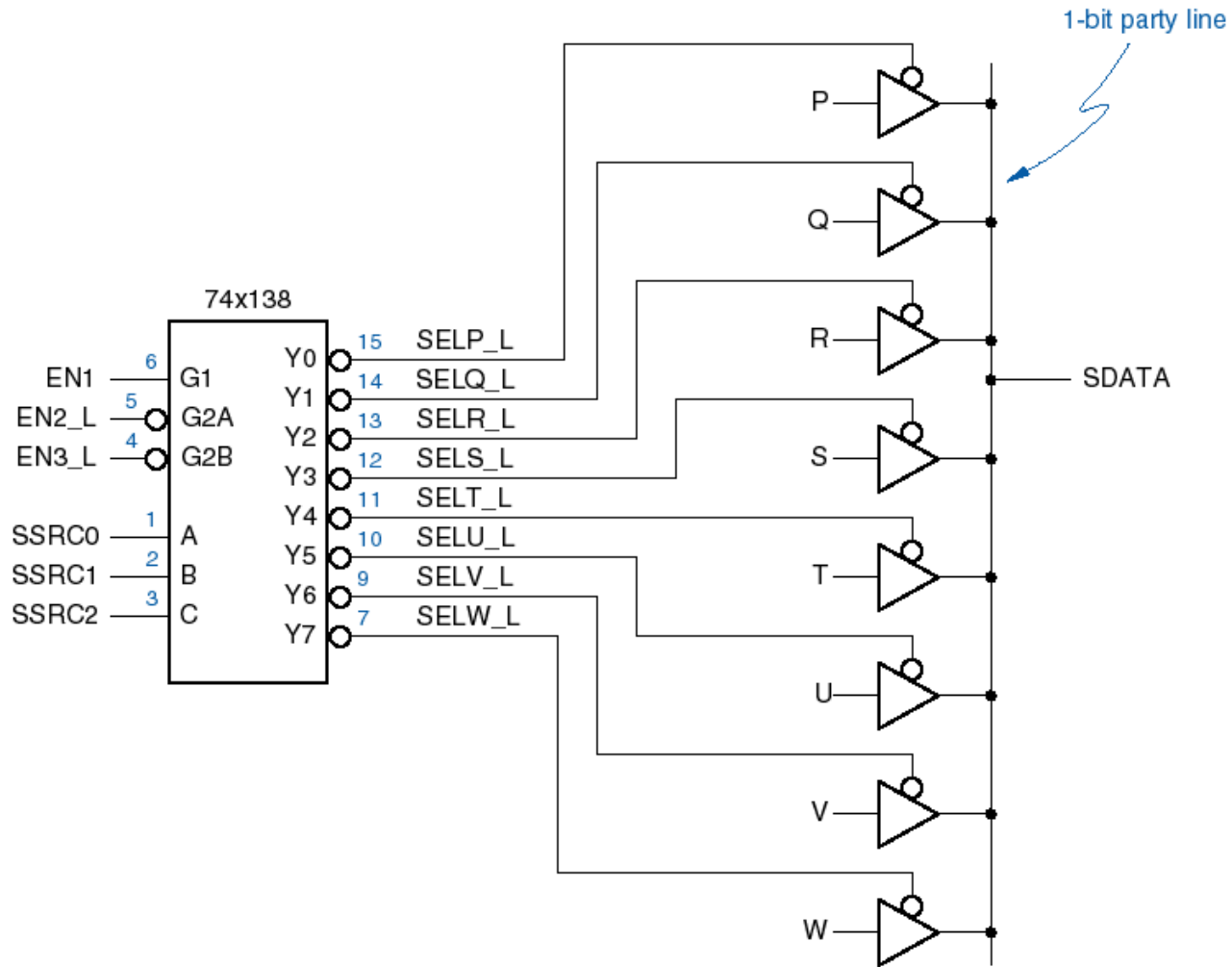

# Timing Considerations

 

# SSI/MSI Three-State Buffers

74x125: 4 independent buffers, Active Low enable

74x126: 4 independent buffers, Active High enable

74x540: 8 inverters with a common enable input

**74x541**: 8 buffers with a common enable input



74x240: 2 sets of 4 inverters with a common enable for each set

74x241: 2 sets of 4 buffers with a common enable for each set

**74x245**: *Octal three-state transceiver*


8 pairs of buffers connected in opposite directions

# Three-State Drivers

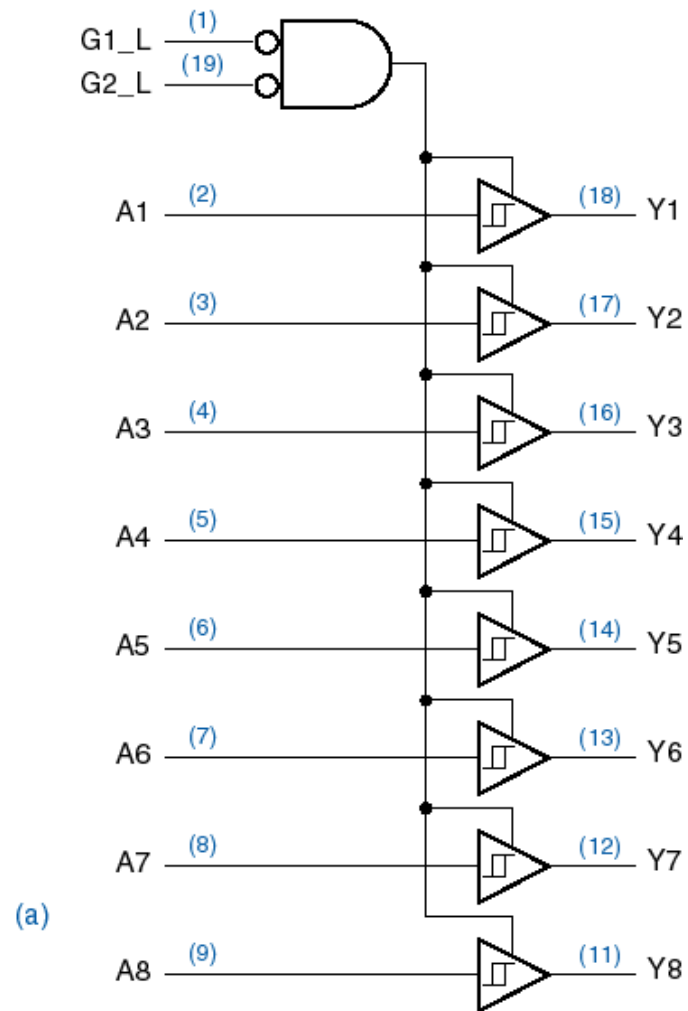
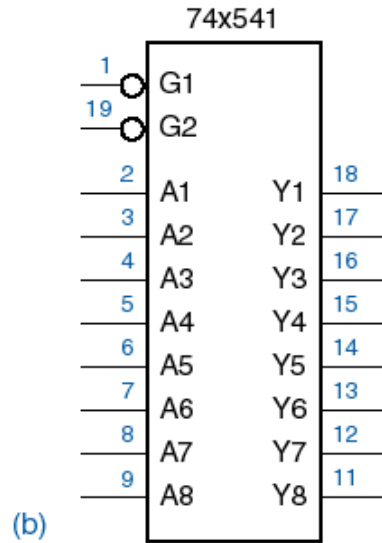




# Driver Application

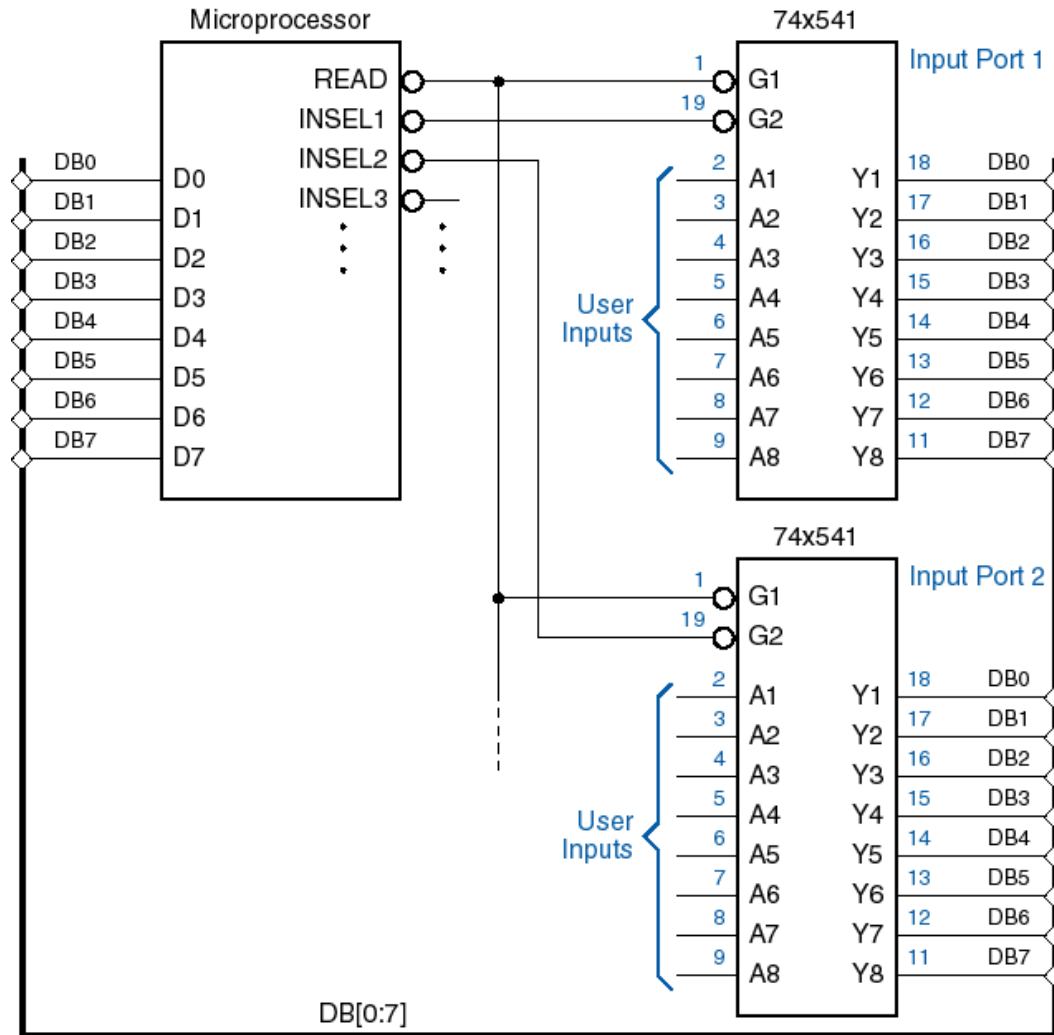

# Three-State Transceiver

 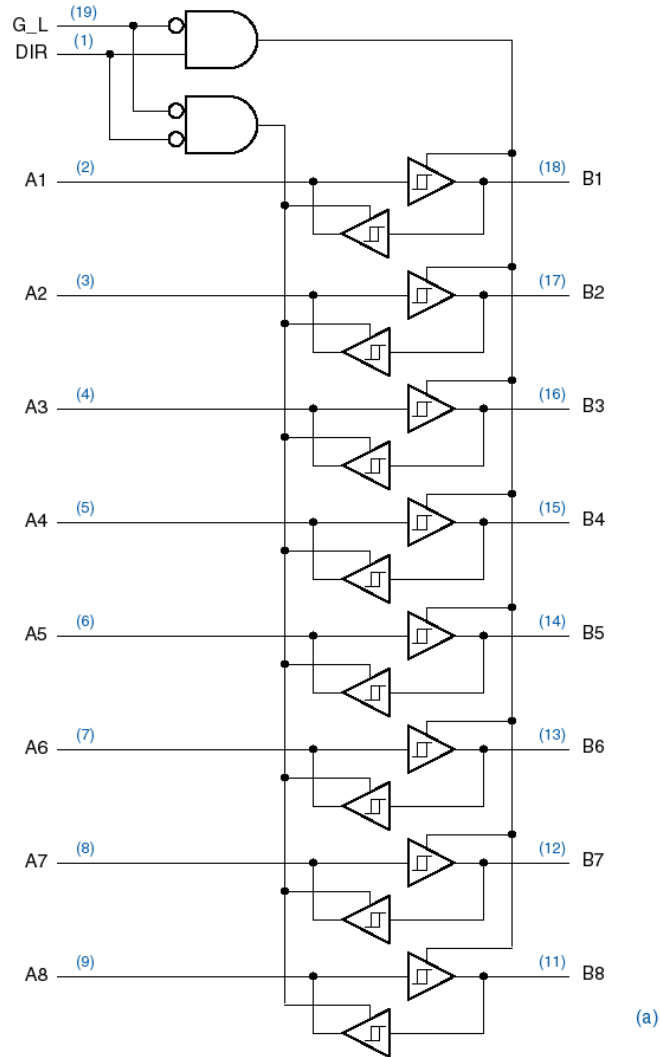

# Transceiver Application

