



Faculty of Engineering

**CSE115: Digital Design**

**Lecture 18:**  
**Multiplexers and Demultiplexers**

# Suggested Reading

- [Section 5.7](#)

# Multiplexers



**Multiplexing:** transmitting large number of signals over a small number of channels or lines

Digital multiplexer (**MUX**): selects one of many input lines and directs it to a single output.

Selection lines controls the selection of a particular input


n selection lines,  $2^n$  inputs, single output

# Multiplexers

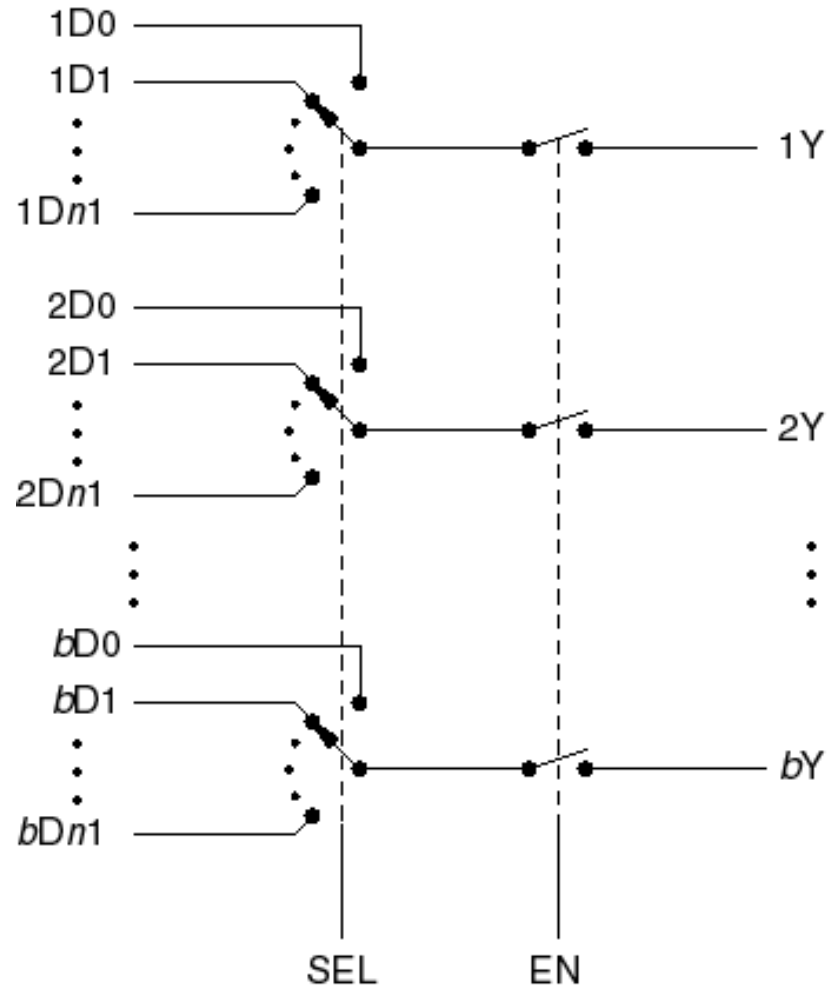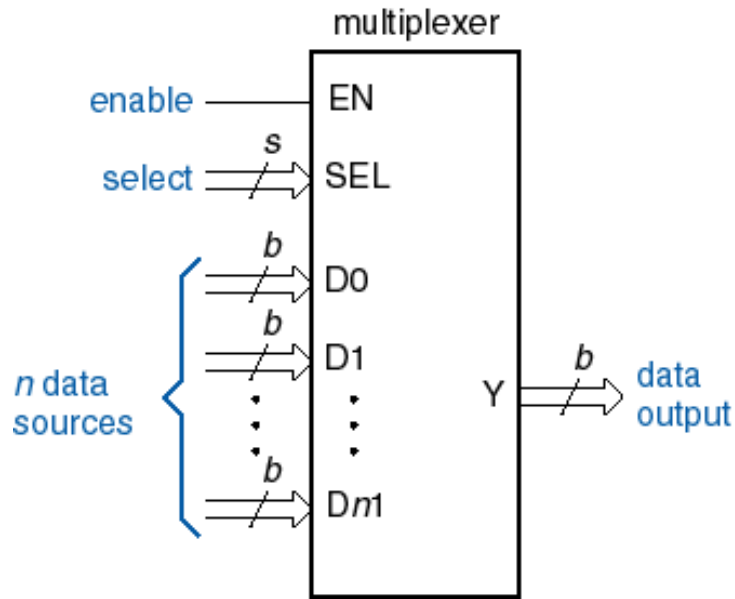


# 4-to-1 Line Multiplexer

S1	S0	Y
0	0	I0
0	1	I1
1	0	I2
1	1	I3

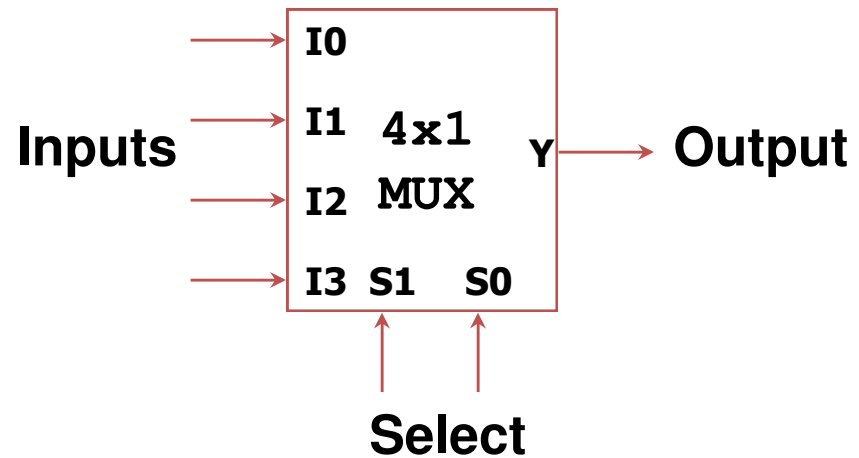

# Logic Diagram of 4-to-1 Multiplexer

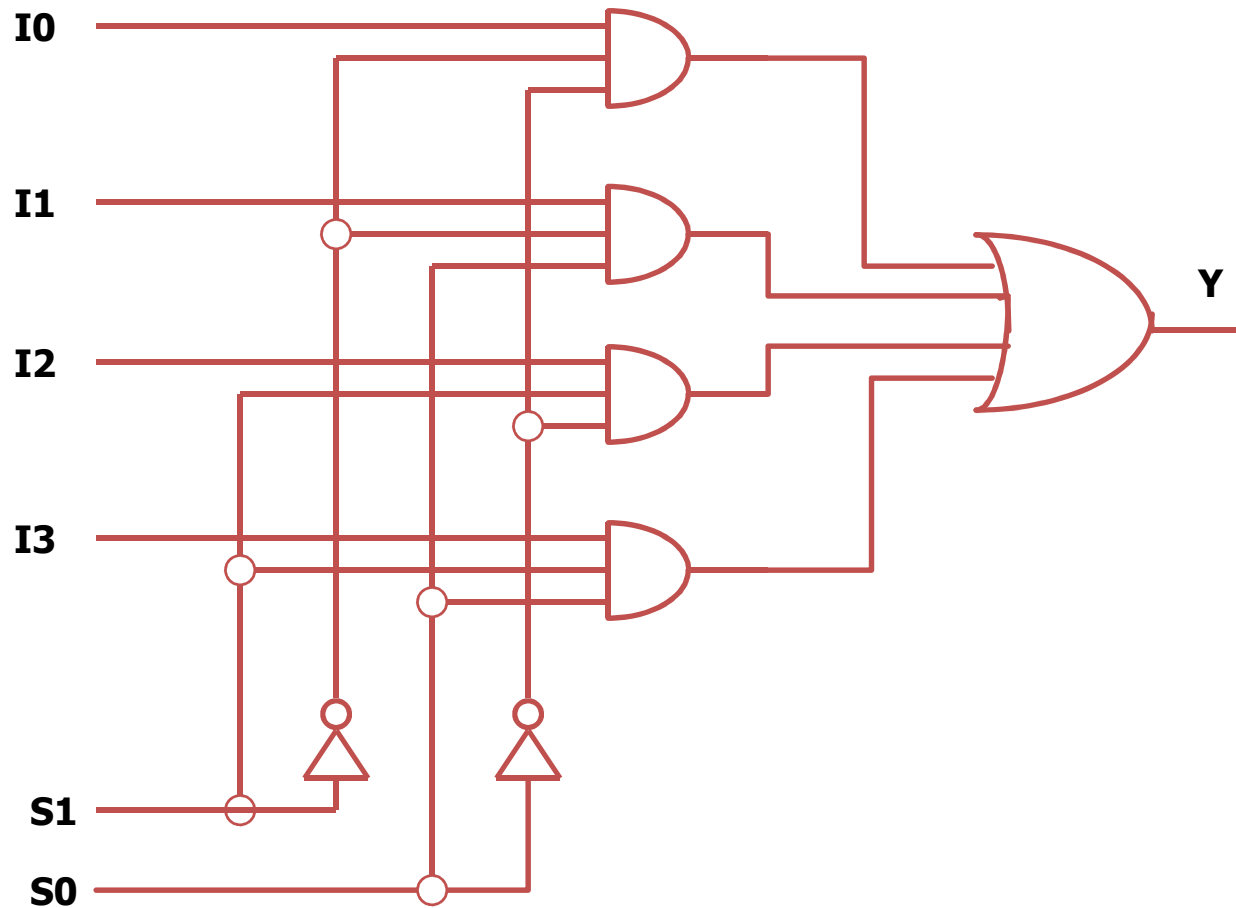

# Properties of Different Approaches


74x151: 8-to-1 MUX

74x251: 8-to-1 MUX with three-state output

74x153: 4-to-1 2 bit MUX

74x157: 2-to-1 4 bit MUX

# 74x151 8-Input Multiplexer

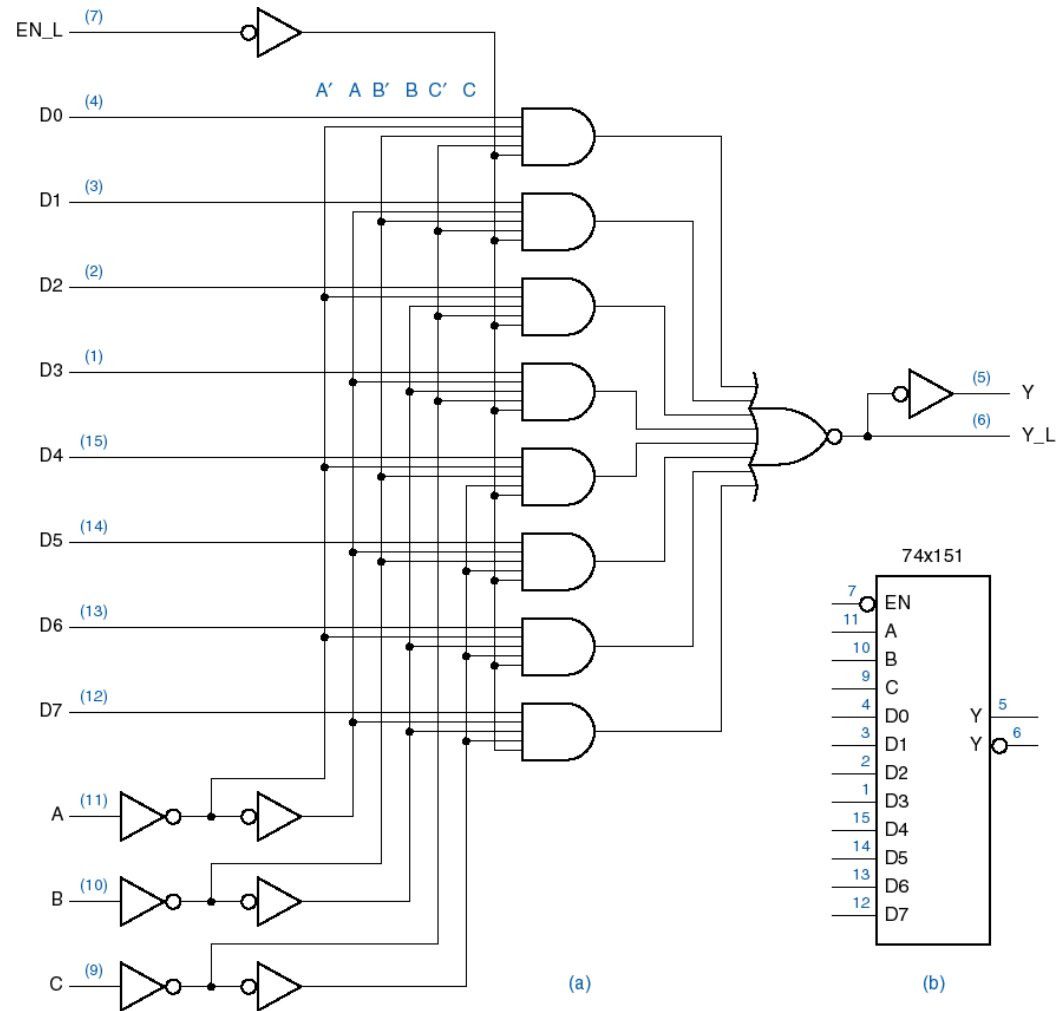



# 74x151 Truth Table

<i>Inputs</i>				<i>Outputs</i>	
EN_L	C	B	A	Y	Y_L
1	x	x	x	0	1
0	0	0	0	D0	D0'
0	0	0	1	D1	D1'
0	0	1	0	D2	D2'
0	0	1	1	D3	D3'
0	1	0	0	D4	D4'
0	1	0	1	D5	D5'
0	1	1	0	D6	D6'
0	1	1	1	D7	D7'


# Implementing Logic Functions

n- variable logic function can be implemented using  $2^n$ -to-1 MUX

The inputs variables are connected to the select input.


The function value for each input combination (0 or 1) is connected to the corresponding input of the MUX

**Example:  $F = \Sigma_{x,y} (1,3)$**

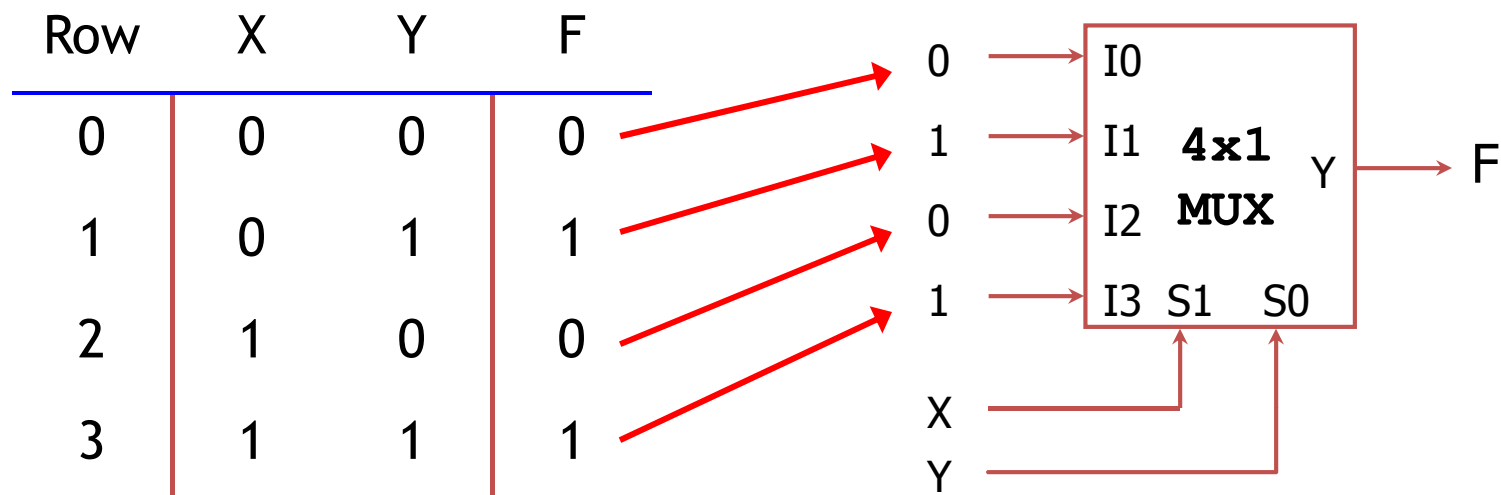

# Example: $F = \Sigma_{x,y,z} (2,4,7)$ using 74x151

Row	X	Y	Z	F
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	1	1

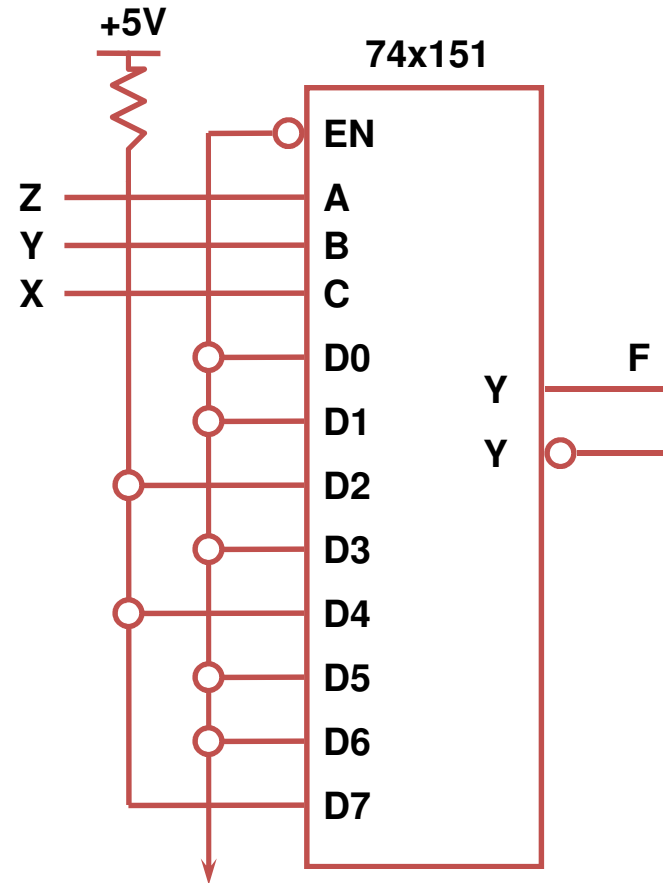


# Functional Decomposition

An effective way for using MUX to implement Logic Functions.

n-row truth table can be implemented using **n/2-to-1 MUX**:

- Write the Logic function in terms of the least significant input variable.
- The truth table is reduced by one half.

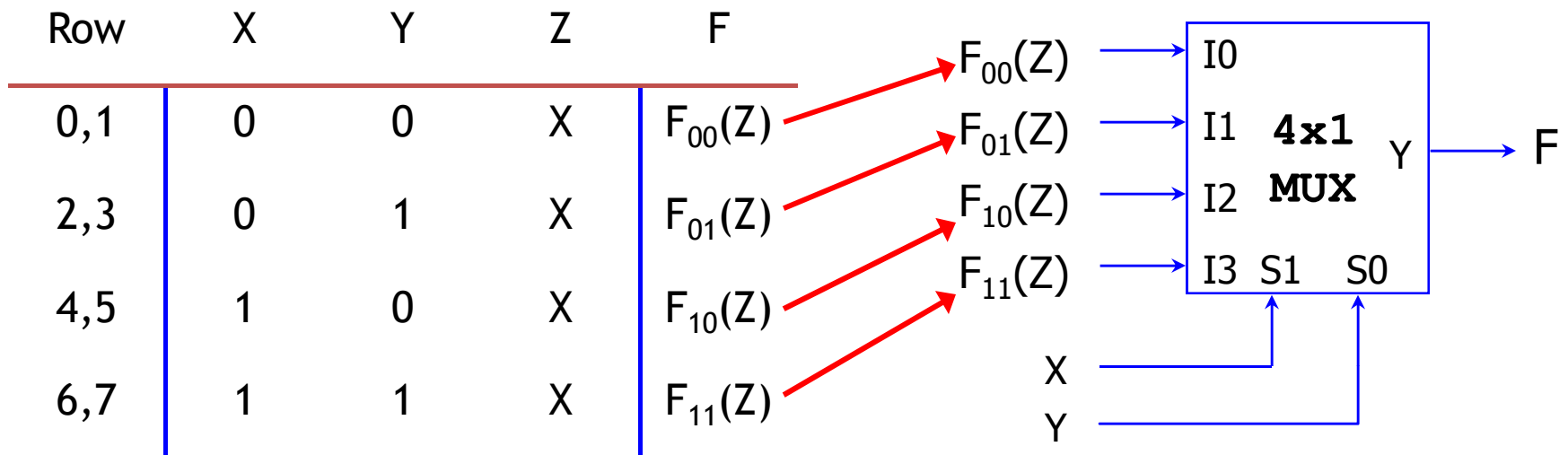For 3-variable Logic Function, the decomposed truth table is:




# Functional Decomposition Example

Truth Table  $\longrightarrow$  Decomposed Truth Table

Row	X	Y	Z	F
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	1	1

$F_{00}(Z) = 0$   
 $F_{01}(Z) = Z'$   
 $F_{10}(Z) = Z'$   
 $F_{11}(Z) = Z$

Row	X	Y	Z	F
0,1	0	0	0	0
2,3	0	1	X	Z'
4,5	1	0	X	Z'
6,7	1	1	X	Z

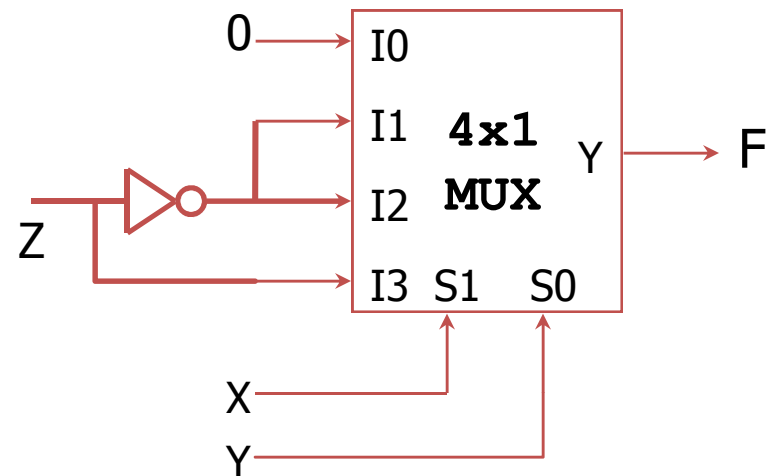


# Demultiplexers

Demultiplexer (**DMUX**) performs the opposite function of a MUX.



A digital Demultiplexer receives input data on a single input and transmits it on one of  $2^n$  possible outputs according to the value of the  $n$  select inputs

MUX/DMUX are used in data transmission

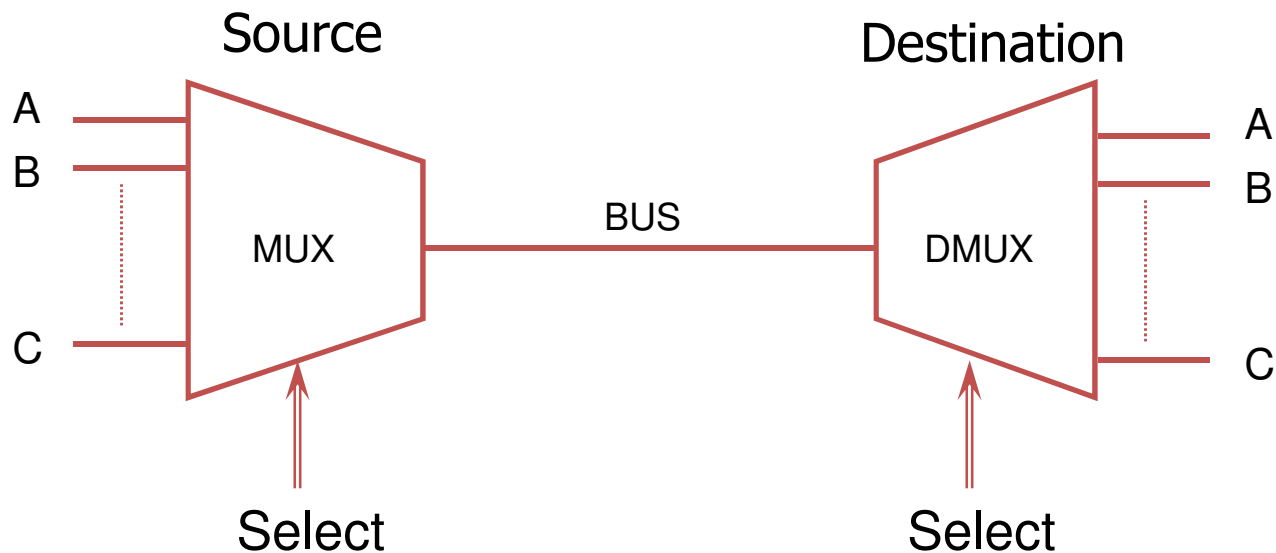

# 1-to-4 DMUX

IN	S1	S2	D0	D1	D2	D3
X	0	0	IN	0	0	0
X	0	1	0	IN	0	0
X	1	0	0	0	IN	0
X	1	1	0	0	0	IN

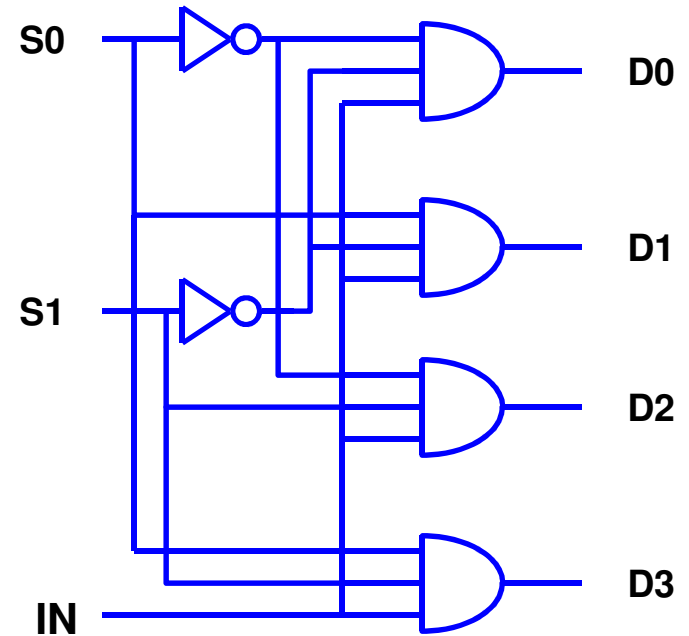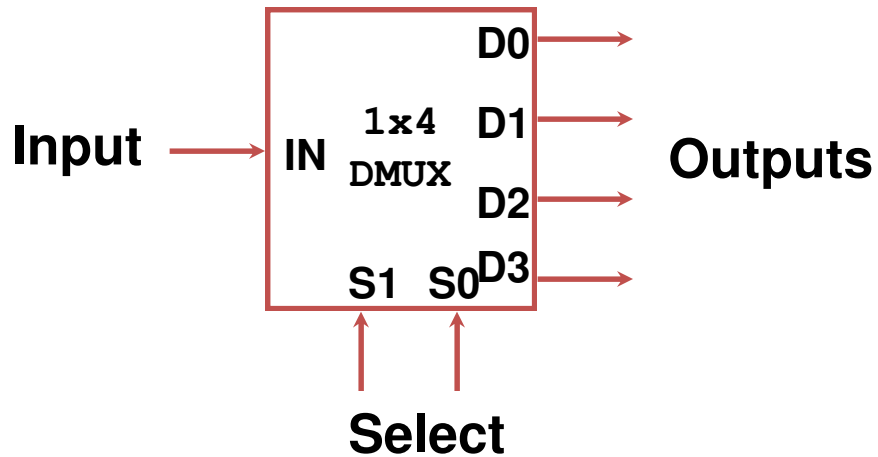

# Using Decoders as DMUX

A DMUX has the same structure of a Decoder with enable input.

Decoder can be used as a DMUX by connecting the input data to the enable input.

**Example:** 2-to-4 Decoder can be used as 1-to-4 DMUX

IN	S1	S2	D0	D1	D2	D3
X	0	0	IN	0	0	0
X	0	1	0	IN	0	0
X	1	0	0	0	IN	0
X	1	1	0	0	0	IN

