



Faculty of Engineering

CSE115: Digital Design

Lecture 19: XORs and Parity Circuits


Suggested Reading

- Section 5.8


2-input XOR Gates

Like an OR gate, but **excludes** the case where both inputs are 1.

X	Y	XOR	XNOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

 


$$X \oplus Y = X' \cdot Y + X \cdot Y'$$

 


$$(X \oplus Y)' = X \cdot Y + X' \cdot Y'$$

XOR and XNOR Symbols

 

Gate-level XOR Circuits

 
No direct realization with just a few transistors.




SSI XOR

74x86: 4 XOR gates

74x266: 4 XNOR gates

 

Parity Circuit: Daisy Chain

 


Odd Parity Circuit: The output is 1 if odd number of inputs are 1

Even Parity Circuit: The output is 1 if even number of inputs are 1

- Used to generate and check parity bits in computer systems.
- Detects any single-bit error


Parity Tree

Faster with balanced tree structure

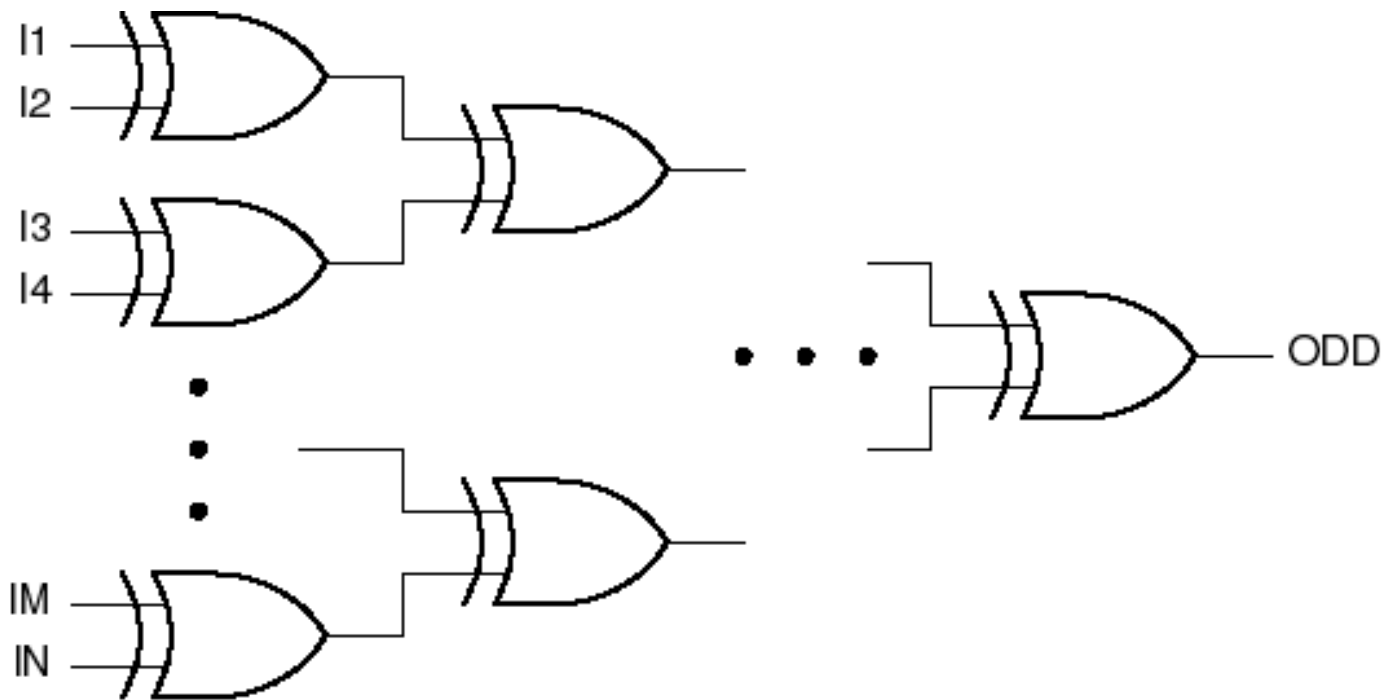


XOR Example:

Daisy-Chain Structure

 

Tree structure

 

Input: 1101

Even Parity output: 0

Odd Parity output: 1