



Faculty of Engineering


**CSE115: Digital Design**


**Lecture 23:  
Latches & Flip-Flops**

# Suggested Reading


- Sections 7.1-7.2

# A Generic Digital Processor

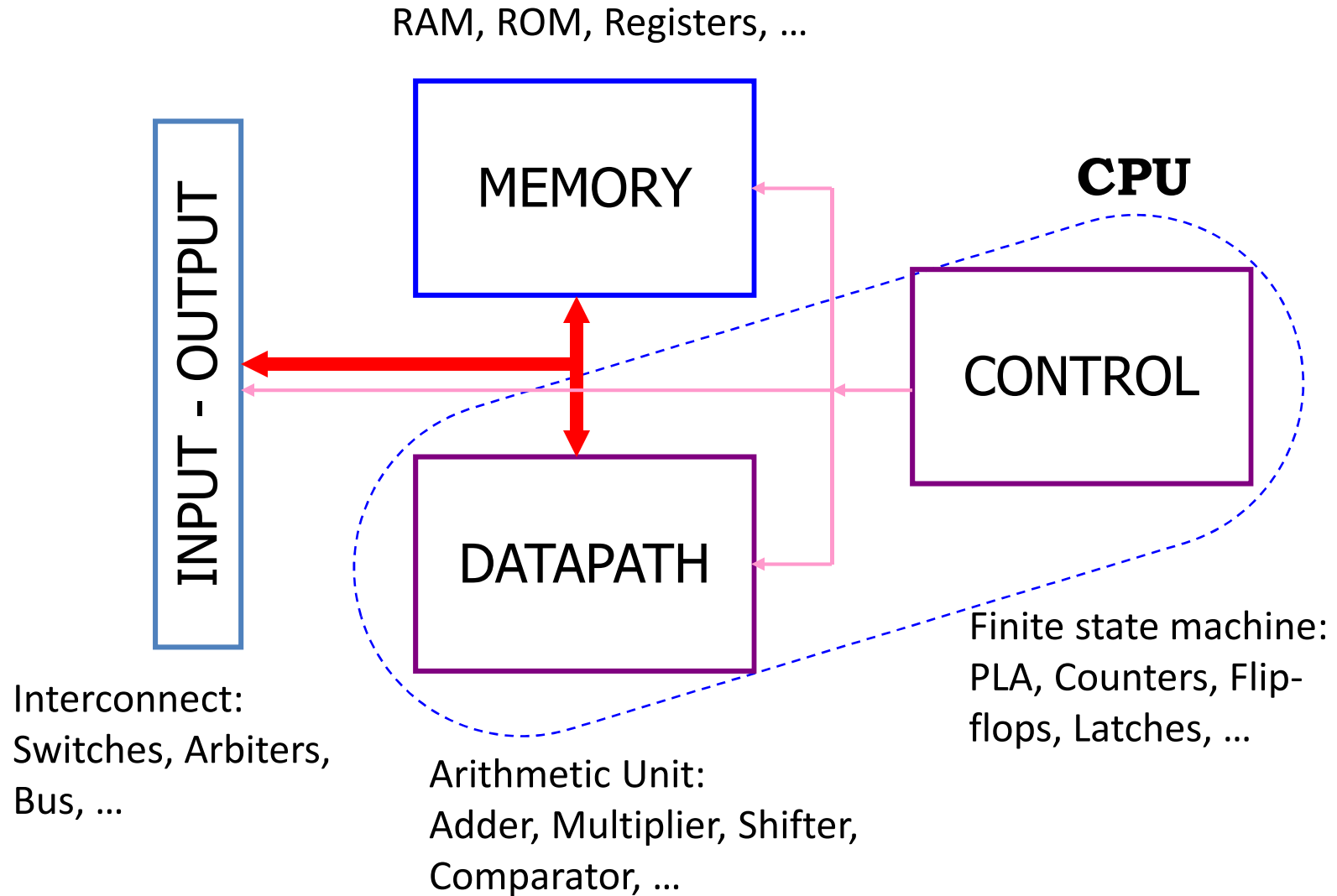

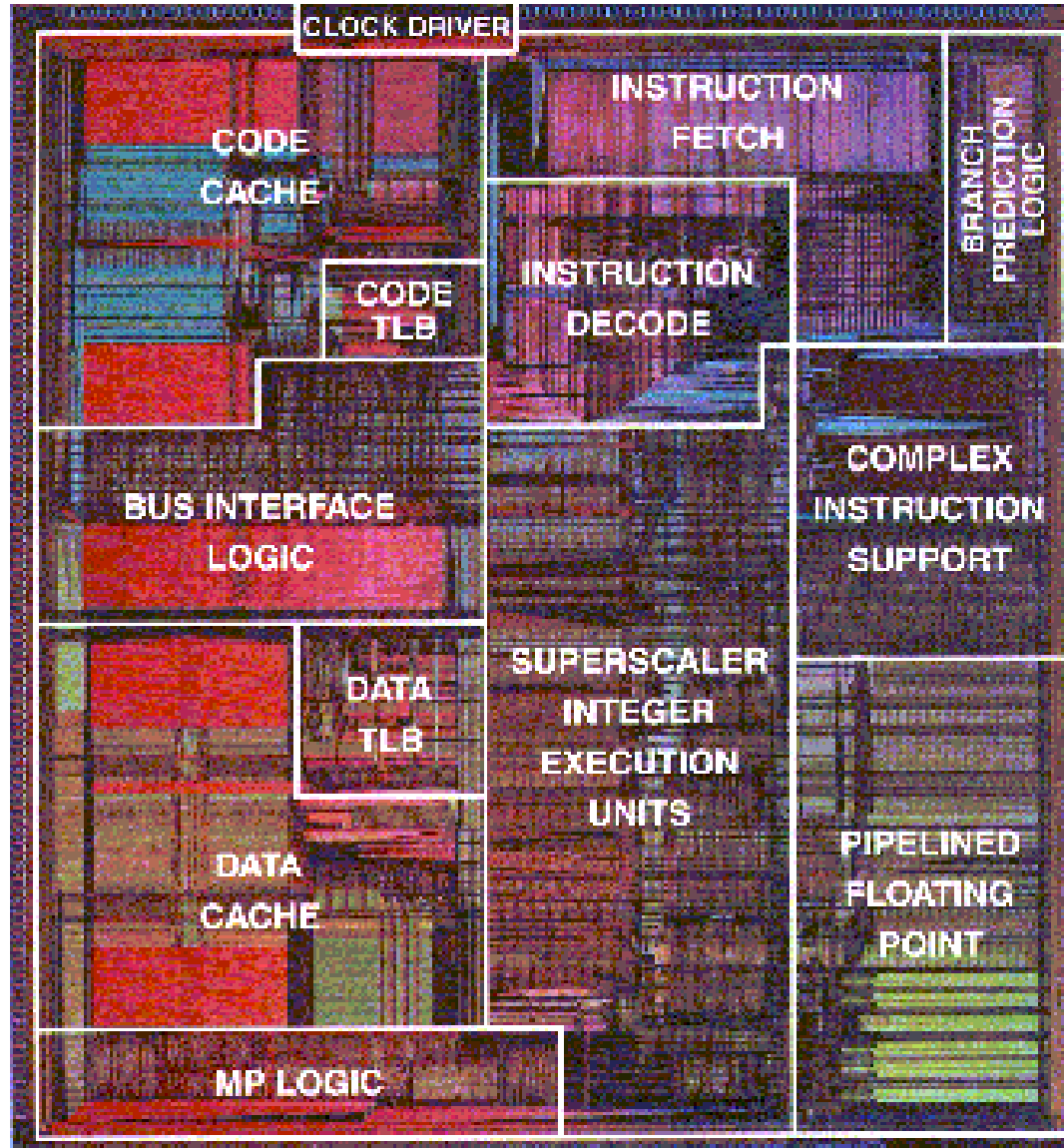

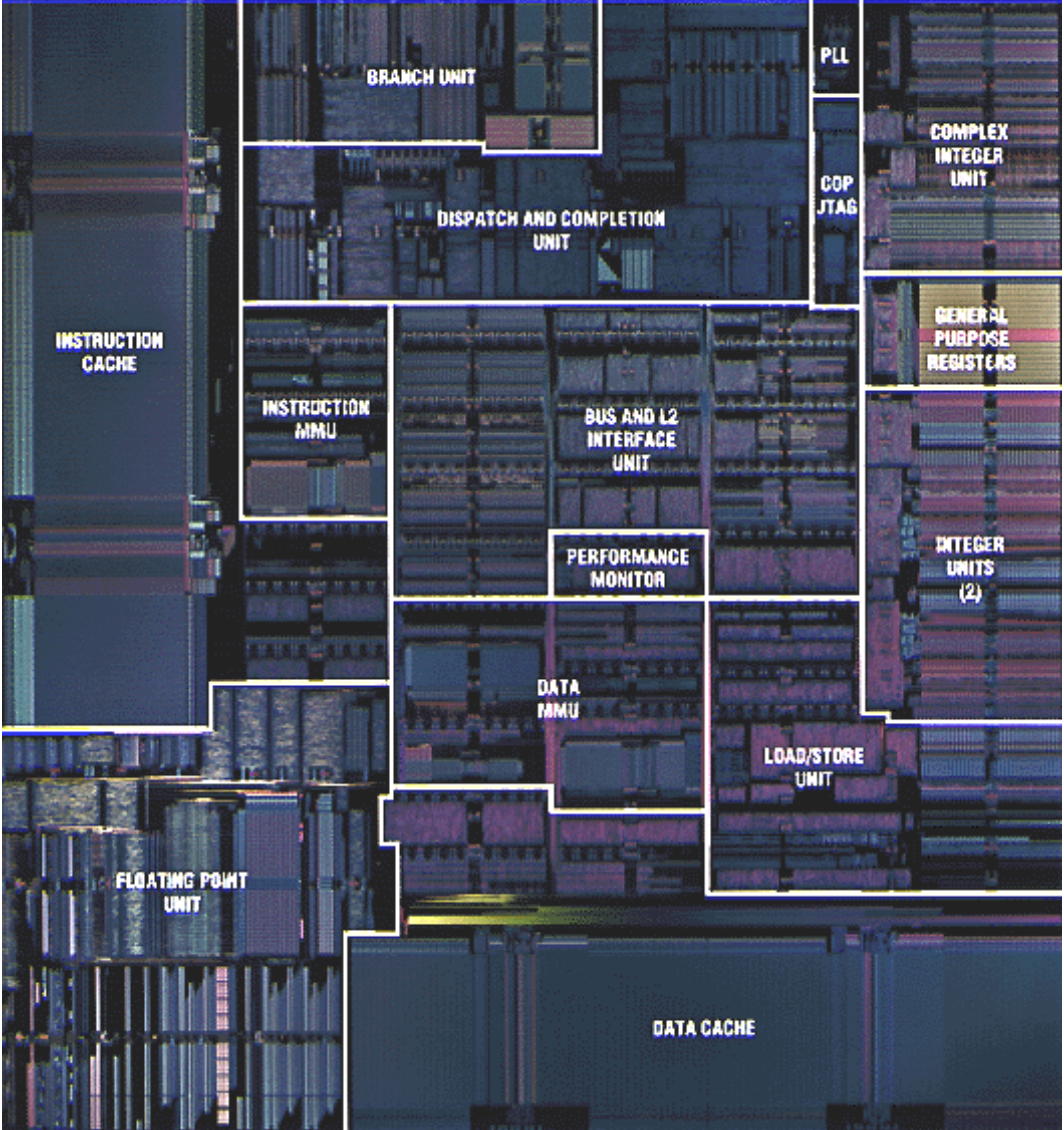Motorola's PowerPC™ 620 32/64-Bit RISC Microprocessor



# Logic Devices


- **Combinational Logic:** Current output depends on current input only

- ⇒ Gates
- ⇒ Decoders
- ⇒ Multiplexers
- ⇒ ALUs



- **Sequential Logic:** Current output depends on **past inputs** as well as **current input**; thus has a **memory (state)**.

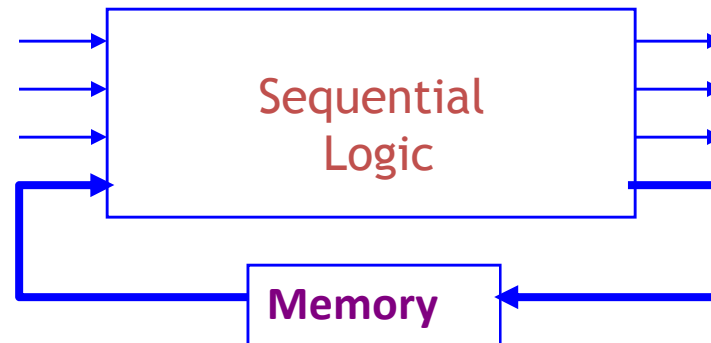- ⇒ Latches and Flip-Flops
- ⇒ State Machines
- ⇒ Counters
- ⇒ Shift Registers



# Sequential Logic Definitions

- **STATE:**


- A collection of state variables whose values contain all the information about the past values necessary to account for future behavior. (e.g. a TV tuner with up/down button)
- Circuit with  $n$  binary state variables has  $2^n$  possible states
- Changes usually synchronized with a system **clock**

- **Digital sequential logic**

- Also known as a *finite state machine (FSM)*.

 
# Clock Characteristics

**Clock** - the master timing element behind the state changes.



$$\text{Frequency} = 1/\text{Period}$$

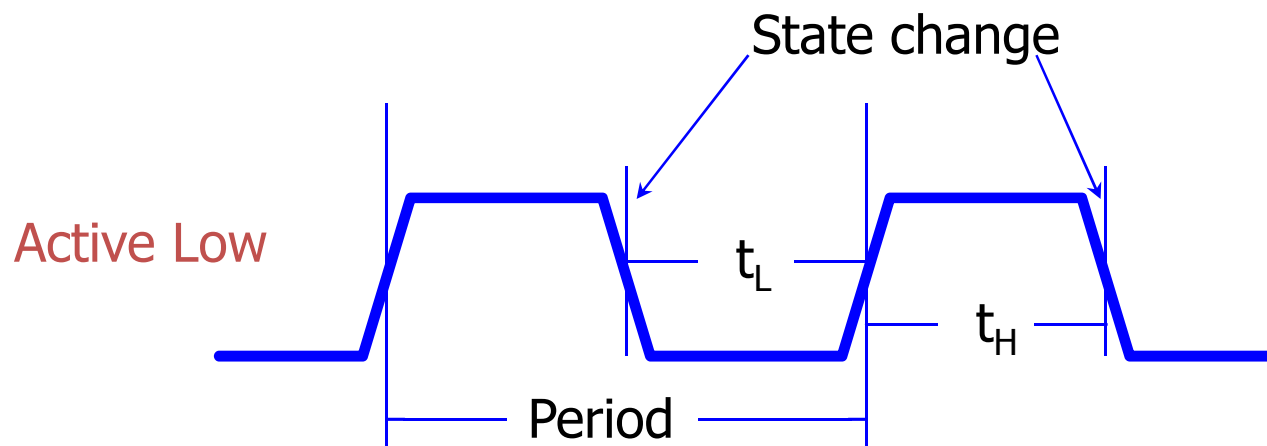**Period:** time between successive transitions in the same direction



$$\text{Duty Cycle} = t_H/\text{Period}$$

**Duty Cycle:** the percentage of time that a clock is at its assertion level. =  $t_L/\text{Period}$




# Types of Sequential Logic

- A **Feedback Sequential Circuit** uses gates with feedback to form memory elements (latches and flip/flops) used in state machines.
- A **Clocked Synchronous State Machine** uses clocked flip-flops to form useful sequential logic functions or application.
 
# Bistable Element

- The simplest possible feedback sequential logic circuit:




It is **bistable** because it has two stable states:

- State 1:** If  $Q$  ( $Q = V_{out1} = V_{in2}$ ) is high, the bottom inverter output ( $/Q = V_{out2} = V_{in1}$ ) is low, which keeps the top inverter output  $Q$  high.
- State 2:** If  $Q$  is low, the bottom inverter output  $/Q$  is high, which keeps the top inverter output  $Q$  low.


 
# Bistable Element

- The simplest sequential circuit
- Two states
  - One state variable,  $Q$




# Analog Analysis of Bistable


Top Inverter alone

 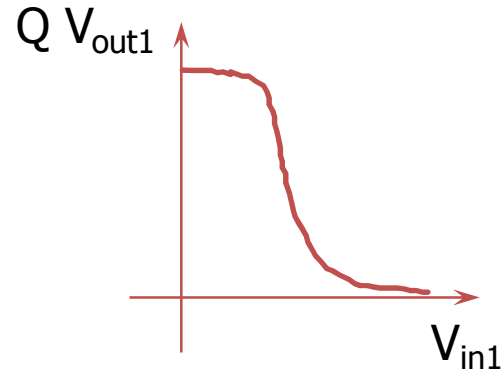

Bottom Inverter alone

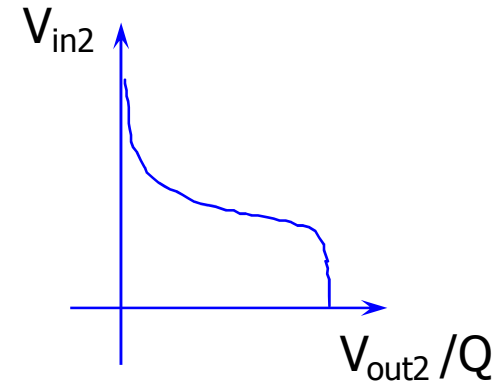

Complete Bistable

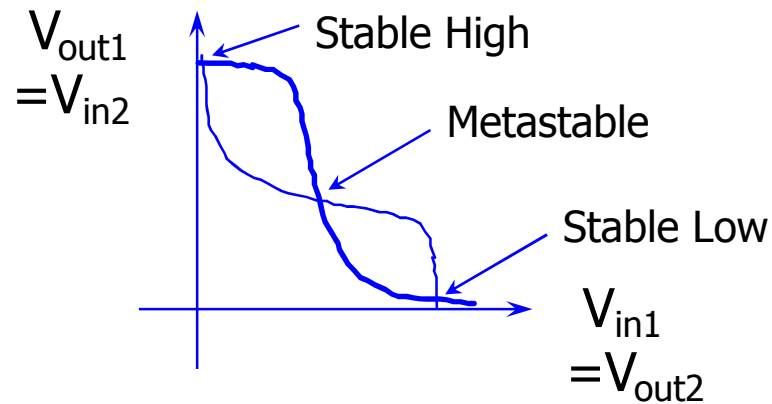


# Bistable and Metastability

There are not two stable states, but 3 states (**a problem!**)




**Metastable** point occurs when both outputs are halfway between high and low

- not a valid logic level!!!

 Could last forever, but noise pushes towards a stable state.



# Metastability

   

# Latches and Flip-flops

- Common feedback sequential circuits
- **Latch**
  - Single-bit storage (memory)
  - Changes state at **any time** due to input change
- **Flip-flop**
  - Also single-bit storage
  - Changes state **ONLY** when a **clock** edge or pulse is applied

# Types of Latches and Flip-flops

- **Latches**


- S-R Latch
- $\overline{S}$ - $\overline{R}$  Latch
- S-R Latch with Enable
- D Latch

- **Flip-flops**

- Edge-Triggered D Flip-Flop
- Master/Slave S-R Flip-Flop
- Master/Slave J-K Flip-Flop
- Edge-Triggered J-K Flip-Flop
- T Flip-Flop




# Back to the Bistable....

 

- How to control it?
  - Screwdriver
  - Control inputs
- **S-R latch (set-reset)**

# S-R Latch

Symbol

 

Hold

Reset


Set

ILLEGAL

Function Table

S	R	Q	/Q
0	0	Last Q	Last /Q
0	1	0	1
1	0	1	0
1	1	0	0



Schematic

 


## Consider:

1. Timing Diagram
2. Propagation delay
3. Minimum pulse width
4. Oscillation

# S-R latch Operation

  

 
**Metastability** is possible if S and R are negated simultaneously.






# S-R latch Timing Parameters

Propagation delay



Minimum pulse width

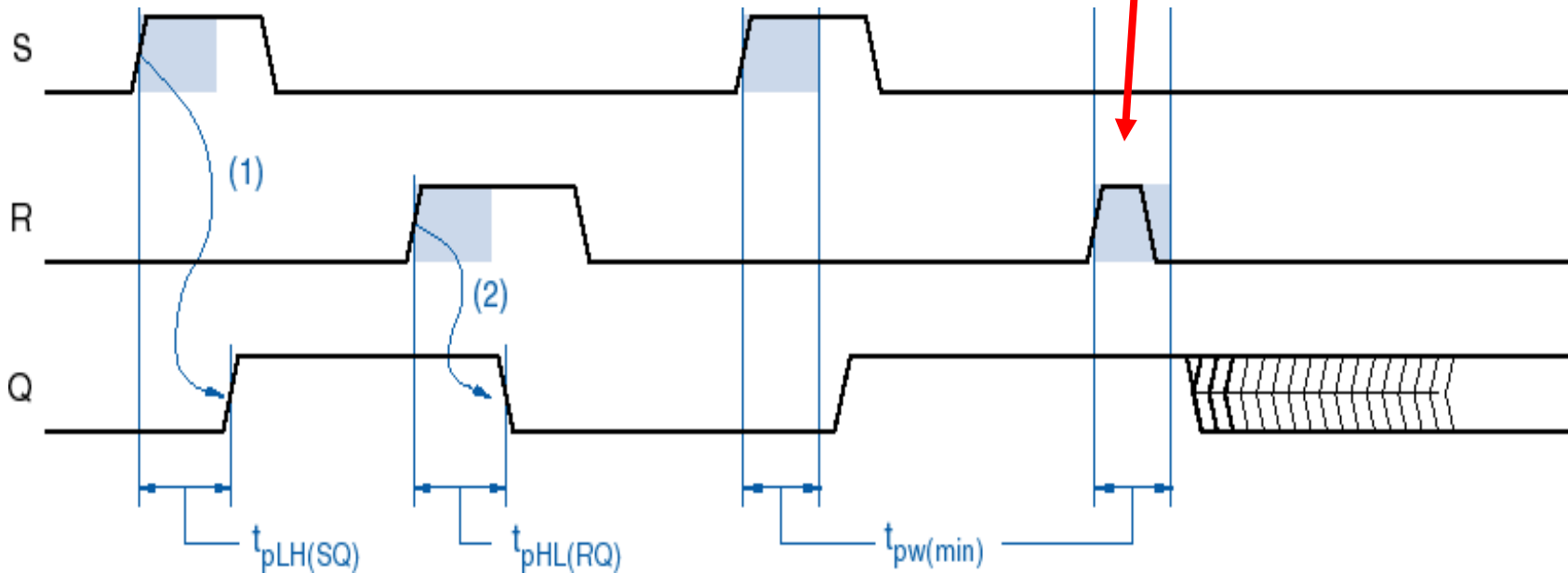

# S-R latch Symbols

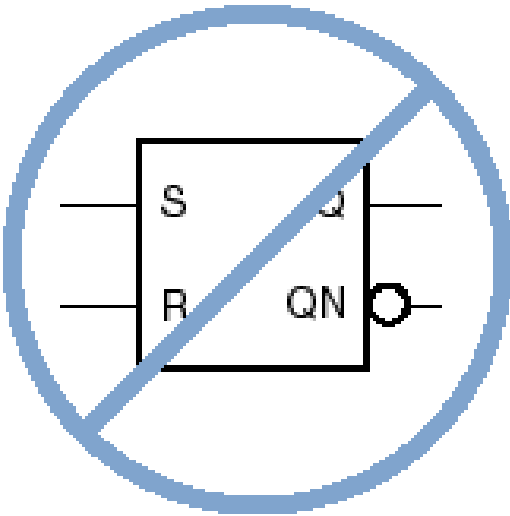  
  
# S-R latch using NAND gates: /S-/R Latch



$S_L$	$R_L$	$Q$	$QN$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	last Q	last QN

Function Table

$/S$	$/R$	$Q$	$/Q$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	Last Q	Last /Q


Illegal

Set


Reset

Hold

# S-R Latch with Enable

 


<i>/S</i>	<i>/R</i>	<i>C</i>	<i>Q</i>	<i>/Q</i>
0	0	1	Last Q	Last /Q
0	1	1	0	1
1	0	1	1	0
1	1	1	1	1
x	x	0	Last Q	Last /Q

 


Only sensitive to S and R  
when enabled ( $C=1$ )

Same oscillation problem

# D Latch

 

C	D	Q	QN
1	0	0	1
1	1	1	0
0	x	last Q	last QN

 

Store a data bit, not set/reset

'Transparent latch'


Setup and Hold time




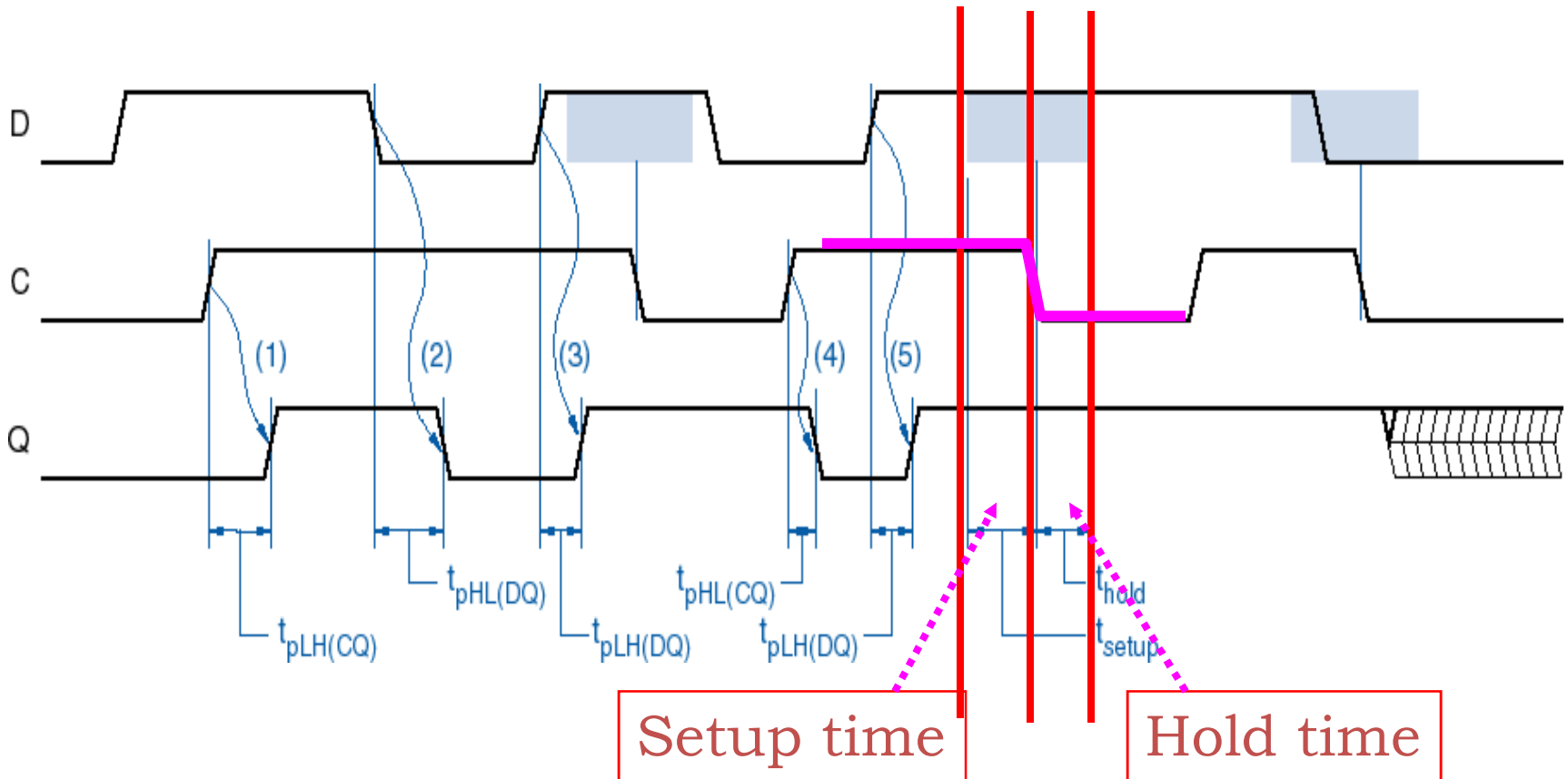
# D-latch Timing Parameters

Propagation delay  
from C or D



D should not change during:  
 $t_{\text{setup}}$  (before C edge) +  $t_{\text{hold}}$  (after C edge)



# Positive-Edge-Triggered D Flip-Flop

  


D	CLK	Q	QN
0	↑	0	1
1	↑	1	0
x	0	last Q	last QN
x	1	last Q	last QN

  

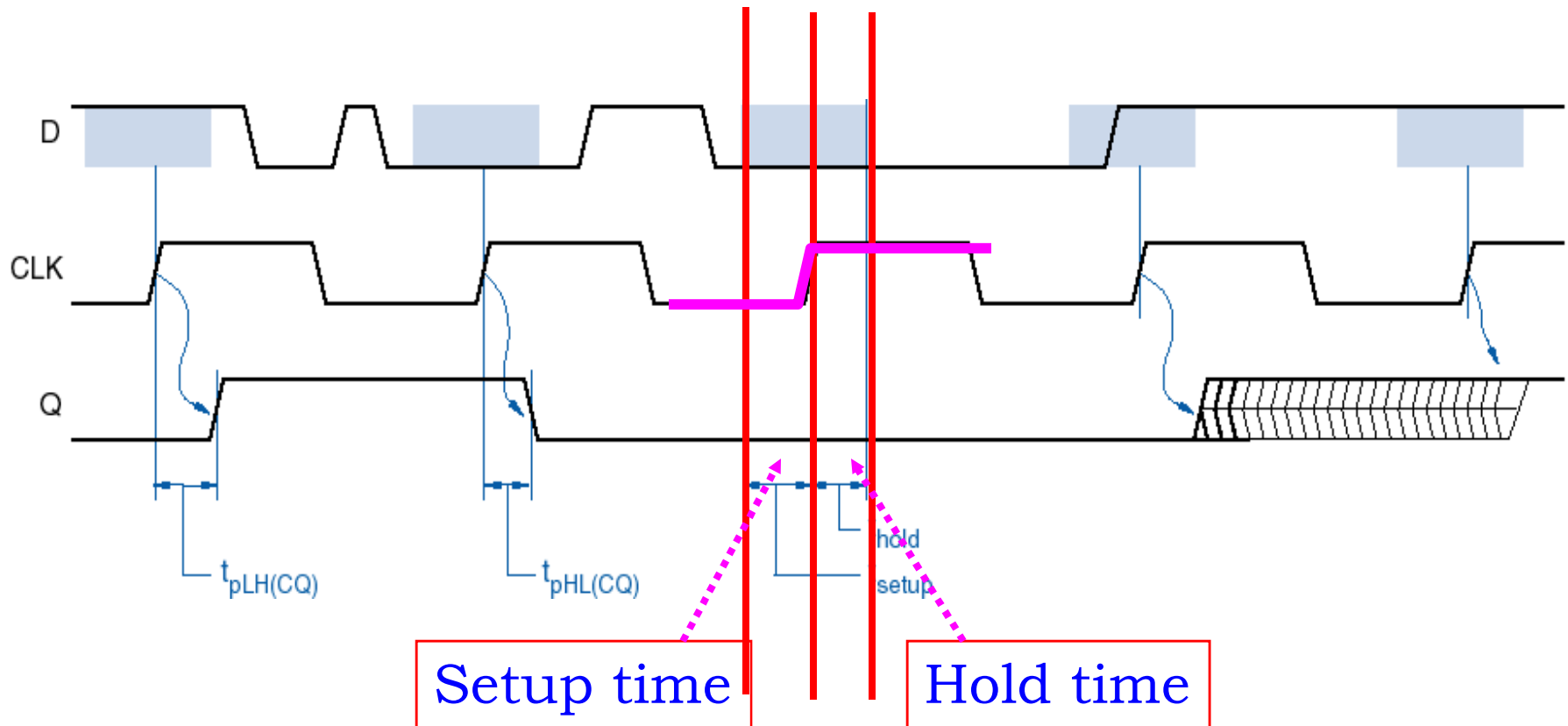
# D Flip-Flop Timing Parameters

Propagation delay  
from CLK

D should not change during:  
 $t_{\text{setup}}$  (before C edge) +  $t_{\text{hold}}$  (after C edge)




# D flip-flop Versus Latch

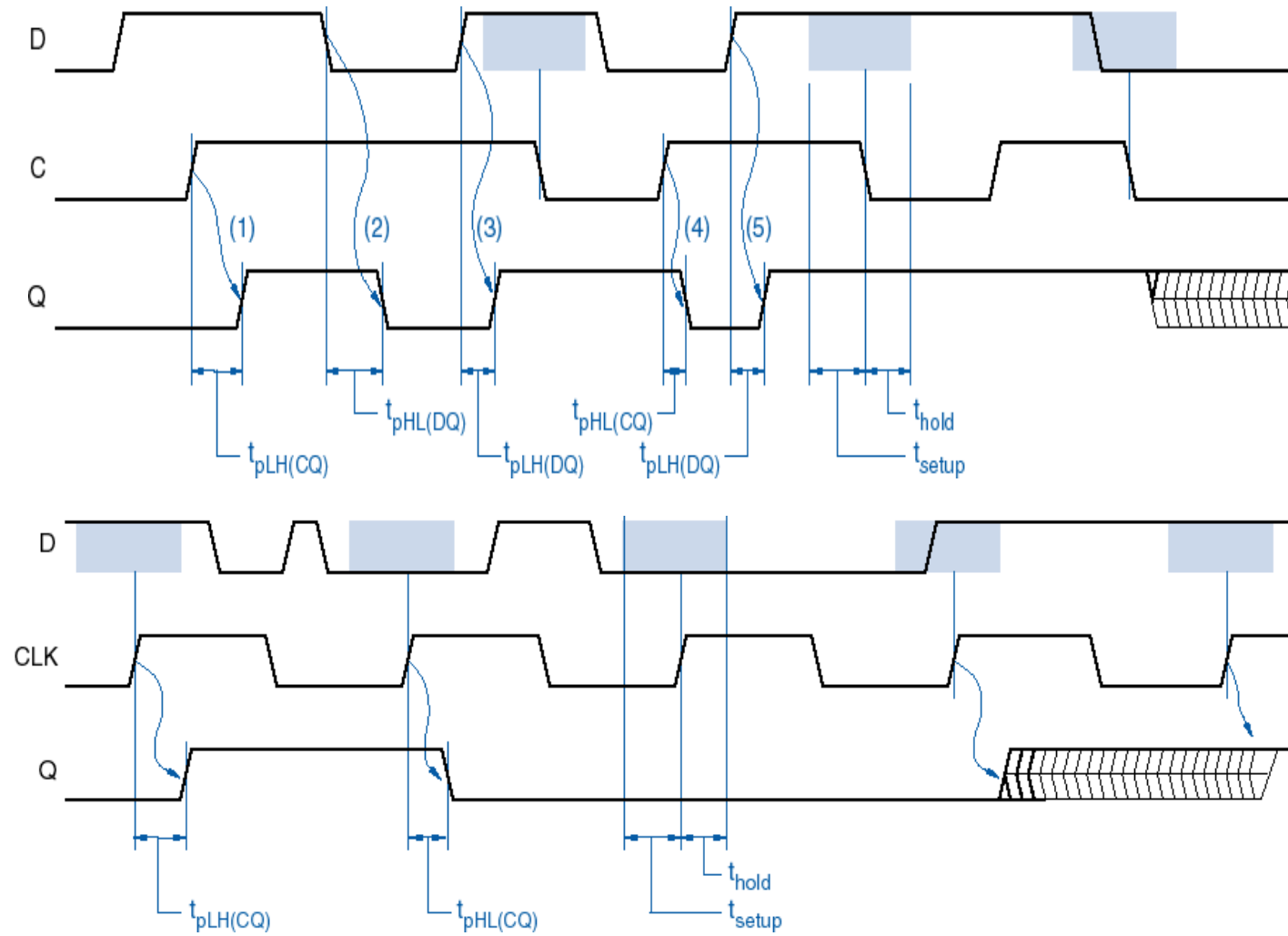


# Other D flip-flop Variations




Negative-edge triggered

 


Clock Enable

 

Scan

   

# Scan Flip-Flops -- for testing

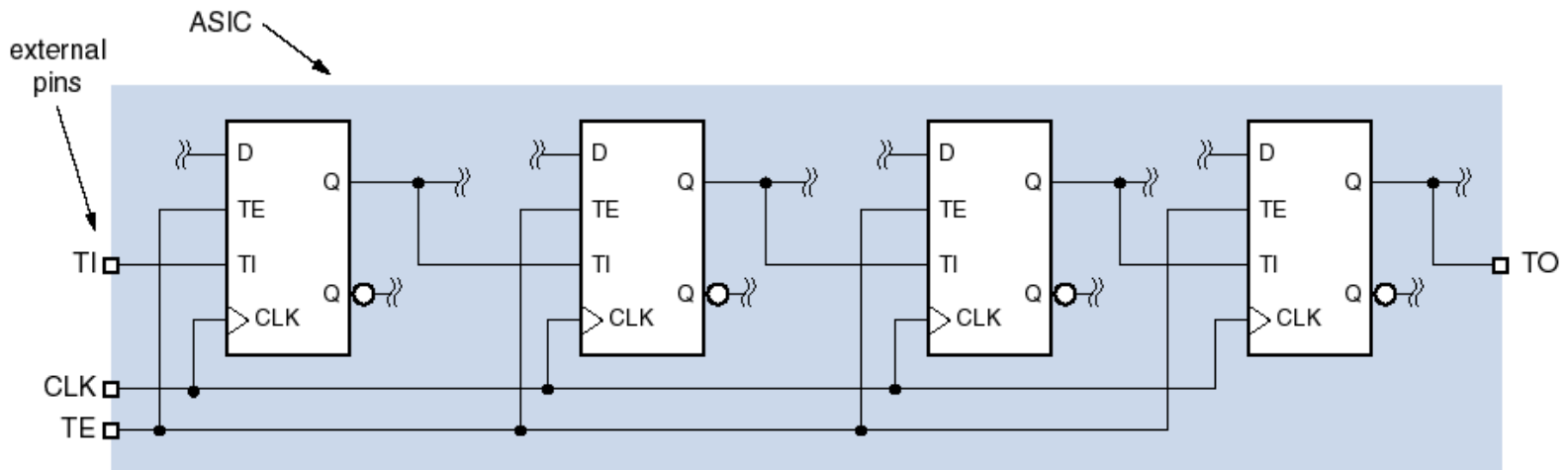

TE = 0 → normal operation


TE = 1 → test operation

 
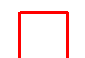
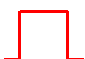
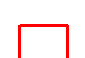
- ❑ All of the flip-flops are hooked together in a daisy chain from external test input TI.
- ❑ Load up ("scan in") a test pattern, do one normal operation, shift out ("scan out") result on TO.


# Asynchronous Inputs

- Most flip-flops have **two asynchronous inputs**
- **Preset** and **Reset** (or Clear)
- Directly set or reset the /S-/R latches
- Operate independent of clock
- USE asynchronous inputs for logic functions **ONLY** for system **INITIALIZATION** to a known state

# Master/Slave S-R Flip-Flop




S	R	C	Q	/Q
x	x	0	Last Q	Last /Q
0	0		Last Q	Last /Q
0	1		0	1
1	0		1	0
1	1		Undef	undef

 


"Pulse-triggered" S-R flip-flop  
Pulse-catching behavior



# J-K Flip-flops

 





J	K	CLK	Q	QN
x	x	0	last Q	last QN
x	x	1	last Q	last QN
0	0		last Q	last QN
0	1		0	1
1	0		1	0
1	1		last QN	last Q

 


- Not used much anymore
    
# T (toggle) Flip-Flop

- T flip-flop changes state on every clock tick.
- Important for counters



# Sequential PALs

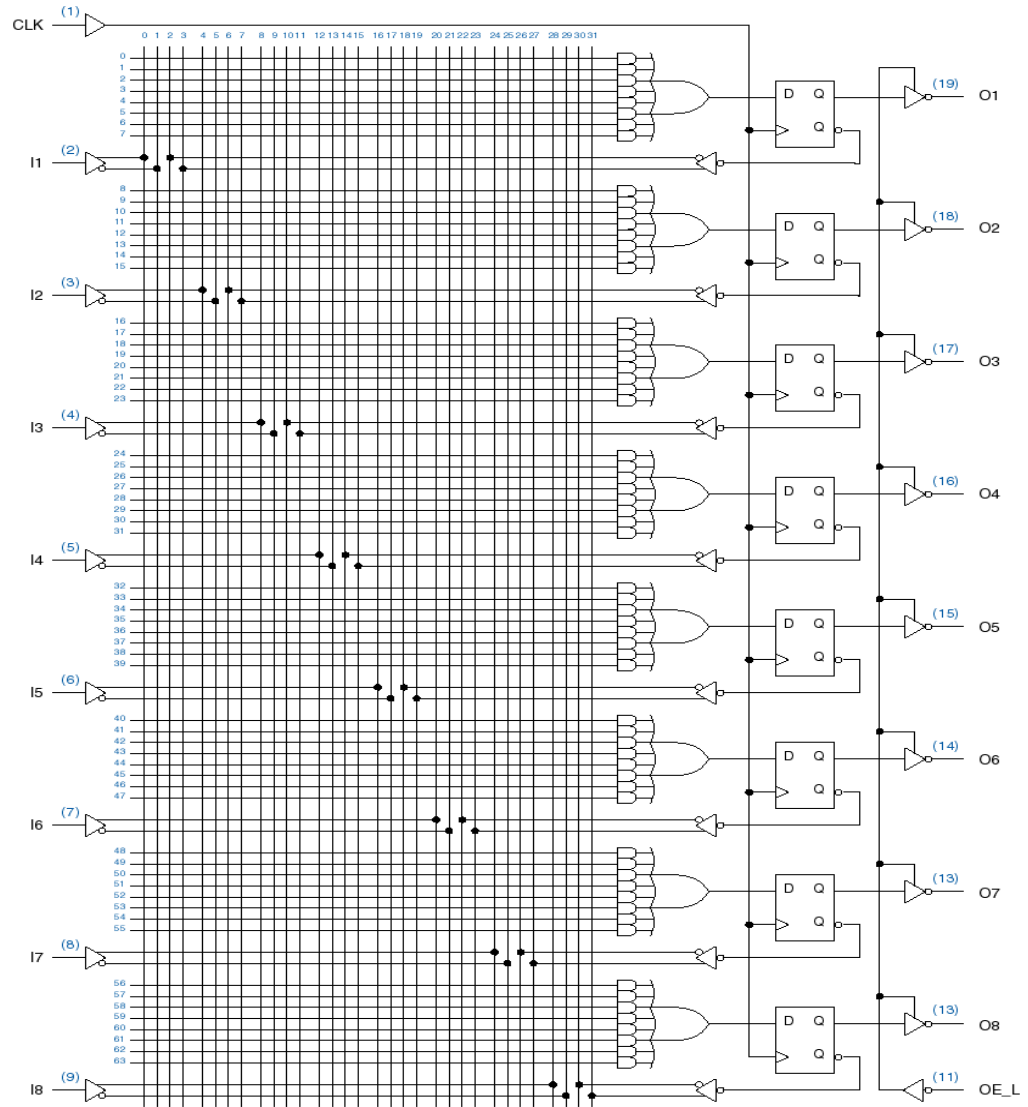

# Analysis of State Machines

## Characteristic Equations

Describe the next state (QN) of a flip-flop as function of current state (Q) and inputs:

$$QN = f(Q, \text{inputs}) \quad [\text{or } Q^* = f(Q, \text{inputs})]$$

Derived from basic function table for a given flip-flop type

# Characteristic Equations

Input	Present state	Next state
D	Q	Q*
0	0	0
0	1	0
1	0	1
1	1	1

$$Q^* = D$$

Input		Present state	Next state
S	R	Q	Q*
0	0	0	0
0	0	1	1
0	1	x	0
1	0	x	1
1	1	x	x

$$Q^* = S + R' Q$$

# Characteristic Equations

J	K	Q	Q*	
0	0	0	0	hold
0	0	1	1	
0	1	0	0	reset
0	1	1	0	
1	0	0	1	set
1	0	1	1	
1	1	0	1	toggle
1	1	1	0	

$$Q^* = J Q' + K' Q$$

EN	Q	Q*
0	0	0
0	1	1
1	0	1
1	1	0

$$Q^* = EN Q' + EN' Q$$

# Characteristic Equations Summary

<u>Device Type</u>	<u>Characteristic Eq.</u>
• S-R latch	$Q^* = S + R' Q$
• D latch	$Q^* = D$
• Edge-triggered D flip-flop	$Q^* = D$
• Master/slave S-R flip-flop	$Q^* = S + R' Q$
• Master/slave J-K flip-flop	$Q^* = J Q' + K' Q$
• Edge-triggered J-K flip-flop	$Q^* = J Q' + K' Q$
• T flip-flop	$Q^* = Q'$
• T flip-flop with enable	$Q^* = EN Q' + EN' Q$