



Faculty of Engineering

CSE115: Digital Design

**Lecture 24:
State Machines**

Suggested Reading

- Sections 7.3-7.6

Clocked Synch State-Machine Analysis

- **Analysis**

- How does a given circuit work? What does it do?
- How do input sequences map to output sequences?

- **Mealy Machine**


- Next state = F (current state, inputs)
- **Output** = G (current state, inputs)

- **Moore Machine**


- Next state = F (current state, inputs)
- **Output** = G (current state)

Diff between Mealy & Moore Machines

Mealy Machine

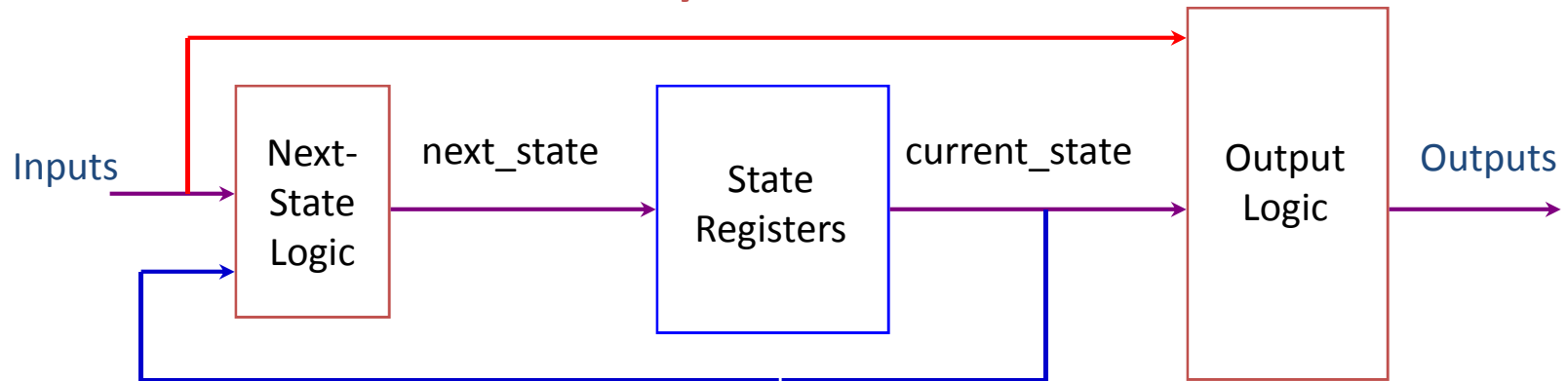

Moore Machine

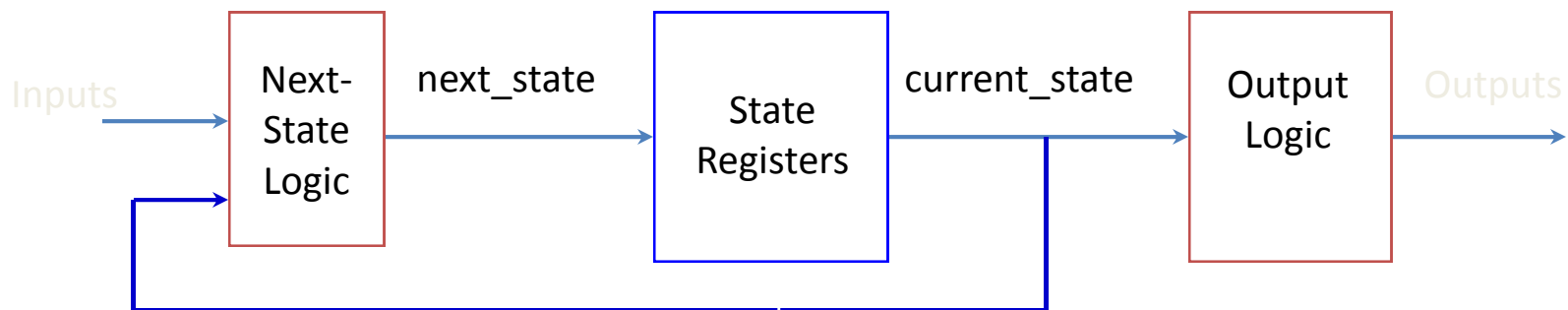


Basic Analysis of State Machines

1. Determine **next-state** and **output functions** **F** and **G**
2. Use **F** and **G** to construct a **state table**
3. Draw a **state diagram** that represents the state table in graphical form

Detailed Analysis of State Machines

- Find flip-flop input **excitation equations**, $D = f_1(\text{state}, \text{inputs})$
- Substitute excitation equations into flip-flop characteristic equations, giving **transition equations**, $Q^* = f_2(\text{state}, \text{inputs})$
- Construct a **transition table** from transition equations
- Find **output equations**, $\text{OUT} = g(\text{state})$ or $g(\text{state}, \text{inputs})$
- Add outputs to transition table to form **transition/output table**
- Name states in transition/output table, giving **state/output table**
- Draw a **state diagram** and **timing diagram** from state/output table

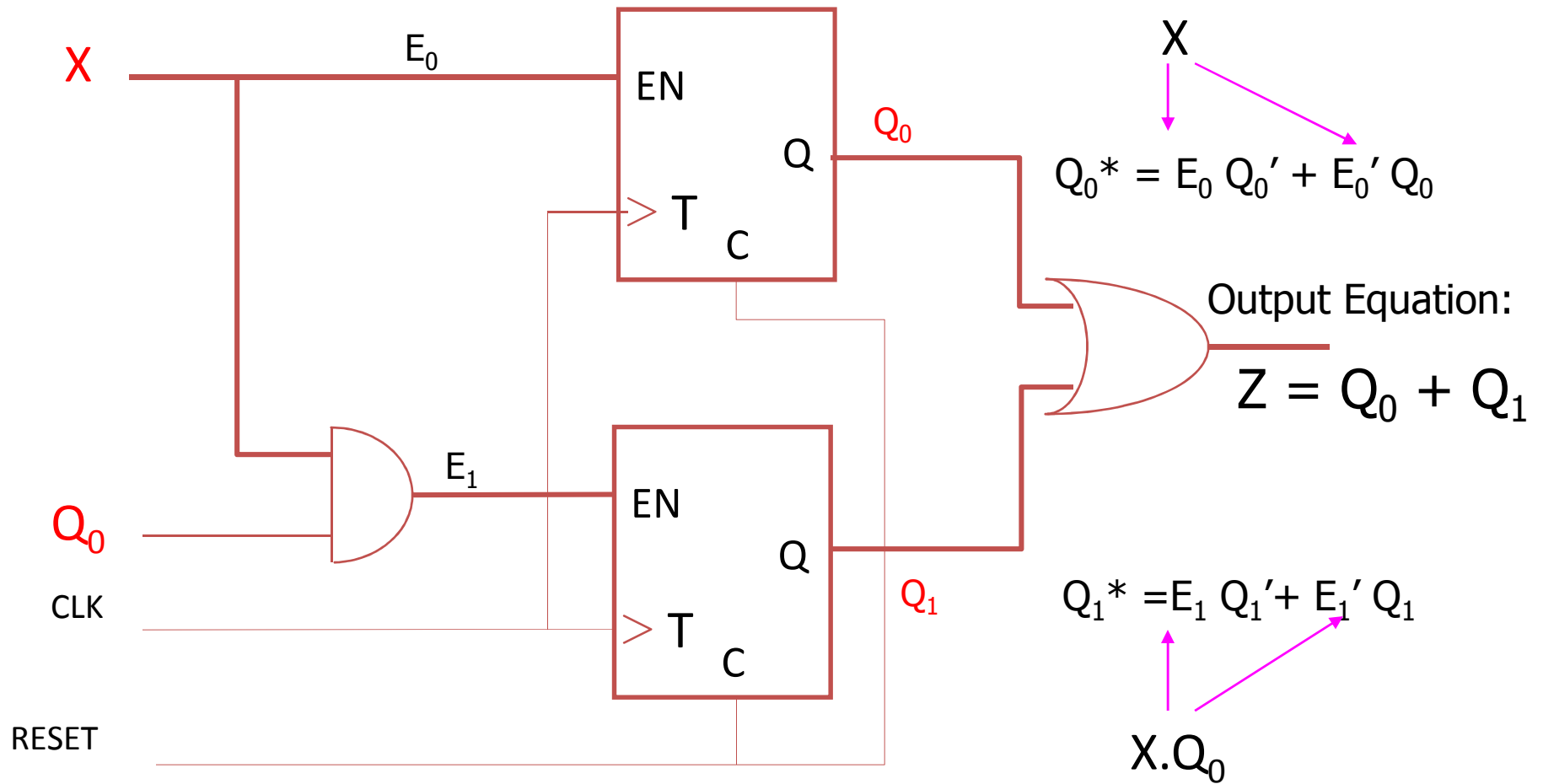Example 1 - State Machine with T flip-flops



Characteristic Equation for T: $Q^* = EN \cdot Q' + EN' Q$

Example 1 – Transition-State/Output Table

Transition Equations:

$$Q_0^* = X Q_0' + X' Q_0$$

$$Q_1^* = X Q_0 Q_1' + X' Q_1 + Q_0' Q_1$$

Output Equation:

$$Z = Q_0 + Q_1$$

Moore Machine

$Q_1 Q_0$	X		Z
	0	1	
A = 0 0	0 0	0 1	0
B = 0 1	0 1	1 0	1
C = 1 0	1 0	1 1	1
D = 1 1	1 1	0 0	1

$Q_1^* Q_0^*$




S	X		Z
	0	1	
A	A	B	0
B	B	C	1
C	C	D	1
D	D	A	1

S^*


Example 1 - State Diagram

S	X		Z
	0	1	
A	A	B	0
B	B	C	1
C	C	D	1
D	D	A	1

S^*

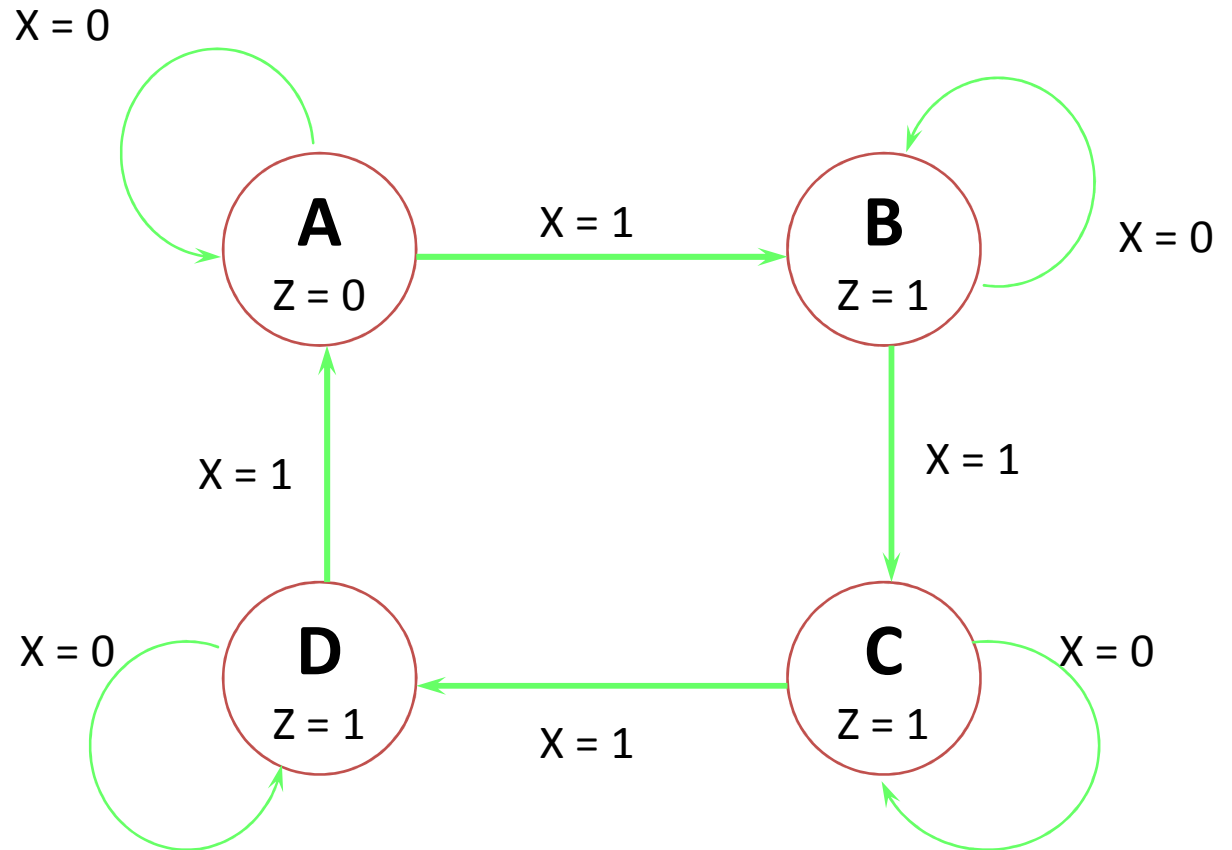


Example 1 - Timing diagram

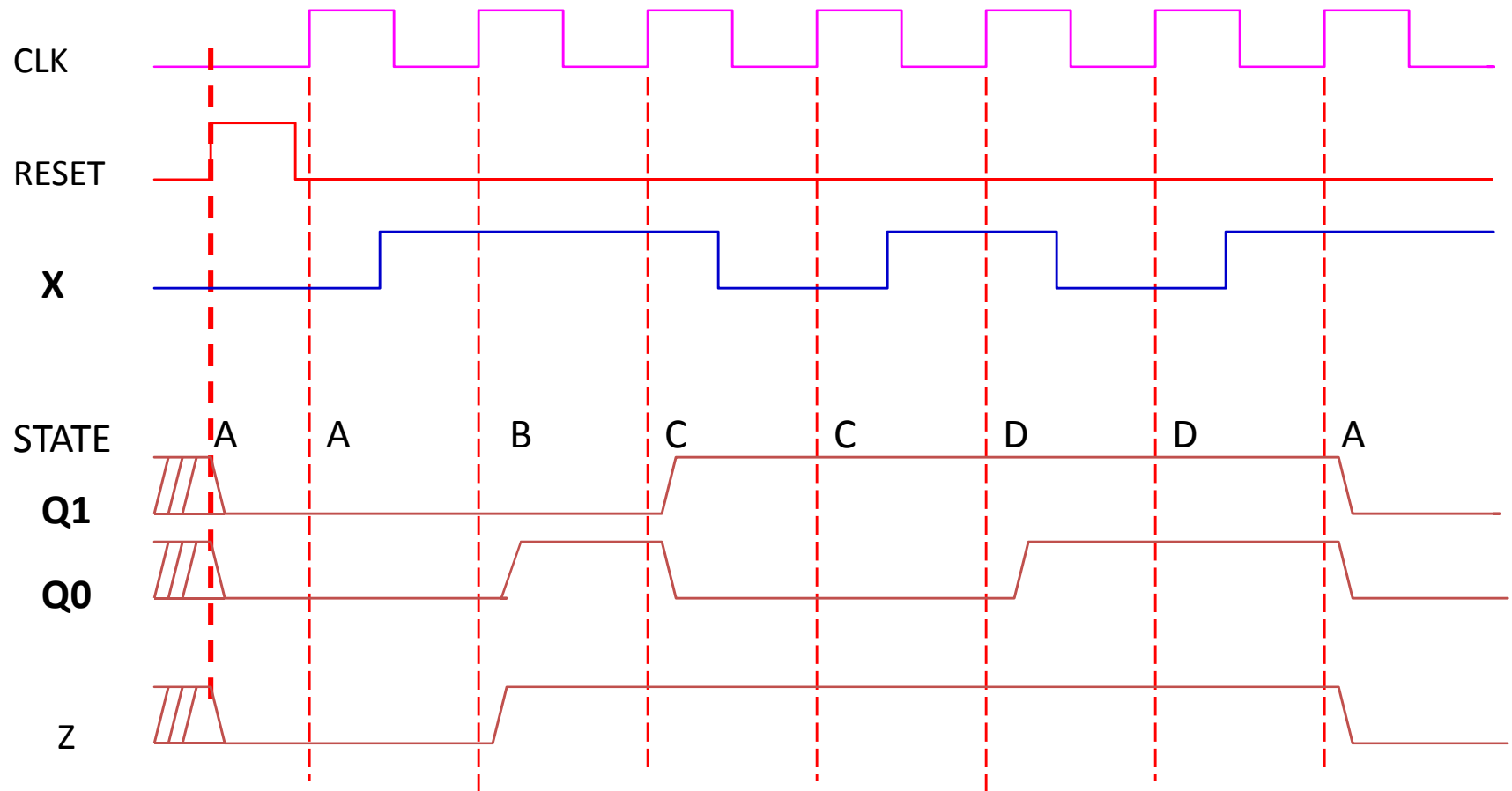

Example 2 - State Machine with D Flip-flops

Excitation Equations: $D0 = X Y' Q2'$; $D1 = X Q0$; $D2 = Y' + Q1$

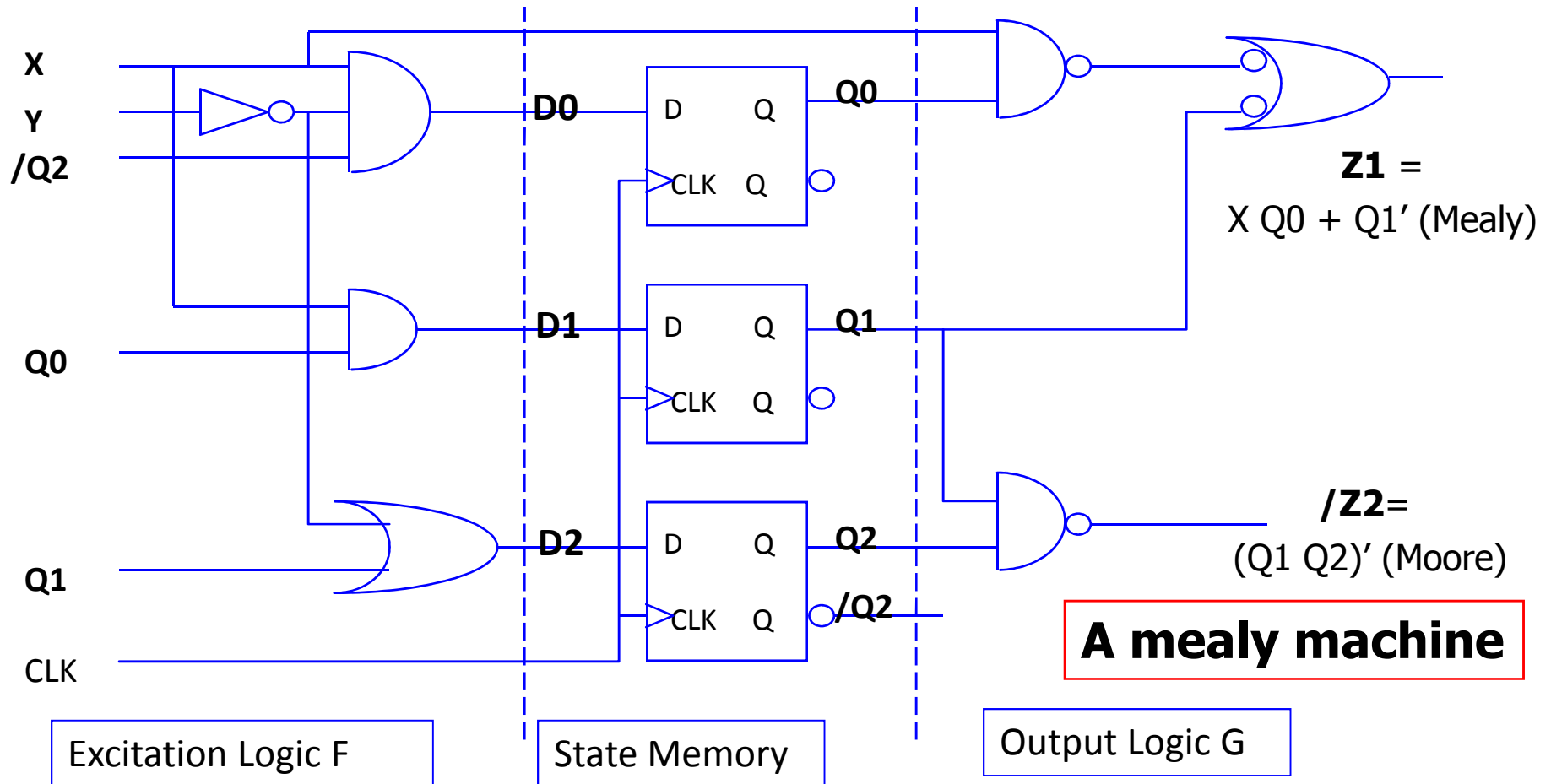

Example 2 - Equations

Characteristic Equation for D flip-flop: $Q^* = D$

Excitation Equations:

$$D_0 = X Y' Q_2'$$

$$D_1 = X Q_0$$

$$D_2 = Y' + Q_1$$



Next State Equations:

$$Q_0^* = X Y' Q_2'$$

$$Q_1^* = X Q_0$$

$$Q_2^* = Y' + Q_1$$

Output Equations:

$$Z_1 = X Q_0 + Q_1' \text{ (Mealy)}$$

$$Z_2 = (Q_1 Q_2)' \text{ (Moore)}$$

Example 2 - Transition / Output table

<i>Q2 Q1 Q0</i>	<i>XY</i>			
	<i>00</i>	<i>01</i>	<i>11</i>	<i>10</i>
A = 0 0 0	100, 11	000, 11	000, 11	101, 11
B = 0 0 1	100, 11	000, 11	010, 11	111, 11
C = 0 1 0	100, 01	100, 01	100, 01	101, 01
D = 0 1 1	100, 01	100, 01	110, 11	111, 11
E = 1 0 0	100, 11	000, 11	000, 11	100, 11
F = 1 0 1	100, 11	000, 11	010, 11	110, 11
G = 1 1 0	100, 00	100, 00	100, 00	100, 00
H = 1 1 1	100, 00	100, 00	110, 10	110, 10

Q2* Q1* Q0*, Z1 /Z2

$$Q0^* = X Y' Q2'$$

$$Q1^* = X Q0$$

$$Q2^* = Y' + Q1$$

$$Z1 = X Q0 + Q1'$$


$$Z2 = (Q1 Q2)'$$

Example 2 - State / Output table

<i>XY</i>				
<i>S</i>	<i>00</i>	<i>01</i>	<i>11</i>	<i>10</i>
A	E, 11	A, 11	A, 11	F, 11
B	E, 11	A, 11	C, 11	H, 11
C	E, 01	E, 01	E, 01	F, 01
D	E, 01	E, 01	G, 11	H, 11
E	E, 11	A, 11	A, 11	E, 11
F	E, 11	A, 11	C, 11	G, 11
G	E, 00	E, 00	E, 00	E, 00
H	E, 00	E, 00	G, 10	G, 10


S*, Z1 / Z2

Example 2 - State Diagram

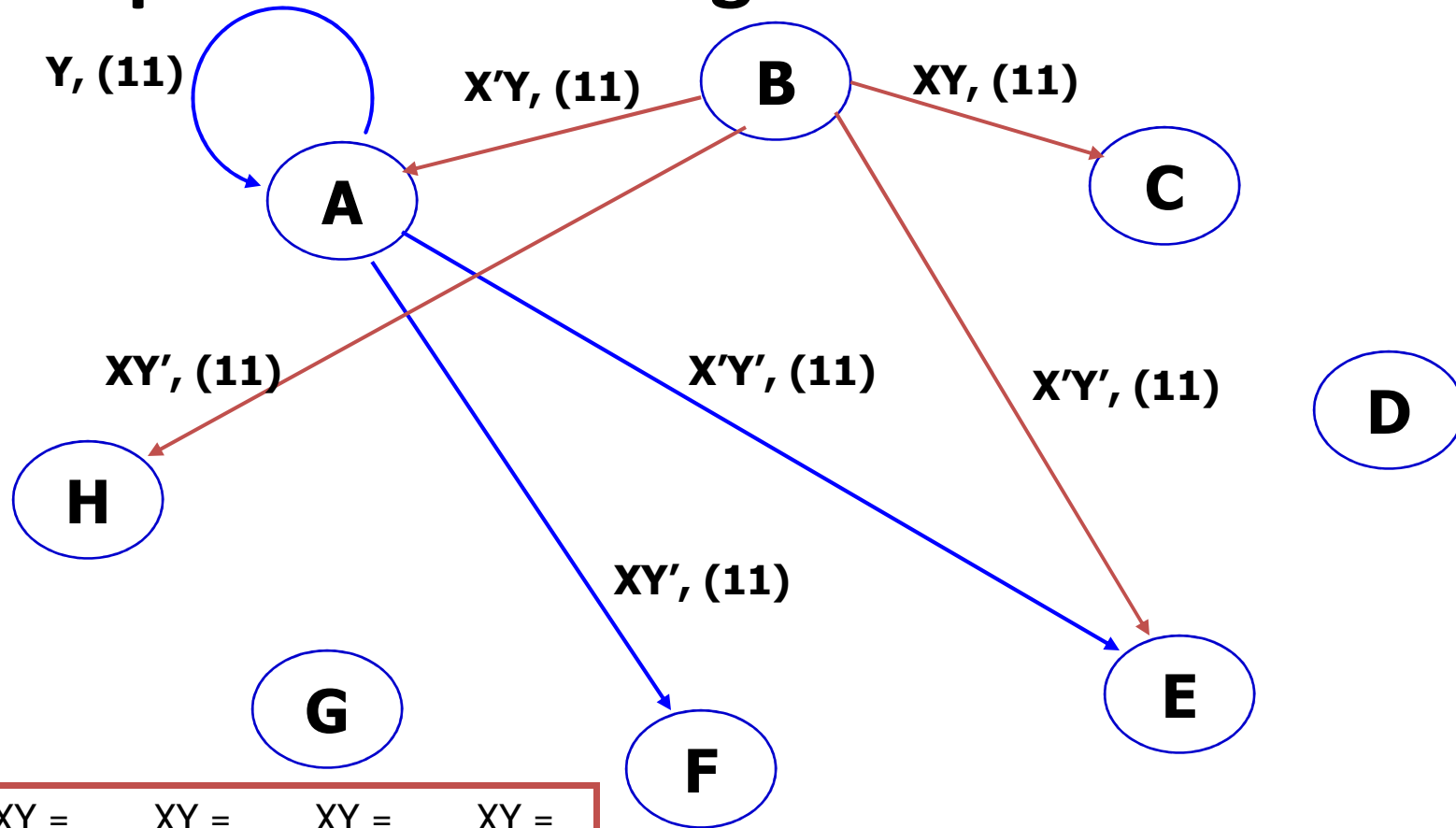

S	$XY = 00$	$XY = 01$	$XY = 11$	$XY = 10$
A	E, 11	A, 11	A, 11	F, 11
B	E, 11	A, 11	C, 11	H, 11

Example 3 - Circuit and Equations

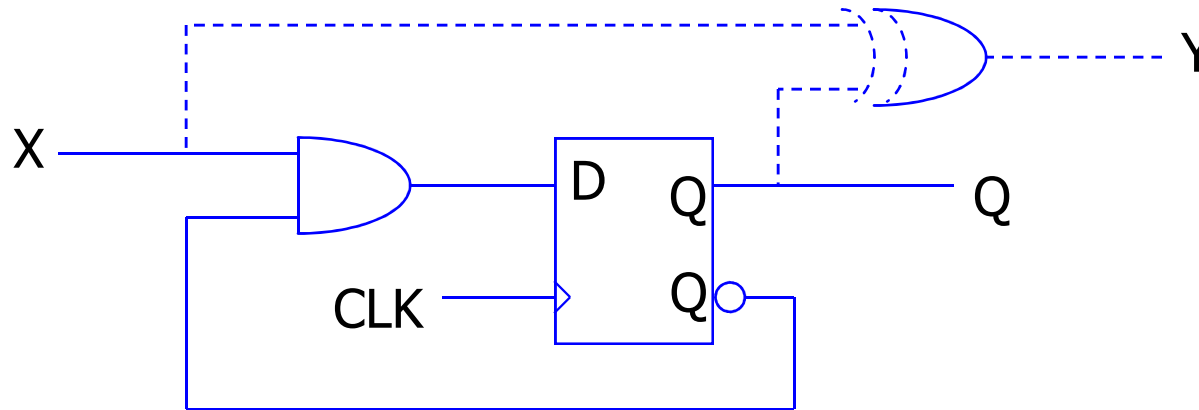

Moore

Excitation: $D = X \cdot Q' = Q^*$

Output: $Q = Q$

Mealy

Excitation: $D = X \cdot Q' = Q^*$

Output: $Y = X \oplus Q$

Example 3 - Tables

Excitation/Output Tables:

Q	X		Z
	0	1	
0	0	1	0
1	0	0	1

Q^*

Q	X	
	0	1
0	$0,0$	$1,1$
1	$0,1$	$0,0$

Q^*, Y

Moore

Mealey

State/Output Tables:


S	X		Z
	0	1	
A	A	B	0
B	A	A	1

Q^*

S	X	
	0	1
A	$A, 0$	$B, 1$
B	$A, 1$	$A, 0$

S^*, Y

Example 3 - State Diagrams

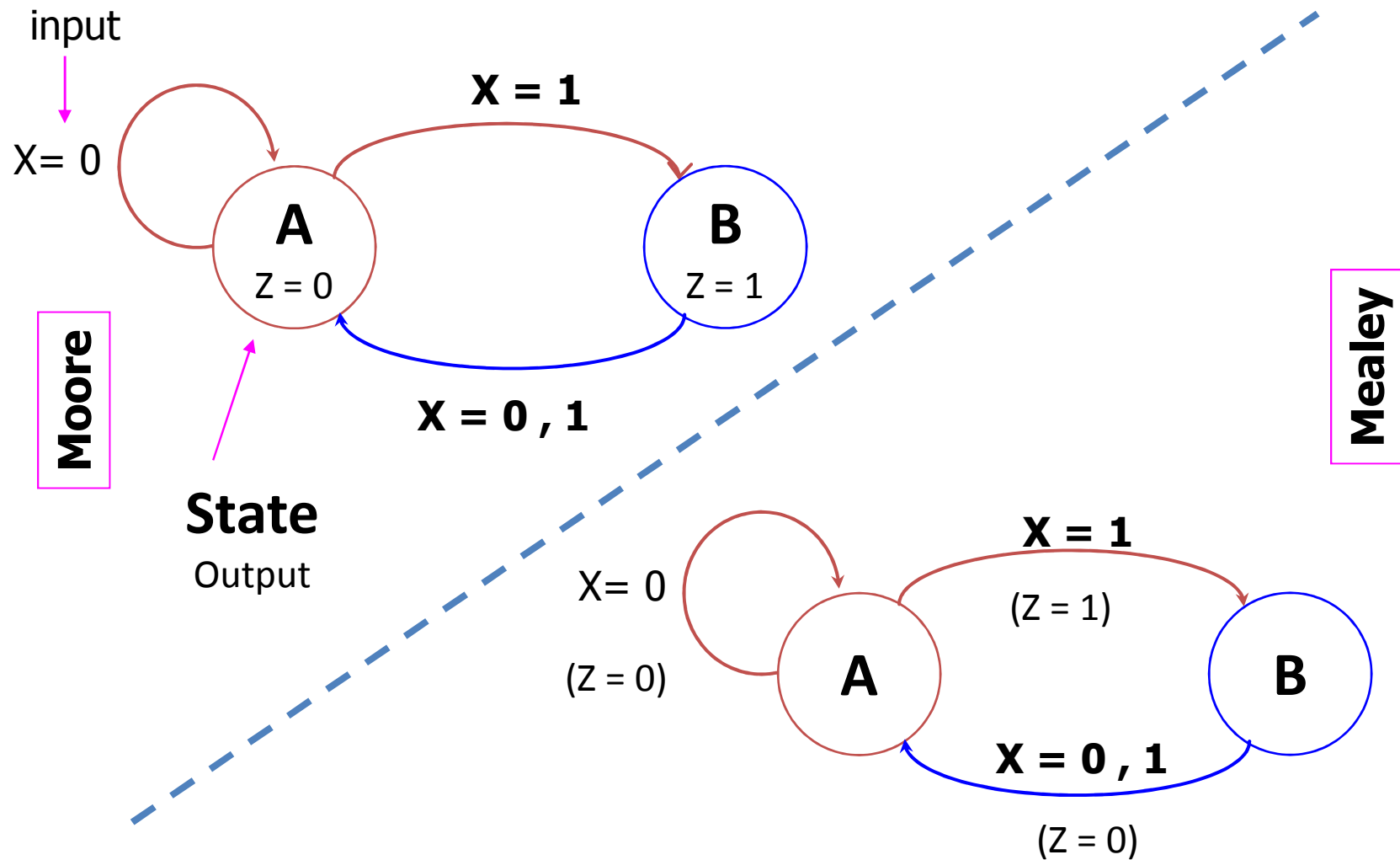

Synchronous Design with State Machines :


State Diagram Design

- **State Table** covers **all** input combinations and states
- **State Diagram** has arcs with input combinations or transition equations
 - **More graphical** than state table design
 - Often simpler, but error prone
 - No guarantee of all input combinations
 - Possibly ambiguous - possibly no next state or more than one next state for some input combinations

Example- T-bird Tail Lights

- 3 inputs - LEFT, RIGHT, HAZ


Layout of tail lights

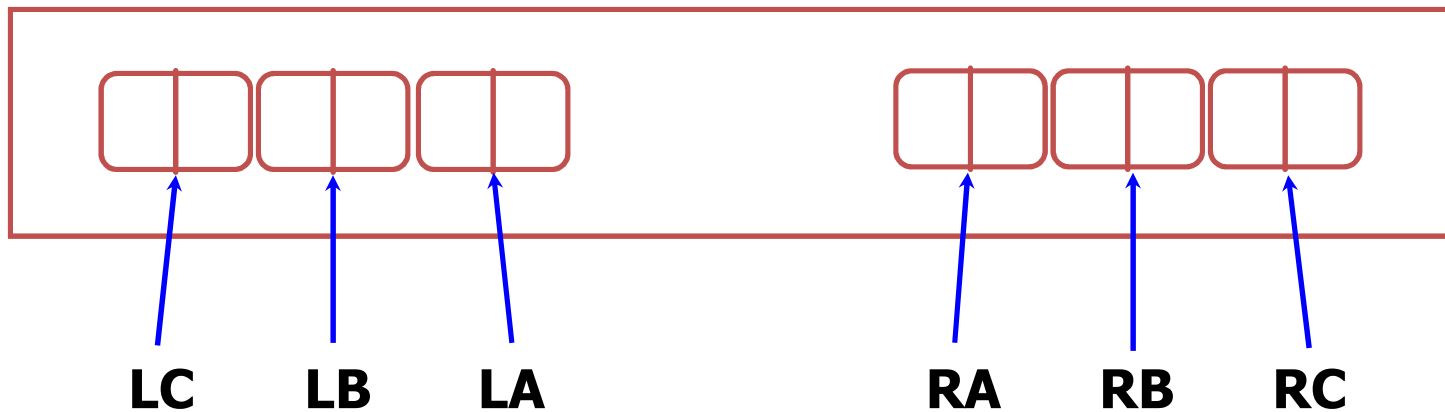

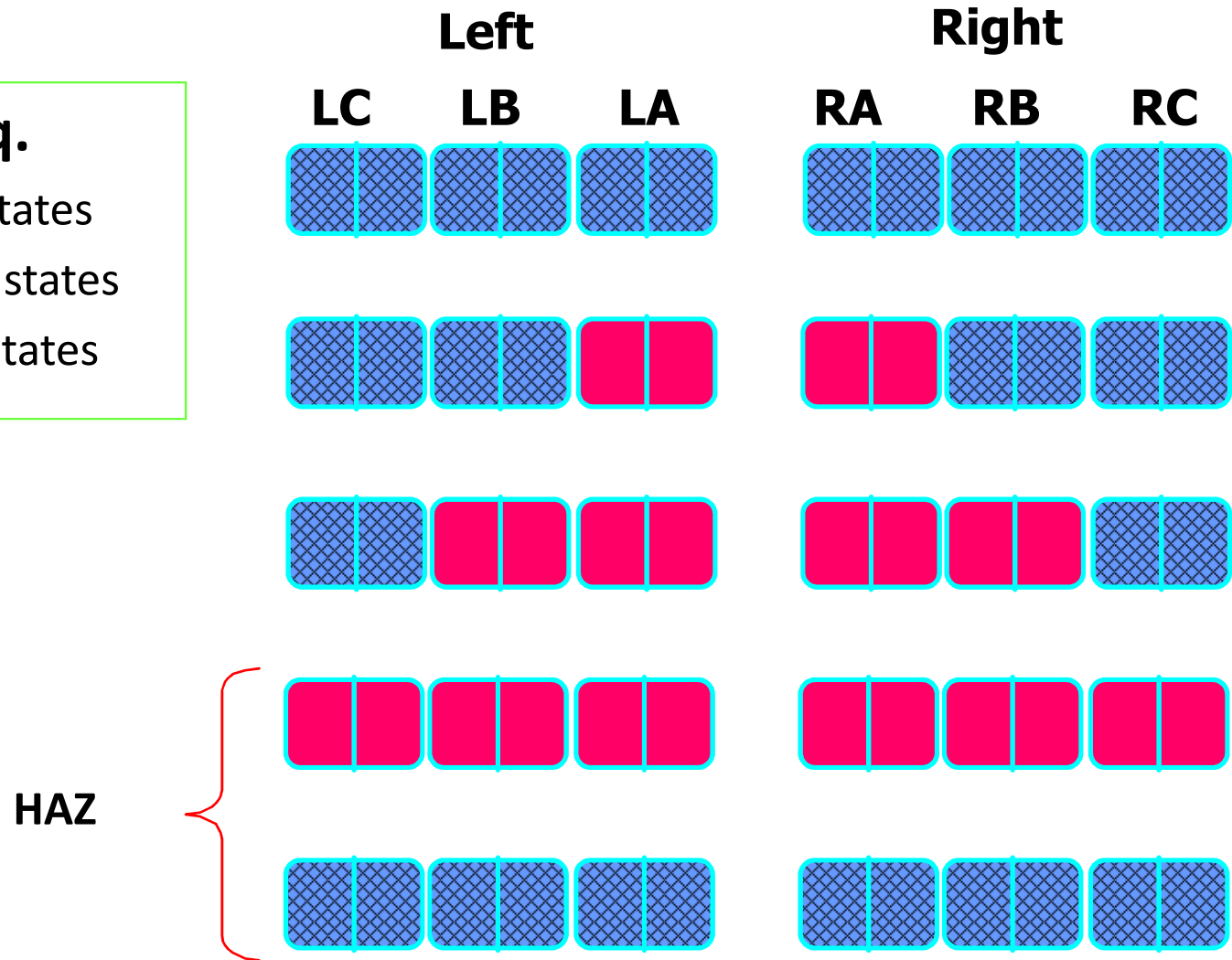Example- T-bird Tail Lights


Tail Light seq.

- Left = 4 states
- Right = 4 states
- HAZ = 2 states



Example- First State Diagram

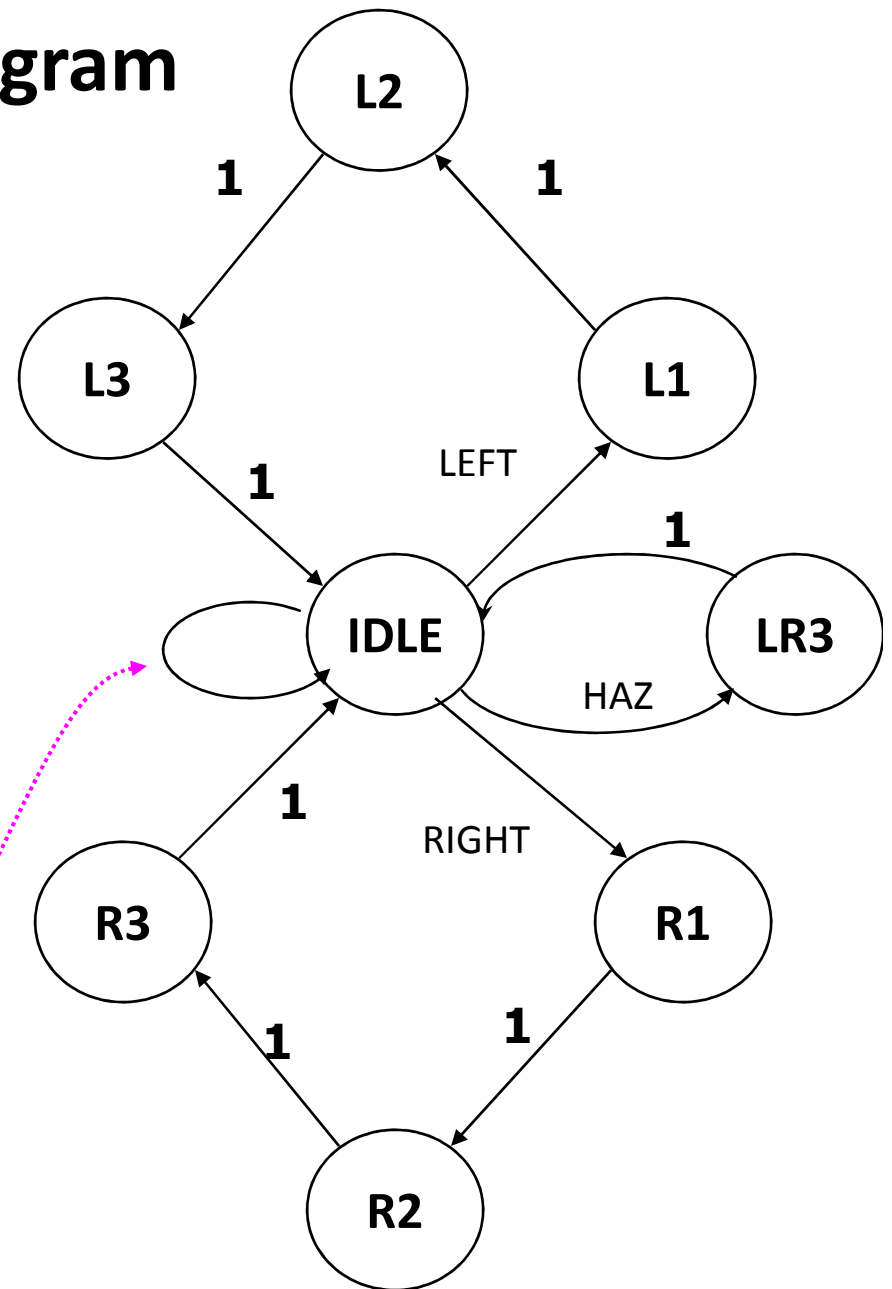1. Moore Machine design
2. LEFT + RIGHT + HAZ starts sequence, continues unconditionally
3. If multiple inputs TRUE? → multiple next states! PROBLEM!
4. Transitions need to be **mutually exclusive** and **all inclusive**




(LEFT + RIGHT + HAZ)'

Example- Output Table

State	LC	LB	LA	RA	RB	RC
IDLE	0	0	0	0	0	0
L1	0	0	1	0	0	0
L2	0	1	1	0	0	0
L3	1	1	1	0	0	0
R1	0	0	0	1	0	0
R2	0	0	0	1	1	0
R3	0	0	0	1	1	1
LR3	1	1	1	1	1	1

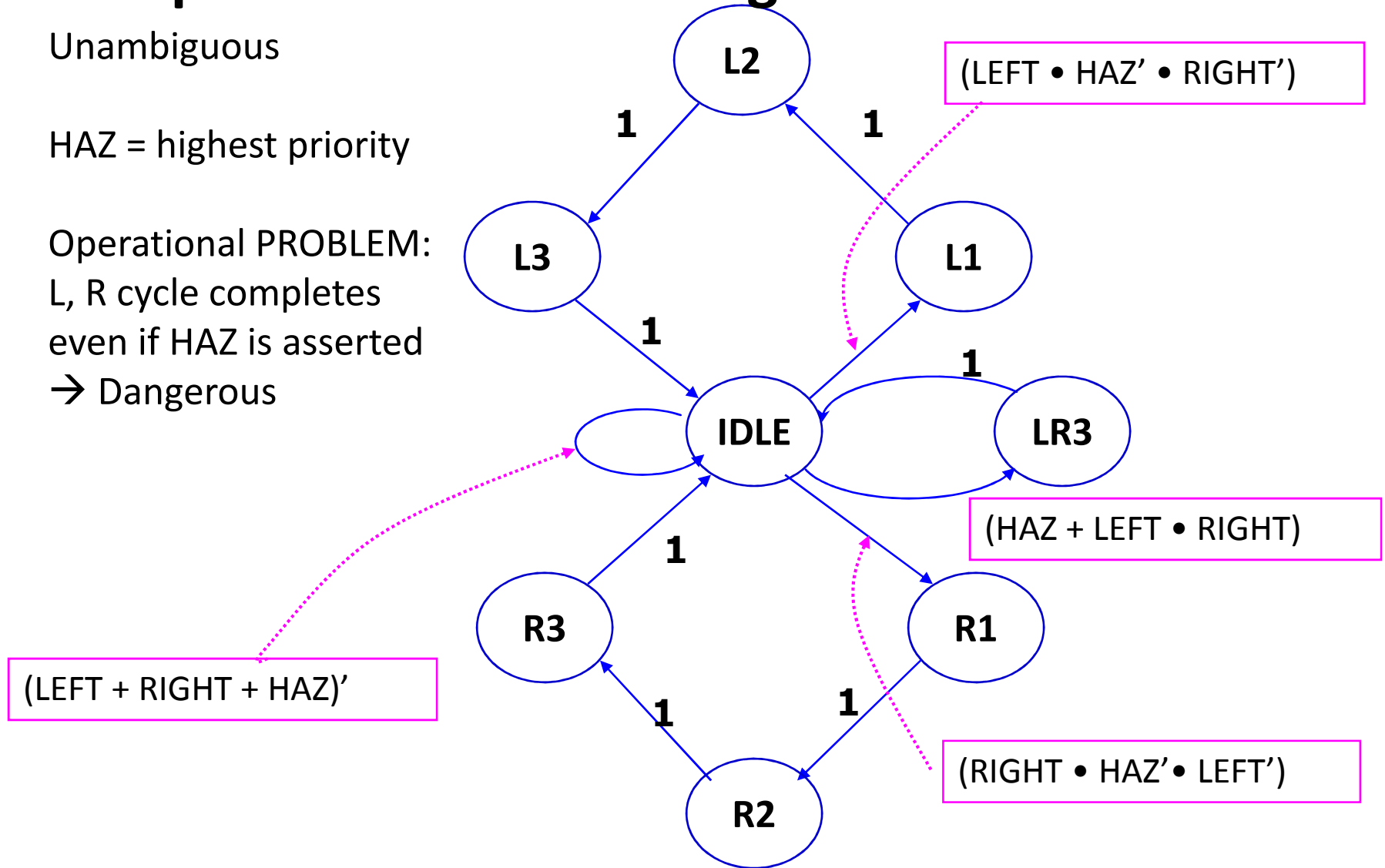
Example- Second State Diagram

- Unambiguous
- HAZ = highest priority
- Operational PROBLEM:
L, R cycle completes even if HAZ is asserted
→ Dangerous



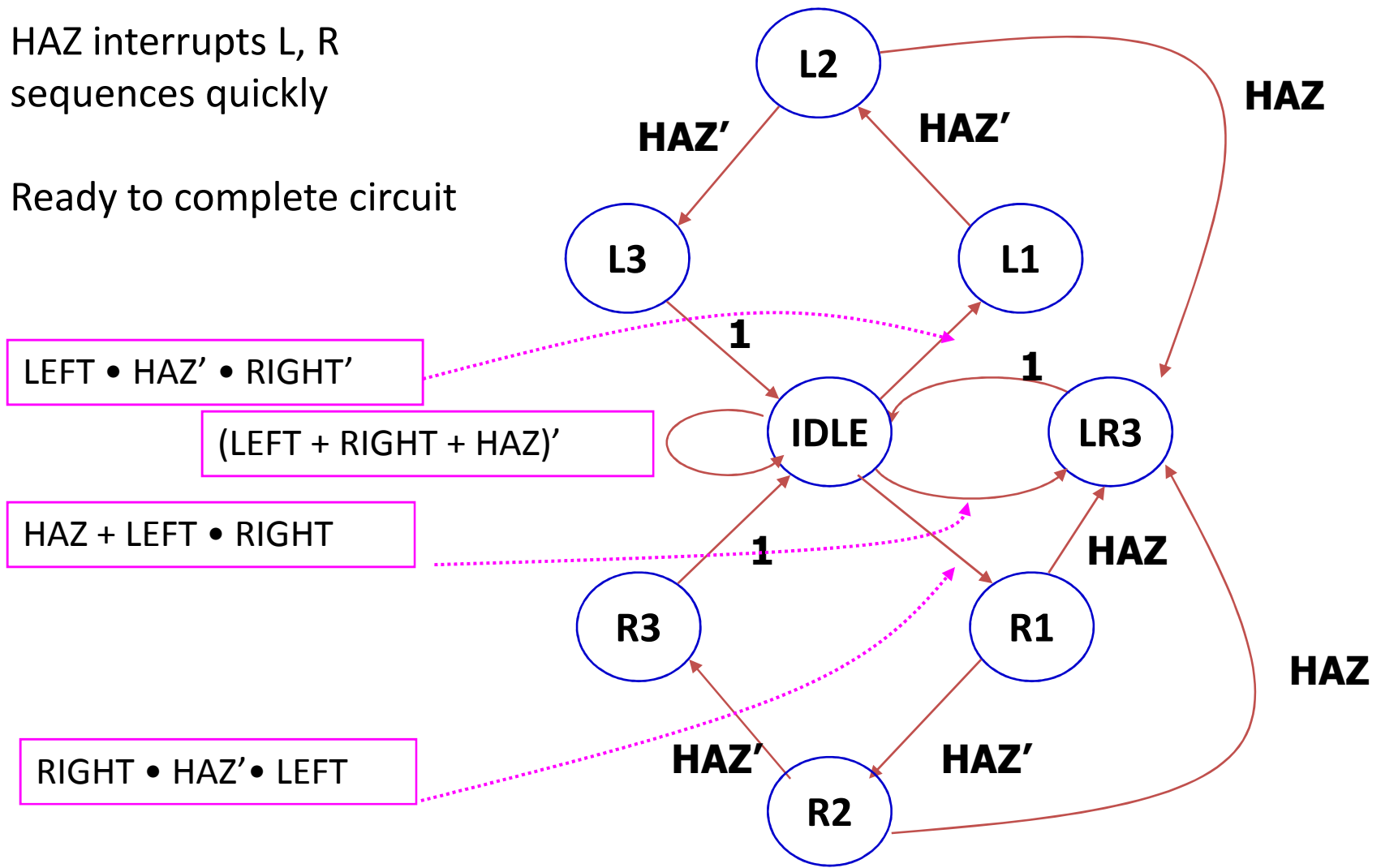Example- Third State Diagram

- HAZ interrupts L, R sequences quickly
- Ready to complete circuit



Example- State Assignment

State Assignment:

- Initially all zeros
- Q2** determines Left vs. Right turn sequence
- Q1 Q0** count gray-code sequence to minimize state variable transitions

Example- Transition List

Alternative to transition table for state diagram design method

One row per transition

S	Q2 Q1 Q0	Transition Expr	S*	Q2*Q1*Q0*
IDLE	0 0 0	(LEFT+RIGHT+HAZ)'	IDLE	0 0 0
IDLE	0 0 0	LEFT+HAZ'.RIGHT'	L1	0 0 1
IDLE	0 0 0	HAZ+LEFT.RIGHT	LR3	1 0 0
IDLE	0 0 0	RIGHT.HAZ'.LEFT'	R1	1 0 1
L1	0 0 1	HAZ'	L2	0 1 1
L1	0 0 1	HAZ'	LR3	1 0 0
L2	0 1 1	HAZ'	L3	0 1 0
L2	0 1 1	HAZ	LR3	1 0 0
L3	0 1 0	1	IDLE	0 0 0
R1	1 0 1	HAZ'	R2	1 1 1
R1	1 0 1	HAZ	LR3	1 0 0
R2	1 1 1	HAZ'	R3	1 1 0
R2	1 1 1	HAZ	LR3	1 0 0
R3	1 1 0	1	IDLE	0 0 0
LR3	1 0 0	1	IDLE	0 0 0

Example- Next State and Output Generation

$$Q2^* = Q2'.Q1'.Q0'.(HAZ+RIGHT) + Q2'.Q0.HAZ+Q2.Q0$$

$$Q1^* = Q0.HAZ'$$

$$Q0^* = Q2.Q1'.HAZ'.(LEFT\oplus RIGHT) + Q1'.Q0.HAZ'$$

Example- Output Table

	State	LC	LB	LA	RA	RB	RC
000	IDLE	0	0	0	0	0	0
001	L1	0	0	1	0	0	0
011	L2	0	1	1	0	0	0
010	L3	1	1	1	0	0	0
101	R1	0	0	0	1	0	0
111	R2	0	0	0	1	1	0
110	R3	0	0	0	1	1	1
100	LR3	1	1	1	1	1	1

$$LA = Q2'.Q0 + Q2'.Q1 + Q2.Q1'.Q0'$$

$$LB = Q2'.Q1 + Q2.Q1'.Q0'$$


$$LC = Q2'.Q1.Q0' + Q2.Q1'.Q0'$$

$$RA = Q2$$

$$RB = Q2.Q0' + Q2.Q1$$

$$RC = Q2.Q0'$$

Example- Circuit Block Diagram

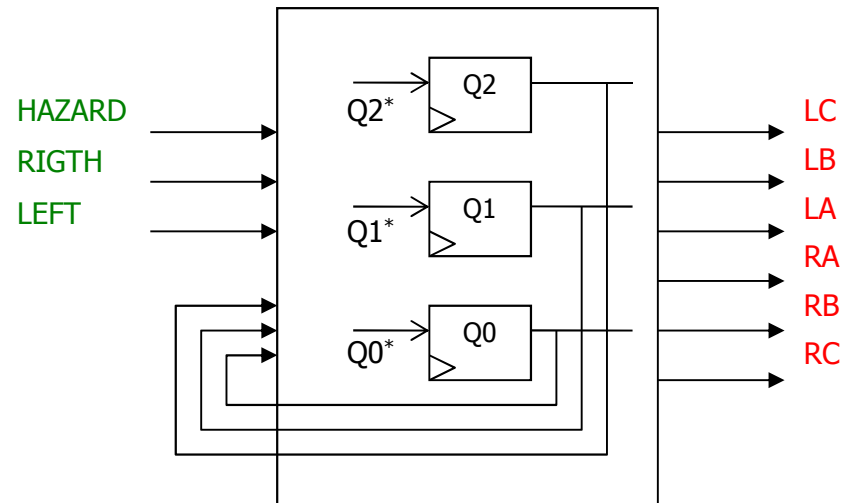

Example- Circuit Diagram

