



Faculty of Engineering


CSE115: Digital Design

Lecture 25:
Timing, Counters and Shift Registers

Suggested Reading

- Sections 8.1.4, 8.2.5, 8.4, 8.5

Synchronous System - Detailed Timing

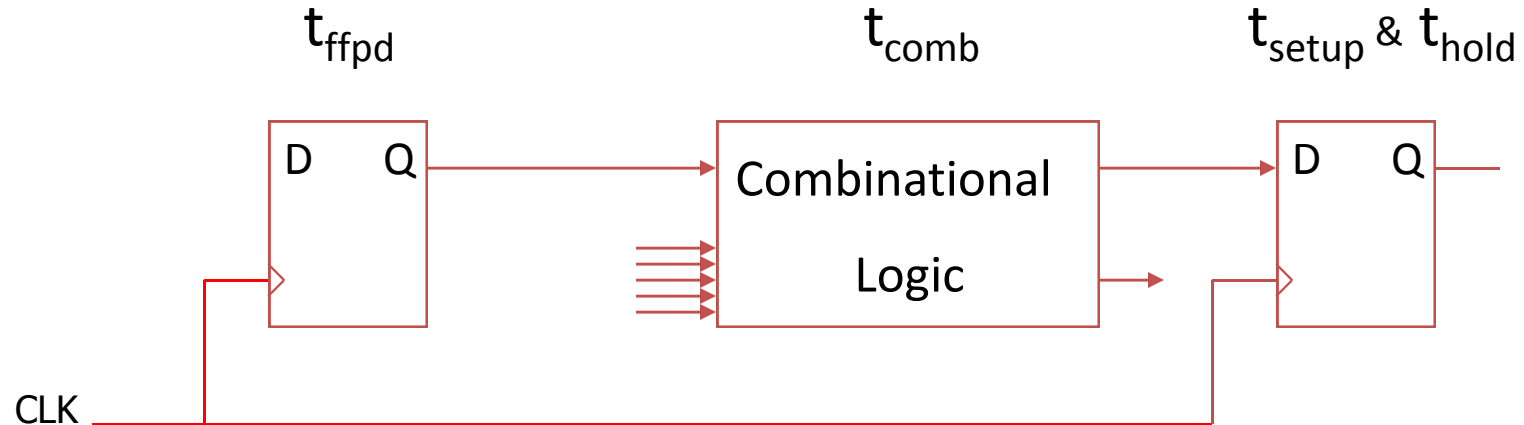


t_{ffpd} - CLK to Q, FF propagation delay (min, max)

t_{comb} - combinational logic delay (min, max)


t_{setup} - input stable before clock (min)

t_{hold} - input stable after clock (min)

Synchronous System - Detailed Timing

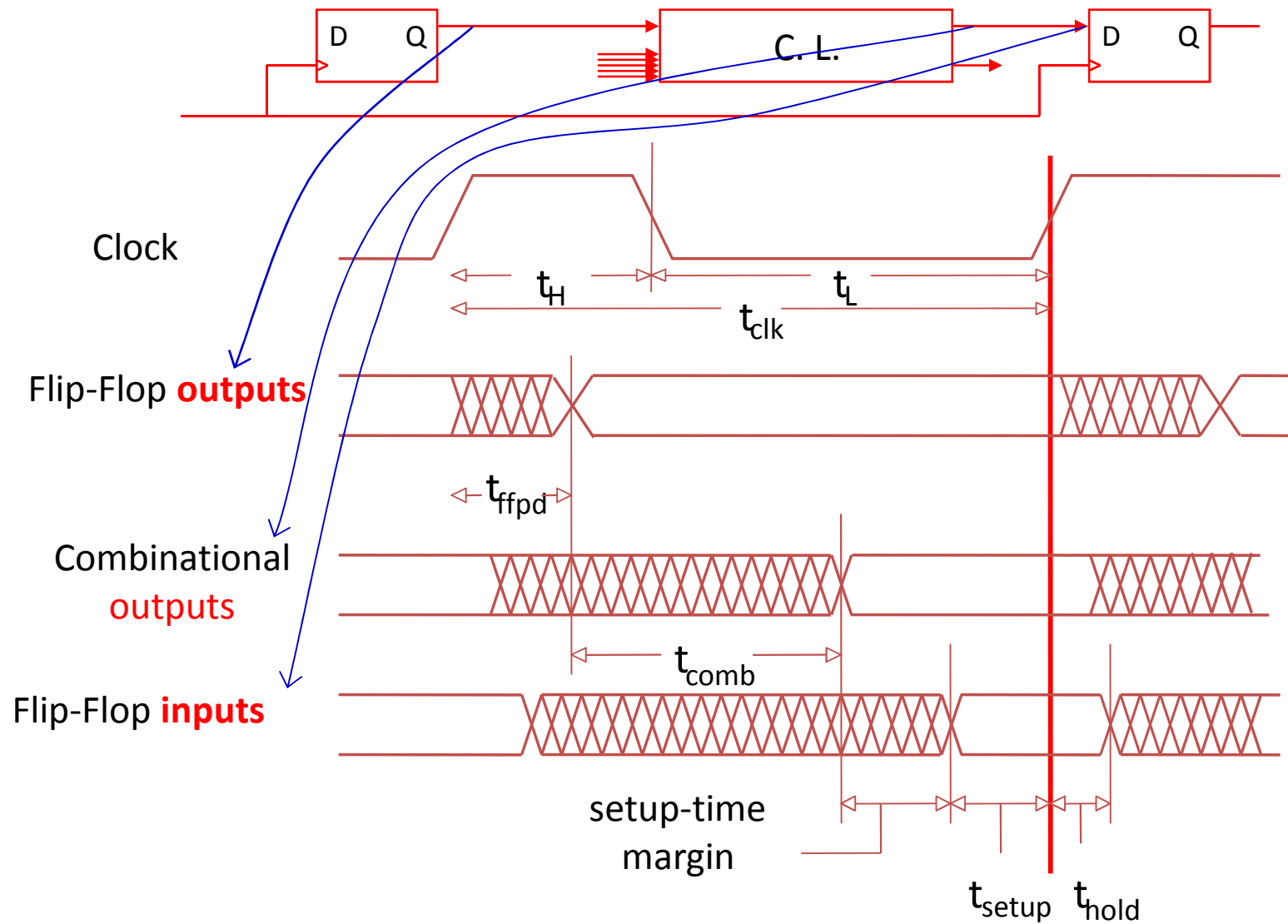

Synchronous System - Detailed Timing

 

Required


$$t_{\text{clk,min}} > t_{\text{ffpd,max}} + t_{\text{comb,max}} + t_{\text{setup,min}}$$

Difference \rightarrow Setup time margin

$$t_{\text{ffpd,min}} + t_{\text{comb,min}} > t_{\text{hold,min}}$$

Difference \rightarrow Hold time margin

Synchronous System Example

 

$t_{\text{comb}} = 2 \text{ ns, min and } 20 \text{ ns, max}$

$t_{\text{ffpd}} = 3 \text{ ns, min and } 15 \text{ ns, max}$

$t_{\text{setup}} = 5 \text{ ns, min}$

$t_{\text{hold}} = 2 \text{ ns, min}$

Setup Margin: $t_{\text{clk,min}} > t_{\text{ffpd,max}} + t_{\text{comb,max}} + t_{\text{setup,min}}$

Hold Time Margin: $t_{\text{ffpd,min}} + t_{\text{comb,min}} > t_{\text{hold,min}}$




At 10 MHz clk

Setup margin: $100 - (15 + 20 + 5) = 60 \text{ ns}$

Hold Margin: $(3 + 2) - 2 = 3 \text{ ns}$



Max Frequency: $t_{\text{clk,min}} \geq 40 \text{ ns} \rightarrow f_{\text{max}} \leq 25 \text{ MHz}$

74x175: Multibit Registers and Latches

 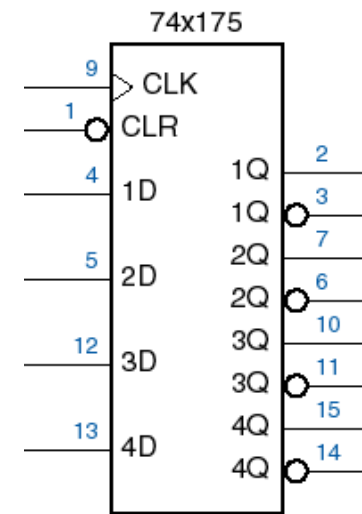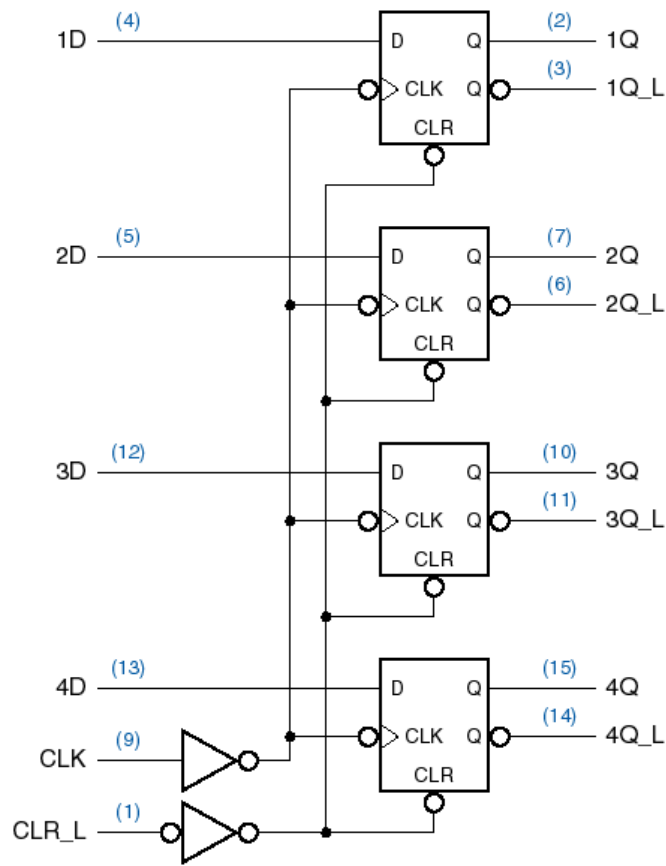




74x373: Octal Latch

  Latch: output follows input when C is asserted



74x374: Octal Register


Register: Edge-Triggered Behavior

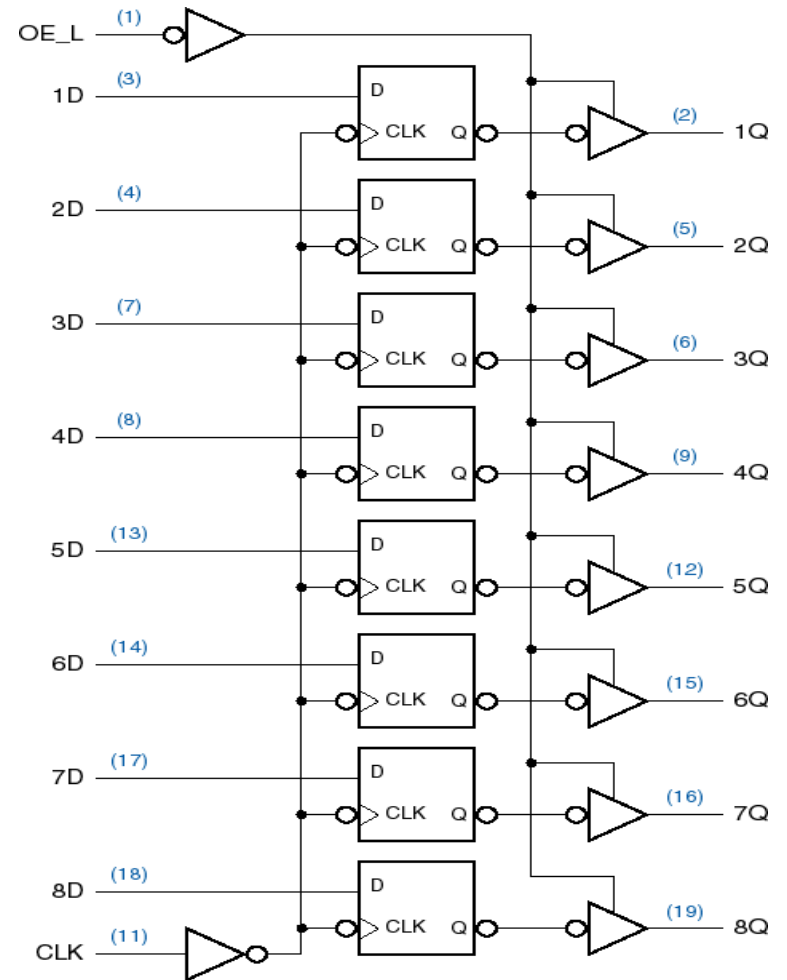 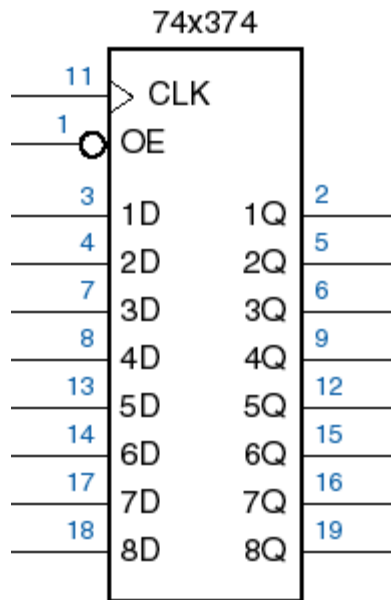

Counters


Clocked sequential circuit with single-cycle state diagram

 Modulo-m counter = **Divide**-by-m counter




Synchronous Counter: Serial Enable Logic

 1. Flip-flops enabled when all lower flip-flops = 1.
2. Enable propagates **serially** — limits speed. Requires: $(n-1) \cdot t < T_{CLK}$
3. All flip-flop outputs change simultaneously t_{cQ} after CLK
4. Most Frequently Used Type of Counter




Synchronous Counter: Parallel Enable Logic

 1. Single-level enable logic per flip-flop
2. Fastest and most complex type of counter. Requires $\mathbf{d t} < \mathbf{T_{CLK}}$
3. All outputs change simultaneously t_{cQ} after CLK




74x163

4-bit Counter

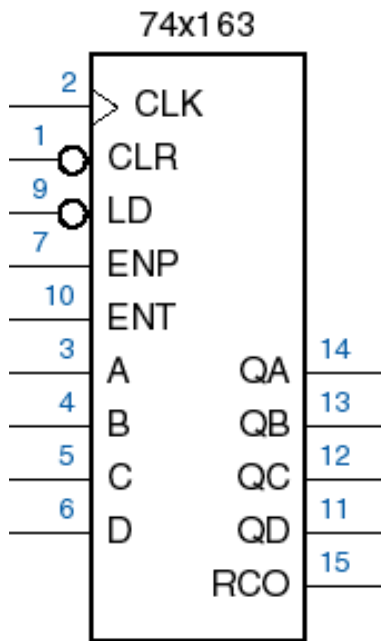


Inputs				Current State				Next State			
CLR_L	LD_L	ENT	ENP	QD	QC	QB	QA	QD*	QC*	QB*	QA*
0	x	x	x	x	x	x	x	0	0	0	0
1	0	x	x	x	x	x	x	D	C	B	A
1	1	0	x	x	x	x	x	QD	QC	QB	QA
1	1	x	0	x	x	x	x	QD	QC	QB	QA
1	1	1	1	0	0	0	0	0	0	0	1
1	1	1	1	0	0	0	1	0	0	1	0
1	1	1	1	0	0	1	0	0	0	1	1
1	1	1	1	0	0	1	1	0	1	0	0
1	1	1	1	0	1	0	0	0	1	0	1
1	1	1	1	0	1	0	1	0	1	1	0
1	1	1	1	0	1	1	0	0	1	1	1
1	1	1	1	0	1	1	1	1	0	0	0
1	1	1	1	1	0	0	0	1	0	0	1
1	1	1	1	1	0	0	1	1	0	1	0
1	1	1	1	1	0	1	0	1	0	1	1
1	1	1	1	1	0	1	1	1	1	0	0
1	1	1	1	1	1	1	0	0	1	0	1
1	1	1	1	1	1	1	0	1	1	1	0
1	1	1	1	1	1	1	1	0	1	1	1
1	1	1	1	1	1	1	1	0	0	0	0

74x163 4-bit Counter

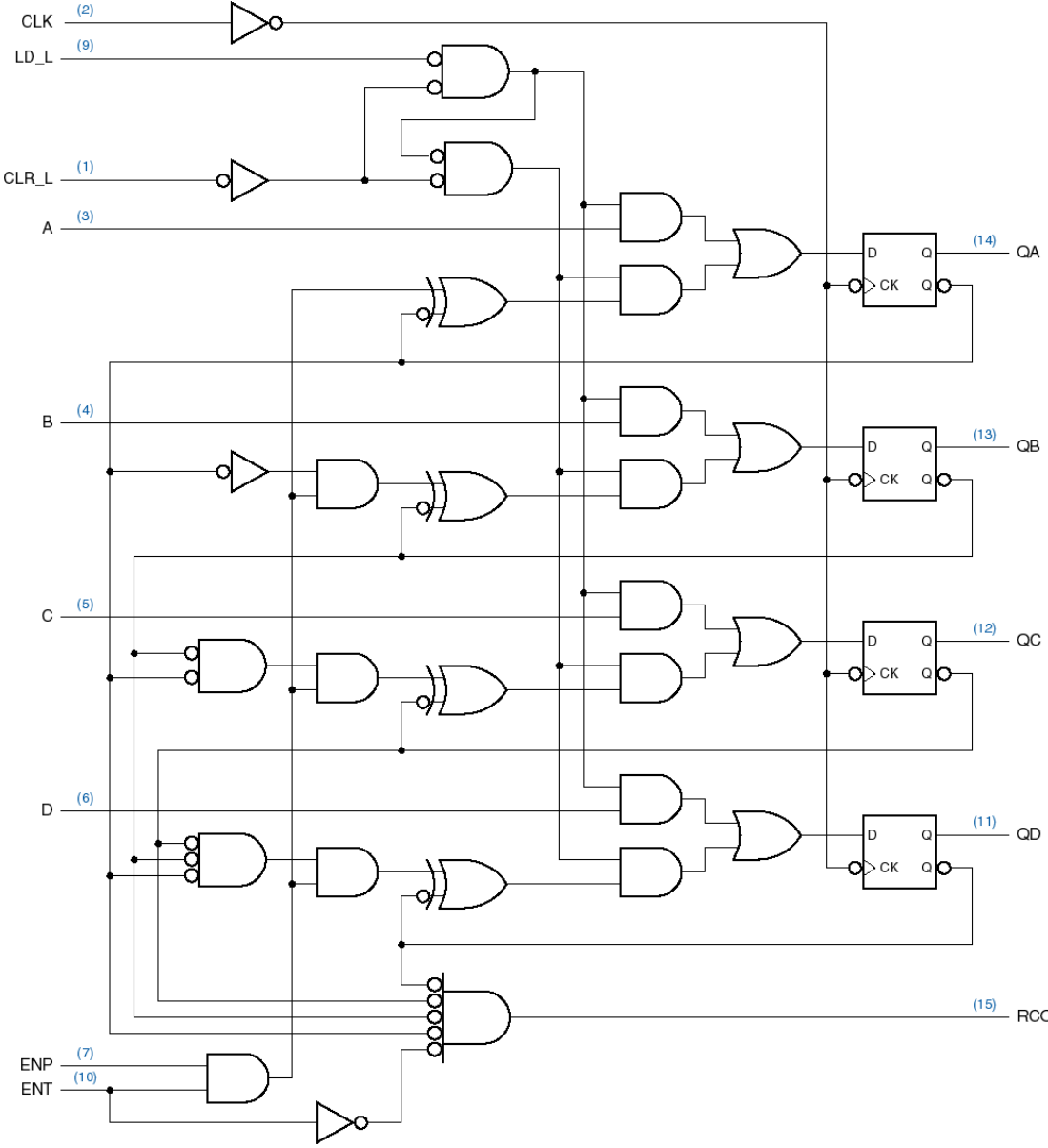


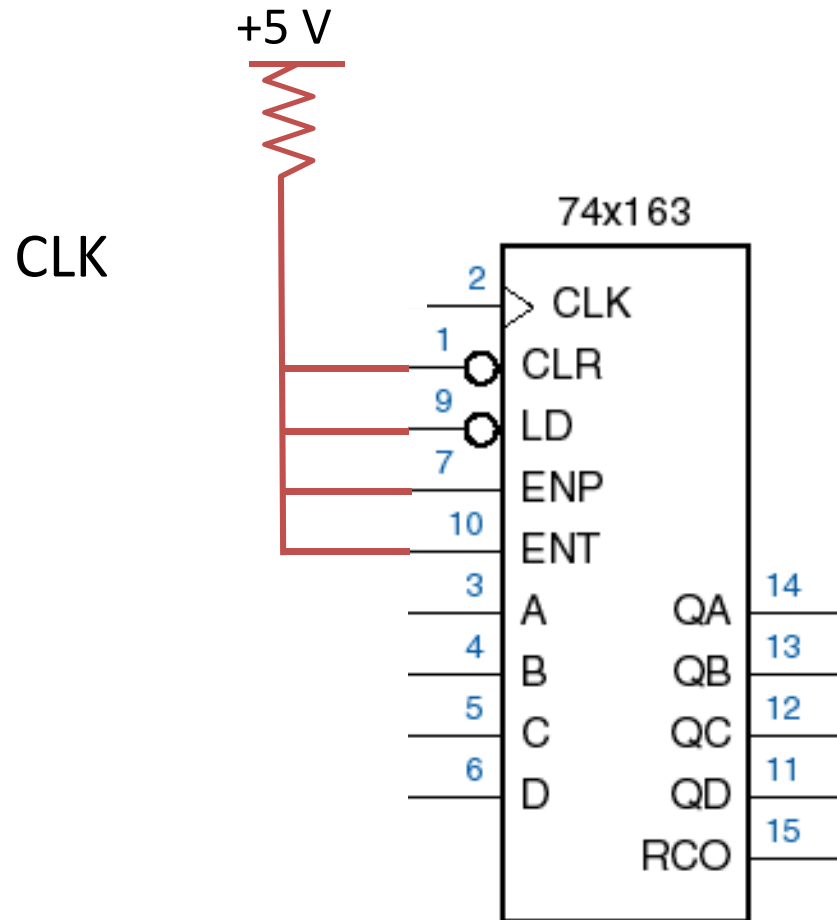Counter Application-1: Free Running Modulo-16 Counter




0, 1, 2, 3, 4, ..., 15, 0, 1, ...

Counter Application-1:

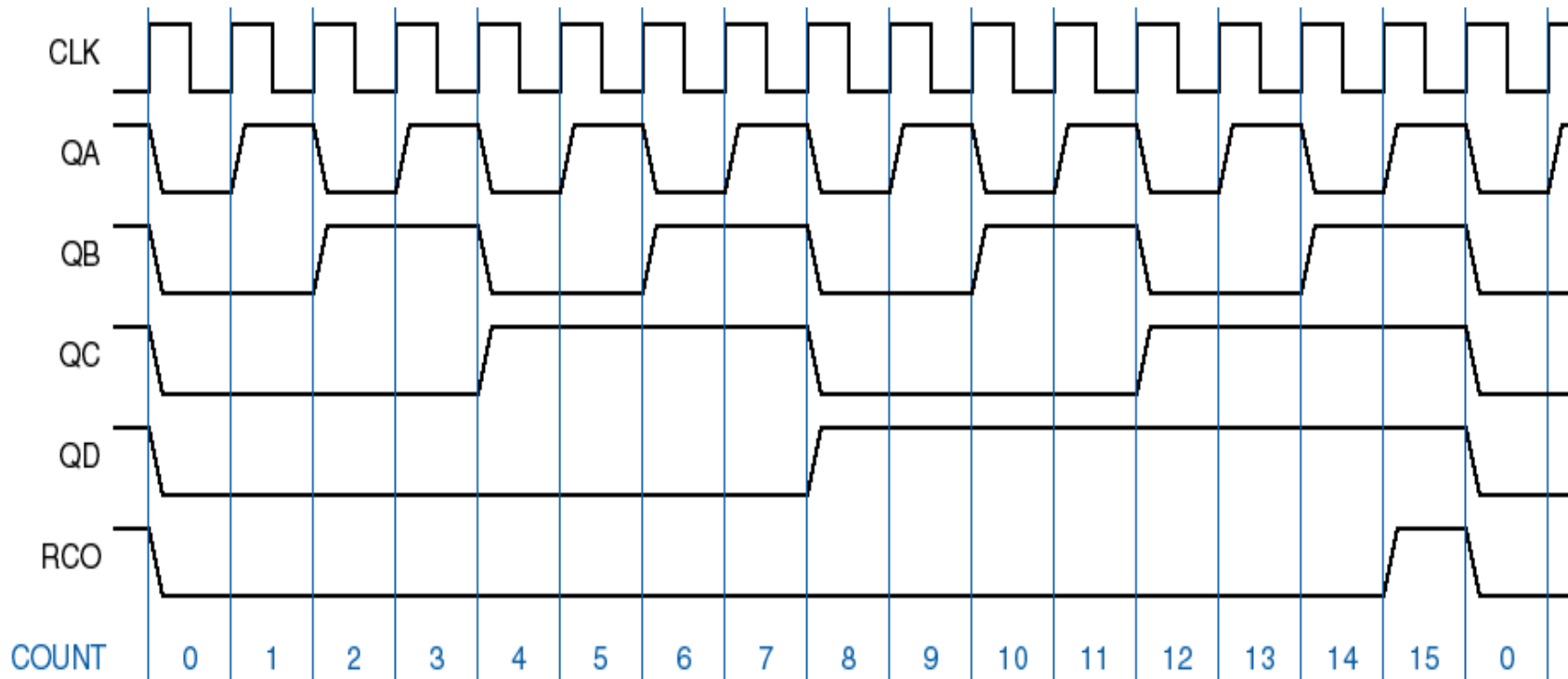

“Divide-by-16” counter

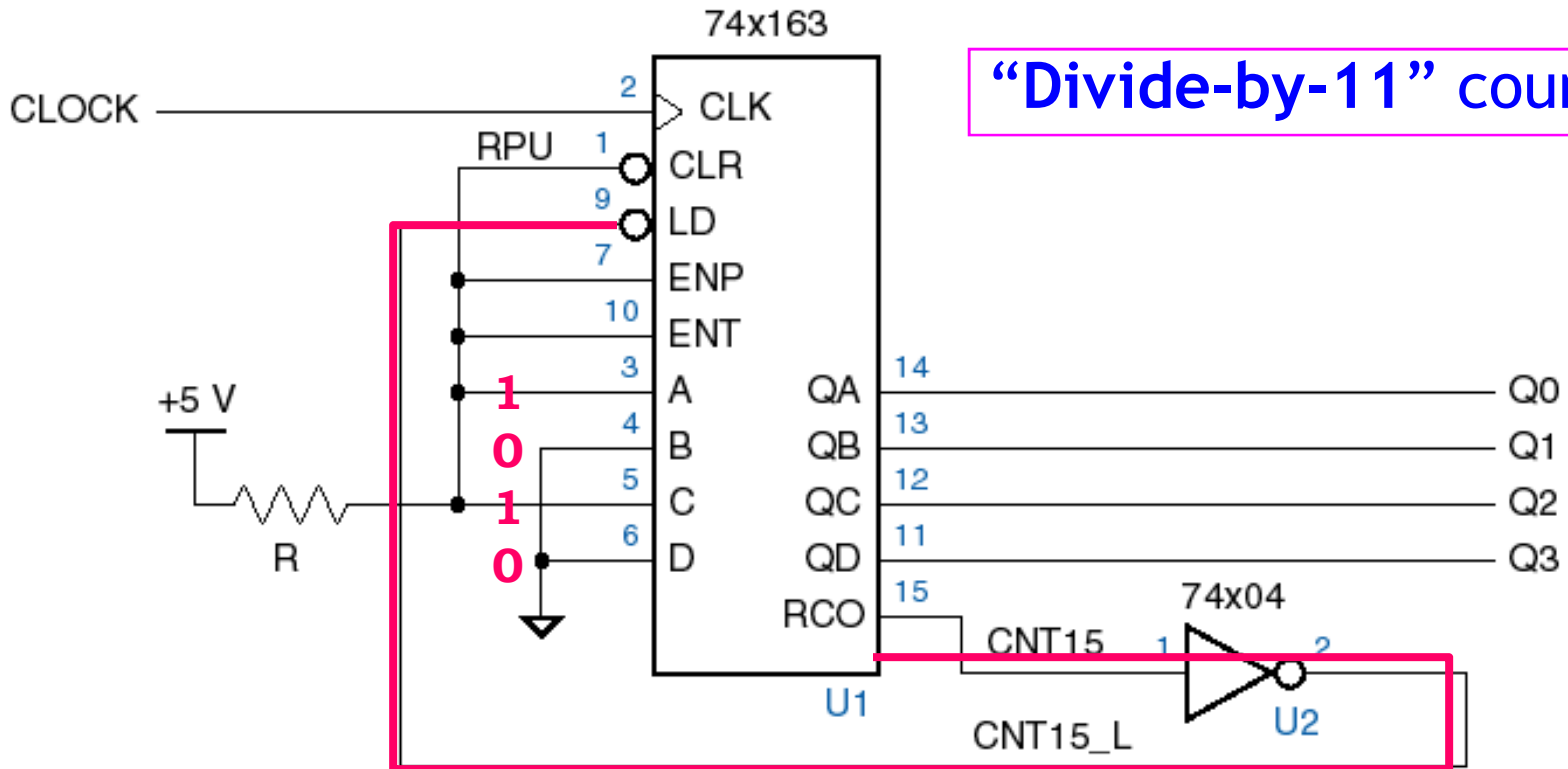Counter Application-2: Modified Counting Sequence




Load 0101 (5) after Count = 15

5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 5, 6, ...

Counter Application-2: Modified counting sequence

Another Way


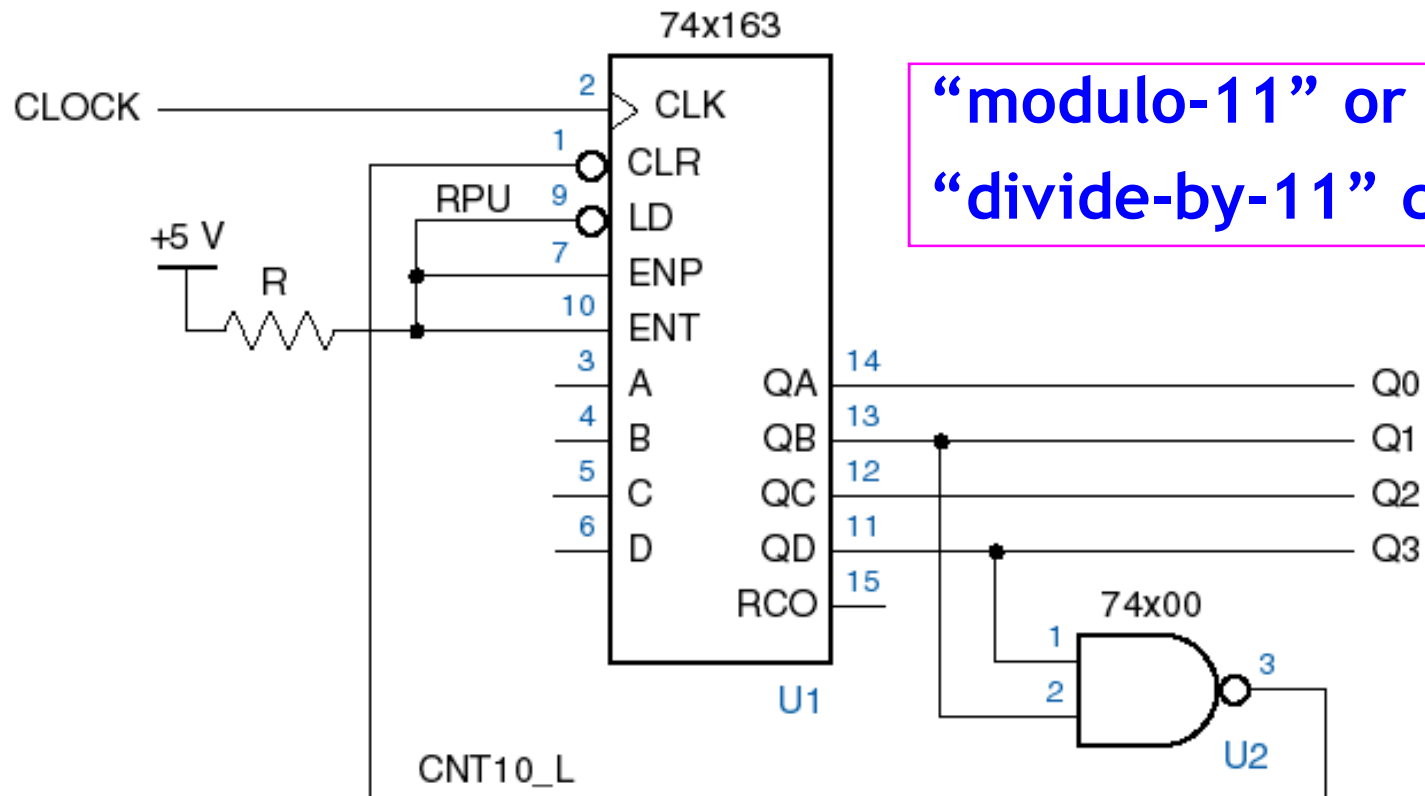


“modulo-11” or
“divide-by-11” counter

Clear after Count = 1010 (10)


0, 1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 0, 1, 2, 3, ...

 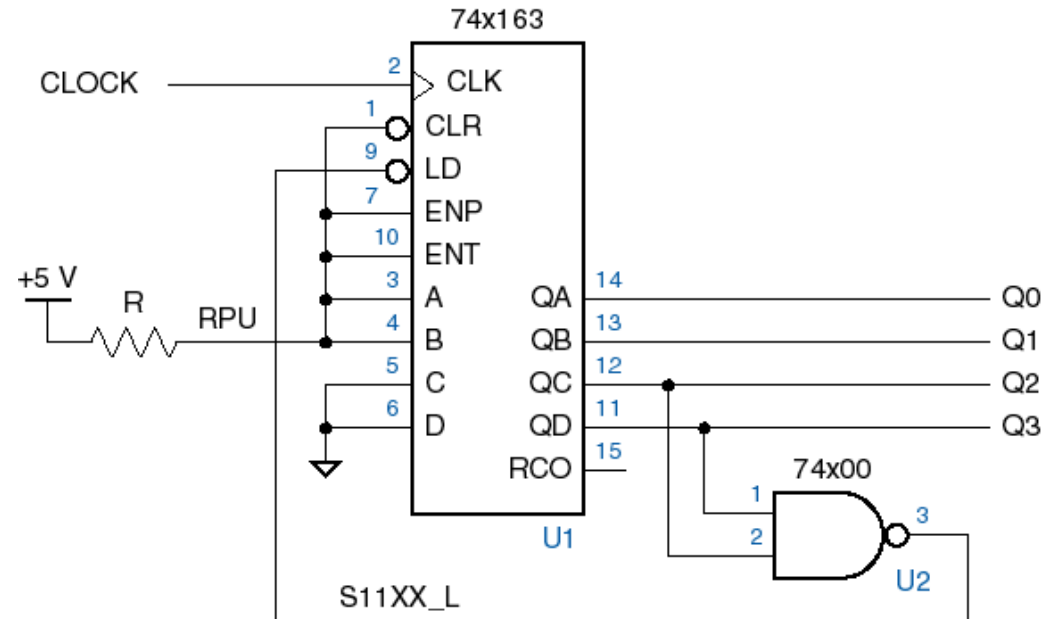Counter Application-3: Counting from 3 to 12



Shift Registers

 Multi-bit register that moves data “sideways”
left/right (1 bit/clock)




To rearrange bits or **Multiply/Divide by 2**

Shift Registers: Serial-in, Serial-out

For handling serial data,
e.g.

 
- RS-232 and
- modem transmission,
- Ethernet links,
- SONET,
- etc.




Serial-to-Parallel Conversion

Serial-In, Parallel-Out
shift register

Serial-in


 


Parallel-out

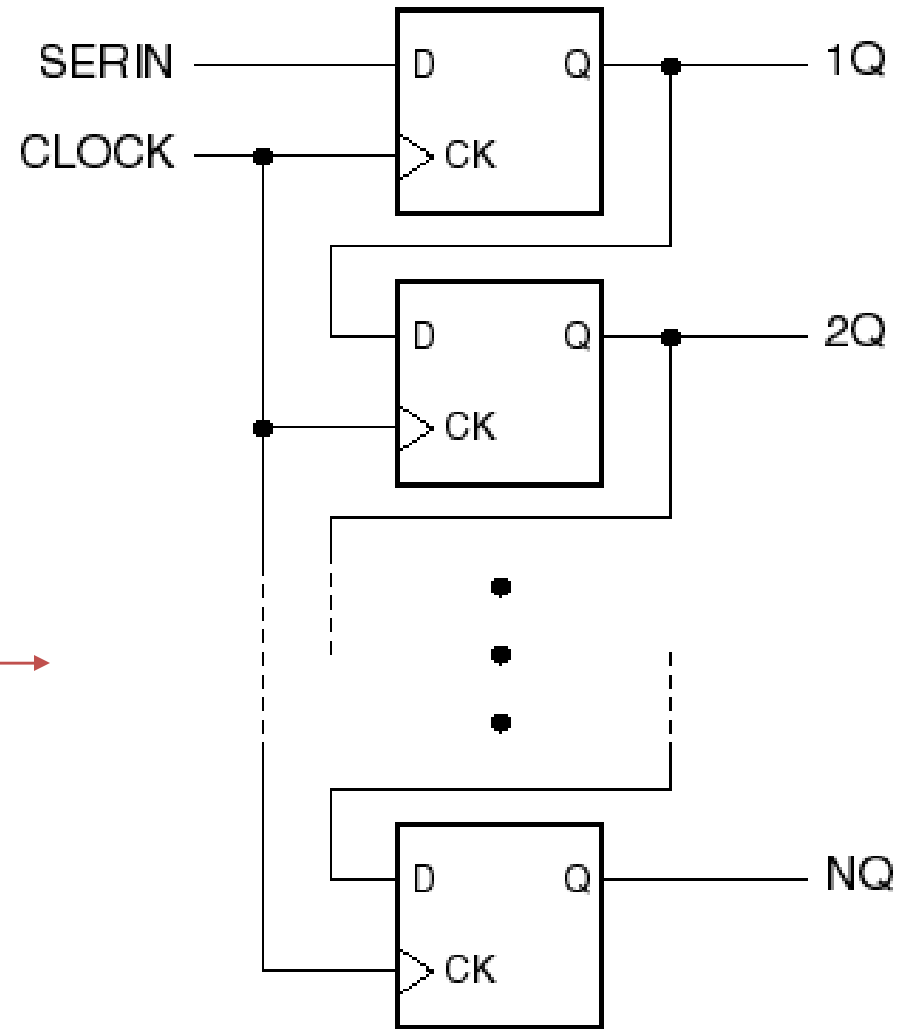

Parallel-to-Serial Conversion

Parallel-In, Serial-Out
shift register

 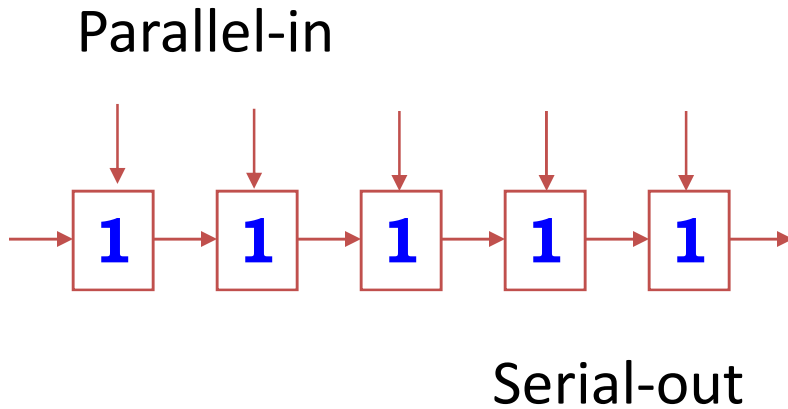

Do both: Parallel-in, Parallel-out Shift Register

Parallel-In, Parallel-Out shift register

