



Faculty of Engineering

ECE 334: Electronic Circuits

Lecture 2:
BJT Large Signal Model

Agenda

- I & V Notations
- BJT Devices & Symbols
- BJT Large Signal Model

I, V Notations (1)

- It is critical to understand the notation used for voltages and currents in the following discussion of transistor amplifiers.
- This is therefore dealt with explicitly ‘up front’.
- As with dynamic resistance in diodes we will be dealing with a.c. signals superimposed on d.c. bias levels.


I, V Notations (2)

- We will use a capital (upper case) letter for a d.c. quantity (e.g. I , V).
- We will use a lower case letter for a time varying (a.c.) quantity (e.g. i , v)

I, V Notations (3)

- These primary quantities will also need a subscript identifier (e.g. is it the base current or the collector current?).
- For d.c. levels this subscript will be in *upper case*.
- We will use a *lower case subscript* for the a.c. signal bit (e.g. i_b).
- And an *upper case subscript* for the **total** time varying signal (i.e. the a.c. signal bit plus the d.c. bias) (e.g. i_B). This will be less common.

I, V Notations (4)

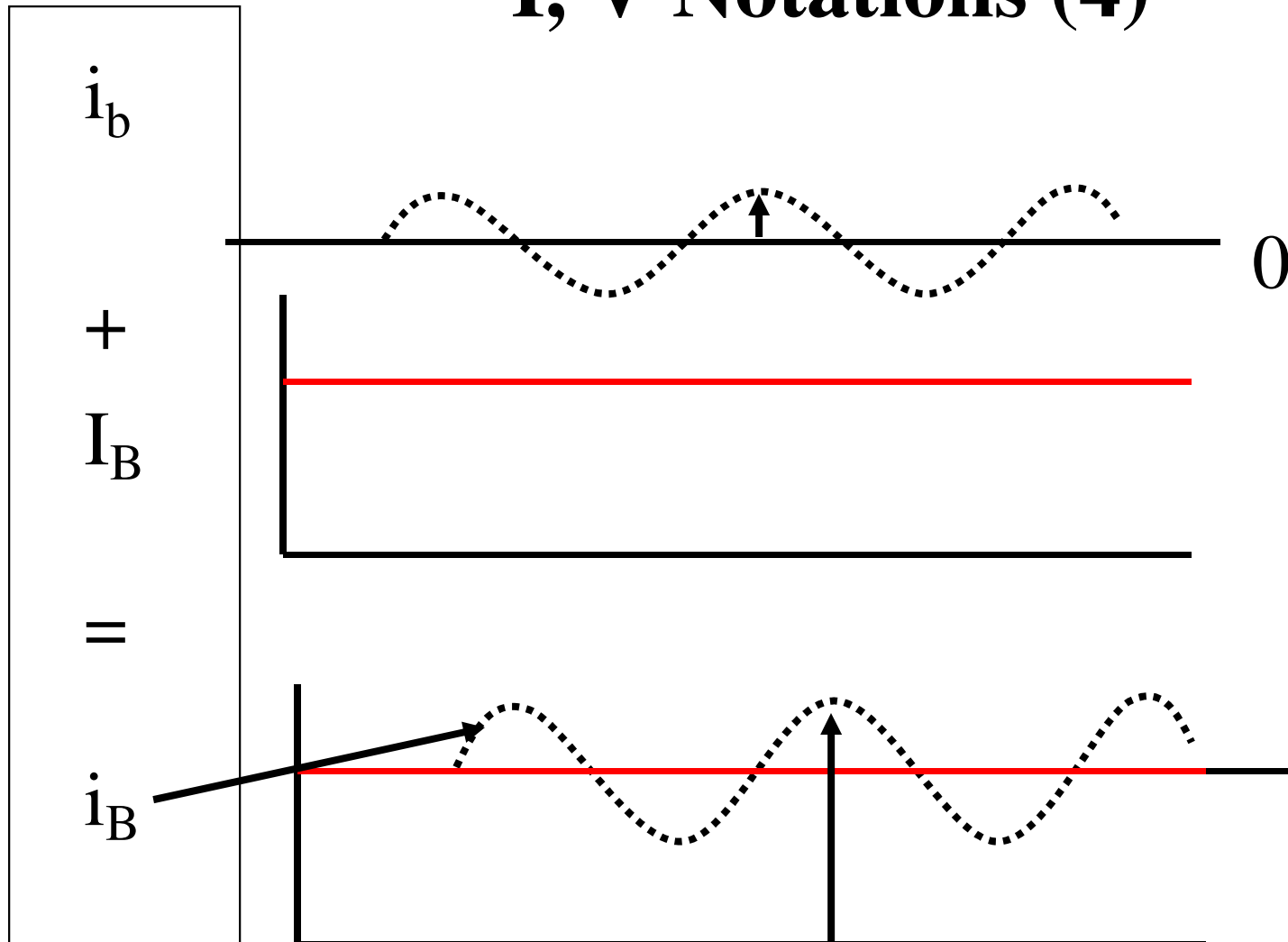

I, V Notations (5)

- It is convention to refer all transistor voltages to the 'common' terminal.
- Thus in the CE configuration we would write V_{CE} for a d.c. collector emitter voltage and V_{BE} for a d.c. base emitter voltage.

NPN Bipolar Junction Transistor

- One N-P (Base Collector) diode one P-N (Base Emitter) diode


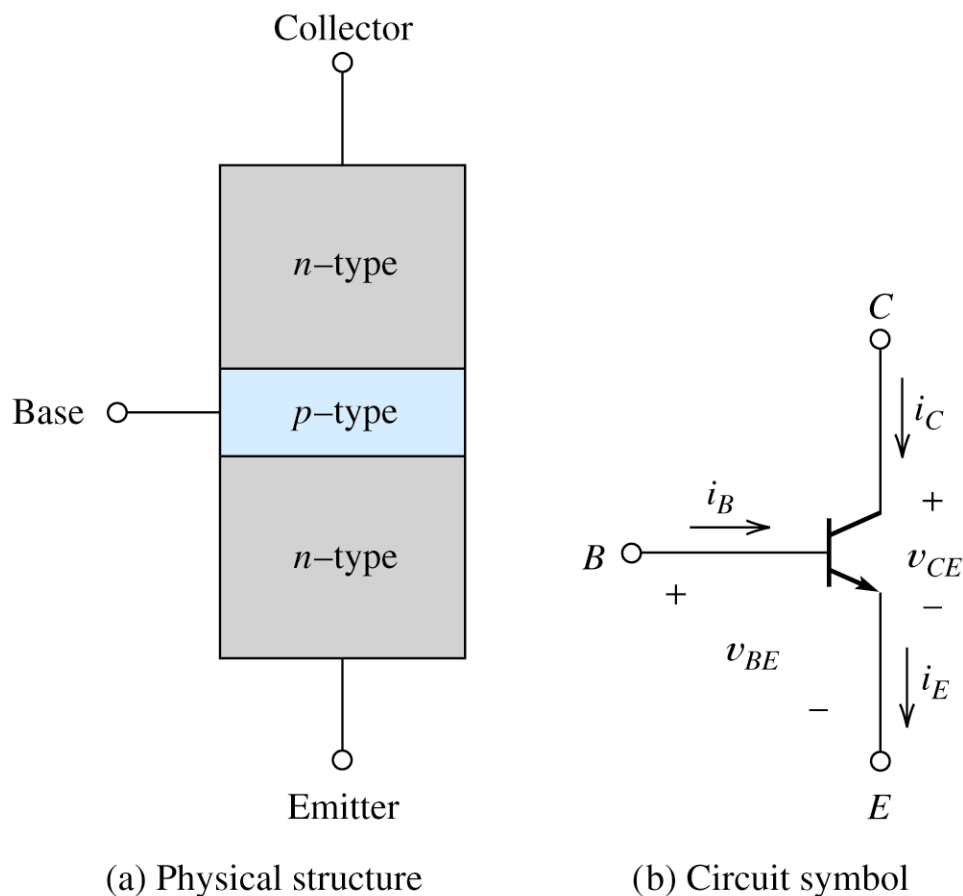



Figure 13.1 The *npn* BJT.

PNP Bipolar Junction Transistor

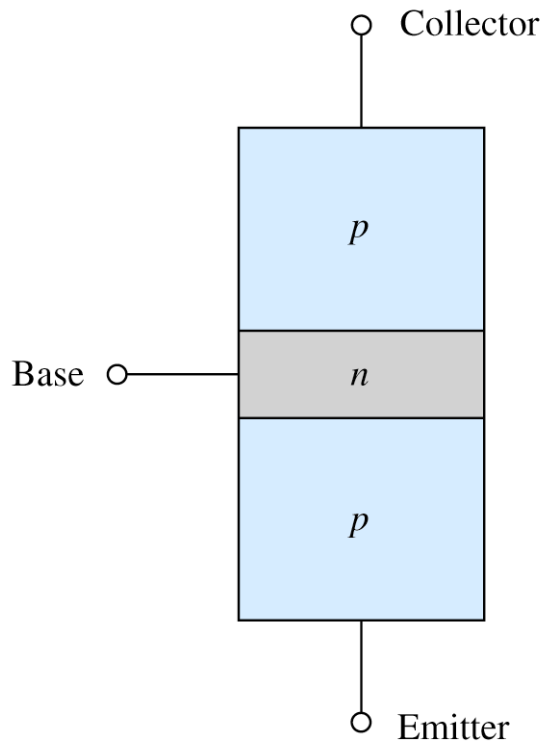- One P-N (Base Collector) diode one N-P (Base Emitter) diode



(a) Physical structure

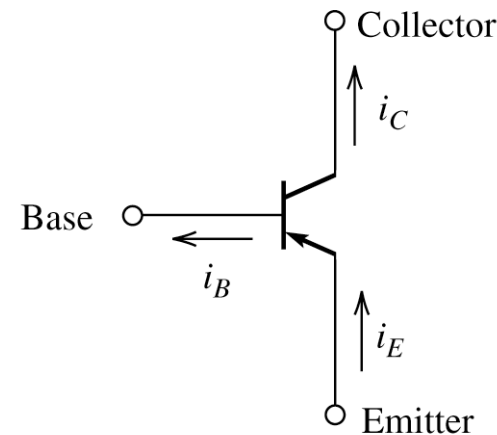

(b) Circuit symbol with reference directions for currents

Figure 13.13 The *pn*p BJT.

NPN BJT Current flow


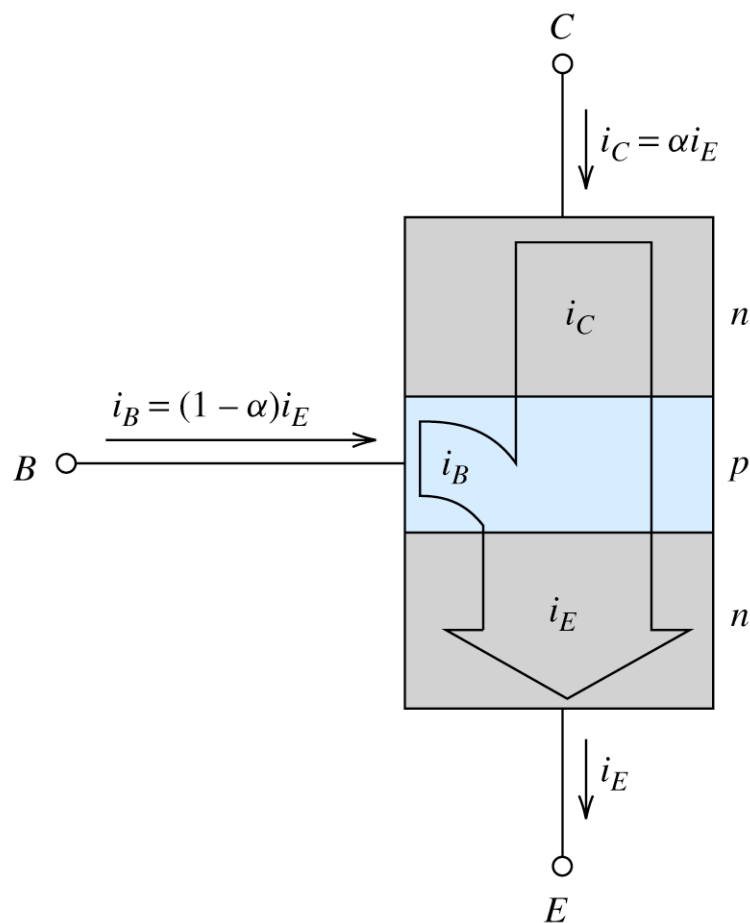


Figure 13.3 Only a small fraction of the emitter current flows into the base (provided that the collector–base junction is reverse biased and the base–emitter junction is forward biased).

BJT α and β

- From the previous figure $i_E = i_B + i_C$
- Define $\alpha = i_C / i_E$
- Define $\beta = i_C / i_B$
- Then $\beta = i_C / (i_E - i_C) = \alpha / (1 - \alpha)$
- Then $i_C = \alpha i_E$; $i_B = (1 - \alpha) i_E$
- Typically $\beta \approx 100$ for small signal BJTs (BJTs that handle low power) operating in active region (region where BJTs work as amplifiers)

BJT in Active Region

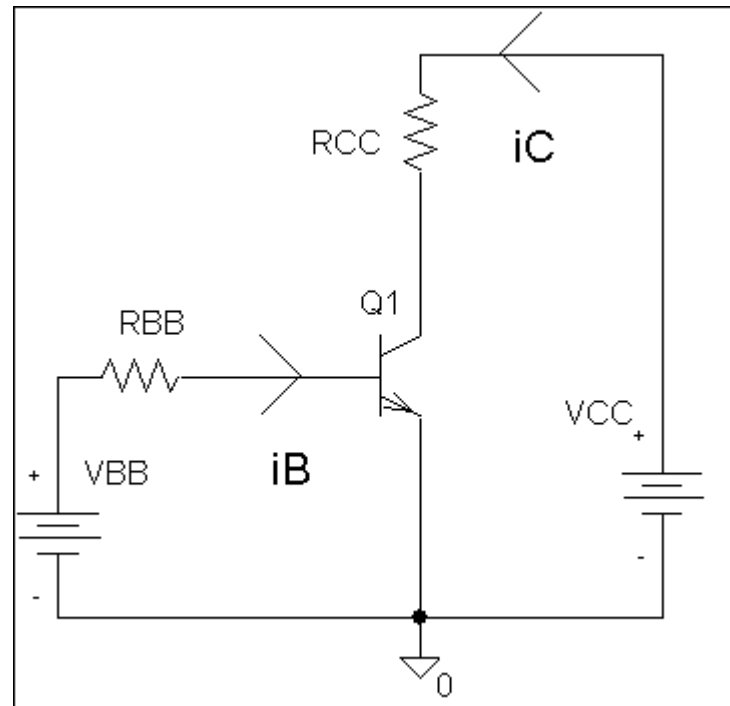

Common Emitter(CE) Connection

- Called CE because emitter is common to both V_{BB} and V_{CC}

BJT in Active Region (2)

- Base Emitter junction is forward biased
- Base Collector junction is reverse biased
- **For a particular i_B , i_C is independent of R_{CC}**
 \Rightarrow transistor is acting as current controlled current source (i_C is controlled by i_B , and $i_C = \beta i_B$)
- Since the base emitter junction is forward biased, from Shockley equation

$$i_C = I_{CS} \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right]$$

BJT in Active Region (3)

• *Normally the above equation is never used to calculate i_C , i_B . Since for all small signal transistors $v_{BE} \approx 0.7$. It is only useful for deriving the small signal characteristics of the BJT.*

• For example, for the CE connection, i_B can be simply calculated as,

$$i_B = \frac{V_{BB} - V_{BE}}{R_{BB}}$$



or by drawing load line on the base –emitter side

Deriving BJT Operating points in Active Region –An Example

In the CE Transistor circuit shown earlier $V_{BB} = 5V$, $R_{BB} = 107.5 k\Omega$, $R_{CC} = 1 k\Omega$, $V_{CC} = 10V$. Find I_B, I_C, V_{CE}, β and the transistor power dissipation using the characteristics as shown below

By Applying KVL to the base emitter circuit


$$I_B = \frac{V_{BB} - V_{BE}}{R_{BB}}$$

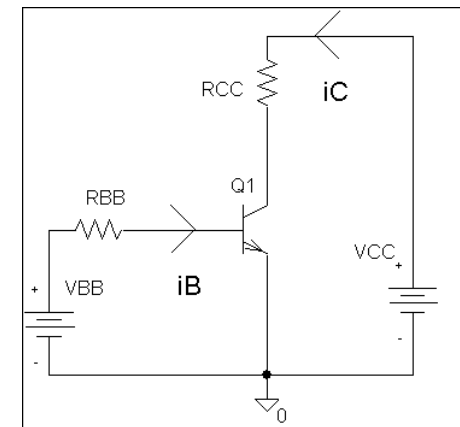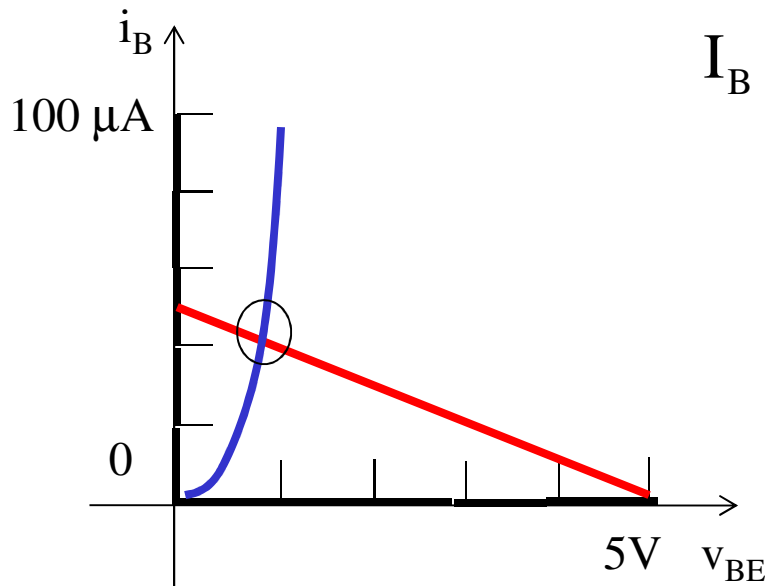

By using this equation along with the i_B / v_{BE} characteristics of the base emitter junction, $I_B = 40 \mu A$

Deriving BJT Operating points in Active Region –An Example (2)

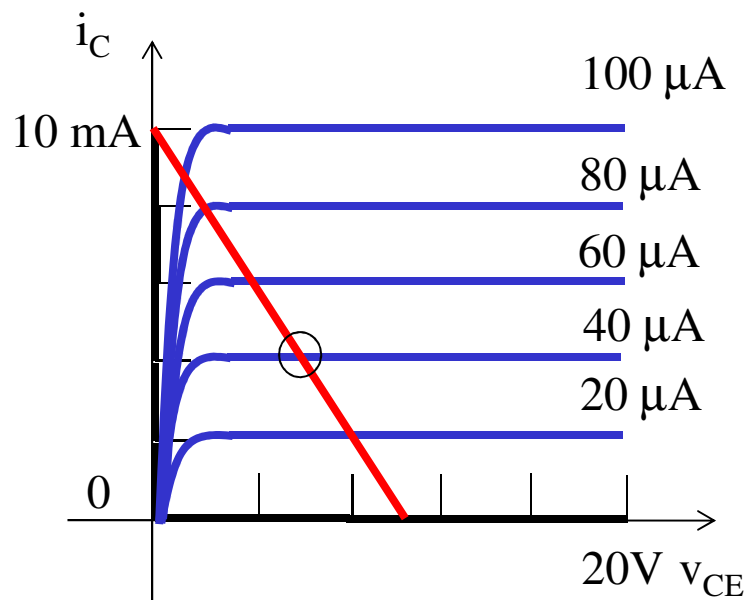By Applying KVL to the collector emitter circuit



$$I_C = \frac{V_{CC} - V_{CE}}{R_{CC}}$$

By using this equation along with the i_C / v_{CE} characteristics of the base collector junction, $i_C = 4 \text{ mA}$, $V_{CE} = 6\text{V}$

$$\beta = \frac{I_C}{I_B} = \frac{4\text{mA}}{40\mu\text{A}} = 100$$

$$\text{Transistor power dissipation} = V_{CE}I_C = 24 \text{ mW}$$

We can also solve the problem without using the characteristics if β and V_{BE} values are known


BJT in Cutoff Region

- Under this condition $i_B = 0$
- As a result i_C becomes negligibly small
- Both base-emitter as well base-collector junctions may be reverse biased
- Under this condition the BJT can be treated as an off switch

BJT in Saturation Region

- Under this condition $i_C / i_B < \beta$ in active region
- Both base emitter as well as base collector junctions are forward biased
- $V_{CE} \approx 0.2 \text{ V}$
- Under this condition the BJT can be treated as an on switch

BJT in Saturation Region (2)

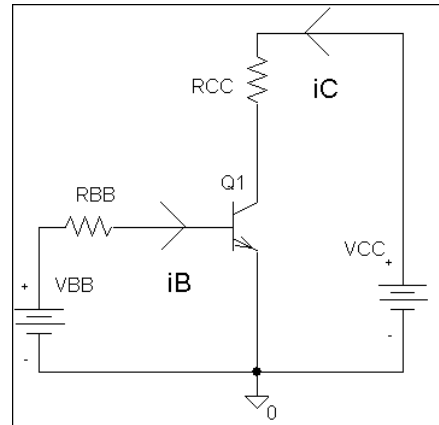


- A BJT can enter saturation in the following ways (refer to the CE circuit)
- For a particular value of i_B , if we keep on increasing R_{CC}
- For a particular value of R_{CC} , if we keep on increasing i_B
- For a particular value of i_B , if we replace the transistor with one with higher β

BJT in Saturation Region – Example 1

In the CE Transistor circuit shown earlier $V_{BB} = 5V$, $R_{BB} = 107.5 \text{ k}\Omega$, $R_{CC} = 10 \text{ k}\Omega$, $V_{CC} = 10V$. Find I_B, I_C, V_{CE}, β and the transistor power dissipation using the characteristics as shown below

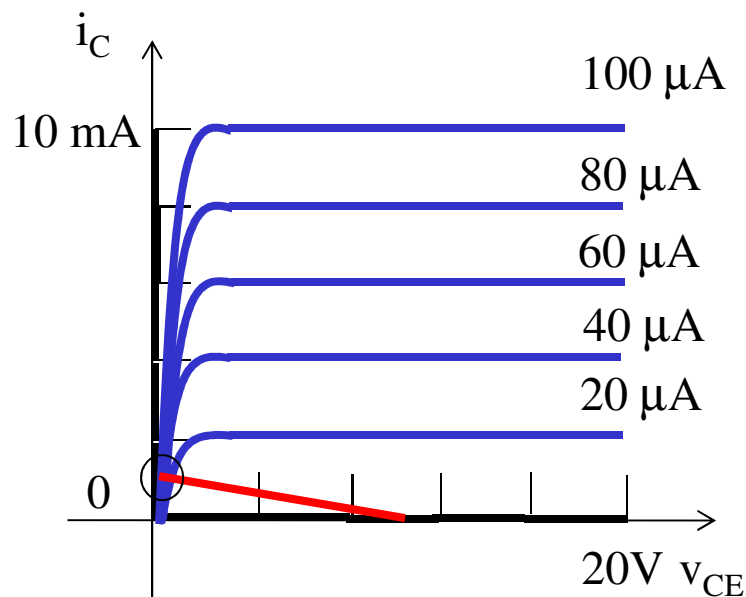Here even though I_B is still $40 \mu\text{A}$; from the output characteristics, I_C can be found to be only about 1mA and $V_{CE} \approx 0.2V (\Rightarrow V_{BC} \approx 0.5V$ or base collector junction is forward biased (how?))



$$\beta = I_C / I_B = 1\text{mA} / 40 \mu\text{A} = 25 < 100$$

BJT in Saturation Region – Example 2

In the CE Transistor circuit shown earlier $V_{BB} = 5V$, $R_{BB} = 43\text{ k}\Omega$, $R_{CC} = 1\text{ k}\Omega$, $V_{CC} = 10V$. Find I_B, I_C, V_{CE}, β and the transistor power dissipation using the characteristics as shown below


Here I_B is $100\text{ }\mu\text{A}$ from the input characteristics; I_C can be found to be only about 9.5 mA from the output characteristics and $V_{CE} \approx 0.5V$ ($\Rightarrow V_{BC} \approx 0.2V$ or base collector junction is forward biased (how?))

$$\beta = I_C / I_B = 9.5\text{ mA} / 100\text{ }\mu\text{A} = 95 < 100$$


$$\text{Transistor power dissipation} = V_{CE} I_C \approx 4.7\text{ mW}$$

Note: In this case the BJT is not in very hard saturation

BJT in Saturation Region – Example 2 (2)

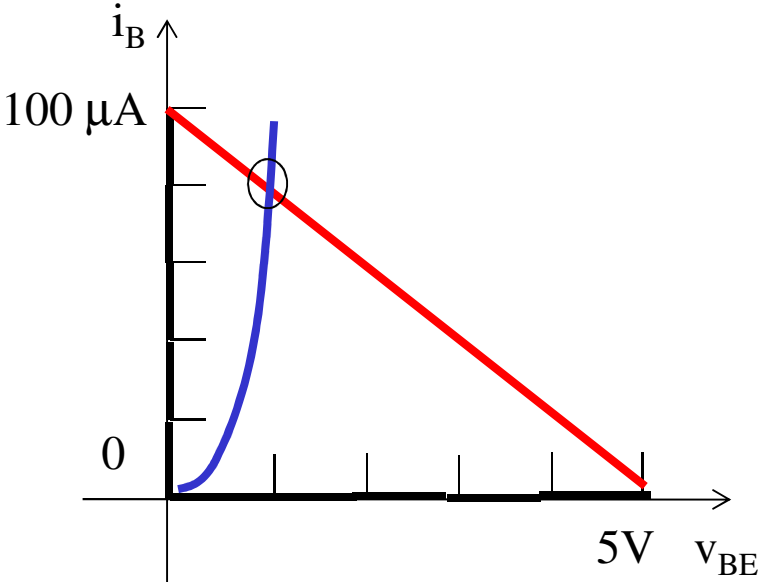

Input Characteristics

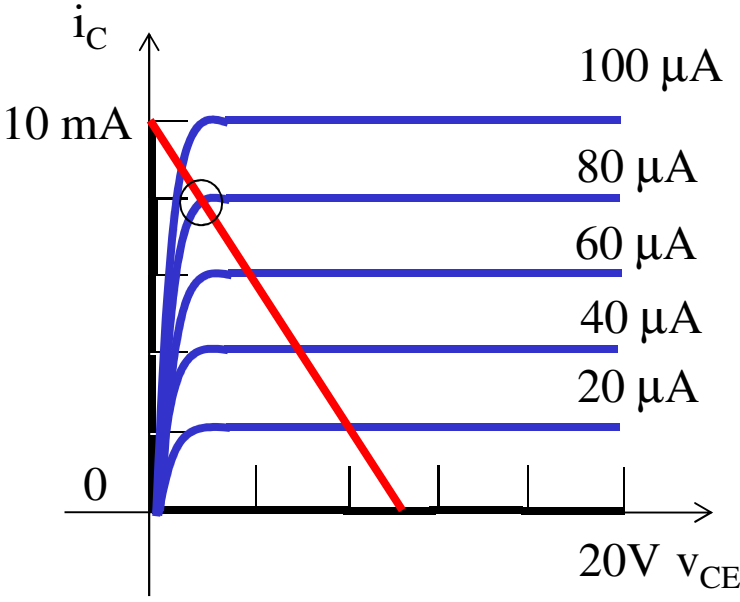

Output Characteristics

BJT in Saturation Region – Example 3

In the CE Transistor circuit shown earlier $V_{BB} = 5V$, $V_{BE} = 0.7V$
 $R_{BB} = 107.5 \text{ k}\Omega$, $R_{CC} = 1 \text{ k}\Omega$, $V_{CC} = 10V$, $\beta = 400$. Find I_B, I_C, V_{CE} ,
and the transistor power dissipation using the characteristics as
shown below

By Applying KVL to the base emitter circuit

$$I_B = \frac{V_{BB} - V_{BE}}{R_{BB}} = 40\mu\text{A}$$

Then $I_C = \beta I_B = 400 * 40 \mu\text{A} = 16000 \mu\text{A}$

and $V_{CE} = V_{CC} - R_{CC} * I_C = 10 - 0.016 * 1000 = -6V(?)$

But V_{CE} cannot become negative (since current can flow only
from collector to emitter).

Hence the transistor is in saturation

BJT in Saturation Region – Example 3(2)

Hence $V_{CE} \approx 0.2V$

$$\therefore I_C = (10 - 0.2) / 1 = 9.8 \text{ mA}$$

Hence the operating $\beta = 9.8 \text{ mA} / 40 \mu\text{A} = 245$

BJT Operating Regions at a Glance (1)

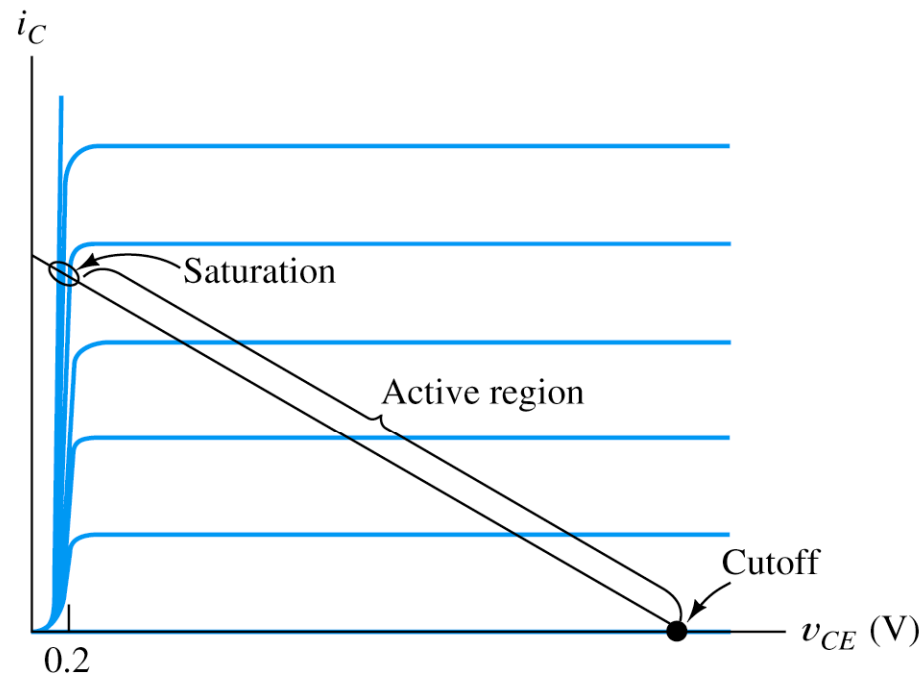


Figure 13.12 Amplification occurs in the active region. Clipping occurs when the instantaneous operating point enters saturation or cutoff.
In saturation, $v_{CE} \cong 0.2$ V.

BJT Operating Regions at a Glance (2)

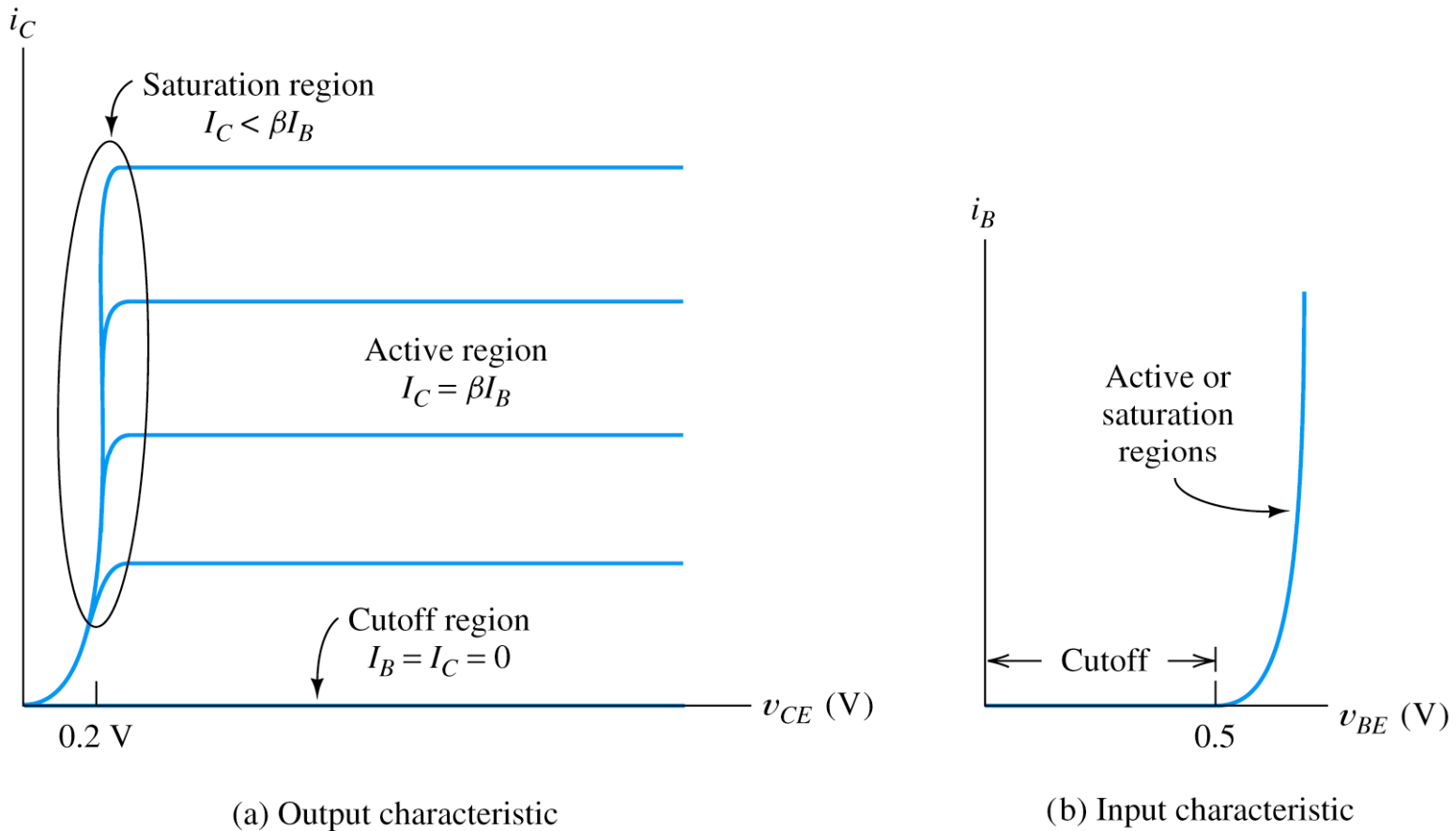


Figure 13.17 Regions of operation on the characteristics of an *npn* BJT.

BJT Large-signal (DC) Model (1)

- $i_E = i_B + i_C$

- $\alpha = i_C / i_E$

- $\beta = i_C / i_B = \alpha / (1 - \alpha)$

- $i_C = \alpha i_E ; i_B = (1 - \alpha) i_E$

BJT Large-signal (DC) Model (2)

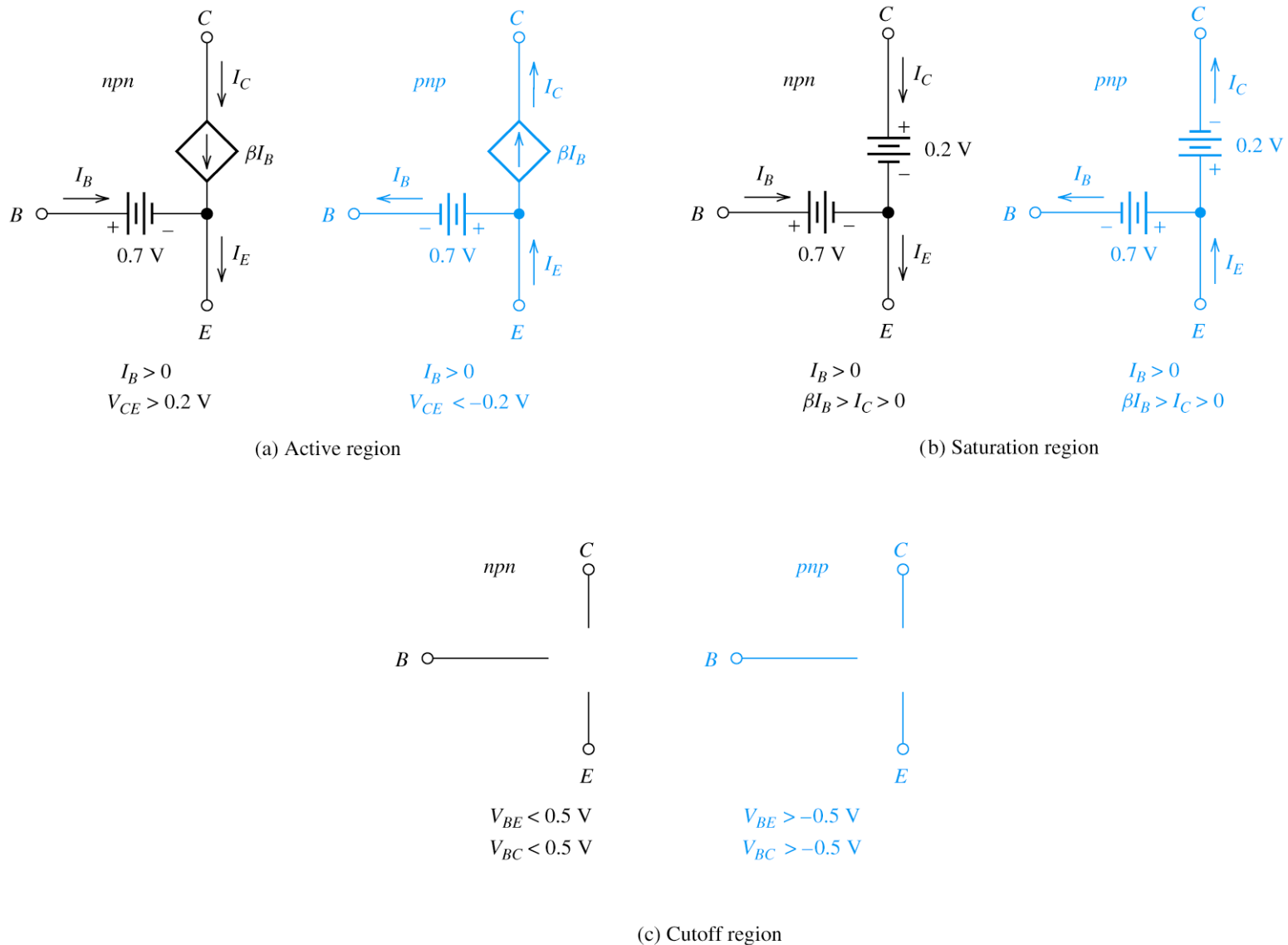


Figure 13.16 BJT large-signal models. (Note: Values shown are appropriate for typical small-signal silicon devices at a temperature of 300 K.)