




Faculty of Engineering

**ECE 335: Electronic Circuits**


**Lecture 8:**  
**MOSFET Small Signal Model**

# Graphical Analysis, Load Lines

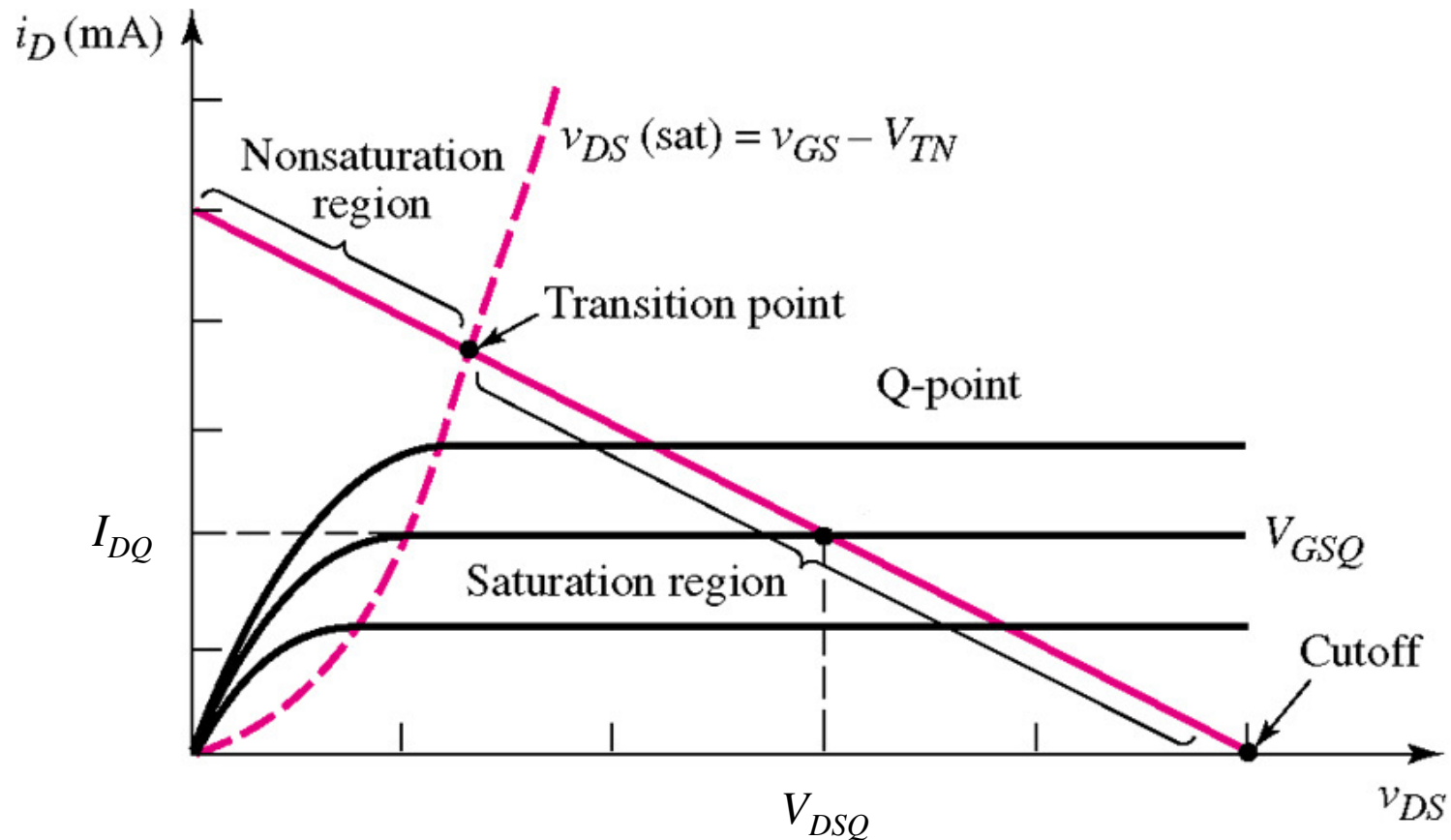

Common-source transistor characteristic

# Graphical Analysis, Load Lines

 


Two load lines and corresponding bias points. Bias point  $Q_1$  does not leave sufficient room for positive signal swing at the drain (too close to  $V_{DD}$ ). Bias point  $Q_2$  is too close to the boundary of the triode region and might not allow for sufficient negative signal swing.
 
# MOSFET Parameters

- Transconductance,  $g_m$

$$g_m = \frac{i_d}{v_{gs}} = \frac{\partial I_D}{\partial V_{GS}}$$
$$= \frac{2I_D}{V_{GS} - V_{th}}$$



# Example: Transconductance

## Exercise

The transistor has  $K_p=50\mu\text{A}/\text{V}^2$ ,  $V_{th}=2\text{V}$ ,  $L=10\mu\text{m}$ , and  $W=400\mu\text{m}$


 


Figure 12.10 Simple NMOS amplifier circuit.


$$I_D = \frac{K_P}{2} \left( \frac{W}{L} \right) (V_{GS} - V_{th})^2 = 4\text{mA}/\text{V}^2$$

$$g_m = \frac{2I_D}{V_{GS} - V_{th}} = \frac{2 \times 4}{4 - 2} = 4\text{mS}$$

# MOSFET Small-Signal Equivalent Circuit

 

 Common source NMOS  
with small signal  
parameters



Simplified small signal  
equivalent circuit for  
NMOS

Small-signal  
output resistance


$$r_o = \frac{V_A}{I_{DQ}} = (\lambda I_{DQ})^{-1}$$

where


$$\lambda = \frac{1}{V_A}$$

# DC Analysis

## – Saturation Region

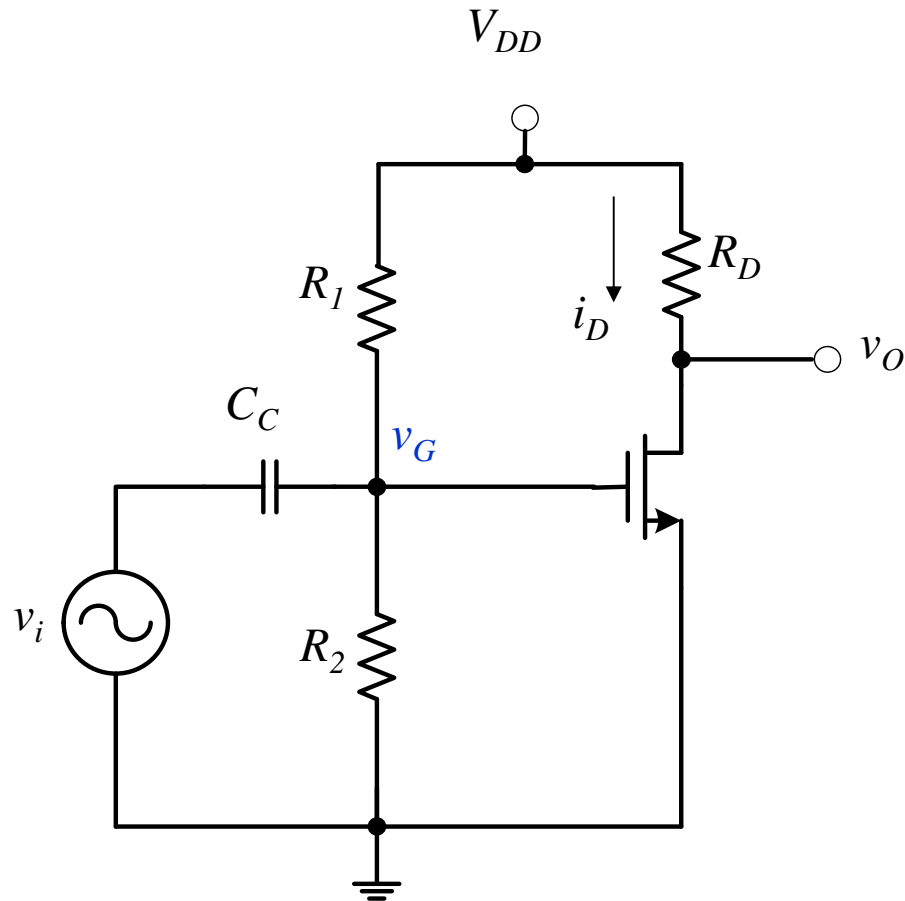


Voltage-divider circuit for MOSFET

 

DC equivalent circuit

# DC Analysis

## – Saturation Region

 

$$V_G = V_{GS} = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$I_D = K(V_{GS} - V_{TN})^2$$


$$V_{DS} = V_{DD} - I_D R_D$$

$$V_{DS}(\text{sat}) = V_{GS} - V_{TN}$$


DC equivalent circuit



# AC Analysis

 

 **NMOS common source circuit  
with time-varying signal source  
in series with gate DC source**




**AC equivalent circuit**


# Example

$$V_{TN} = 1 \text{ V}$$

$$K_n W/L = 0.2 \text{ mA/V}^2$$

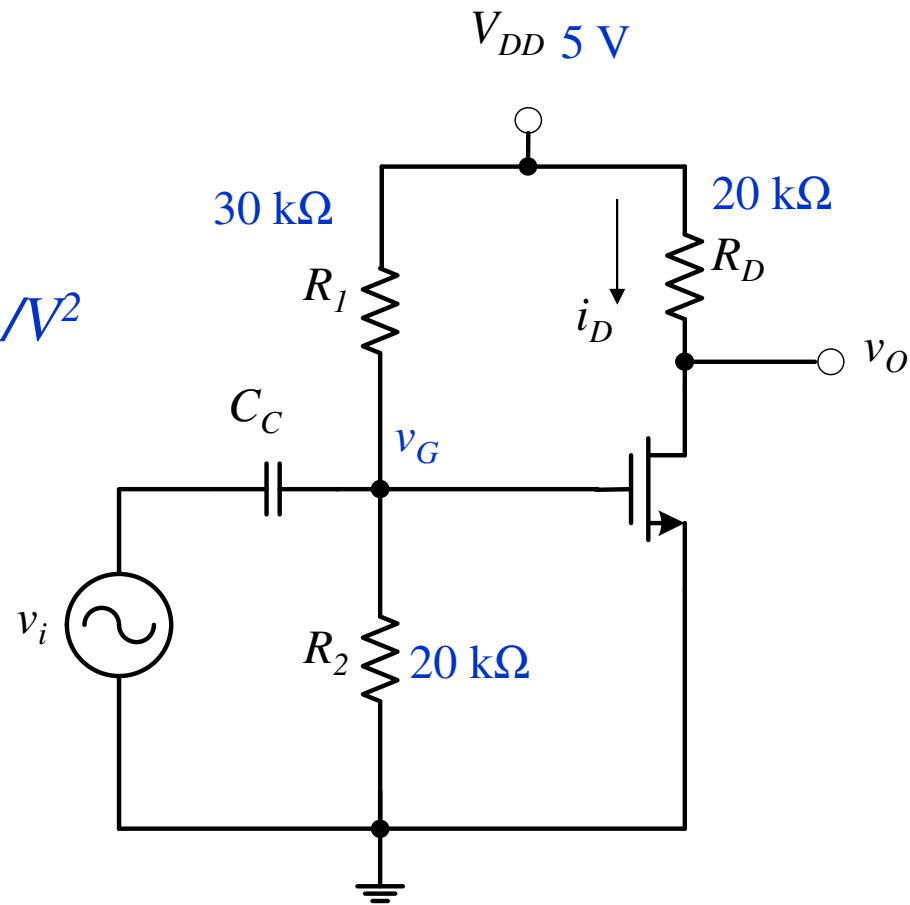

## DC equivalent circuit

 

$$V_G = V_{GS} = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \left( \frac{20}{20 + 30} \right) 5 = 2 \text{ V}$$

$$I_D = \frac{K_n}{2} \frac{W}{L} (V_{GS} - V_{TN})^2 = (0.1)(2 - 1)^2 = 0.1 \text{ mA}$$

$$V_{DS} = V_{DD} - I_D R_D = 5 - (0.1)(20) = 3 \text{ V}$$

The transistor is biased in the **saturation region** because  $V_{DS} > V_{DS(\text{sat})}$  ;

since  $V_{DS(\text{sat})} = V_{GS} - V_{TN} = 2 - 1 = 1 \text{ V}$