



Faculty of Engineering


ECE 335: Electronic Circuits

Lecture 9: MOSFET Amplifiers

- **Common-Source Amplifier**
- **Common-Drain Amplifier**
- **Common-Gate Amplifier**


COMMON-SOURCE AMPLIFIER

- Basic Configuration

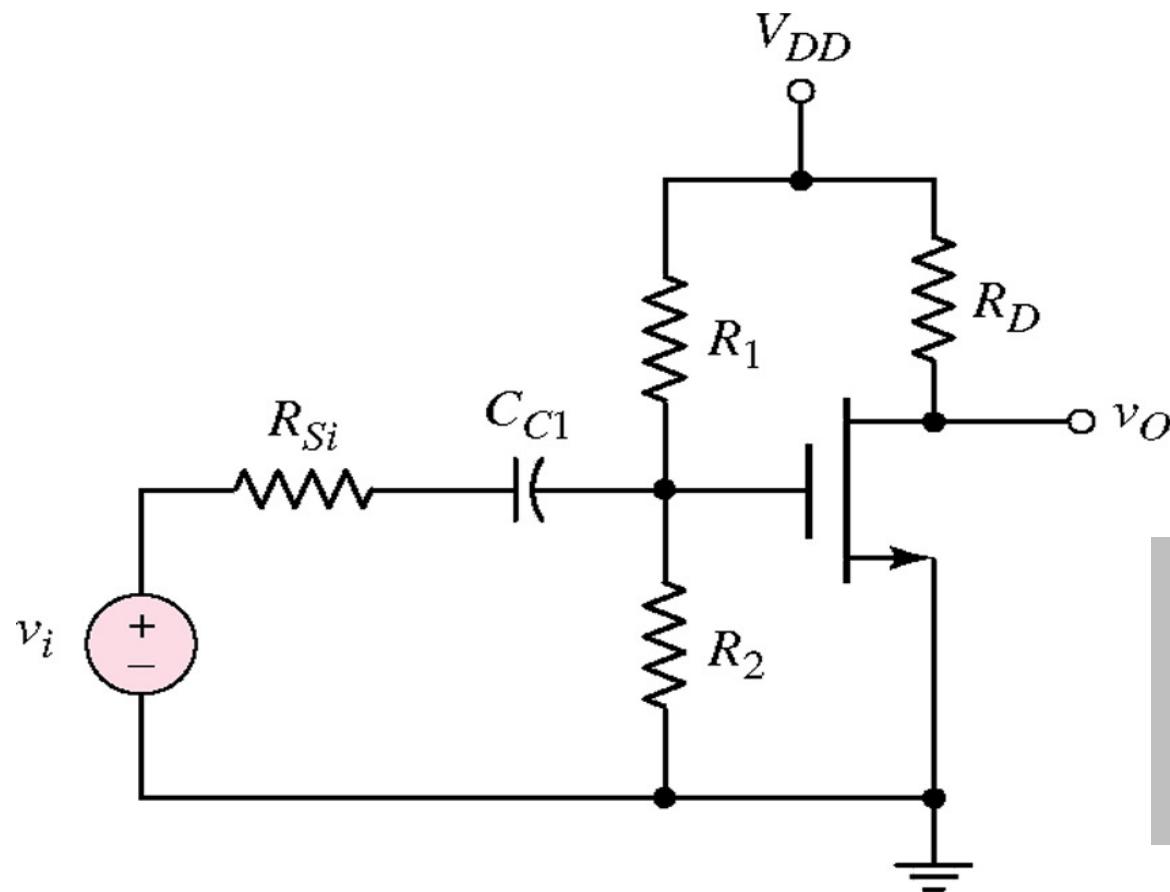

Common-source
circuit with
voltage divider
biasing & coupling
capacitor

Small-signal equivalent circuit

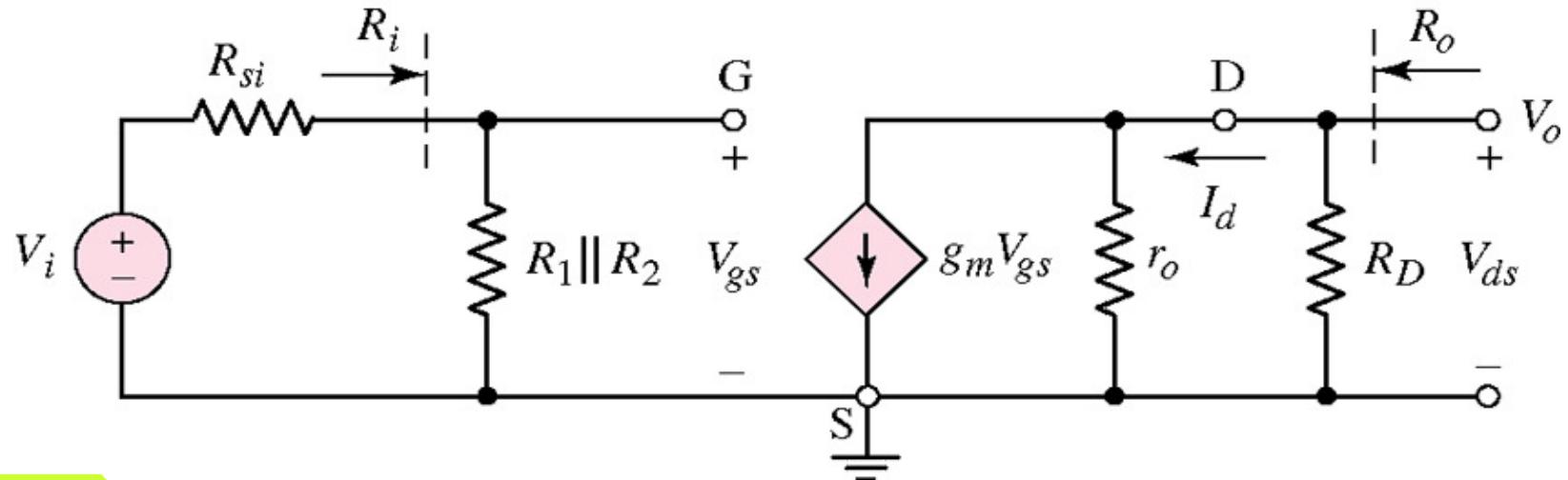

input
resistance

input
voltage

small-signal
voltage gain

$$R_i = R_1 \parallel R_2$$


$$V_{gs} = \left(\frac{R_i}{R_i + R_{Si}} \right) V_i$$

$$V_o = -g_m V_{gs} (r_o \parallel R_D)$$

output
voltage

$$A_v = \frac{V_o}{V_i} = -g_m (r_o \parallel R_D) \left(\frac{R_i}{R_i + R_{Si}} \right)$$

DC Load Line

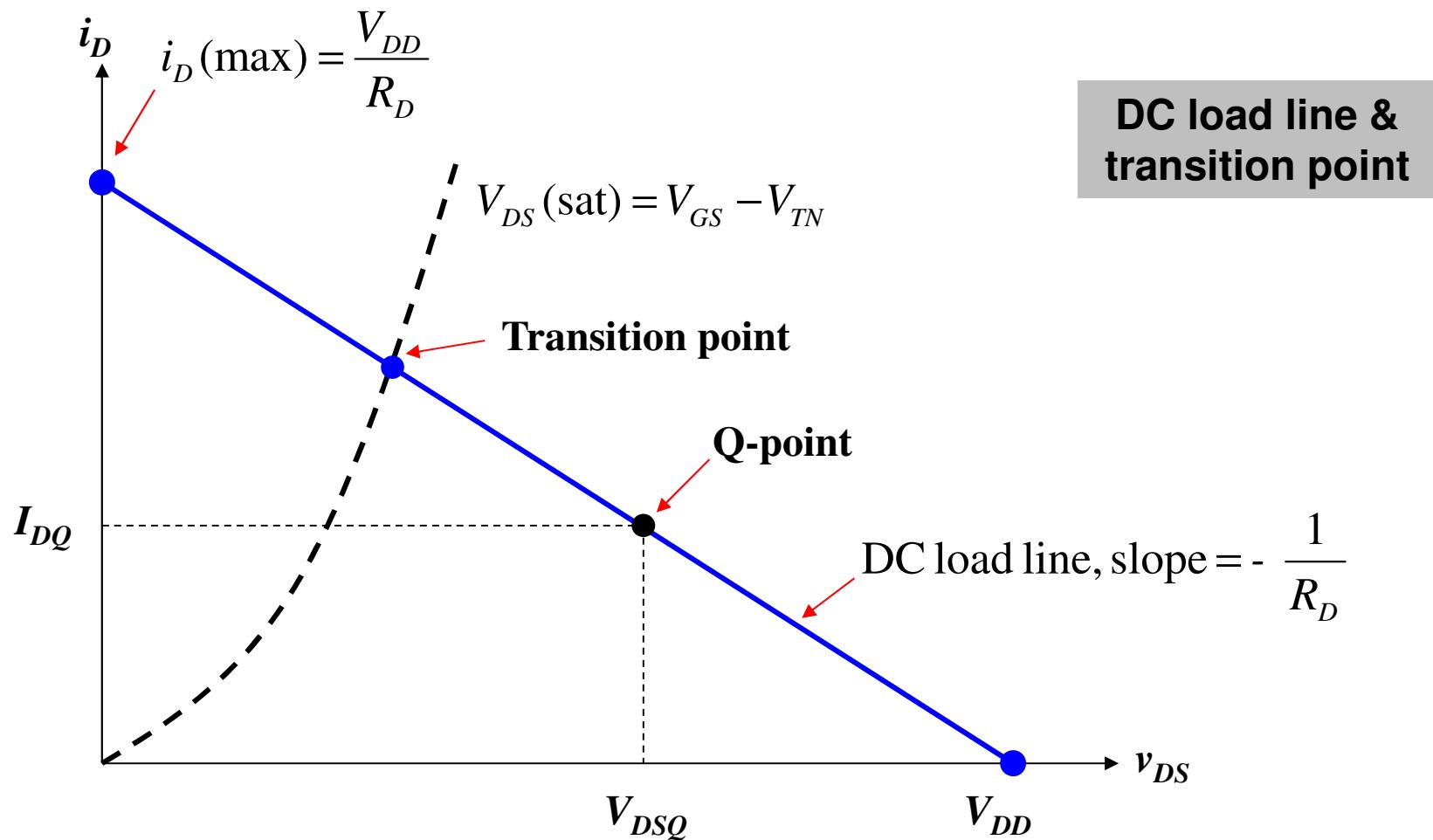

COMMON-SOURCE AMPLIFIER

- with Source Resistor


CALCULATION EXAMPLE

Given:

$$V_{TN} = 2V,$$

$$K_n W/L = 2 \text{ mA/V}^2,$$

$$\lambda = 0$$

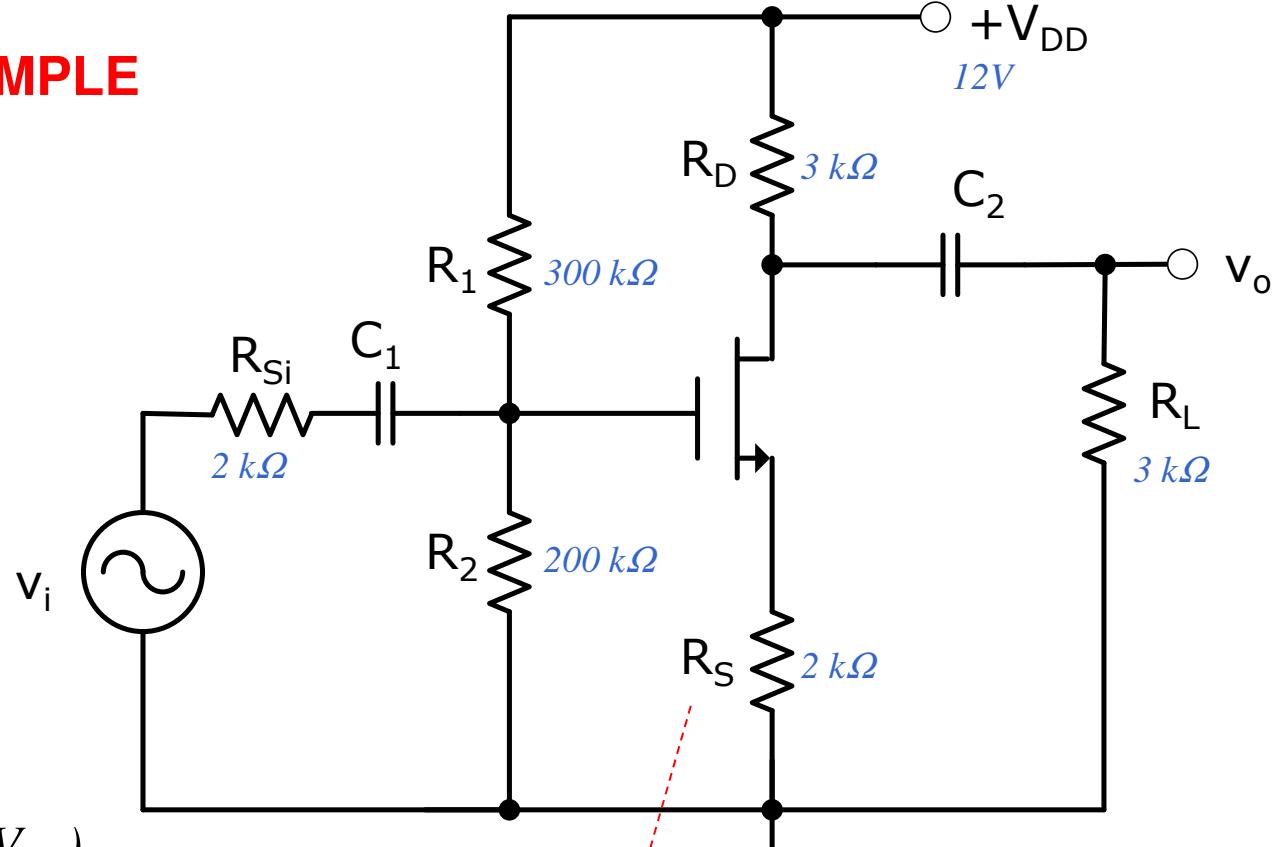


Determine:

- i- Q-point values (I_D , V_{DS})
- ii- small-signal voltage gain

Stabilize the Q-point against variation of transistor parameters

Q-point values

dc equivalent circuit

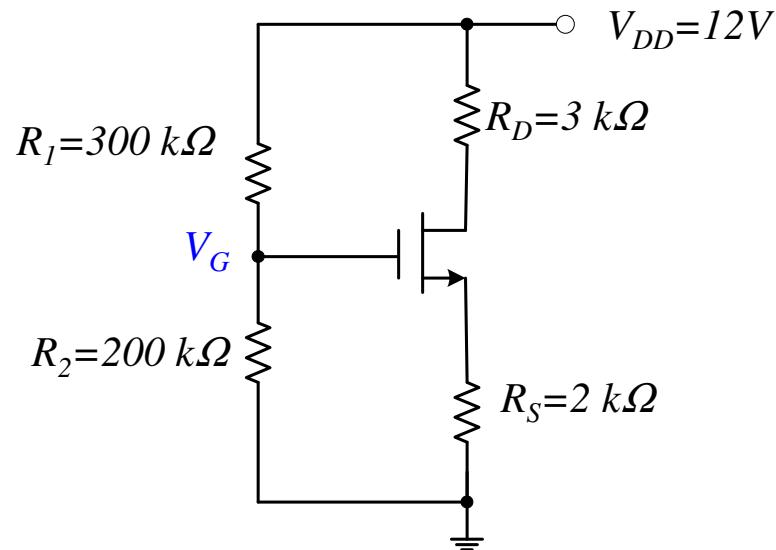

$$V_G = \left(\frac{R_2}{R_1 + R_2} \right) V_{DD} = \left(\frac{200k}{300k + 200k} \right) 12 = 4.8V$$

$$I_D = \frac{V_G - V_{GS}}{R_S} = \frac{K_n}{2} \frac{W}{L} (V_{GS} - V_{TN})^2$$

Q-point values (Cont)

$$4.8 - V_{GS} = (1m)(2k)(V_{GS} - 2)^2$$

$$2(V_{GS})^2 - 7V_{GS} + 3.2 = 0$$

$$V_{GS} = \frac{7 \pm \sqrt{(7)^2 - 4(2)(3.2)}}{2(2)} = 0.54, 2.96$$

For $V_{GS} = 0.54$ V, MOSFET \rightarrow cutoff 'coz $V_{GS} < V_{TN}$.


Therefore, $V_{GS} = 2.96$ V

So, the Q point values:

$$I_D = K(V_{GS} - V_{TN})^2 = (1m)(2.96 - 2)^2 = 0.92mA$$

$$V_{DS} = V_{DD} - I_D(R_S + R_D) = 12 - (0.92m)(5k) = 7.4V$$

Small-signal analysis

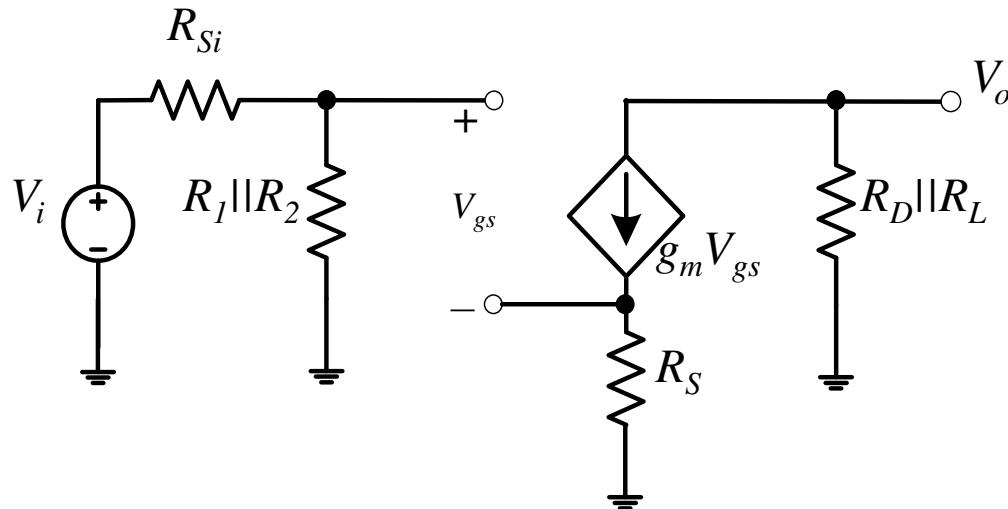

$$V_{gs} = \frac{(R_1 \| R_2)}{R_1 \| R_2 + R_{Si}} \times V_i$$

$$V_o = -g_m V_{gs} (R_D \| R_L)$$

$$A_V = \frac{-g_m (R_D \| R_L)}{1 + g_m R_S}$$


$$\begin{aligned} g_m &= 2K(V_{GS} - V_{TN}) \\ &= 2(1m)(2.96 - 2) = 1.92mS \\ r_o &= (\lambda I_{DQ})^{-1} = \infty \end{aligned}$$

$$V_{gs} = \frac{(R_1 \| R_2)}{R_1 \| R_2 + R_{Si}} \times V_i = 0.984V_i$$

$$\begin{aligned} A_V &= \frac{V_o}{V_i} = \frac{-g_m (R_D \| R_L)}{1 + g_m R_S} \\ &= -0.48 \end{aligned}$$


COMMON-SOURCE AMPLIFIER

- with Bypass Capacitor

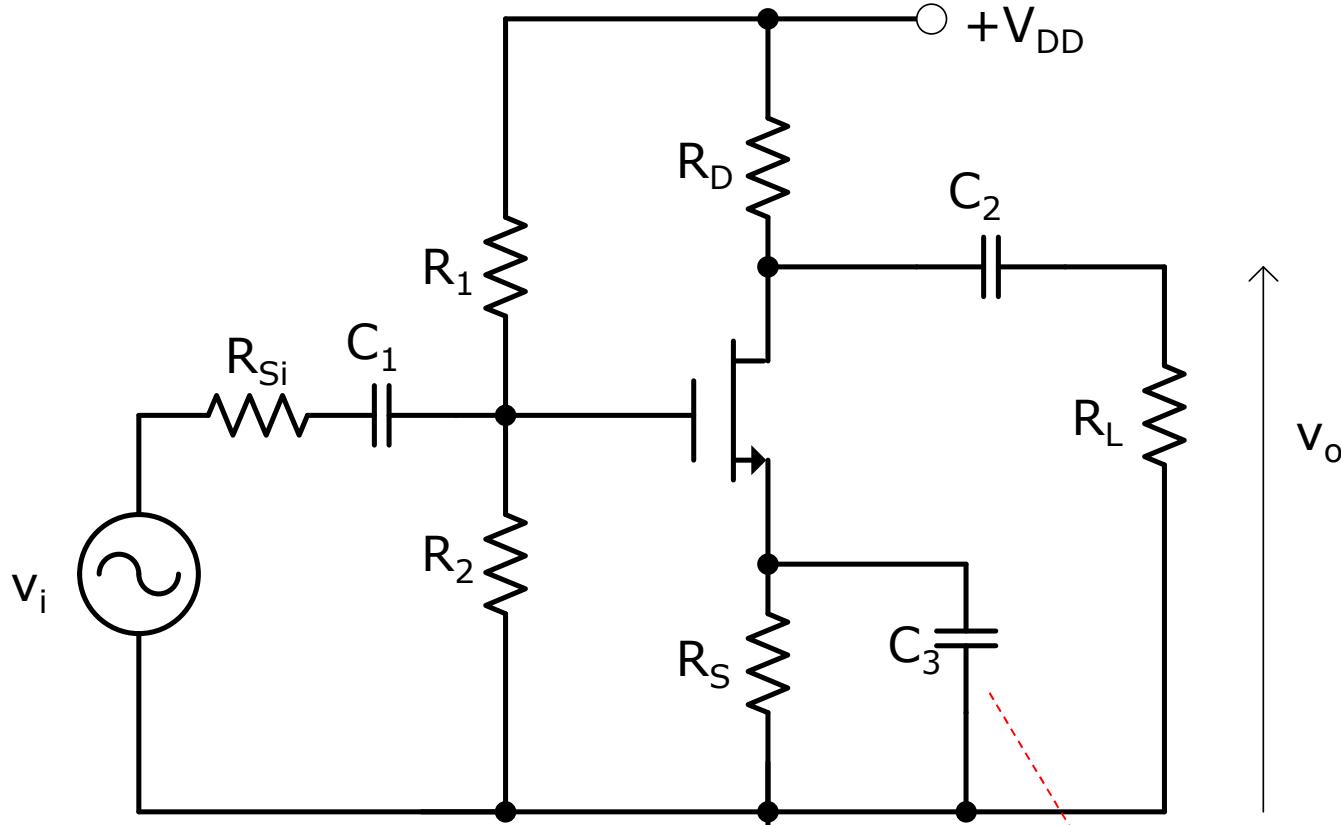


Minimize the loss in small-signal voltage gain while maintaining the Q-point stability


Small signal equivalent circuit

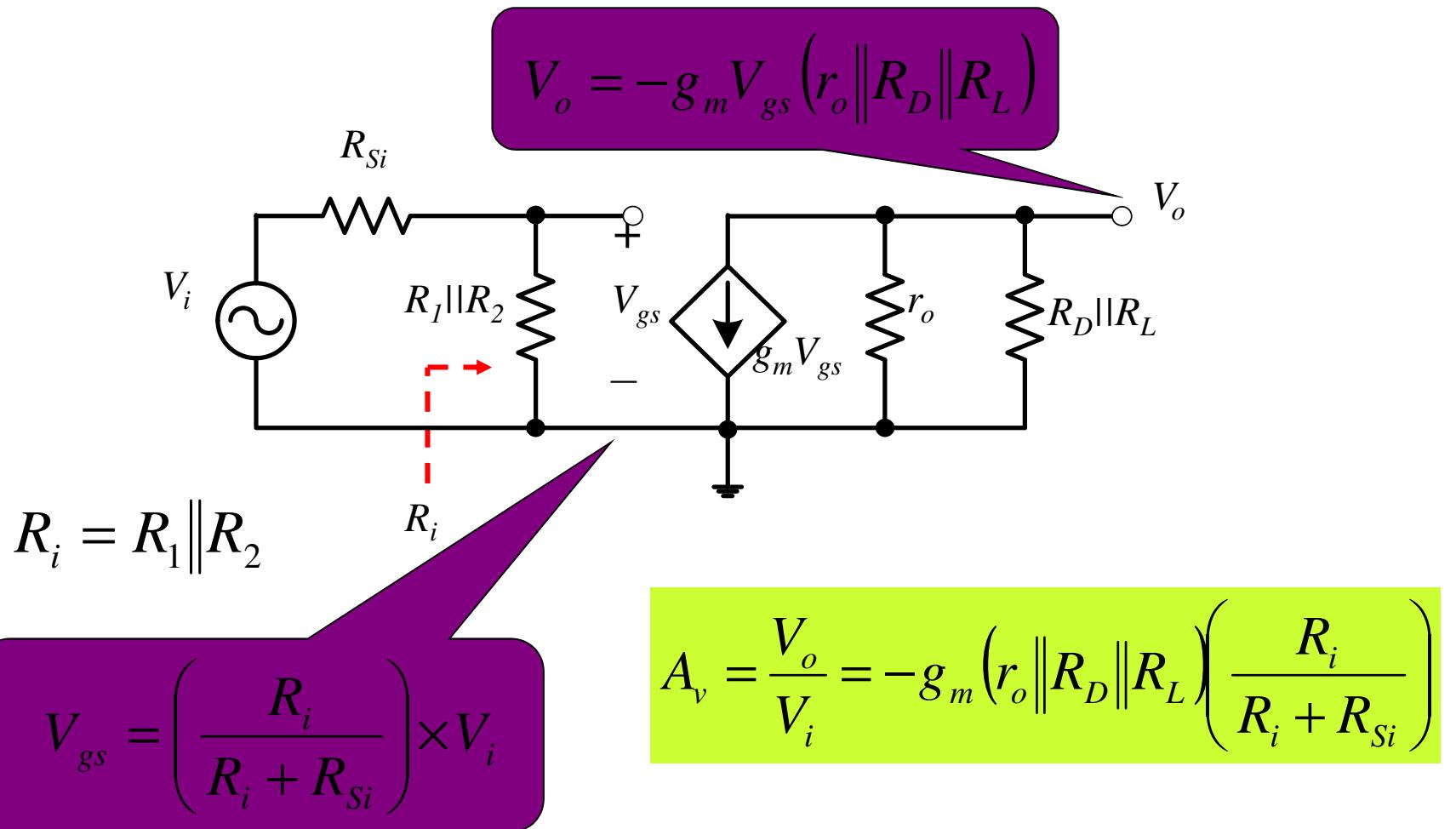

COMMON-DRAIN AMPLIFIER

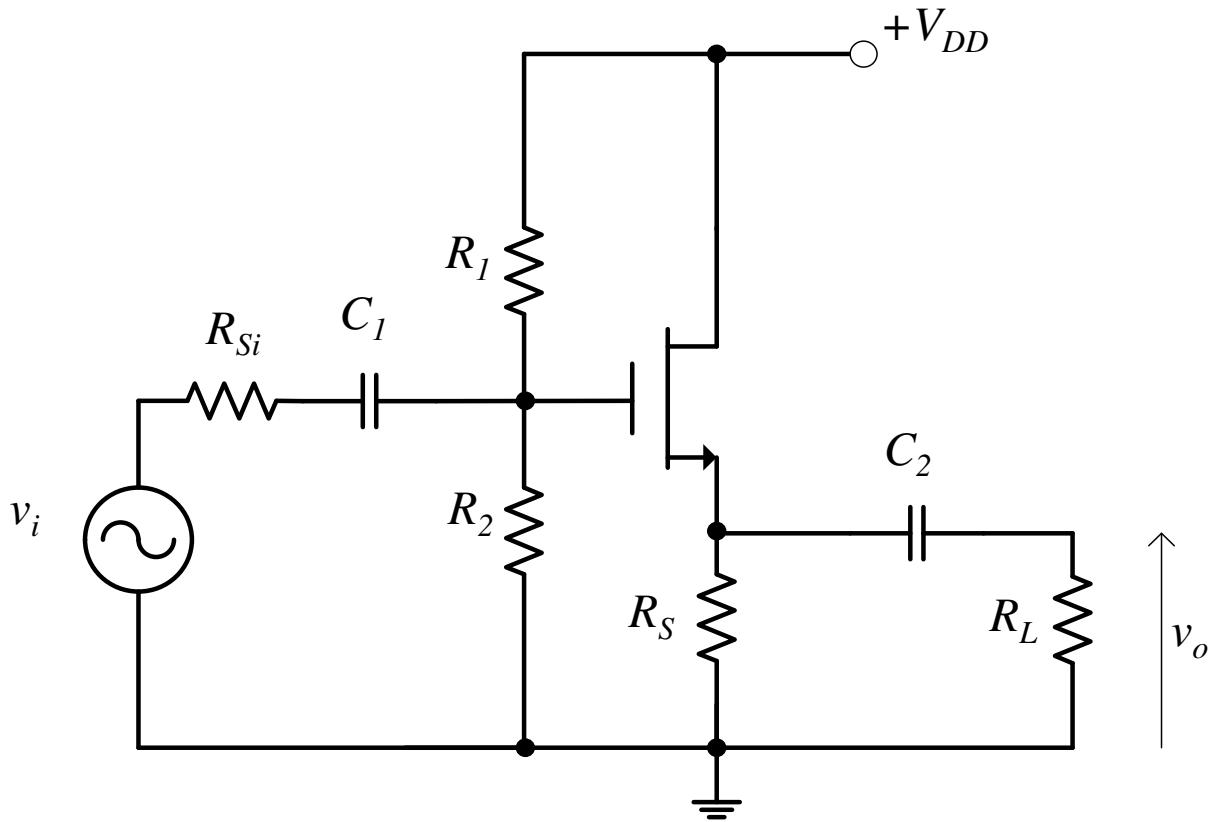

Small signal equivalent circuit

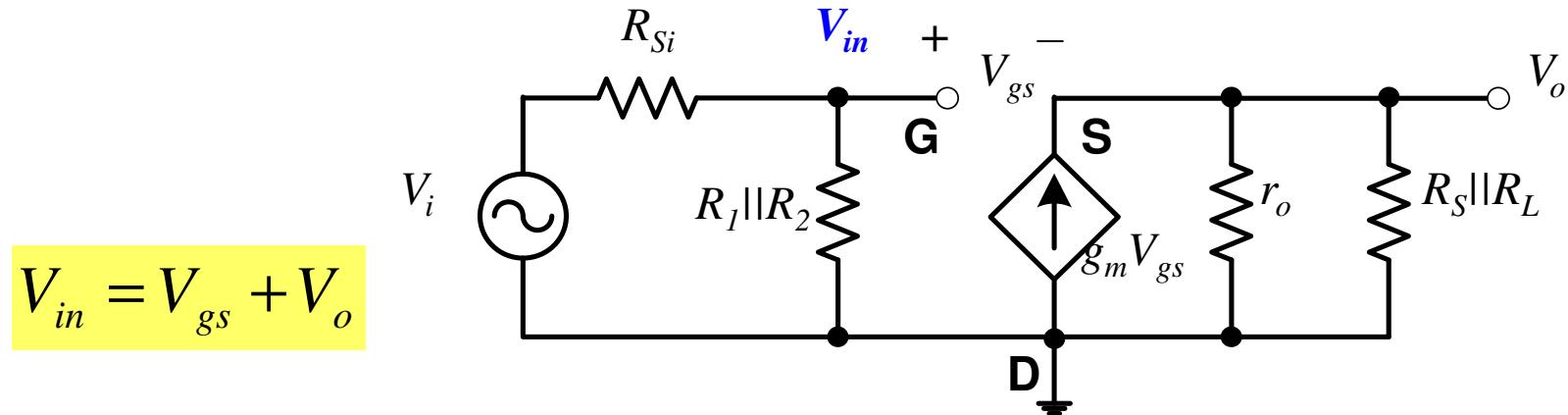

input
impedance

$$R_i = R_1 \parallel R_2$$

$$R_o = \frac{1}{g_m} \parallel R_S \parallel r_o \parallel R_L$$

Output
impedance

input
voltage

$$V_{in} = \left(\frac{R_i}{R_i + R_{Si}} \right) \times V_i$$


$$V_o = g_m V_{gs} (R_S \parallel R_L \parallel r_o)$$

output
voltage


small-signal
voltage gain

$$A_v = \frac{V_o}{V_i} = \frac{g_m (R_S \parallel R_L \parallel r_o)}{1 + g_m (R_S \parallel R_L \parallel r_o)} \left(\frac{R_i}{R_i + R_{Si}} \right)$$

COMMON-GATE AMPLIFIER

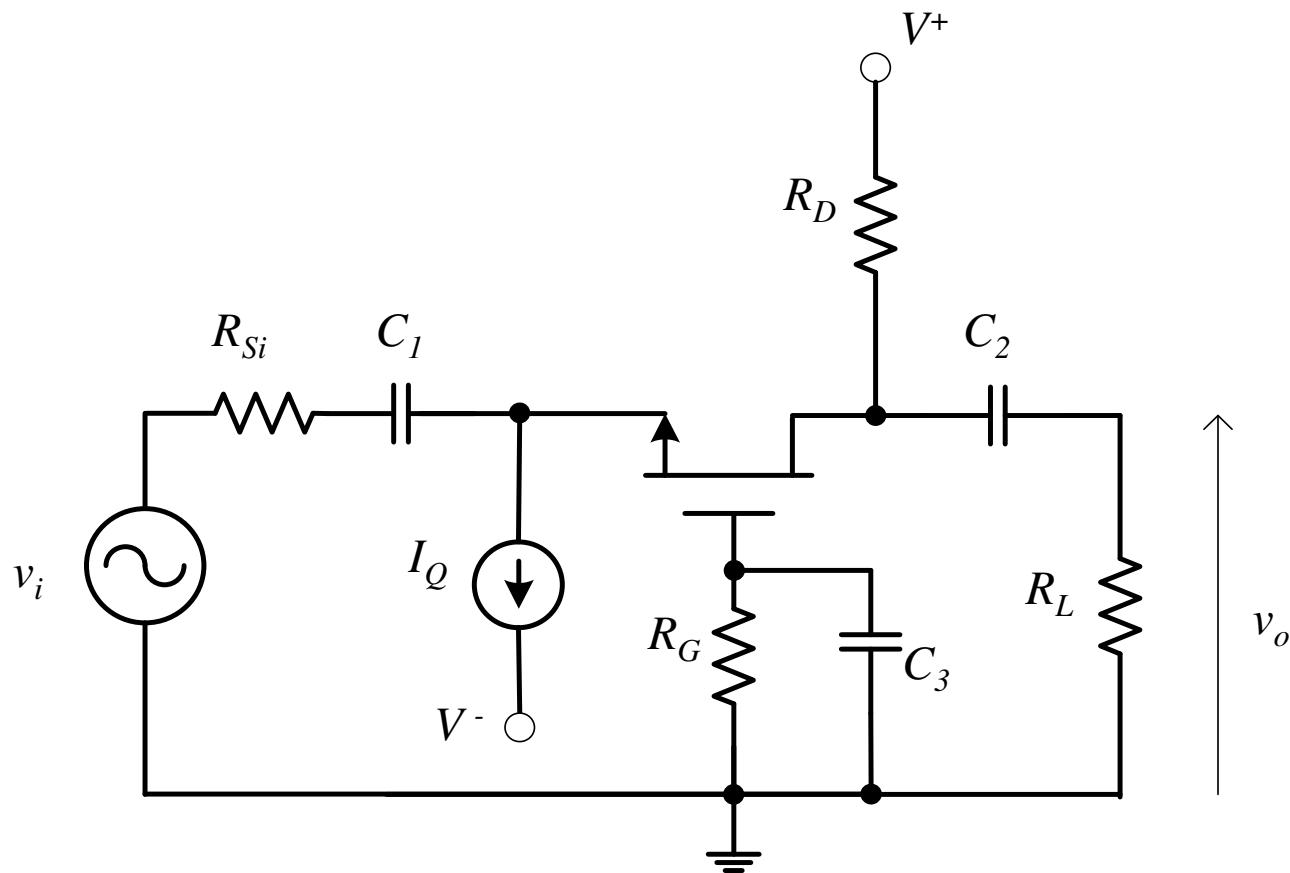

Small-signal equivalent circuit

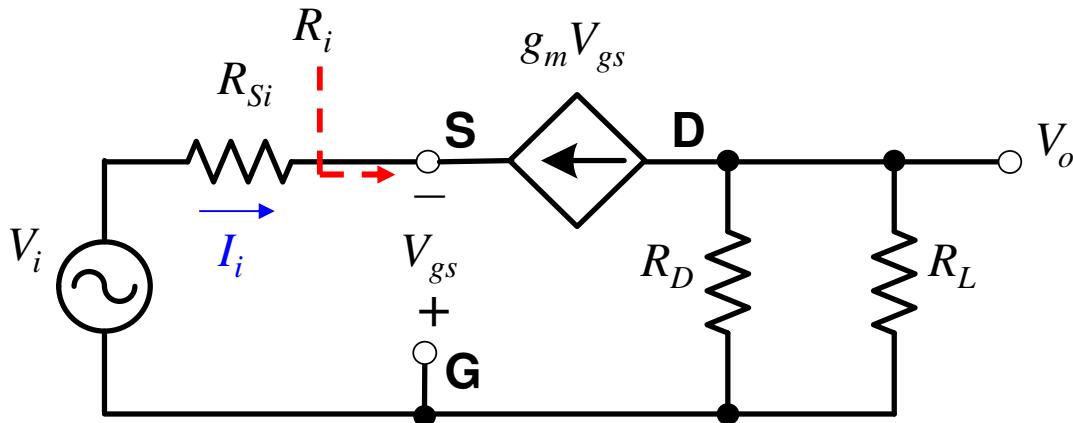

input
impedance

$$R_i = \frac{-V_{gs}}{I_i} = \frac{-V_{gs}}{-g_m V_{gs}} = \frac{1}{g_m}$$

input
voltage

$$V_i = I_i R_{Si} - V_{gs}$$

input
current

$$V_{gs} = \frac{-V_i}{1 + g_m R_{Si}}$$

$$I_i = -g_m V_{gs}$$

$$V_o = -(g_m V_{gs})(R_D \| R_L)$$

output
voltage

$$A_v = \frac{V_o}{V_i} = \frac{g_m (R_D \| R_L)}{1 + g_m R_{Si}}$$

small-signal
voltage gain

Comparison of Amplifier Topologies

Common Source

- Large $A_v < 0$
- Large R_{in}
- $R_{out} \cong R_D$

Common Gate

- Large $A_v > 0$
- Small R_{in}
- $R_{out} \cong R_D$

Source Follower

- $0 < A_v \leq 1$
- Large R_{in}
- Small R_{out}