



Sheet(2): BJT AC Analysis

- 1- For the circuits shown on Figure 1, draw the equivalent AC circuit model. Denote on your schematic the values of r_{π} and r_o . ($\beta = 100$, $V_A = 100\text{ V}$)

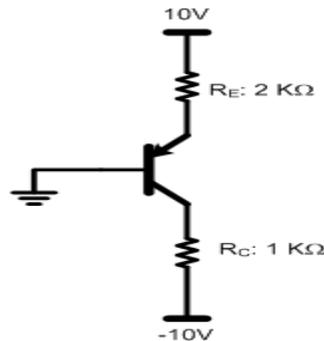


Fig 1

- 2- For the circuits shown on Figure 2, draw the equivalent AC circuit model. Denote on your schematic the values of r_{π} and r_o . ($\beta = 100$, $V_A = 100\text{ V}$)

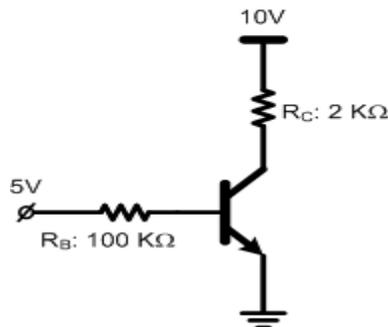


Fig 2

- 3- For the circuits shown on Figure 3, draw the equivalent AC circuit model. Denote on your schematic the values of r_{π} and r_o . ($\beta = 100$, $V_A = 100\text{ V}$)

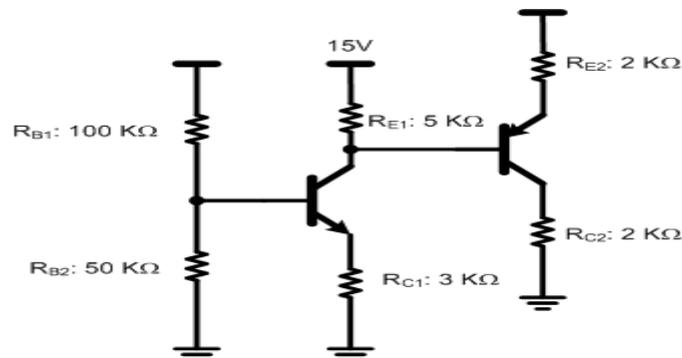


Fig 3

- 4- For the circuits shown on Figure 4, draw the equivalent AC circuit model. Denote on your schematic the values of r_{π} and r_o . ($\beta = 100$, $V_A = 100 \text{ V}$)

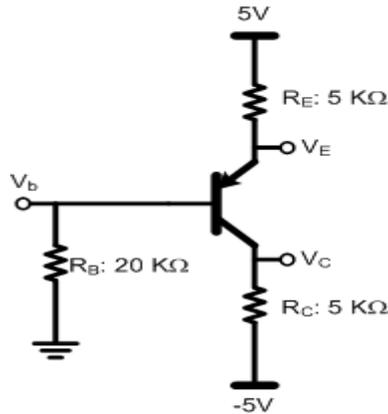


Fig 4

- 5- For the previous problem 4 determine:
 a) The DC load line and its graphical solution.
 b) The AC load line and compare it with the DC load line.
- 6- For the circuits shown on Figure 5, draw the equivalent AC circuit model. Denote on your schematic the values of r_{π} and r_o . ($\beta = 100$, $V_A = 100 \text{ V}$)

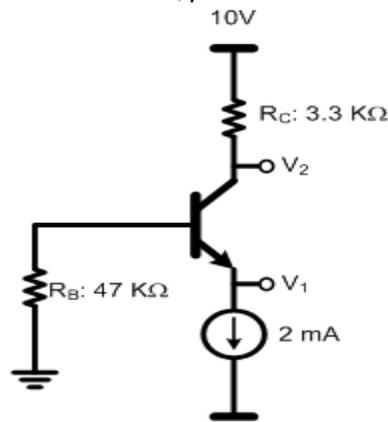


Fig 5

- 7- For the circuits shown on Figure 6, draw the equivalent AC circuit model. Denote on your schematic the values of r_{π} and r_o . ($\beta = 100$, $V_A = 100 \text{ V}$)

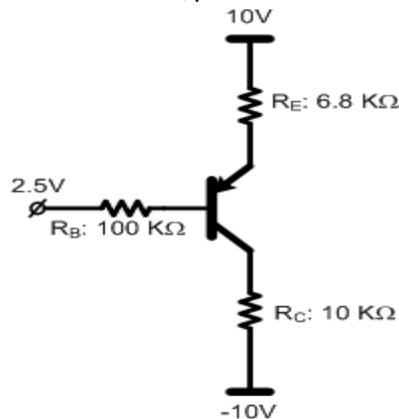


Fig 6

- 8- For the circuits shown on Figure 7, draw the equivalent AC circuit model. Denote on your schematic the values of r_{π} and r_o . ($\beta = 100$, $V_A = 100 \text{ V}$)

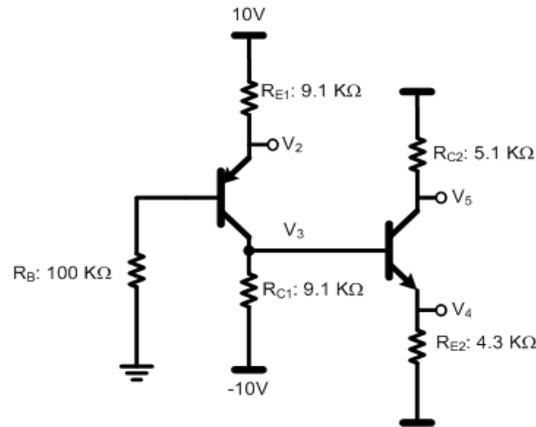


Fig 7

- 9- For the previous problem 8 determine:
- The DC load line and its graphical solution.
 - The AC load line and compare it with the DC load line.

10- For the circuit shown in figure 8:

- Find the values of R_E , R_C , R_{B1} and R_{B2} , given that $I_E = 1 \text{ mA}$, $V_{CE} = 2.5 \text{ V}$, $R_E = R_C$ [Hint: take $R_{B2} = 10 \text{ k}\Omega$]
- Draw the equivalent AC circuit model and calculate g_m , r_{π}
- Assuming all capacitors open circuit and ($r_s = 0$, $R_L = 1 \text{ k}\Omega$), Find the Common emitter A_v , R_{in} and R_{out} in the two cases:
 - SW is short circuit.
 - SW is open circuit

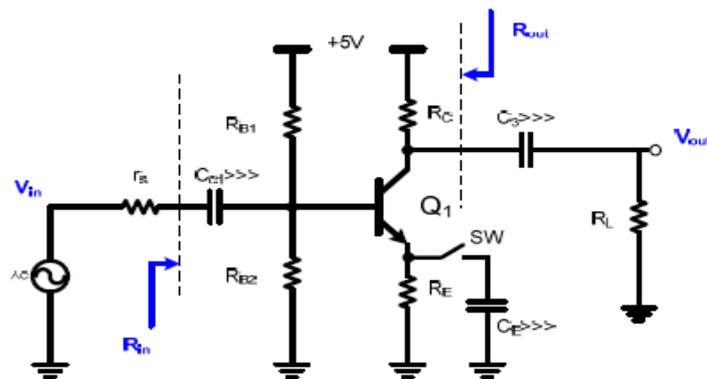


Fig 8

- 11- For the previous problem 10 determine:
- The DC load line and its graphical solution.
 - The AC load line and compare it with the DC load line.

12- Analyze the transistor amplifier shown in figure 9 to determine its voltage gain

Assume $\beta = 100$

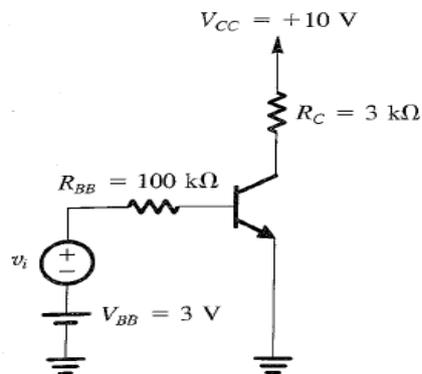


Fig 9

13- Analyze the transistor amplifier shown in figure 10 to determine its voltage gain.

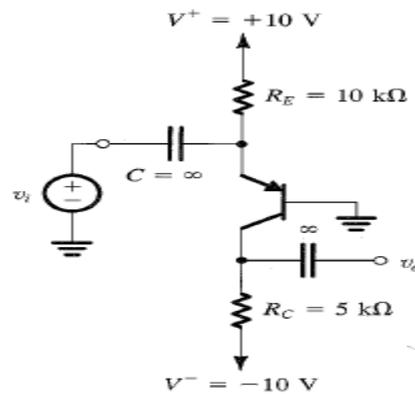


Fig 10

14- For the circuit shown in Fig. 11:

- i. Draw the equivalent AC circuit model, given $\beta = 100$, $g_m = 40\text{mS}$, $r_\pi = 2.5\text{k}\Omega$ and $r_o = 100\text{k}\Omega$
- ii. Find the voltage gain ($A_v = V_o/V_i$) and current gain ($A_I = i_L/i_s$).
- iii. Find R_{in} and R_{out}

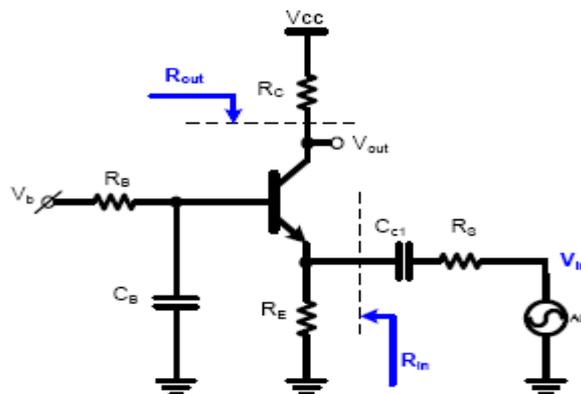


Fig 11

15- For the circuit shown in Fig. 12 :

- i. Draw the equivalent AC circuit model, given $\beta = 100$, $V_{CC} = 12\text{V}$, $V_{BE} = 0.7\text{V}$, $R_C = 6\text{k}\Omega$, $R_B = 50\text{k}\Omega$ & $V_{BB} = 1.2\text{V}$
- ii. Find the voltage gain ($A_v = V_o/V_i$)
- iii. Find R_{in} and R_{out}

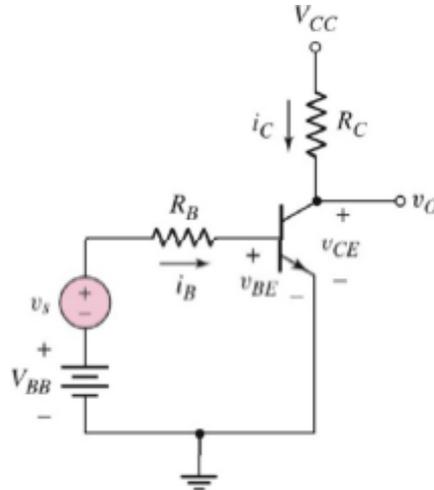


Fig 12

16- For the previous problem 15 determine:

- g) The DC load line and its graphical solution.
- h) The AC load line and compare it with the DC load line.

17- Determine the small-signal voltage gain, input resistance, and output resistance of the circuit shown in attached Figure 13. Assume the transistor parameters are: $\beta=100$, $V_{BE(on)} = 0.7\text{V}$, and $V_A=100\text{V}$

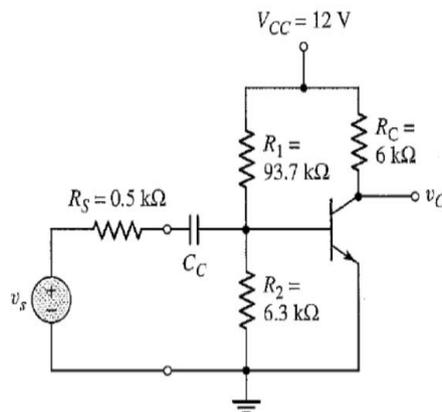


Fig 13

18- For the previous problem 17 determine:

- a) The DC load line and its graphical solution.
- b) The AC load line and compare it with the DC load line.

19- In the figure 14, let $\beta=150$, $V_A=200V$, $V_{CC}=7.5V$, $V_{BE(on)}=0.7V$, $R_C=15K\Omega$, $R_B=100k\Omega$, and $V_{BB}=0.92V$

- Determine the small-signal hybrid- parameters r_π , g_m , and r_o
- Find the small-signal voltage gain A_v

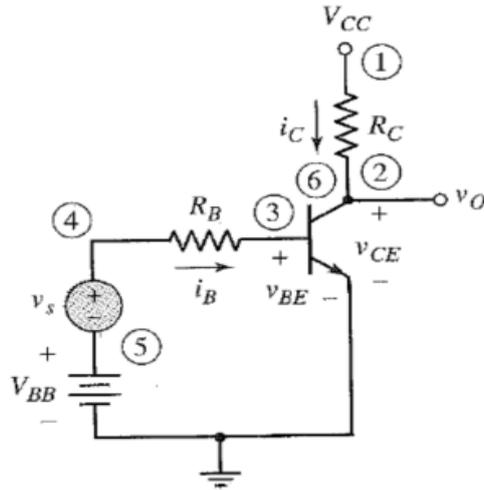


Fig 14

20- For the previous problem 8 determine:

- The DC load line and its graphical solution.
- The AC load line and compare it with the DC load line.