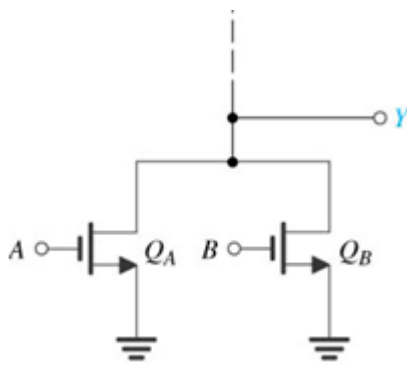





Sheet (5): Digital CMOS logic circuits


- 1- Design a CMOS Inverter gate by CMOS transistors.
- 2- Design a 2- Inputs CMOS AND gate by CMOS transistors.
- 3- Design a 2- Inputs CMOS OR gate by CMOS transistors.
- 4- Design a 2- Inputs CMOS NAND gate by CMOS transistors.
- 5- Design a 2- Inputs CMOS NOR gate by CMOS transistors.
- 6- Write the algebraic functions for the following gates:




(a)

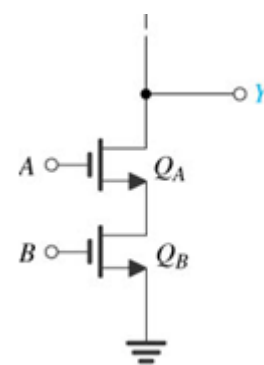


(b)

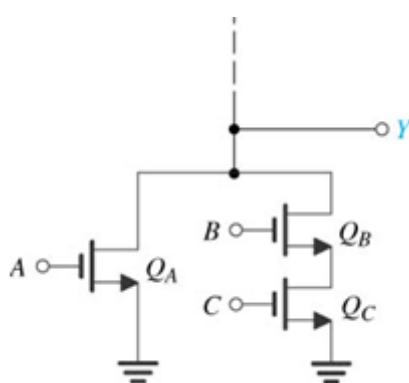


(c)

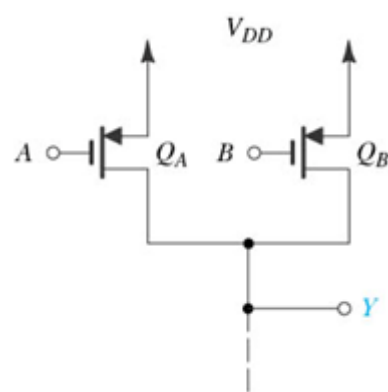

(d)

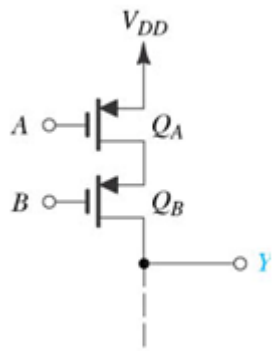

(e)

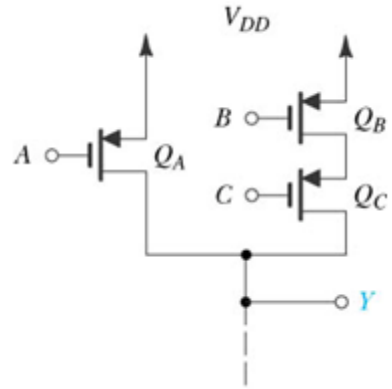

(f)

7- For the following algebraic functions write the truth table and Implement it by switches then by CMOS transistors:

a- $y = AB + C$

b- $y = (A + B)C$

c- $y = A' + B$

d- $y = AB + (AB)'$

e- $y = (A + B + C)'$