



Faculty of Engineering

ECE 335: Electronic Engineering

Lecture 8:

Bipolar Junction Transistors (BJTs)

Agenda

- History
- Basic Understanding
- Practical Aspects
- Structure & Symbol
- Basic Operation
- BJT Amplifier Basics
- Common Emitter Characteristics

HISTORY

First - BJTs

The transistor was probably the most important invention of the 20th Century, and the story behind the invention is one of clashing egos and top secret research.



Reference:

Bell Labs Museum

B. G. Streetman & S. Banerjee 'Solid State Electronic Devices', Prentice Hall 1999.

Interesting story...

Picture shows the workbench of John Bardeen (Stocker Professor at OU) and Walter Brattain at Bell Laboratories. They were supposed to be doing fundamental research about crystal surfaces.

The experimental results hadn't been very good, though, and there's a rumor that their boss, William Shockley, came near to canceling the project. But in 1947, working alone, they switched to using tremendously pure materials.

It dawned on them that they could build the circuit in the picture. It was a working amplifier! John and Walter submitted a patent for the first working point contact transistor.



Interesting story...

Shockley was furious and took their work and invented the junction transistor and submitted a patent for it 9 days later.

The three shared a Nobel Prize in 1955. Bardeen and Brattain continued in research (and Bardeen later won another Nobel).

Shockley quit to start a semiconductor company in Palo Alto. It folded, but its staff went on to invent the integrated circuit (the "chip") and to found Intel Corporation.


By 1960, all important computers used transistors for logic, and ferrite cores for memory.



BASIC UNDERSTANDING


Bipolar Junction Transistors (BJTs)

- The bipolar junction transistor is a semiconductor device constructed with three doped regions.
- These regions essentially form two ‘back-to-back’ p-n junctions in the same block of semiconductor material (silicon).
- The most common use of the BJT is in linear amplifier circuits (linear means that the output is proportional to input). It can also be used as a switch (in, for example, logic circuits).

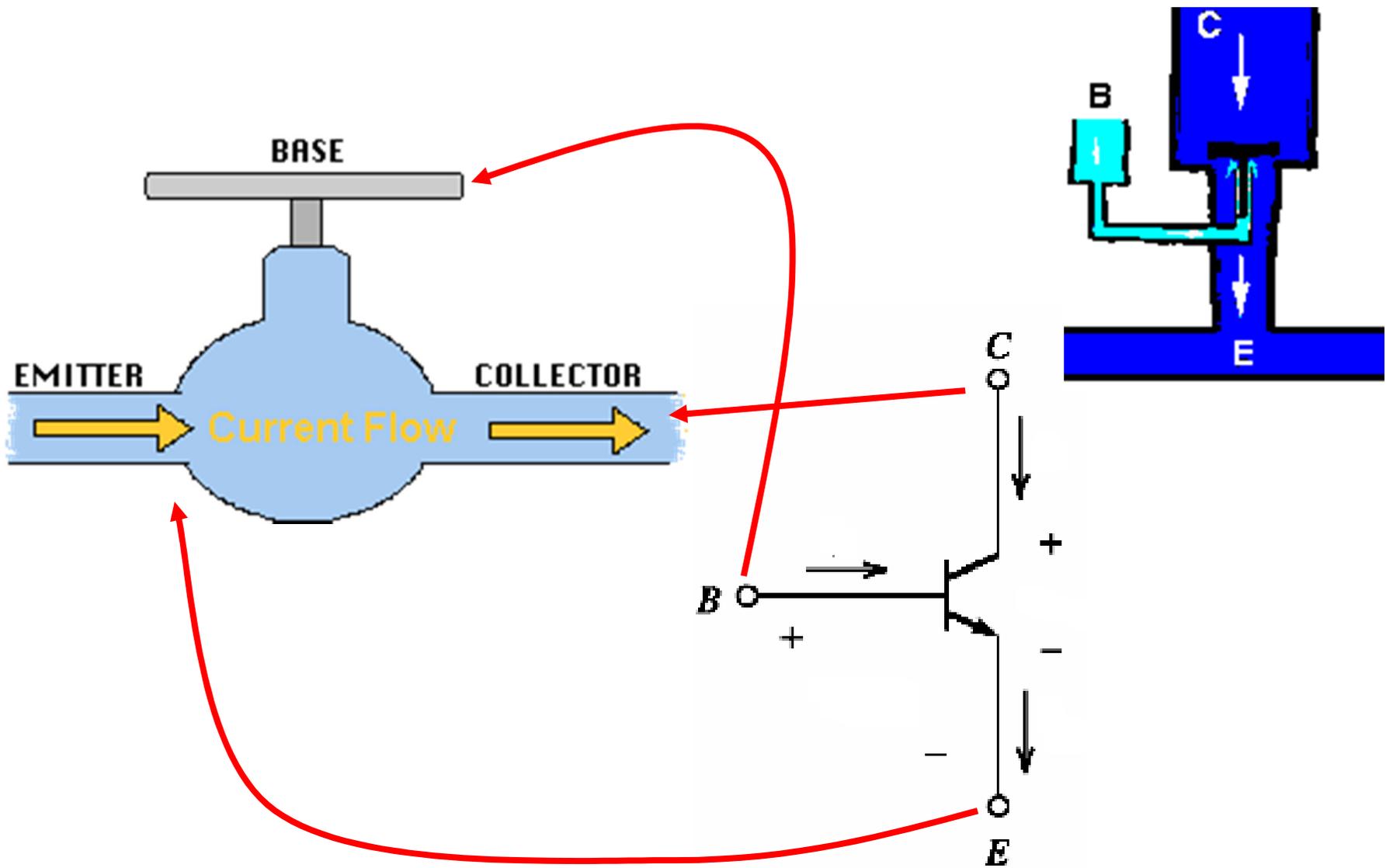


Understanding of BJT

Basic models of BJT

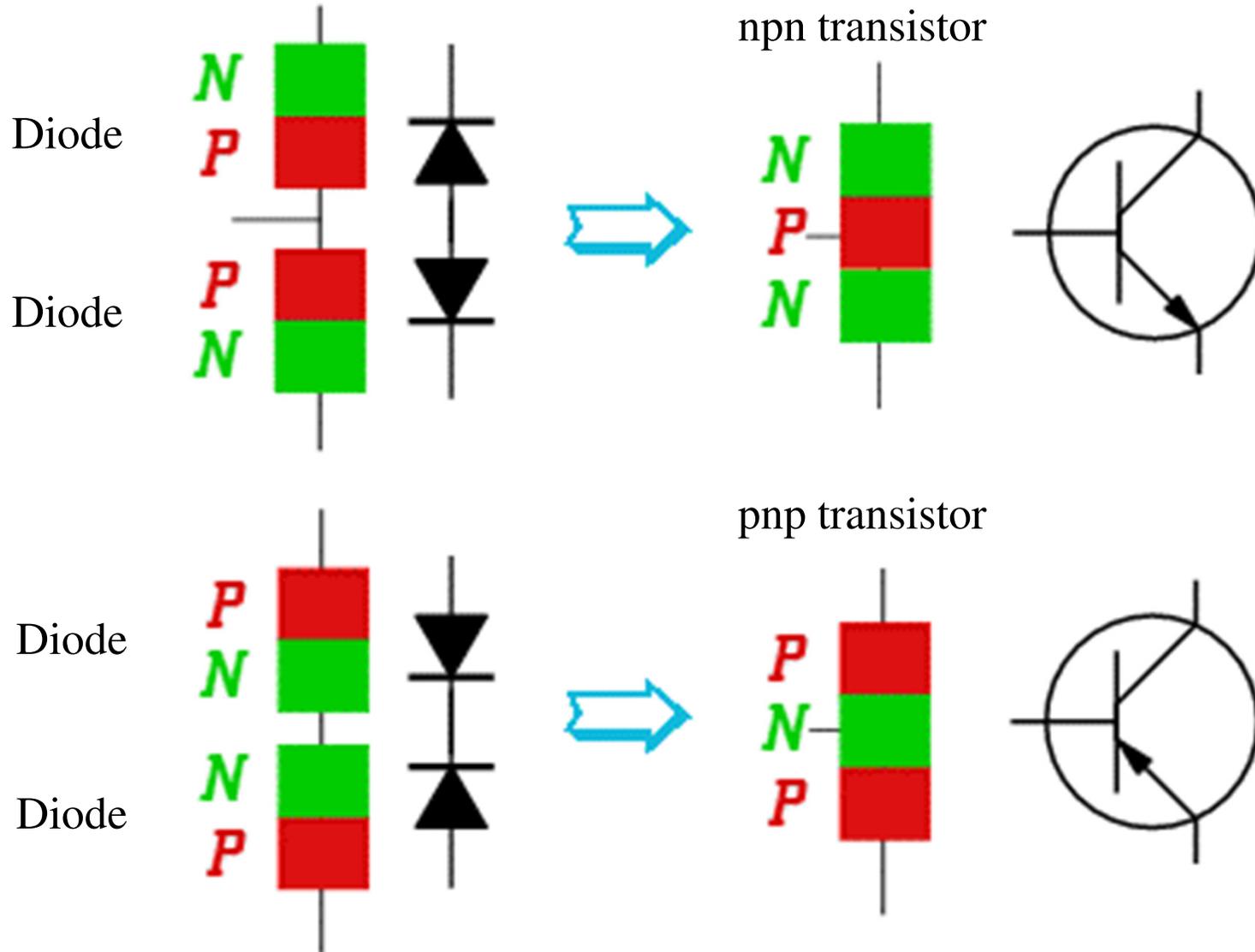


Basic models of BJT

Bipolar Junction Transistor Fundamentals


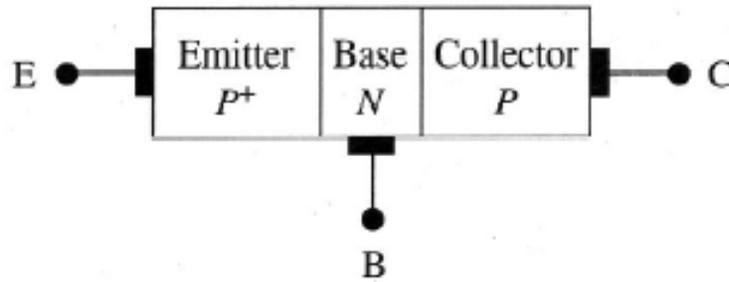


pnp

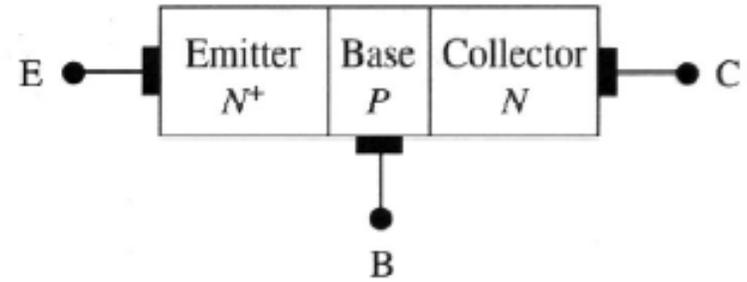


npn

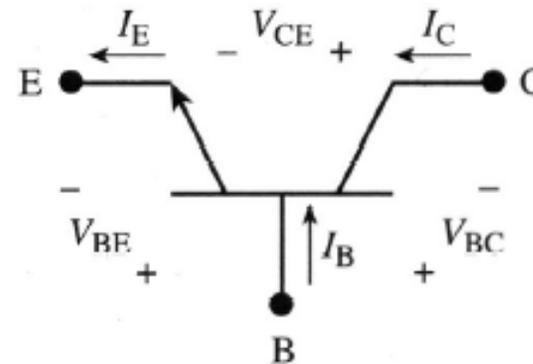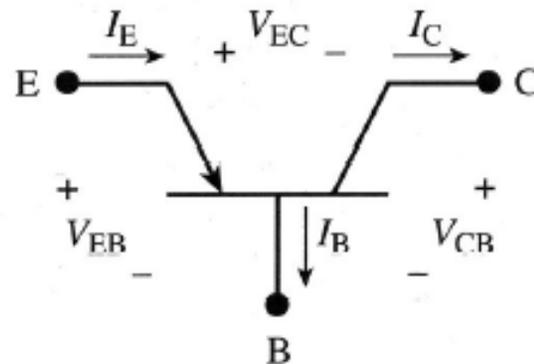Looks sort of
like two diodes
back to back





PRACTICAL ASPECTS


BJTs – Practical Aspects

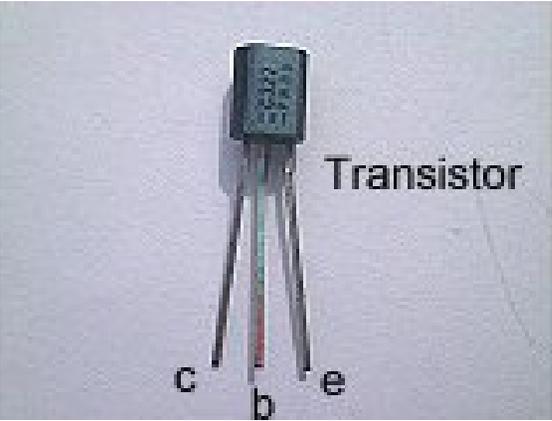

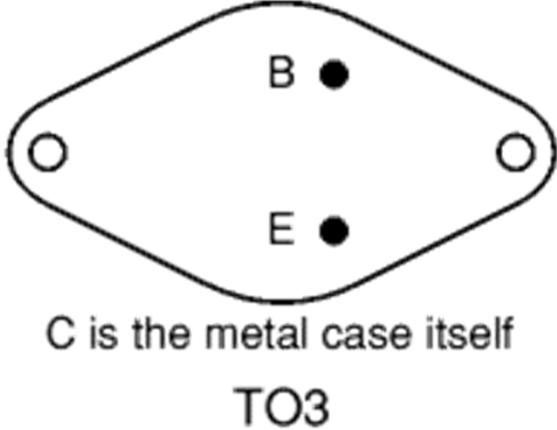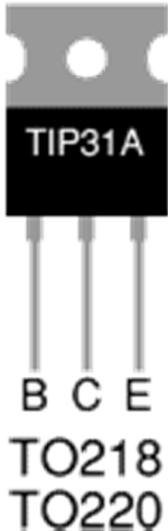Views are from below with the leads towards you.



BJTs – Testing

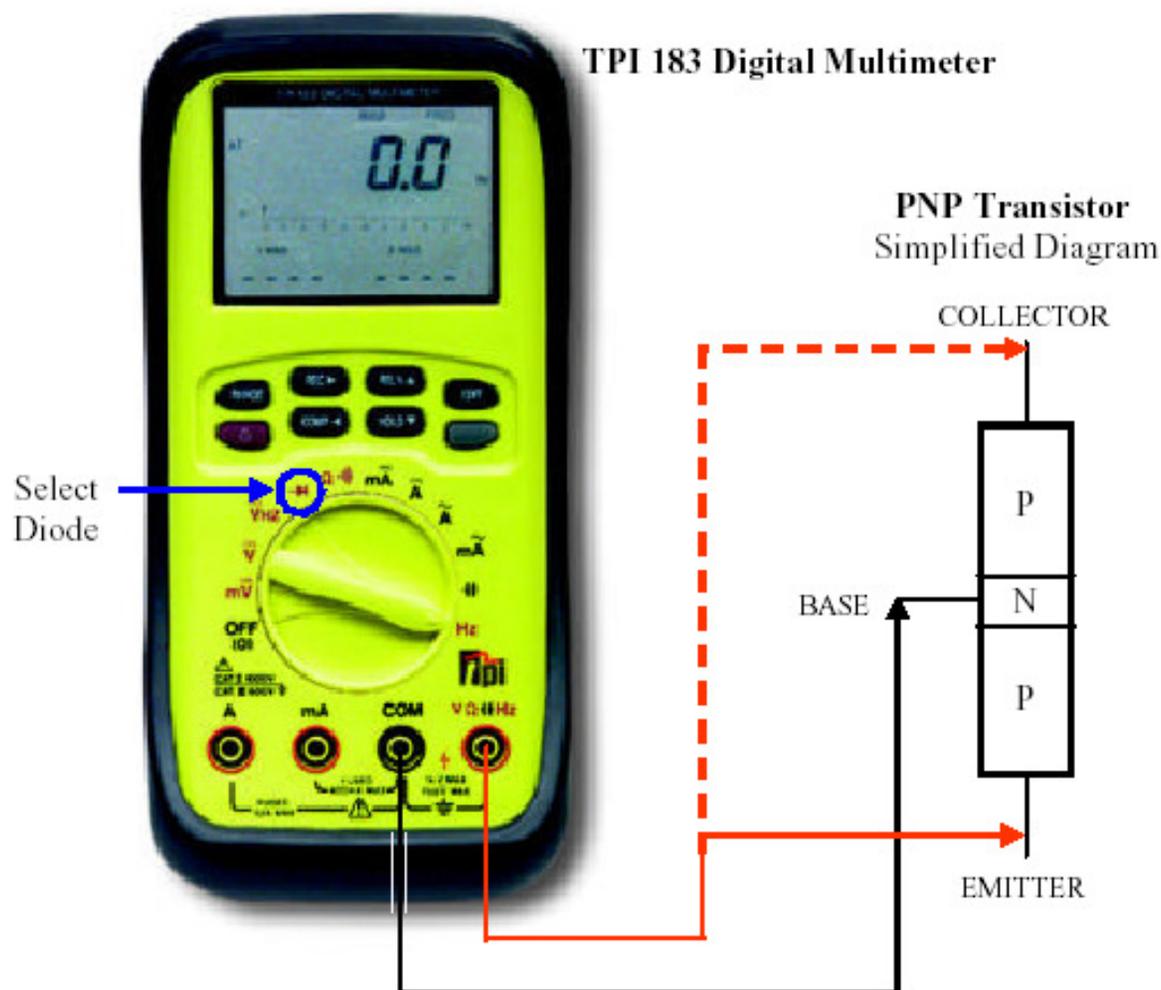

PNP Test Procedure

Connect the meter leads with the polarity as shown and verify that the base-to-emitter and base-to-collector junctions read as a forward biased diode: 0.5 to 0.8 VDC.

Reverse the meter connections to the transistor and verify that both PN junctions do not conduct. Meter should indicate an open circuit. (Display = OUCH or OL.)

Finally read the resistance from emitter to collector and verify an open circuit reading in both directions. (Note: A short can exist from emitter to collector even if the individual PN junctions test properly.)


BJTs – Testing

PNP Test Procedure

Connect the meter leads with the polarity as shown and verify that the base-to-emitter and base-to-collector junctions read as a forward biased diode: 0.5 to 0.8 VDC.

Reverse the meter connections to the transistor and verify that both PN junctions do not conduct. Meter should indicate an open circuit. (Display = OUCH or OL.)

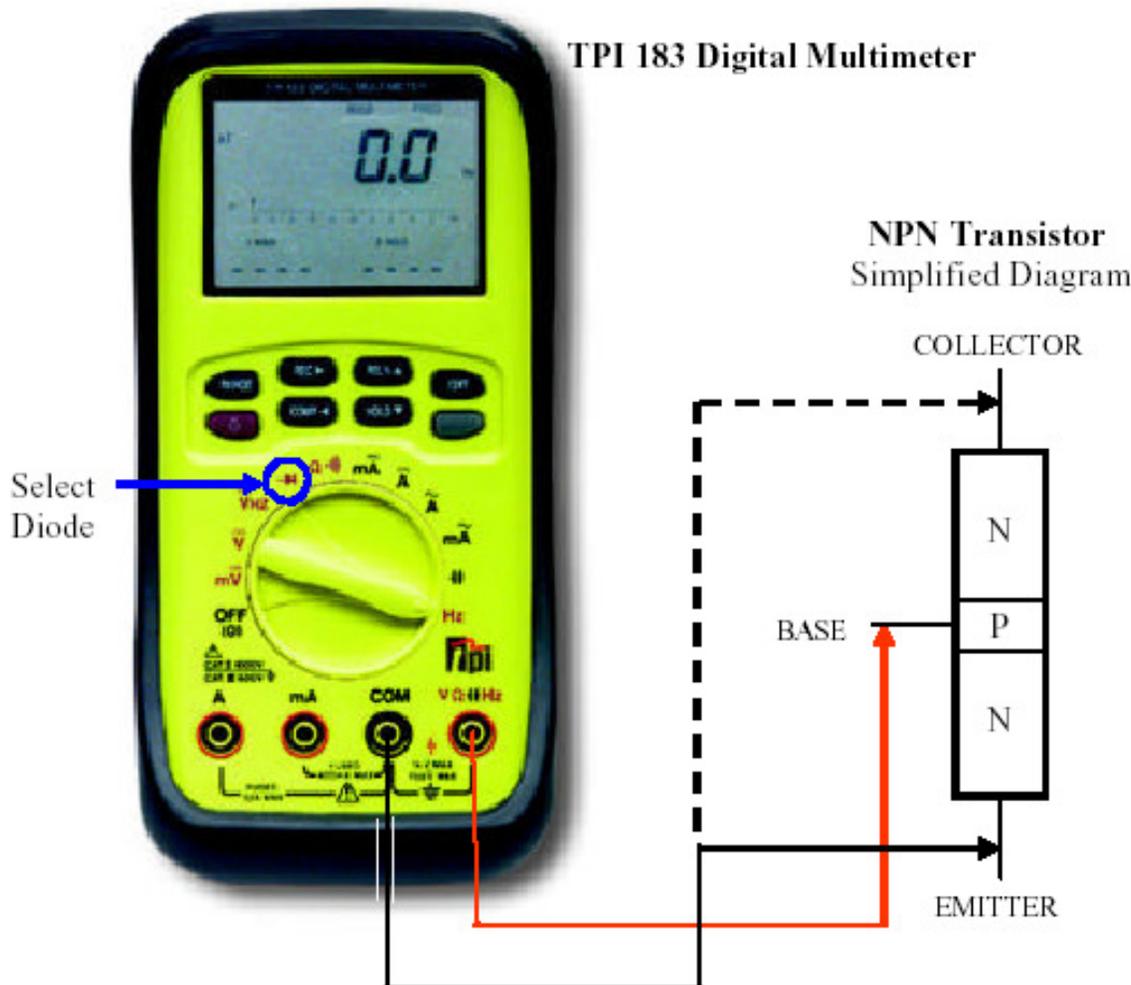
Finally read the resistance from emitter to collector and verify an open circuit reading in both directions. (Note: A short can exist from emitter to collector even if the individual PN junctions test properly.)



BJT STRUCTURE AND SYMBOL

nnp-BJT Structure

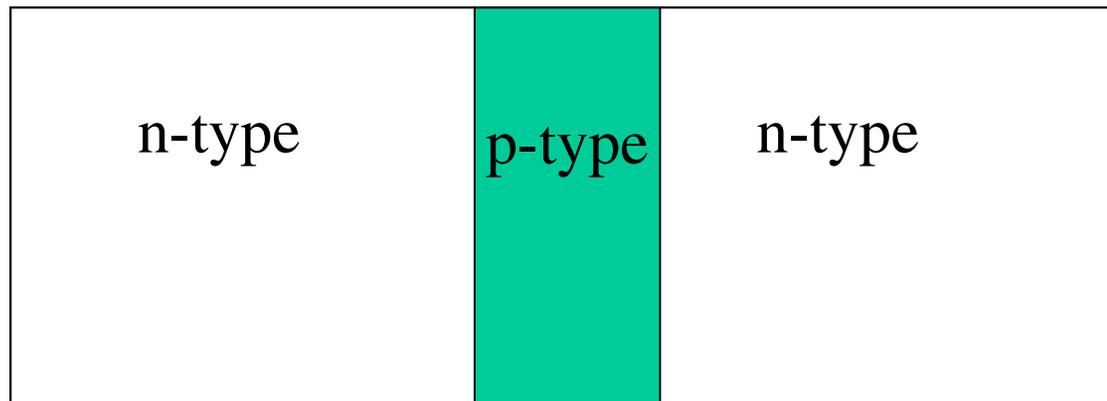
- The 'nnp' version of the BJT consists of two n regions separated by a p region (as the name suggests). A schematic of an nnp transistor is shown.




BJT Structure

- The three regions are known as the emitter, base and collector regions.
- Electrical connections are made to each of these regions.


nnp-BJT Structure

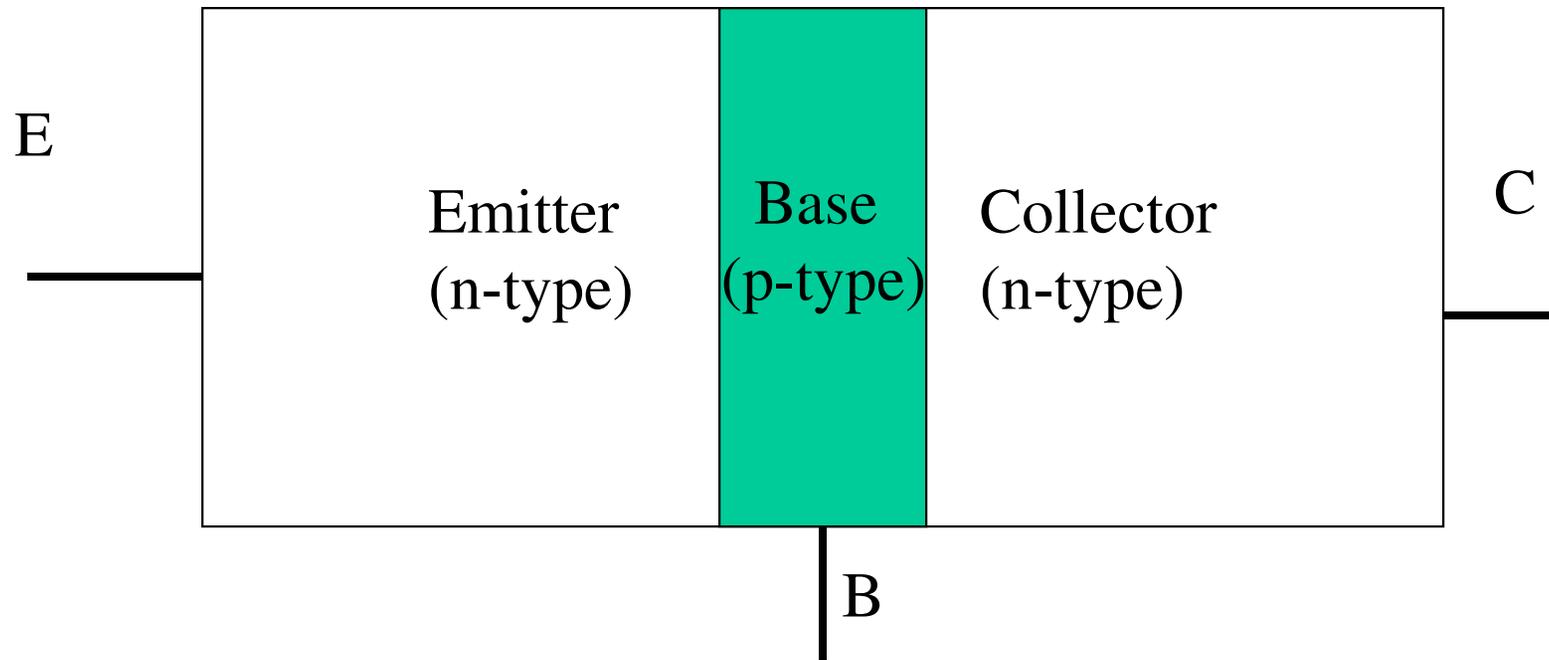

npn BJT Symbol

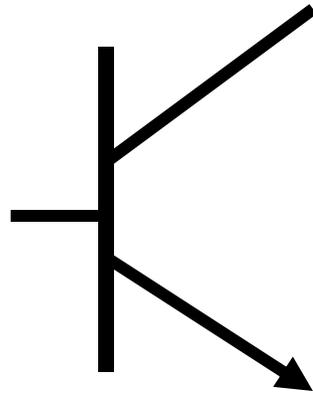


npn BJT Symbol

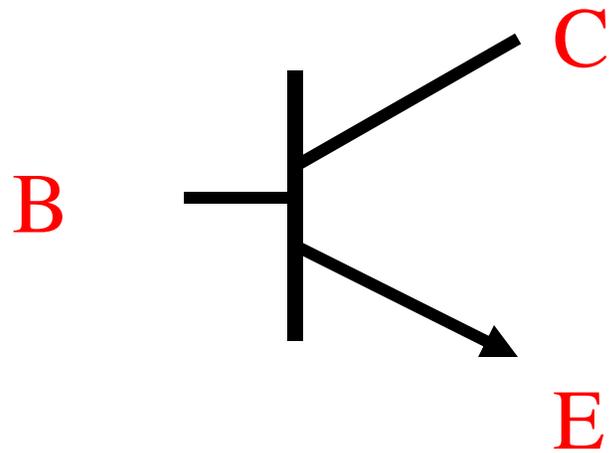

pnp BJT Symbol

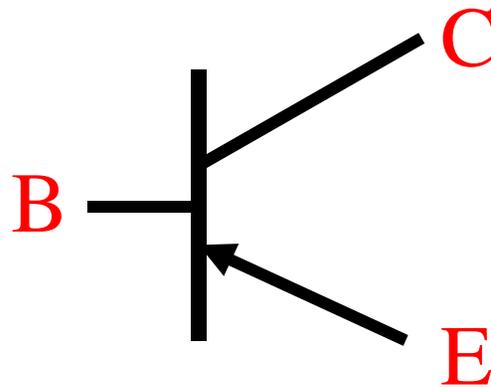- In the symbol for a pnp BJT transistor the direction of the arrow on the emitter is reversed



BJT Circuits

- Most electronic devices take the signal between two input terminals and deliver from it an output signal between two output terminals.
- The BJT has only three terminals so one of these is usually shared (i.e. made common) between input and output circuits.
- We thus talk about common emitter (CE), common base (CB) and common collector (CC) configurations.

BJT Circuits


- The CE configuration is the one most commonly encountered since it provides both good current and voltage gain for ac signals.
- In the CE configuration the **input is between the base and the emitter. The output is between the collector and the emitter.**
- All three configurations will be dealt with next semester

Current Directions (Convention)

- We define currents directions such that the collector current (I_C) and base current (I_B) flow **into** the device whereas the emitter current (I_E) flows **out** of the device.
- **THIS IS IMPORTANT; we shall shortly treat the transistor as a current node and write**

$$I_C + I_B = I_E \quad (\text{Kirchhoff})$$

Current Flow Convention

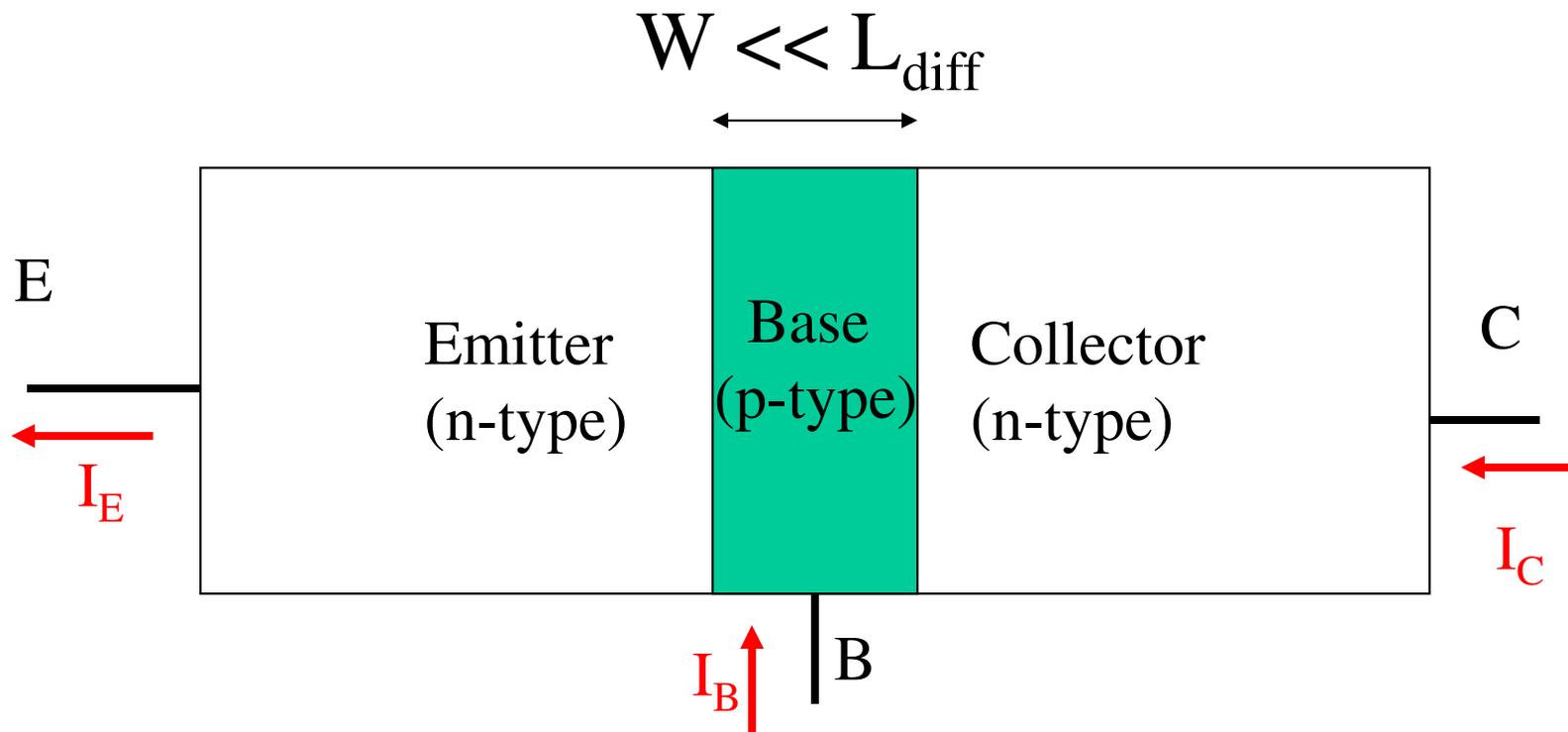

nnp BJT Structure

- The emitter (E) and is **heavily doped** (n-type).
- The collector (C) is also doped n-type.
- The base (B) is **lightly doped** with opposite type to the emitter and collector (i.e. p-type in the npn transistor).
- The base is physically very thin for reasons described below. ($W \ll L_{\text{diff}}$)

B-E and C-B Junctions

- The p-n junction joining the base and emitter regions is called the base-emitter (B-E) junction. (or emitter-base, it doesn't really matter)
- The p-n junction between the base and collector regions is called the collector-base (C-B) junction.(or base-collector)


BASIC OPERATION

(Very) Basic Operation

- In normal operation for analogue (linear amplifier) circuits the **emitter-base junction** is **forward biased** and the **collector-base junction** is **reverse biased**.
- These ‘bias’ or ‘quiescent’ conditions are set by d.c. bias circuits.
- The a.c. (‘analogue’) signal to be amplified is superimposed on top of the d.c. bias voltages and currents. (Exactly as for dynamic resistance, small variations about a Q point, in our discussion of diodes.)

BJT Operation

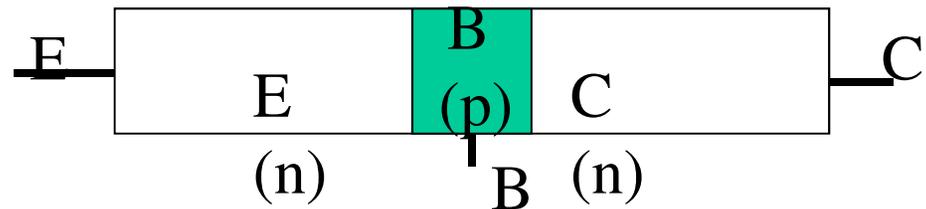- The forward bias between the base and emitter injects electrons from the emitter into the base and holes from the base into the emitter.



BJT Operation

- The forward bias between the base and emitter injects electrons from the emitter into the base and holes from the base into the emitter.
- As the emitter is heavily doped and the base lightly doped most of the current transport across this junction is due to the electrons flowing from emitter to base.

BJT Operation

- The base is lightly doped and physically very thin.
- Thus only a small percentage of electrons flowing across the base-emitter (BE) junction combine with the available holes in this region.

BJT Operation

- Most of the electrons (a fraction α which is close to 1, e.g. 0.98) flowing from the emitter into the base reach the collector-base (CB) junction.
- Once they reach this junction they are ‘pulled’ across the reverse biased CB junction into the collector region i.e. they are collected.
- Those electrons that do recombine in the base give rise to the small base current I_B .

BJT Operation

- The electrons ‘collected’ by the collector at the C-B junction essentially form the collector current in the external circuit.
- There will also be a small contribution to collector current, called I_{CO} , from the reverse saturation current across the CB junction.
- The base current supplies positive charge to neutralise the (relatively few) electrons recombining in the base. This prevents the build up of charge which would hinder current flow.

BJT Operation.

The Critical Knowledge!

- The (relatively large) collector current is directly controlled by the (much smaller) base current.
- **This is further illustrated and clarified in the following discussions of the BJT's current-voltage characteristics.**

BJT Transistor Man (after Horowitz and Hill)

