




Faculty of Engineering

MCT242: Electronic Instrumentation


**Lecture 8:
Active Filters**

Real Filters

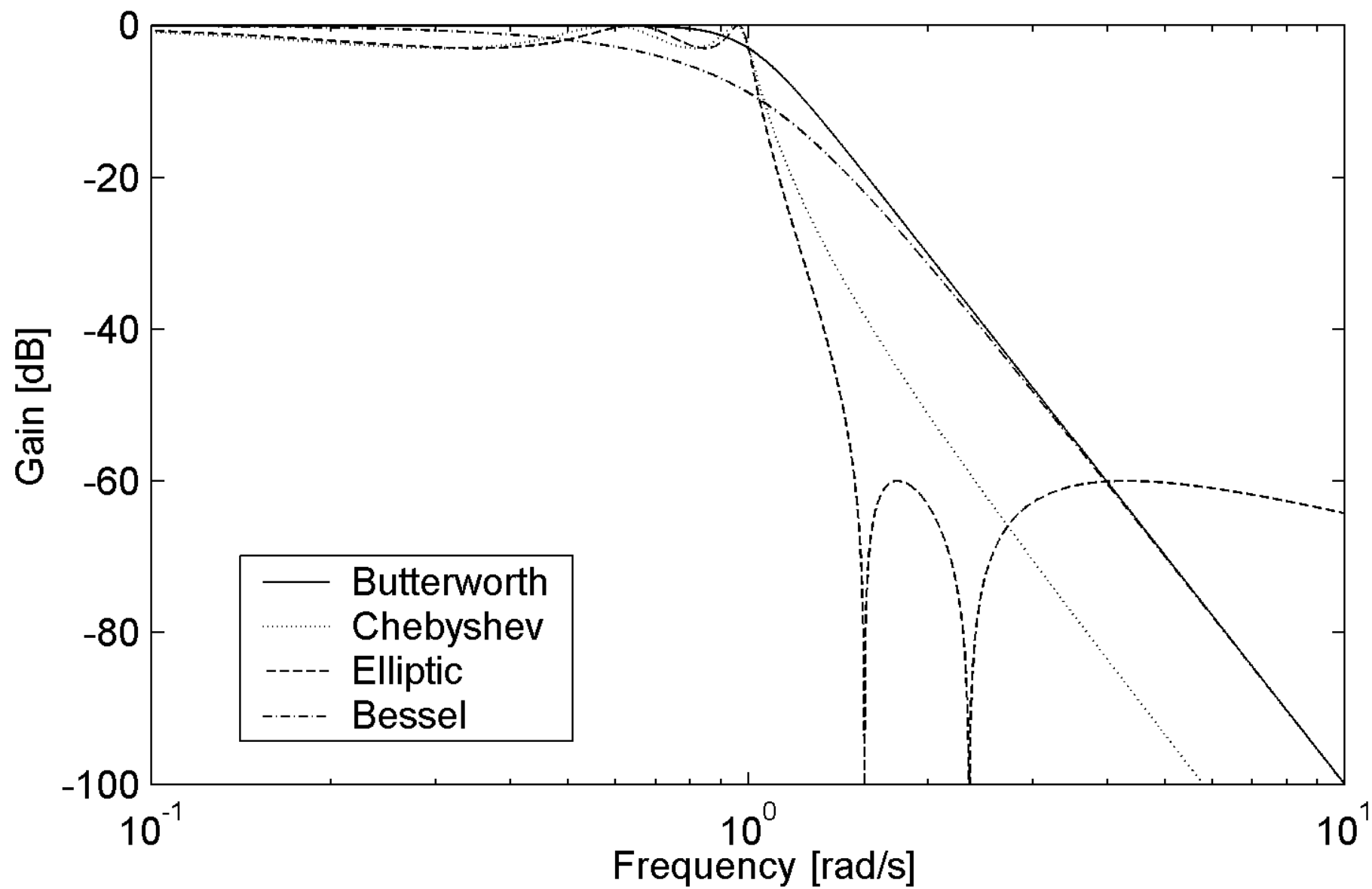- The approximations to the ideal filter are the:
 - Butterworth filter
 - Chebyshev filter
 - Cauer (Elliptic) filter
 - Bessel filter




Filter Response Characteristics

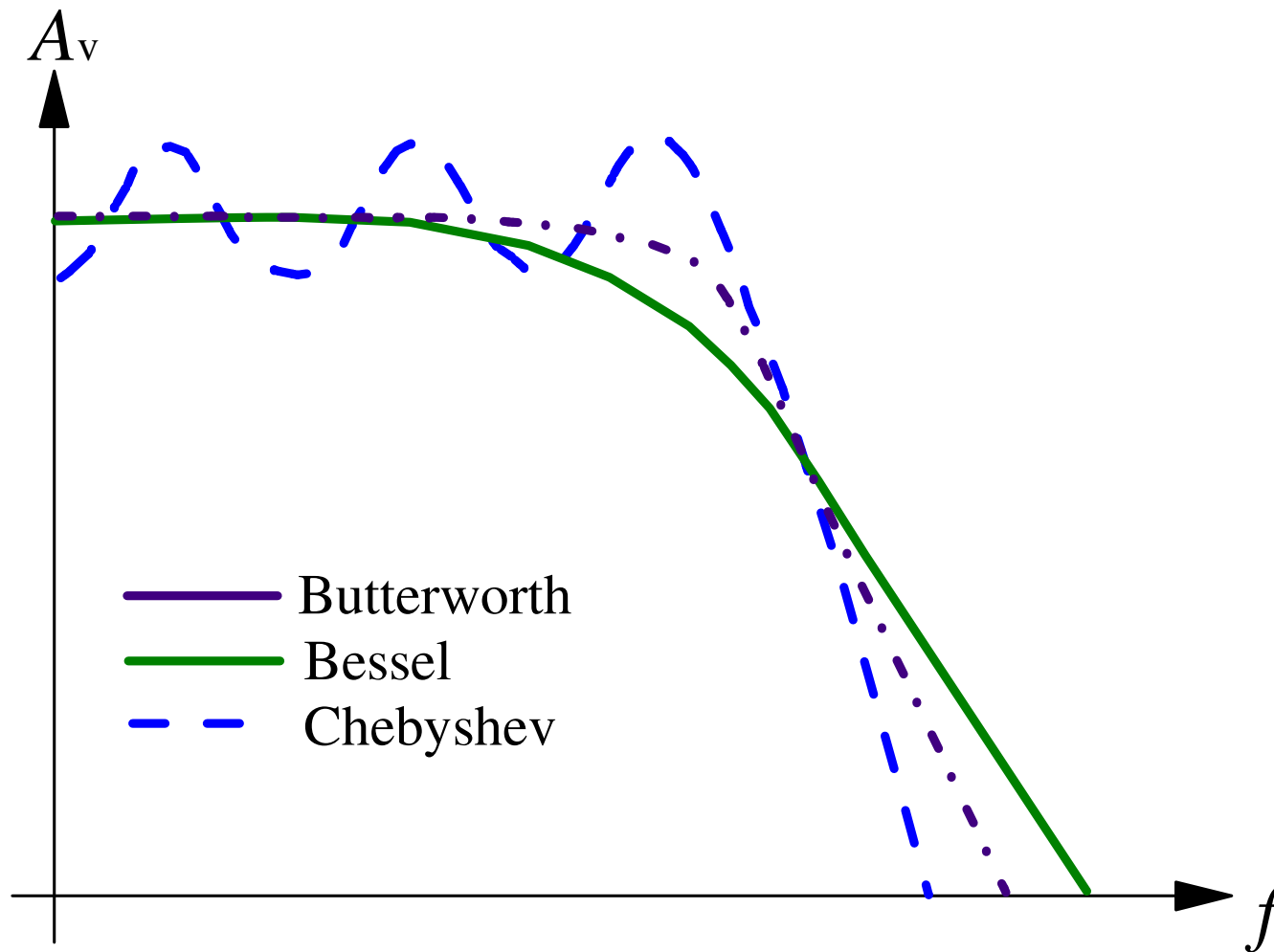

PERFORMANCE CRITERIA

AMPLITUDE RESPONSE

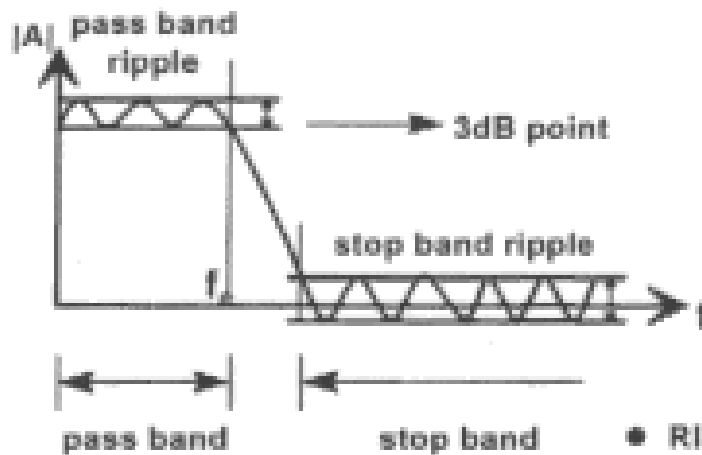

$$20 \log_{10} |A| = \text{Gain in dB}$$


f_c = Cut-off Frequency

$$\text{Gain at 3dB point (at } f_c) = \frac{|A|}{\sqrt{2}}$$

- RIPPLE IN PASS BAND CAUSES NON-LINEARITY
- POSSIBLE TO DESIGN WITH NO RIPPLE
- RIPPLE IN STOP BAND IS LESS IMPORTANT
- FALL OFF dB / Decade (Gain in dB / Decade of f)
- STOP BAND ATTENUATES (SAY - 40dB)


Bessel Characteristic

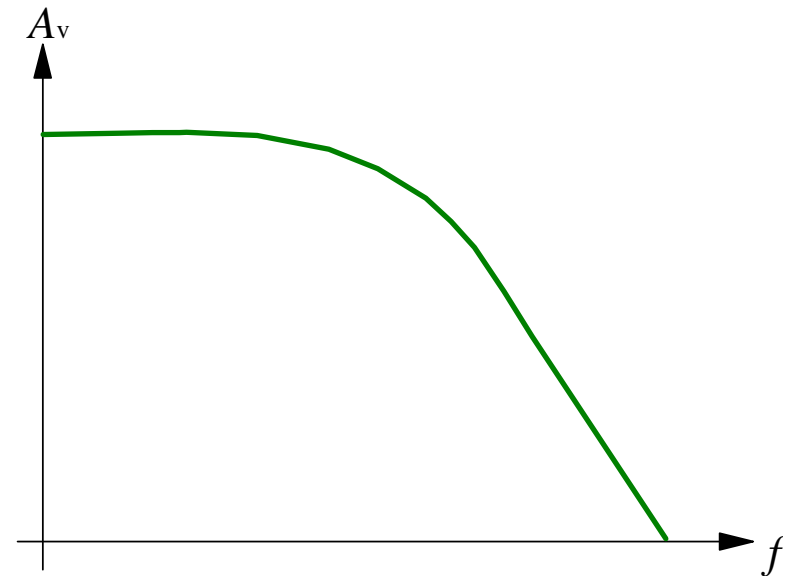- Flat response in the passband.
- Role-off rate less than $20dB/\text{decade}/\text{pole}$.
- Phase response is linear.
- Used for filtering pulse waveforms without distorting the shape of the waveform.




Butterworth Characteristic

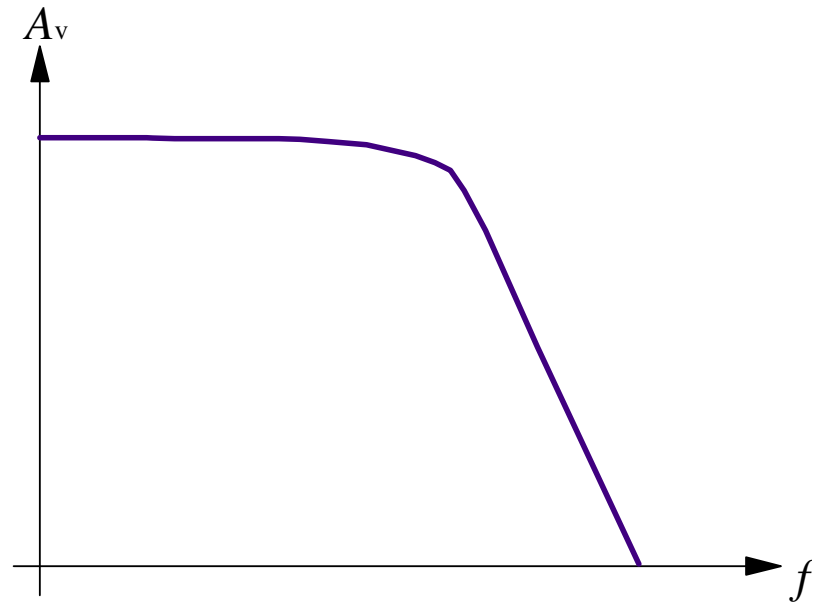- Very flat amplitude, $A_{v(dB)}$, response in the passband.
- Role-off rate is $20dB/decade/pole$.
- Phase response is not linear.
- Used when all frequencies in the passband must have the same gain.
- Often referred to as a *maximally flat response*.



Chebyshev Characteristic

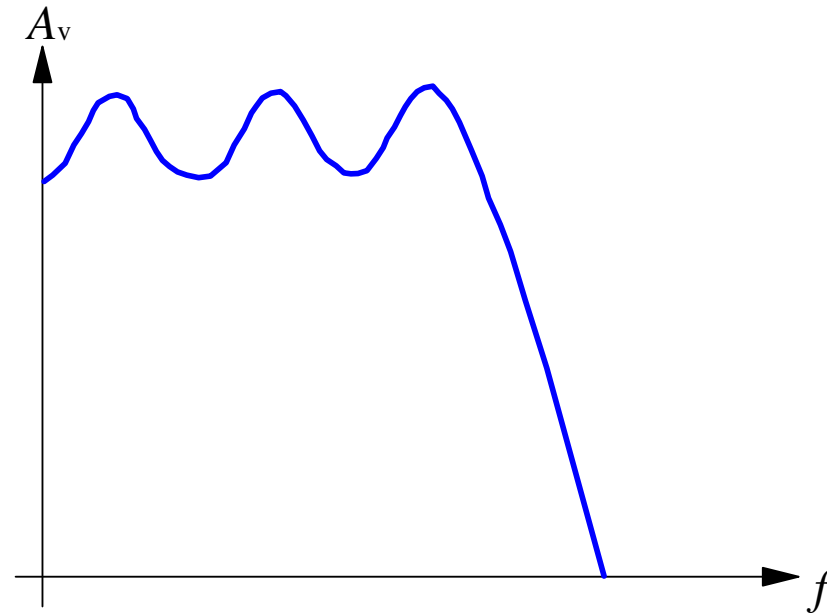
- Overshoot or ripples in the passband.
- Role-off rate greater than $20\text{dB}/\text{decade}/\text{pole}$.
- Phase response is not linear - worse than Butterworth.
- Used when a rapid roll-off is required.




Active Filter Implementations

- Cascading
- Multiple Feedback topology
- Biquad topology
- Sallen-Key topology

Single-Pole Low/High-Pass Filter

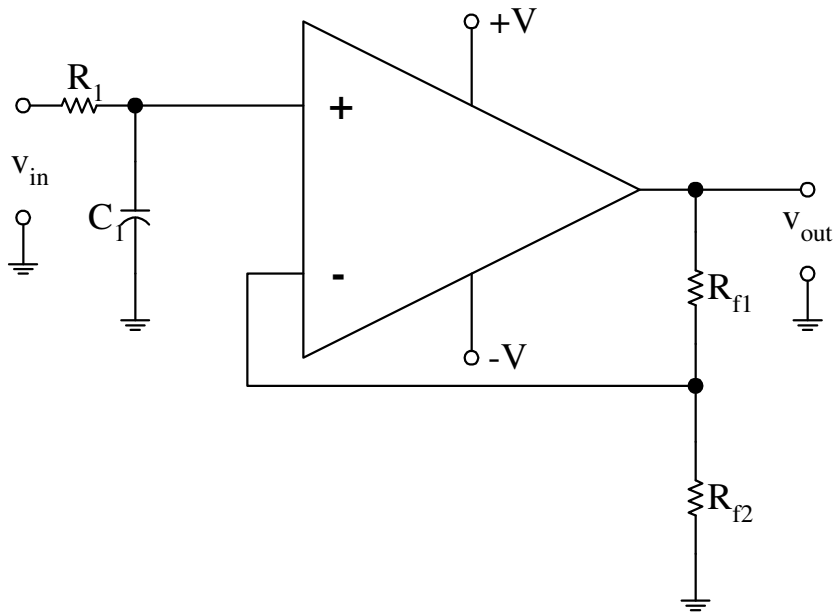


Low Pass Filter

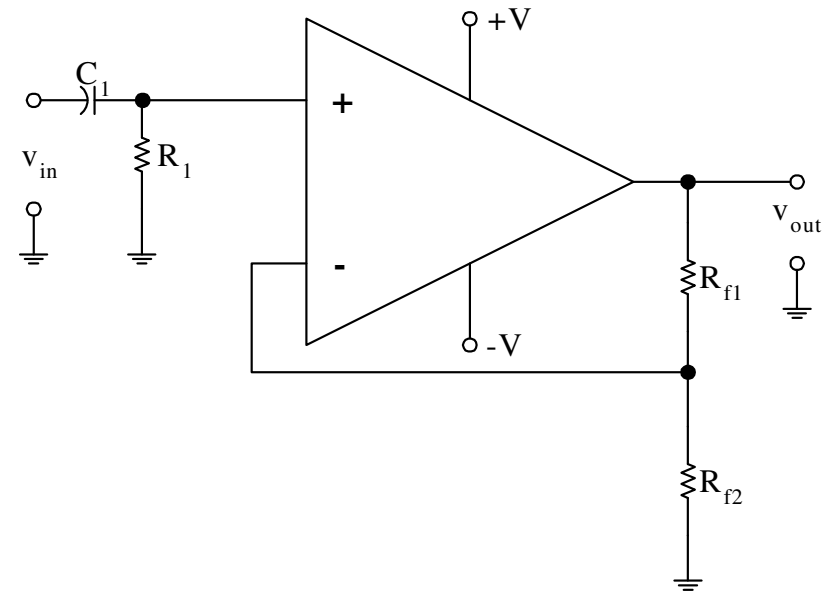


High Pass Filter

Two-Pole (Sallen-Key) Filters

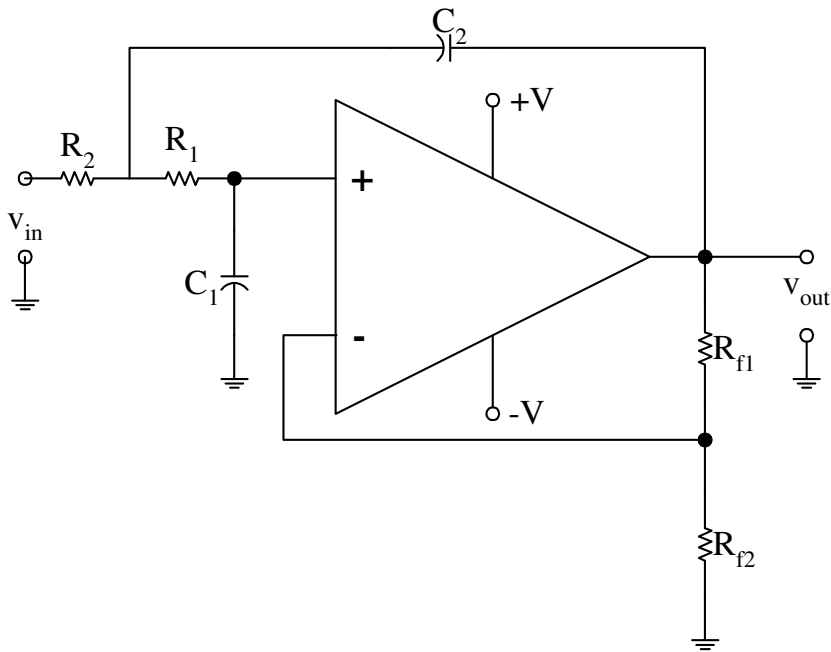


Low Pass Filter


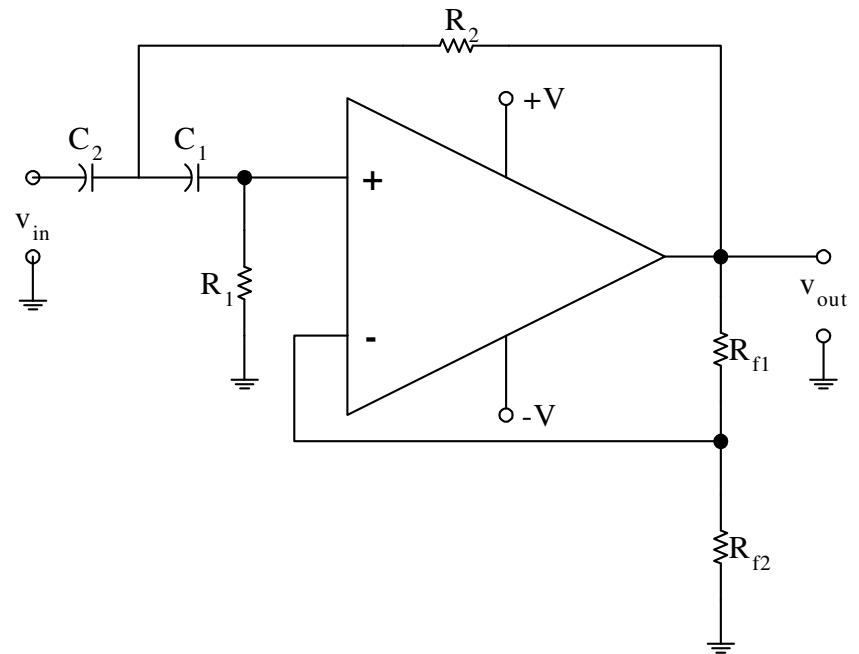


High Pass Filter


Three-Pole Low-Pass Filter

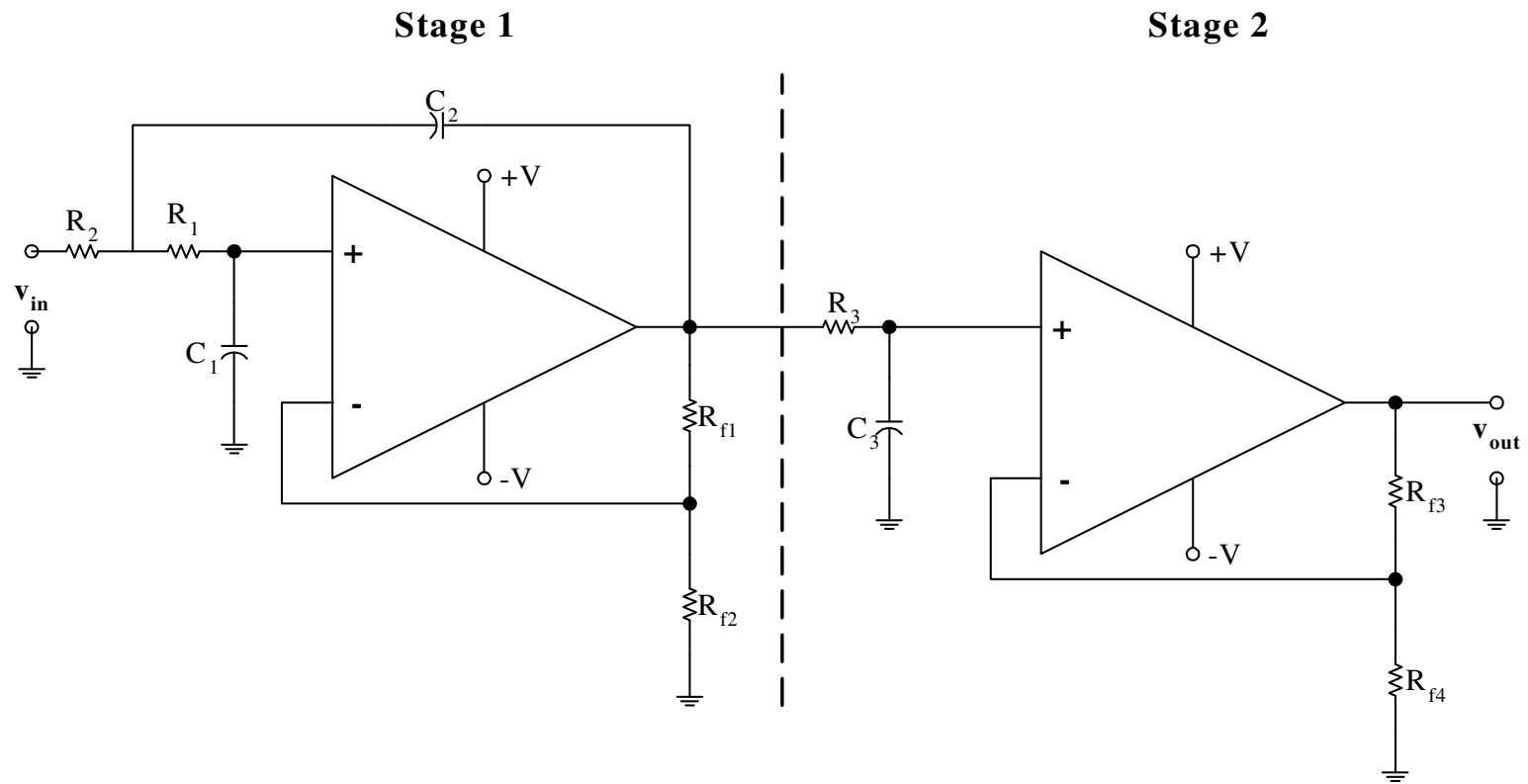

Two-Stage Band-Pass Filter

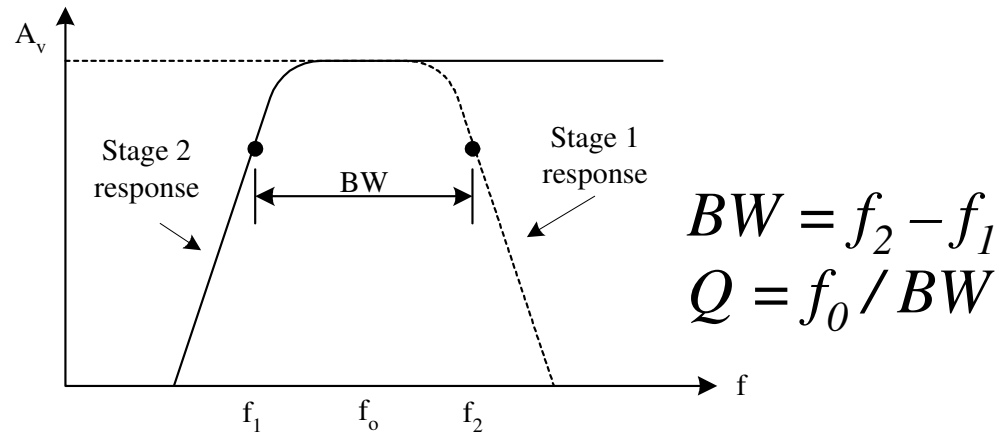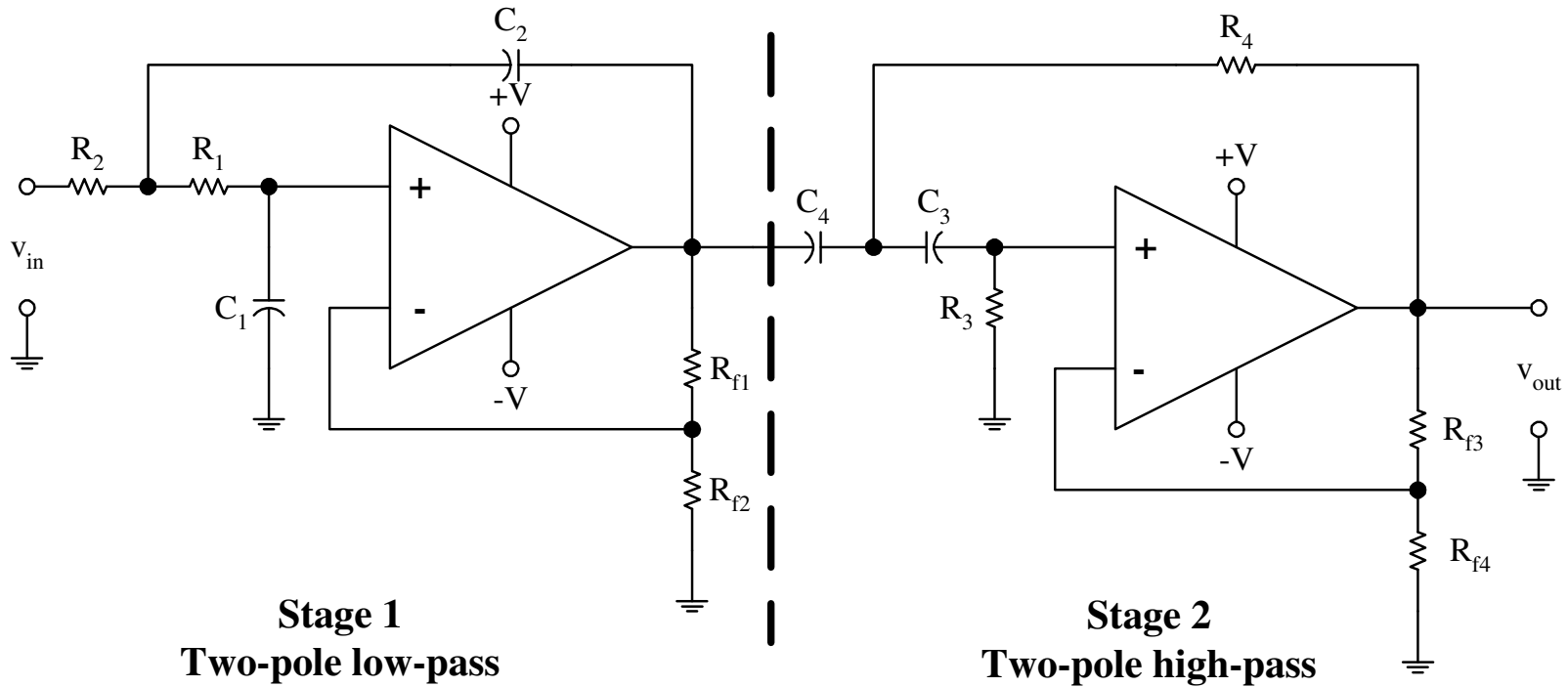


Multiple-Feedback Band-Pass Filter

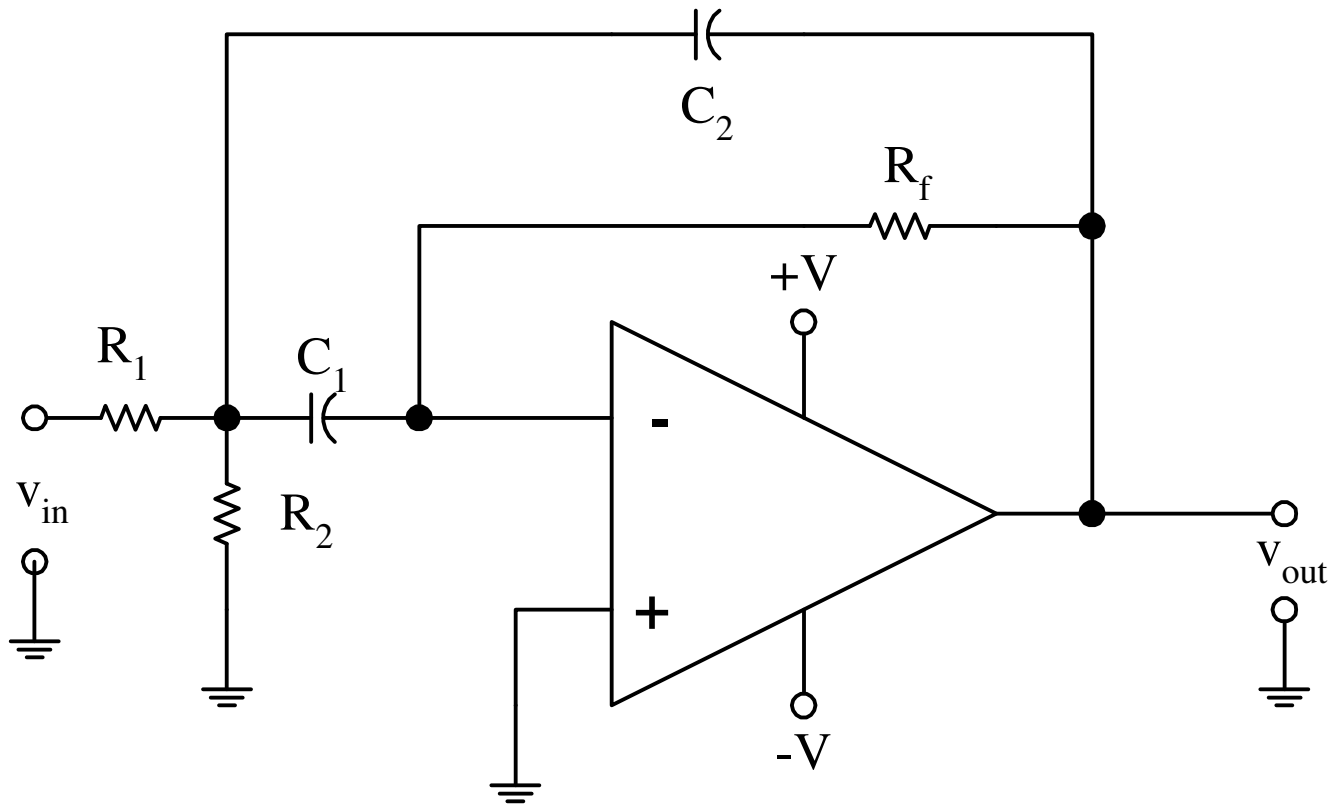


Band-Stop (Notch) Filter

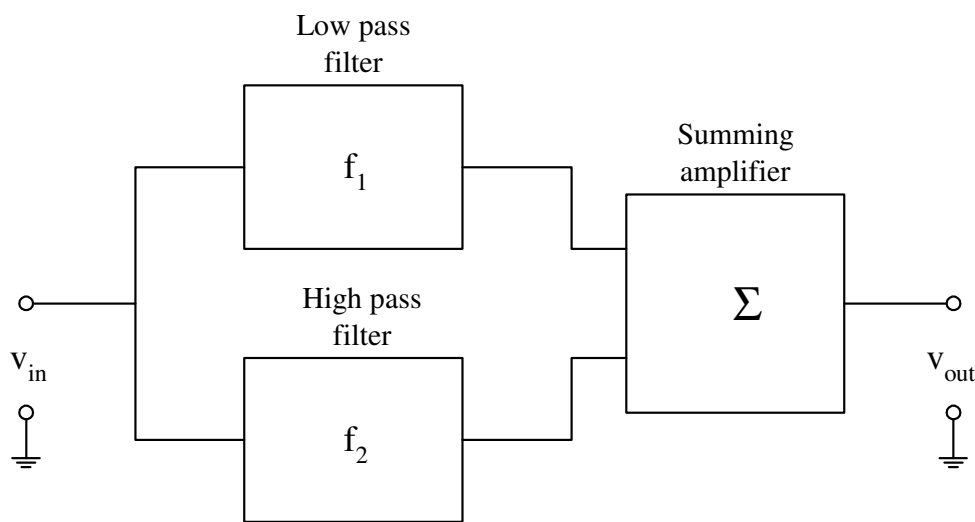The notch filter is designed to block all frequencies that fall within its bandwidth. The circuit is made up of a *high pass filter*, a *low-pass filter* and a *summing amplifier*. The summing amplifier will have an output that is equal to the sum of the filter output voltages.





Block diagram

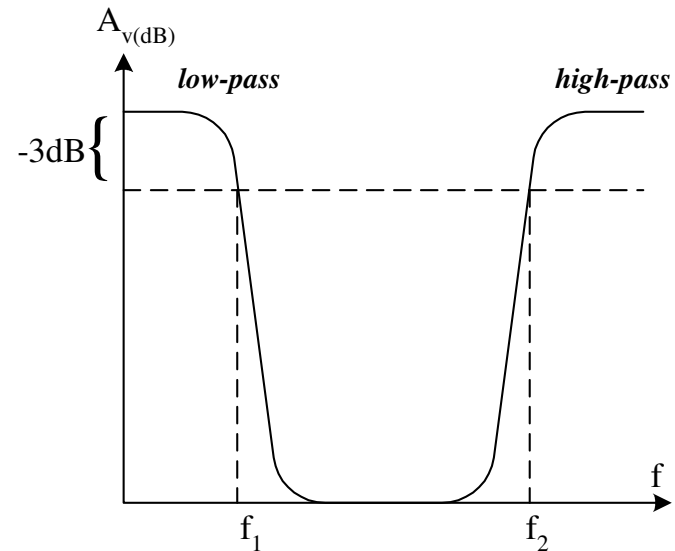

Frequency response

Notch filter

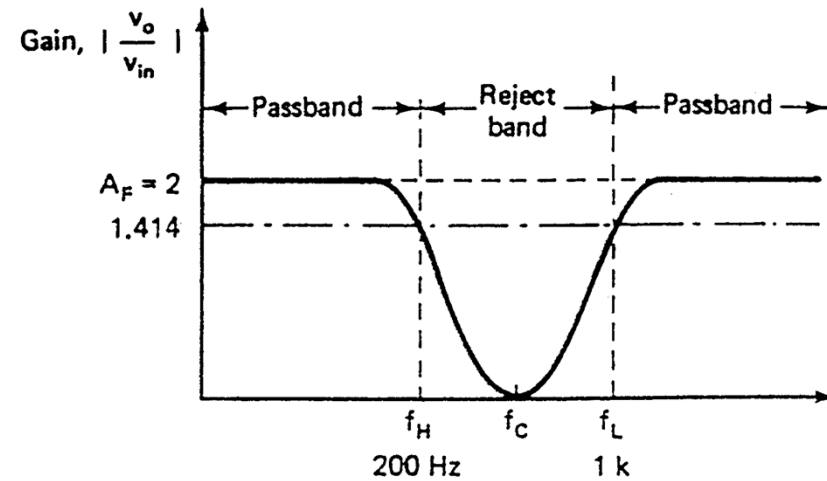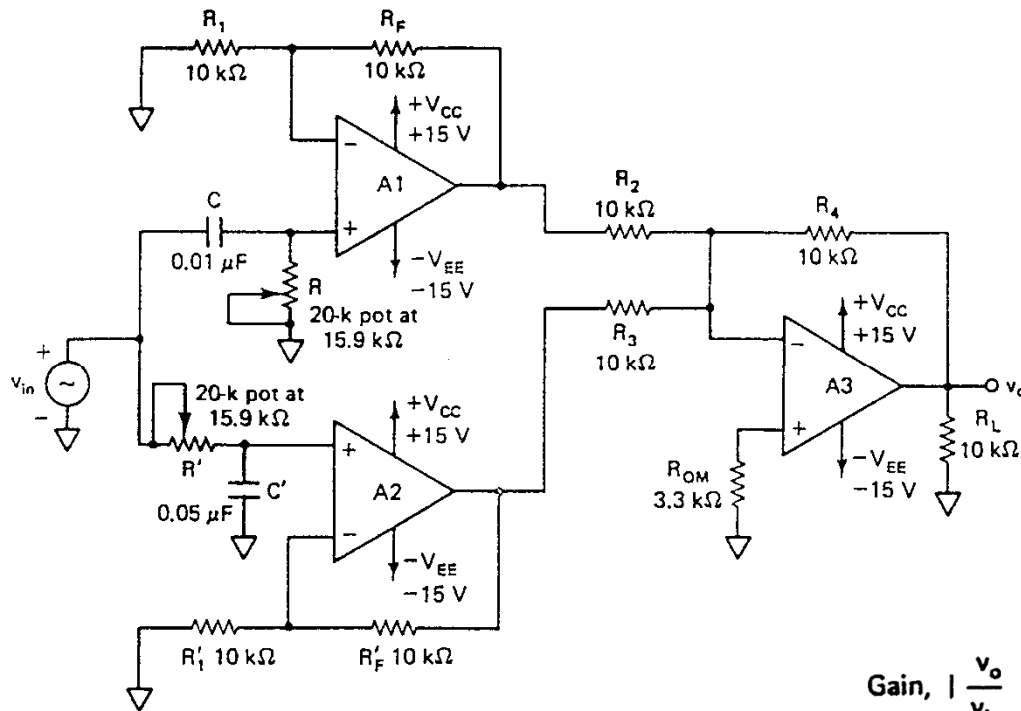

$$f_C = \sqrt{f_H f_L} = 447.2\text{ Hz}$$

Frequency