




Faculty of Engineering

## **MEP 382: Design of Applied Measurement Systems**


# **Lecture 9: Active Filters**
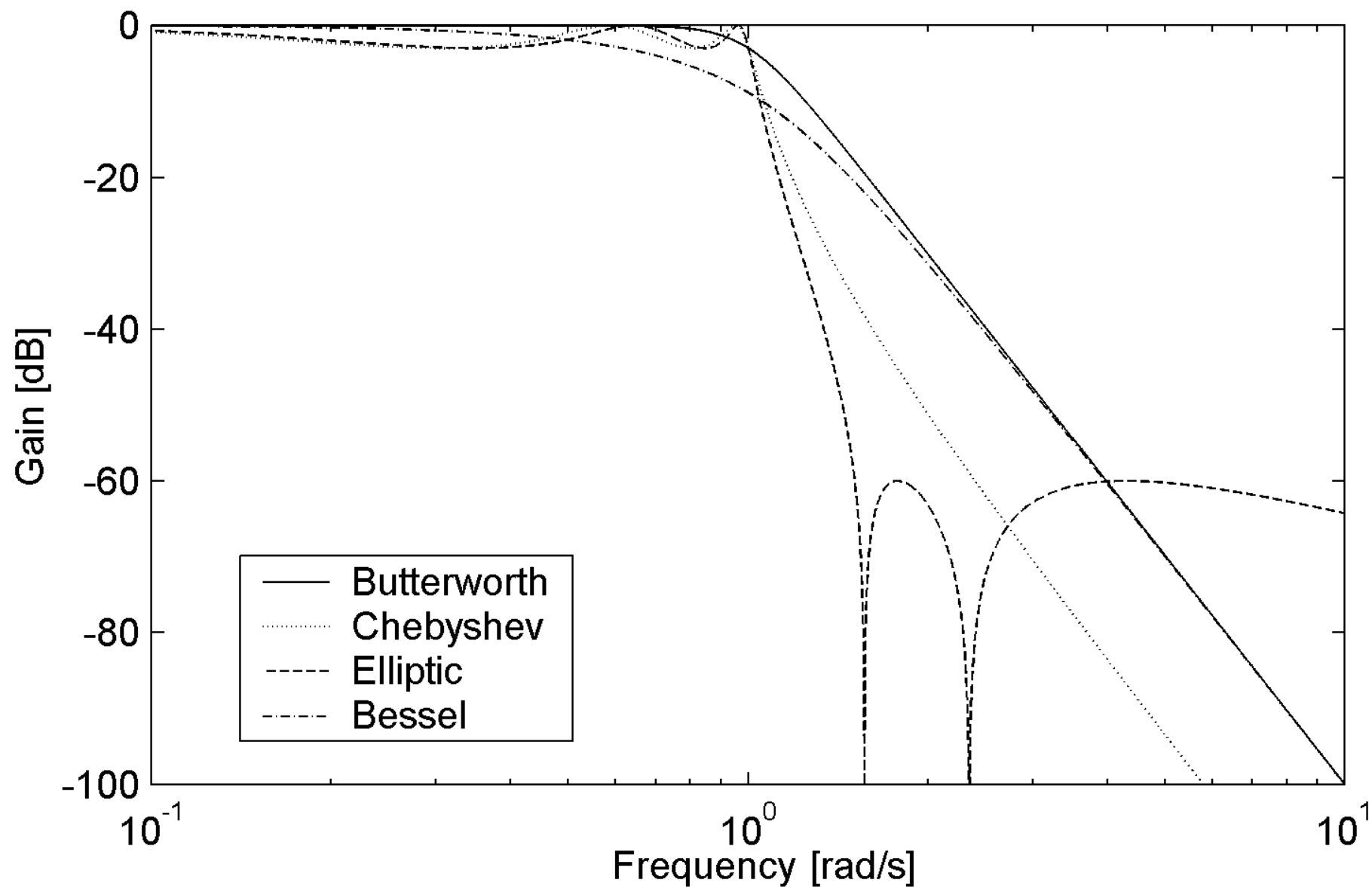
# Real Filters

- The approximations to the ideal filter are the:
  - Butterworth filter
  - Chebyshev filter
  - Cauer (Elliptic) filter
  - Bessel filter




# Filter Response Characteristics

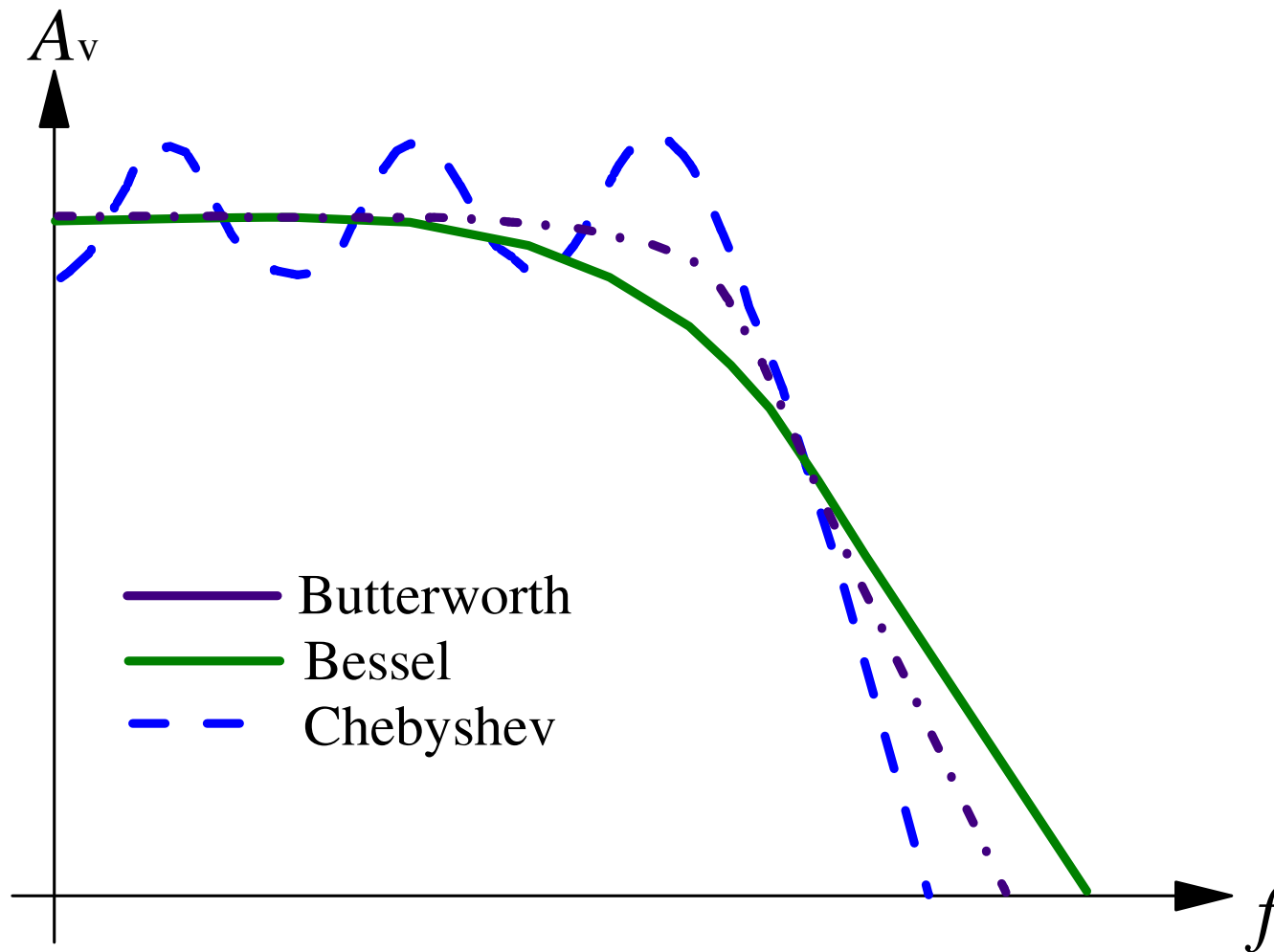

# PERFORMANCE CRITERIA

## AMPLITUDE RESPONSE

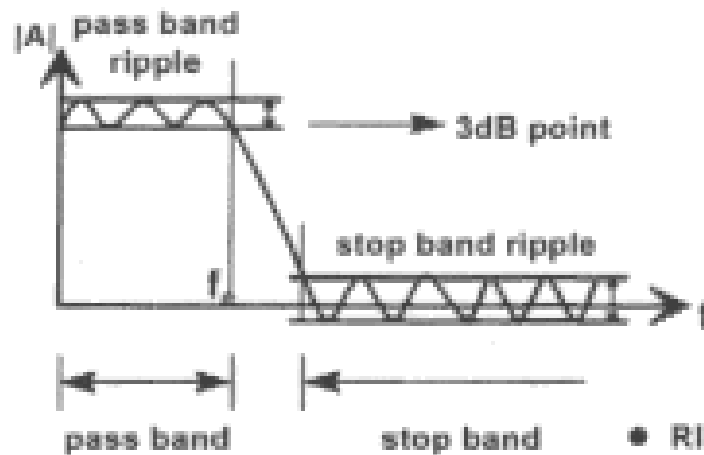

$$20 \log_{10} |A| = \text{Gain in dB}$$


$f_c$  = Cut-off Frequency

$$\text{Gain at 3dB point (at } f_c) = \frac{|A|}{\sqrt{2}}$$

- RIPPLE IN PASS BAND CAUSES NON-LINEARITY
- POSSIBLE TO DESIGN WITH NO RIPPLE
- RIPPLE IN STOP BAND IS LESS IMPORTANT
- FALL OFF dB / Decade (Gain in dB / Decade of  $f$ )
- STOP BAND ATTENUATES (SAY - 40dB)
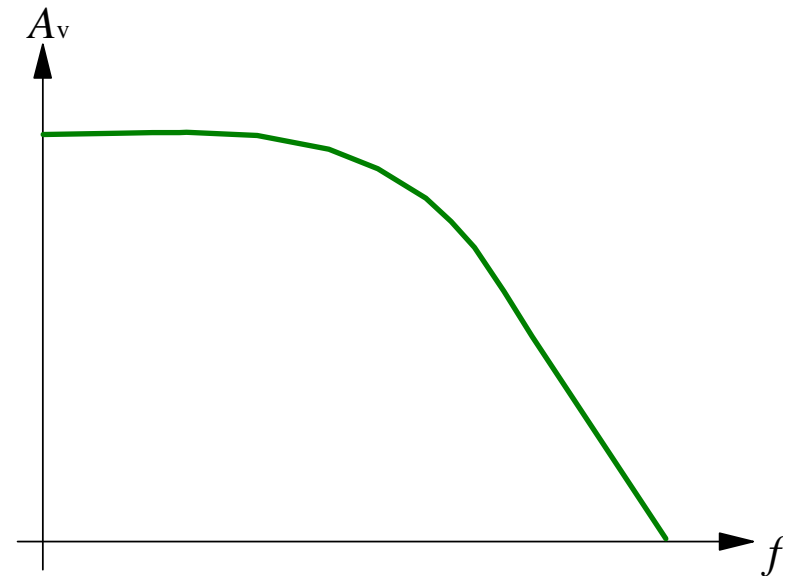
# Bessel Characteristic

- Flat response in the passband.
- Role-off rate less than  $20dB/\text{decade}/\text{pole}$ .
- Phase response is linear.
- Used for filtering pulse waveforms without distorting the shape of the waveform.




# Butterworth Characteristic

- Very flat amplitude,  $A_{v(dB)}$ , response in the passband.
- Role-off rate is  $20dB/decade/pole$ .
- Phase response is not linear.
- Used when all frequencies in the passband must have the same gain.
- Often referred to as a *maximally flat response*.


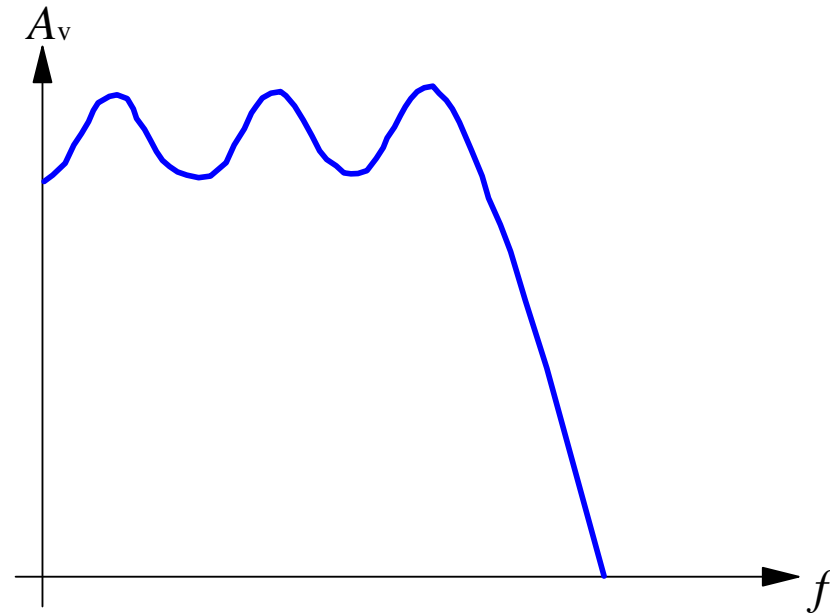
# Chebyshev Characteristic

- Overshoot or ripples in the passband.
- Role-off rate greater than  $20\text{dB}/\text{decade}/\text{pole}$ .
- Phase response is not linear - worse than Butterworth.
- Used when a rapid roll-off is required.







# Active Filter Implementations

- Cascading
- Multiple Feedback topology
- Biquad topology
- Sallen-Key topology

# Single-Pole Low/High-Pass Filter

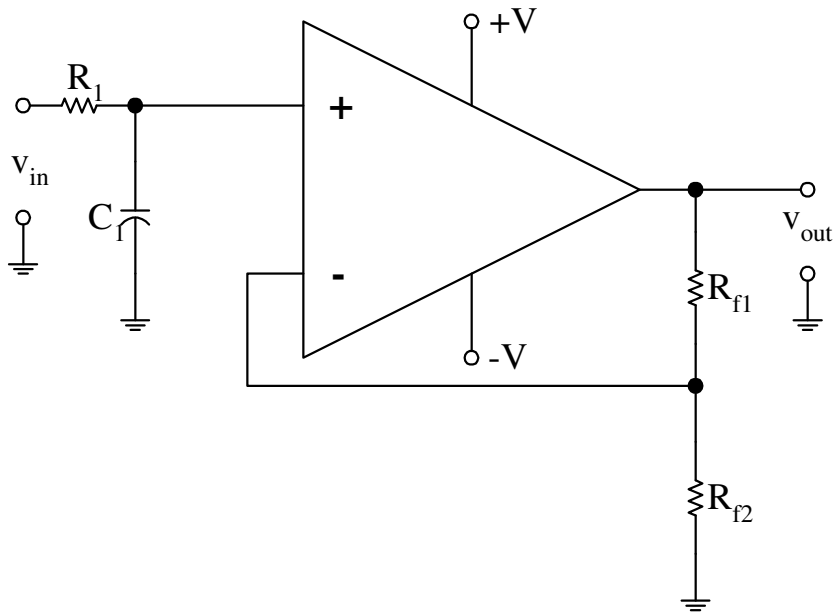


Low Pass Filter

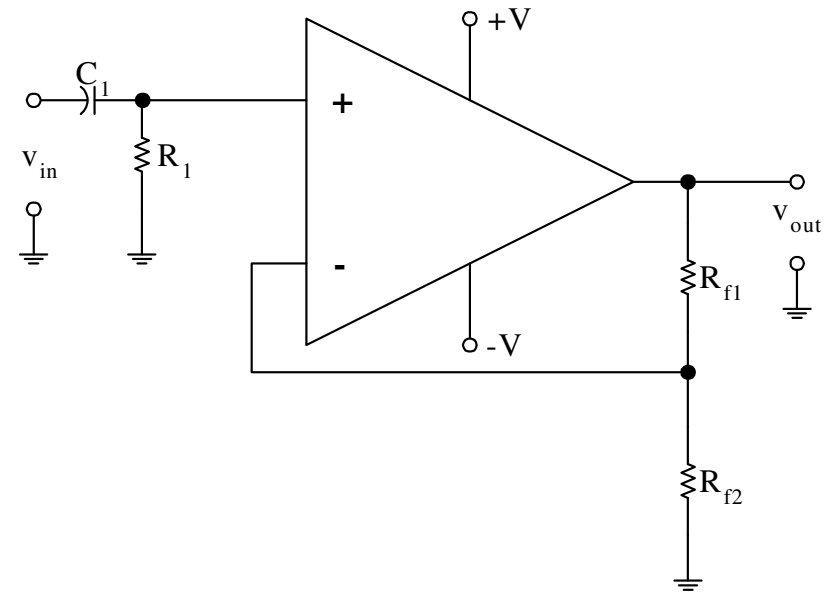


High Pass Filter

# Two-Pole (Sallen-Key) Filters

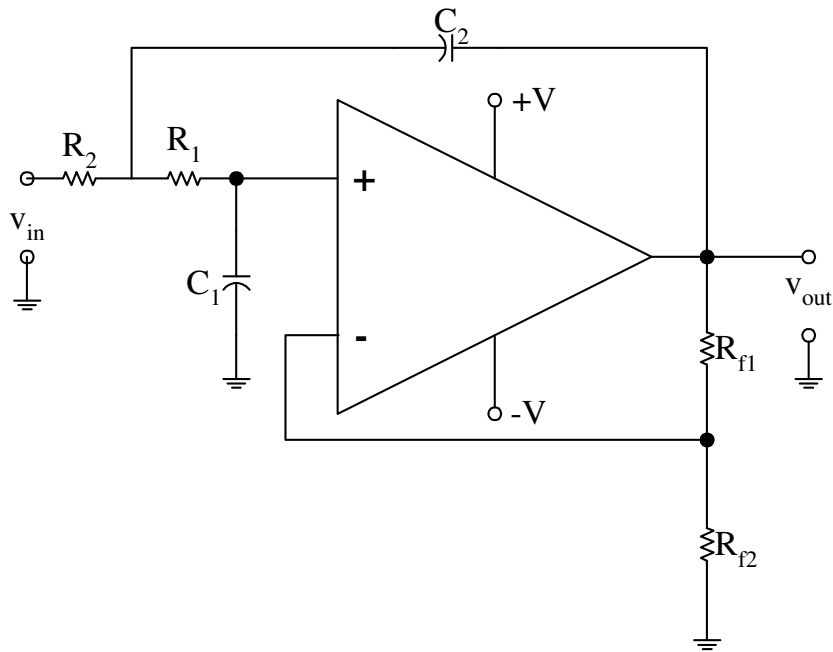


Low Pass Filter


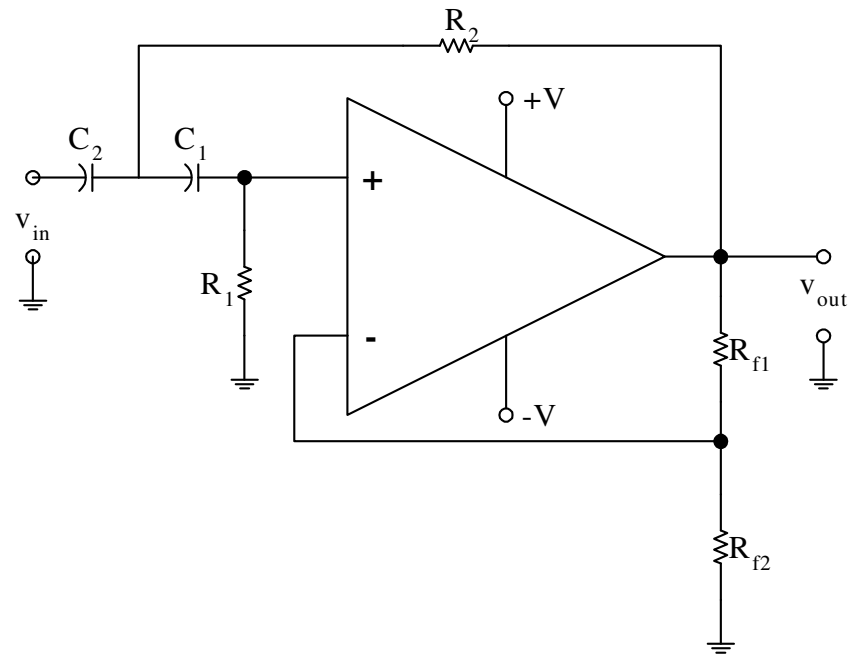


High Pass Filter


# Three-Pole Low-Pass Filter

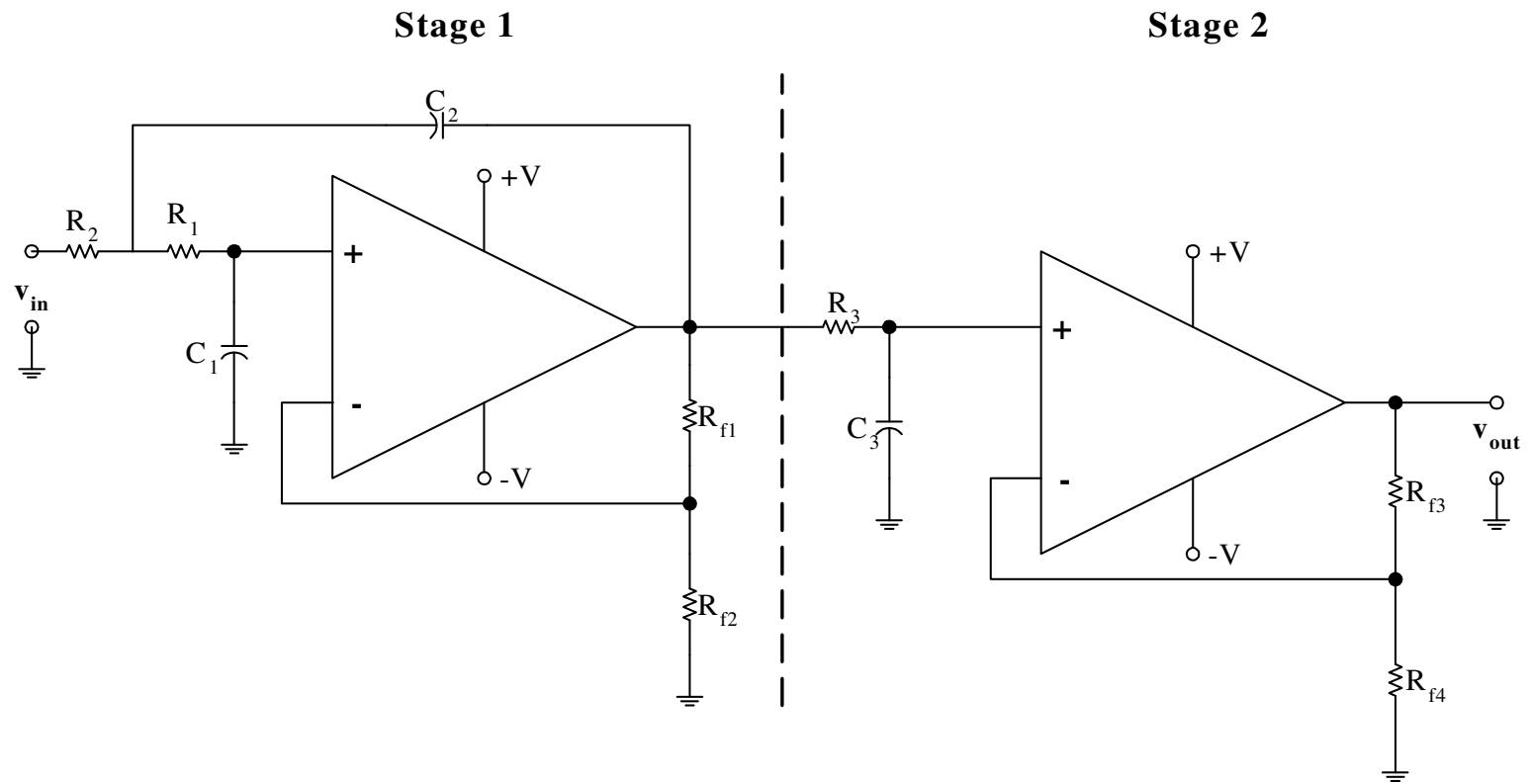

# Two-Stage Band-Pass Filter

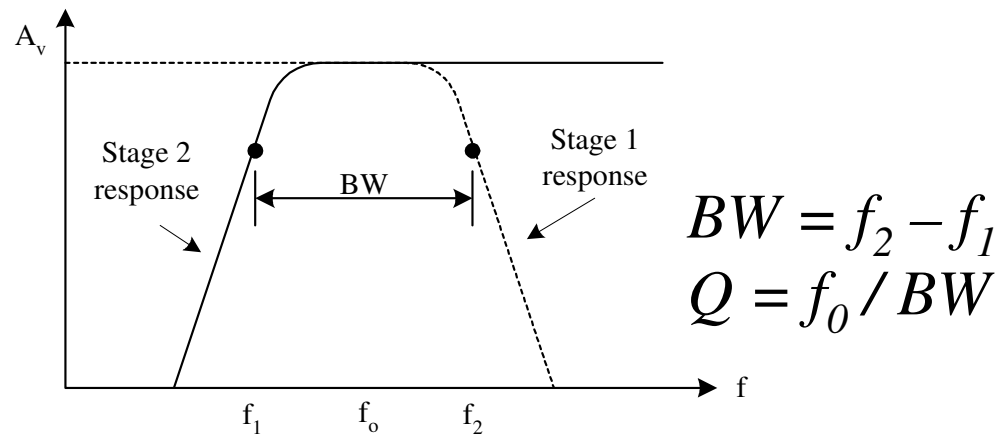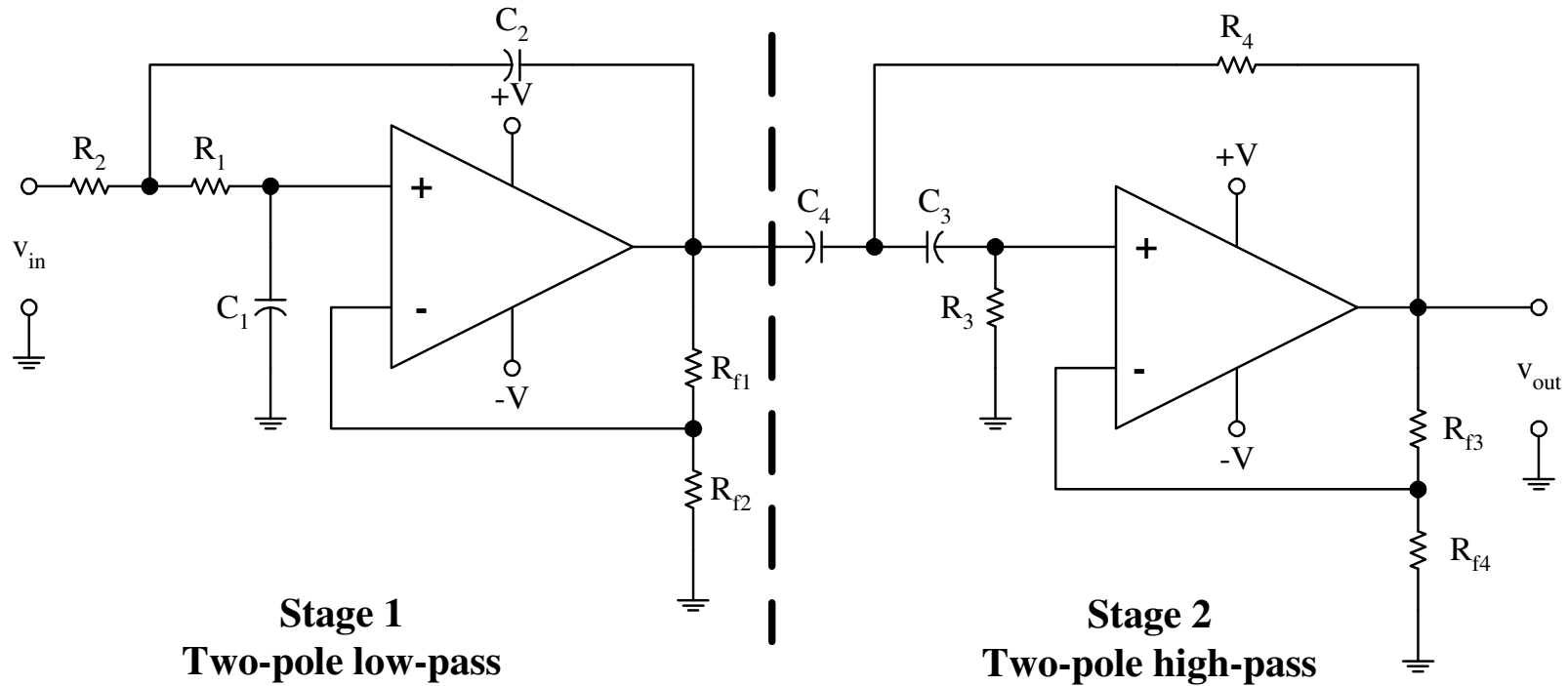


# Multiple-Feedback Band-Pass Filter

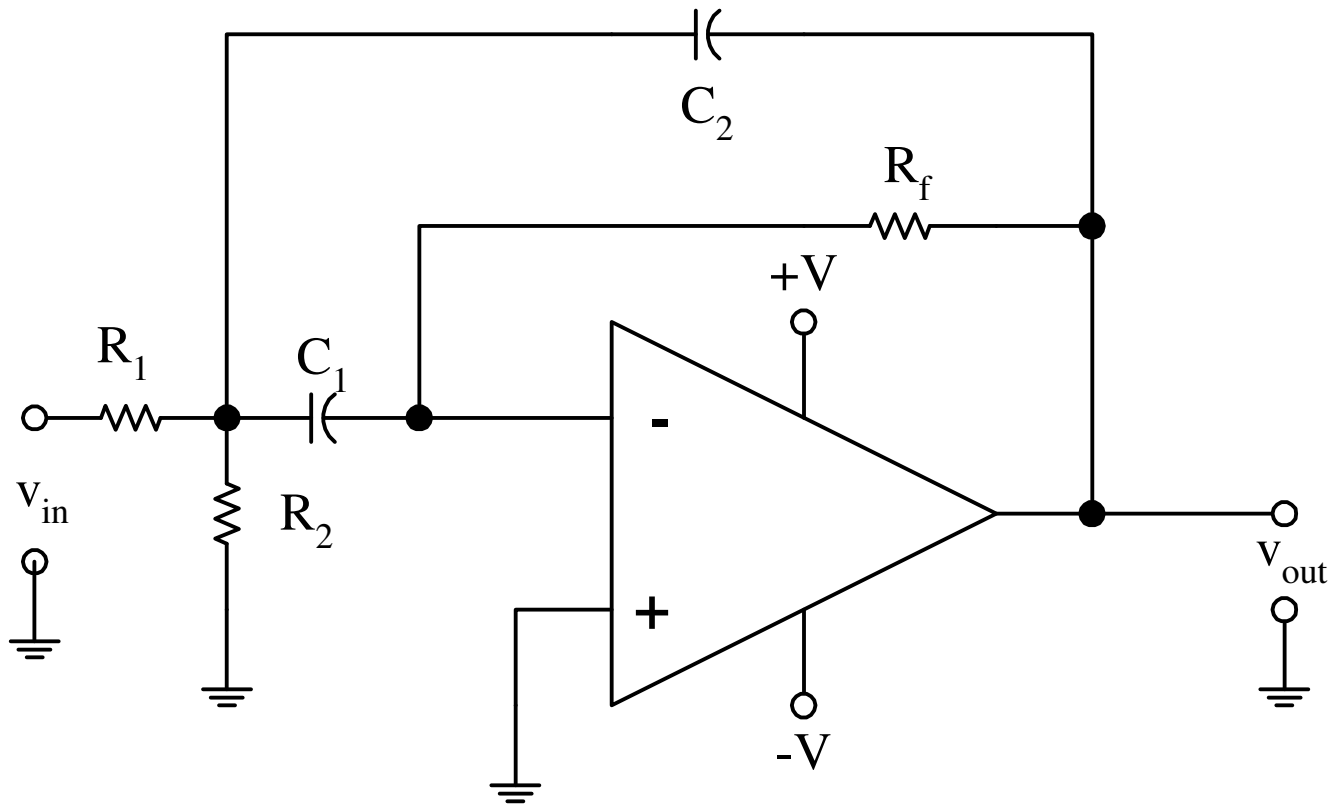

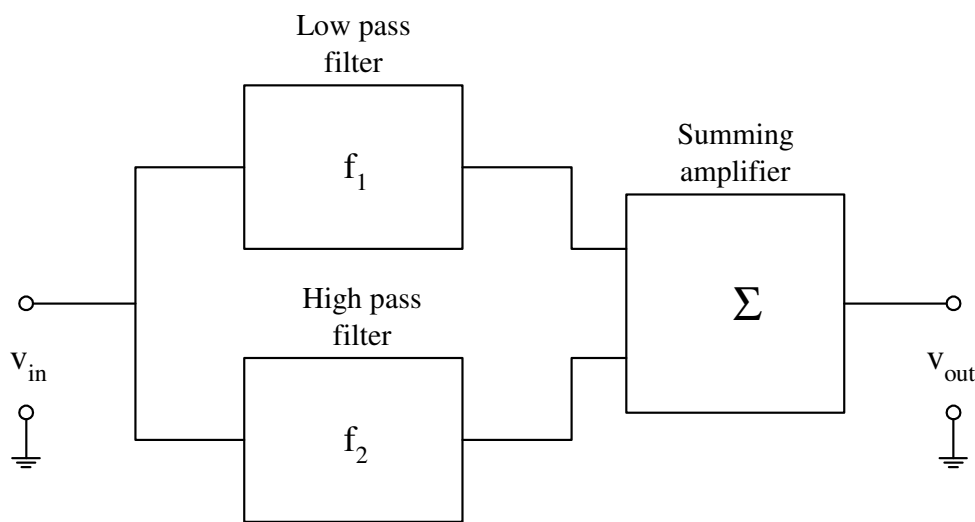
# Band-Stop (Notch) Filter

The notch filter is designed to block all frequencies that fall within its bandwidth. The circuit is made up of a *high pass filter*, a *low-pass filter* and a *summing amplifier*. The summing amplifier will have an output that is equal to the sum of the filter output voltages.



Block diagram

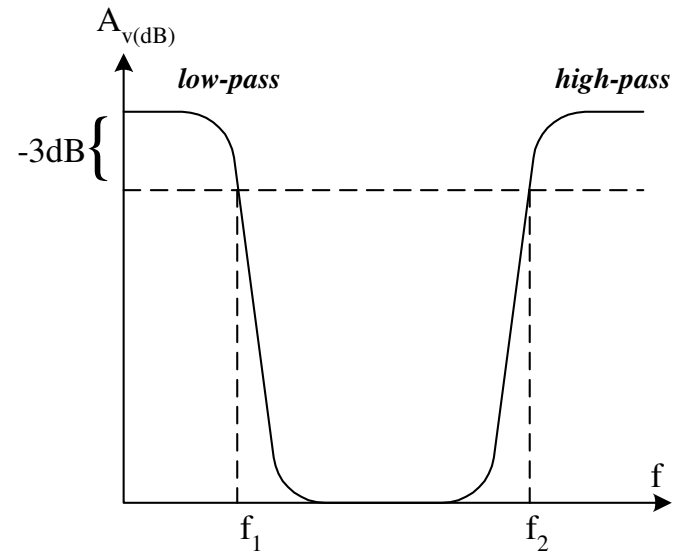

Frequency response

